

Tune that dial shortwave receiver with DDS



**2.4 GHz WLAN antennas
in practice**



**Unusual Christmas presents
gadgets & wannahaves**



**Extra! free 24 page supplement
The i-TRIXX Collection**



**Spy radio stations • Flowcode v. 3 is here •
Boxing up prototypes**

ORDER ONLINE

It's no Prickly Problem



For a FREE copy of our 410+ page catalogue from Australia (It's no prickly problem) log on to our website www.jaycarelectronics.co.uk/catalogue All prices in £ Stg



POST AND PACKING CHARGES:

Order Value	Cost	Order Value	Cost
£20 - £49.99	£5	£200 - £499.99	£30
£50 - £99.99	£10	£500+	£40
£100 - £199.99	£20		

Max weight 12lb (5kg). Heavier parcels POA. Minimum order £20.

IR Remote Control Extender MKII

KC-5432 £7.25 + post & packing
Operate your DVD player or digital decoder using its remote control from another room. It picks up the signal from the remote control and sends it via a 2-wire cable to an infrared LED located close to the device. This improved model features fast data transfer, capable of transmitting Foxtel digital remote control signals using the Pace 400 series decoder. Kit supplied with case, screen printed front panel, PCB with overlay and all electronic components.

Requires 9VDC wall adaptor (Maplin #GS74R £9.99)



Improved Model!

Battery Zapper MKII

KC-5427 £29.00 + post & packing
This kit attacks a common cause of failure in wet lead acid cell batteries: sulphation. The circuit produces short bursts of high level energy to reverse the damaging sulphation effect. This new improved unit features a battery health checker with LED indicator, new circuit protection against badly sulphated batteries, test points for a DMM and connection for a battery charger. Kit includes case with screen printed lid, PCB with overlay, all electronic components and clear English instructions. Suitable for 6, 12 and 24V batteries
• Powered by the battery itself



Improved Model!

Theremin Synthesiser MKII

KC-5426 £43.50 + post & packing
By moving your hand between the metal antennae, create unusual sound effects! The Theremin MkII improves on its predecessor by allowing adjustments to the tonal quality by providing a better waveform. With a multitude of controls, this instrument's musical potential is only limited by the skill and imagination of its player. Kit includes stand, PCB with overlay, machined case with silkscreen printed lid, loudspeaker, pitch antennae, all specified electronic components and clear English instructions.



Improved Model!

Requires 9-12VDC wall adaptor (Maplin #JC91Y £14.99)

As used in the Beach Boys classic hit 'Good Vibrations'

Galactic Voice Kit

KC-5431 £13.25 + post & packing
Be the envy of everyone at the next Interplanetary Conference for Evil Beings with this galactic voice simulator kit. Effect and depth controls allow you to vary the effect to simulate everything from the metallic-challenged C-3PO, to the hysterical ranting of Daleks hell-bent on exterminating anything not nailed down. The kit includes PCB with overlay, enclosure, speaker and all components. For those who really need to get out of the house a lot more. Take me to your leader.
• Requires 9V battery



High Range Adjustable Switch with LCD


KC-5376 £22.75 + post & packing
This temperature switch can be set anywhere up to 1200°C, so it's extremely versatile. The relay can be used to trigger an extra thermo fan on an intercooler, mount a sensor near your turbo manifold and trigger water spray cooling, or a simple alarm to warn you of overheating. The LCD, which can easily be dash mounted, displays the temperature constantly. Kit supplied with solder masked PCB with overlay, LCD panel, temperature probe and all electronic components.



We stock an extensive range of quality automotive kits

Smart Fuel Mixture Display Kit

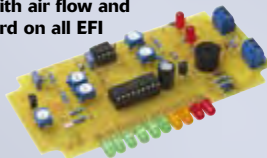
KC-5374 £8.95 + post & packing
This kit features auto dimming for night driving, emergency lean-out alarm, better circuit protection, and a 'dancing' display which functions when the ECU is operating in closed loop. Kit supplied with PCB and all electronic components.
• Car must be fitted with air flow and EGO sensors (standard on all EFI systems) for full functionality.



Recommended box UB3 (HB-6013) £1.40 each

Intelligent Turbo Timer Kit

KC-5383 £14.75 + post & packing
This great module uses input from an airflow, oxygen, or MAP sensor to determine how hard the car has been driven. It then uses this information to calculate how long the car needs to idle, reducing unnecessary idle time. The sensitivity and maximum idle time are both adjustable, so you can be sure your turbo will cool properly. Kit supplied with PCB, and all electronic components.

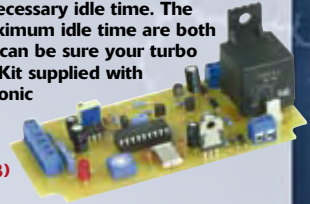

Recommended box UB3 (HB-6013) £1.40 each

Log on to www.jaycarelectronics.co.uk/catalogue for your FREE catalogue!

0800 032 7241

(Monday - Friday 09.00 to 17.30 GMT + 10 hours only).
For those who want to write: 100 Silverwater Rd
Silverwater NSW 2128 Sydney AUSTRALIA

All prices in £ Stg

Free 410+ page Catalogue




Jaycar Electronics

BitScope PC Oscilloscopes & Analyzers

DSO Test Instrument Software for BitScope Mixed Signal Oscilloscopes

DSO 2.0

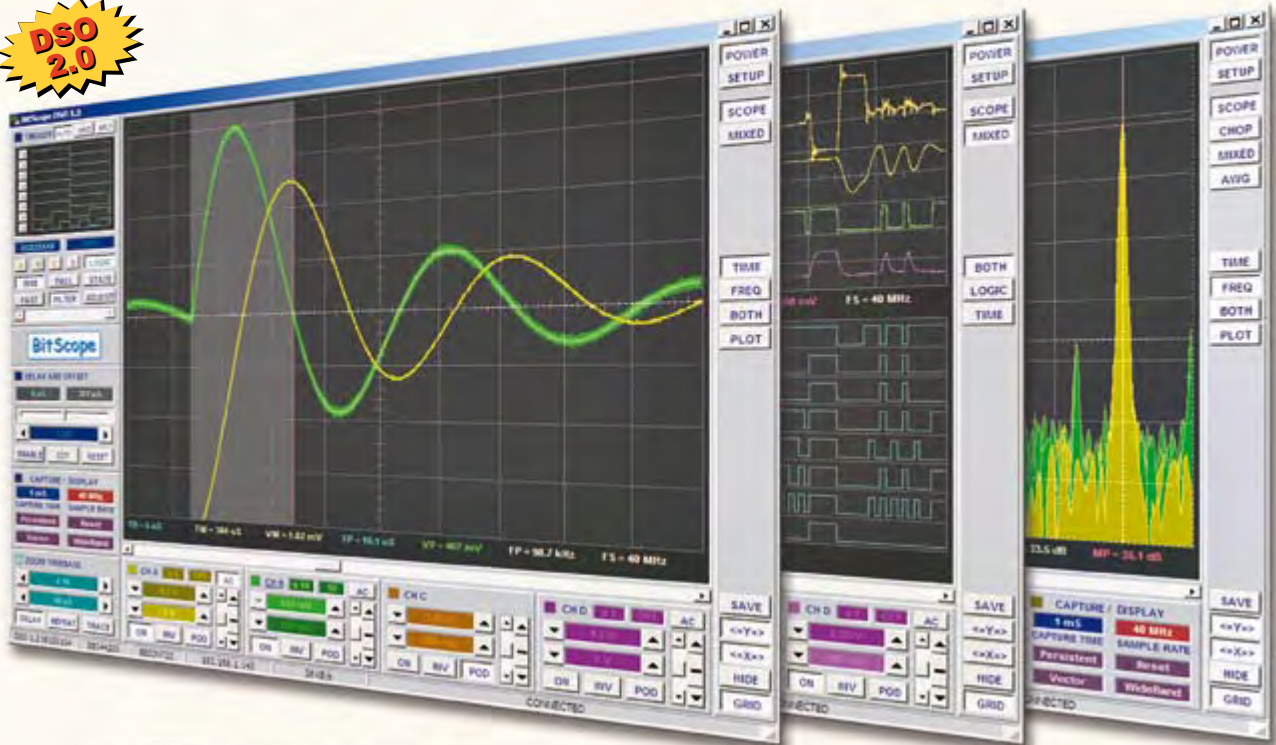

4 Channel BitScope



2 Channel BitScope



Pocket Analyzer

Digital Storage Oscilloscope

- ✓ Up to 4 analog channels using industry standard probes or POD connected analog inputs.

Mixed Signal Oscilloscope

- ✓ Capture and display up to 4 analog and 8 logic channels with sophisticated cross-triggers.

Spectrum Analyzer

- ✓ Integrated real-time spectrum analyzer for each analog channel with concurrent waveform display.

Logic Analyzer

- ✓ 8 logic, External Trigger and special purpose inputs to capture digital signals down to 25nS.

Data Recorder

- ✓ Record anything the DSO can capture and display. Supports live data replay image export.

Networking

- ✓ Flexible network connectivity supporting multi-scope operation, remote monitoring and data acquisition.

Data Export

- ✓ Export data with DSO using portable CSV files or use libraries to build custom BitScope solutions.

BitScope DSO Software for Windows and Linux

BitScope DSO is fast and intuitive multi-channel test and measurement software for your PC or notebook. Whether it's a digital scope, spectrum analyzer, mixed signal scope, logic analyzer, waveform generator or data recorder, BitScope DSO supports them all.

Capture deep buffer one-shots or display waveforms live just like an analog scope. Comprehensive test instrument integration means you can view the same data in different ways simultaneously at the click of a button.

DSO may even be used stand-alone to share data with colleagues, students or customers. Waveforms may be exported as portable image files or live captures replayed on other PCs as if a BitScope was locally connected.

BitScope DSO supports all current BitScope models, auto-configures when it connects and can manage multiple BitScopes concurrently. No manual setup is normally required. Data export is available for use with third party software tools and BitScope's networked data acquisition capabilities are fully supported.



www.bitscope.com

From the Editor's desk

With this extra-thick December issue we close off the publication year 2006. I've a few points to share with you all and I guess it does no harm to mention them in this month's Editorial space — in random order!

All change to dot com. As you may have noticed on last month's front cover, our website is also available at www.elektor.com. We are using this domain name because it is easier to remember (and type!) than www.elektor-electronics.co.uk. However, both websites run 100% in parallel and the old domain name will continue to be used.

The i-TRIXX supplement you get free of charge with this issue is actually the sixth gift our readers get this year. Earlier this year we gave away a Visual Basic booklet (January 2006); a C booklet and an FPGA poster (March 2006); an RFID card (September 2006); and an E-Simulation DVD (October 2006). The circuits in the 24-page i-TRIXX supplement are aimed at the younger generation (11 to 15s) and we would appreciate if you would let us know what you think of it.

We're hiring! Due to our expanding activities we're looking for:

- free-lance translators, German-English and Dutch-English;
- a free-lance News Correspondent (UK based);
- a free-lance Books Acquisition Manager (UK based).

For details regarding these positions, please contact me on editor@elektor.com and I will put you in touch with the responsible person within our organisation.


The Cumulative Index for Elektor Electronics volume 32 (2006) will be available as a free pdf download from our website. Like last year, we feel that the three precious pages taken up by the year index are better used for projects and other articles. Readers without internet access may write or telephone to request a free copy of the document on paper.

Finally, from all of us here at Elektor, we thank all our readers, business partners and advertisers for their continued support during the past year and wish you all a Merry Christmas and a peaceful and prosperous 2007!

Jan Buiting, Editor

24 Shortwave Capture

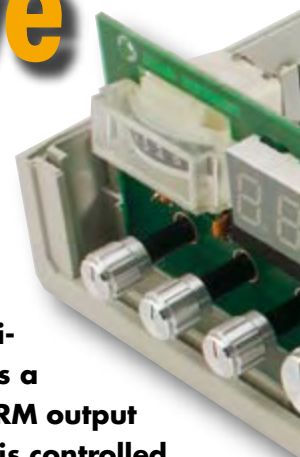As a special treat for all radio amateurs we present a general-coverage AM/FM/SSB receiver with a wide range of features, which uses a DDS chip in the VFO section and also has a DRM output that can be fed into a computer. The receiver is controlled by an 8-bit Atmel RISC processor. The frequency readout is on a clearly legible 7-segment LED display.



20 Tightly Packed


There are an incredible number of options these days for the safe 'packing up' of electronic circuits. Open any catalogue from any well-known mail-order company and you will get an impression of the extensive range on offer. This article gives an overview of the different types with their particular characteristics and provides hints as to how you can make a professional looking front panel yourself.




**FREE 24-page
i-TRIXX supplement**
starts on page 45

70 WLAN Antenna Design

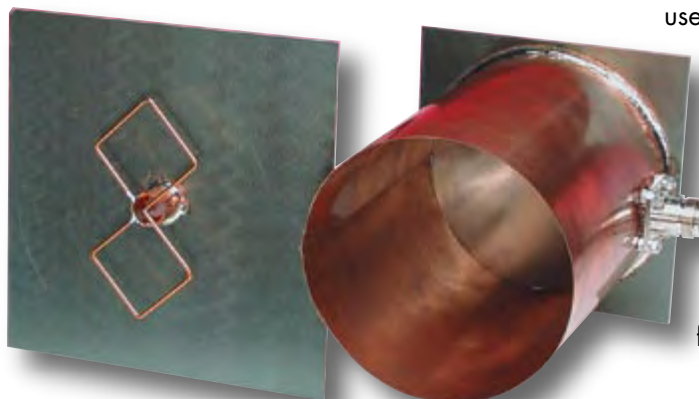The domestic use of WLANs has grown rapidly as DSL routers with built-in wireless Ethernet have become available, and now it is easy to use a notebook PC to surf the Internet wirelessly from the comfort of one's sofa. However, things get trickier if a reinforced concrete wall stands in the way, or if a neighbour happens to be using the same frequency...




CONTENTS

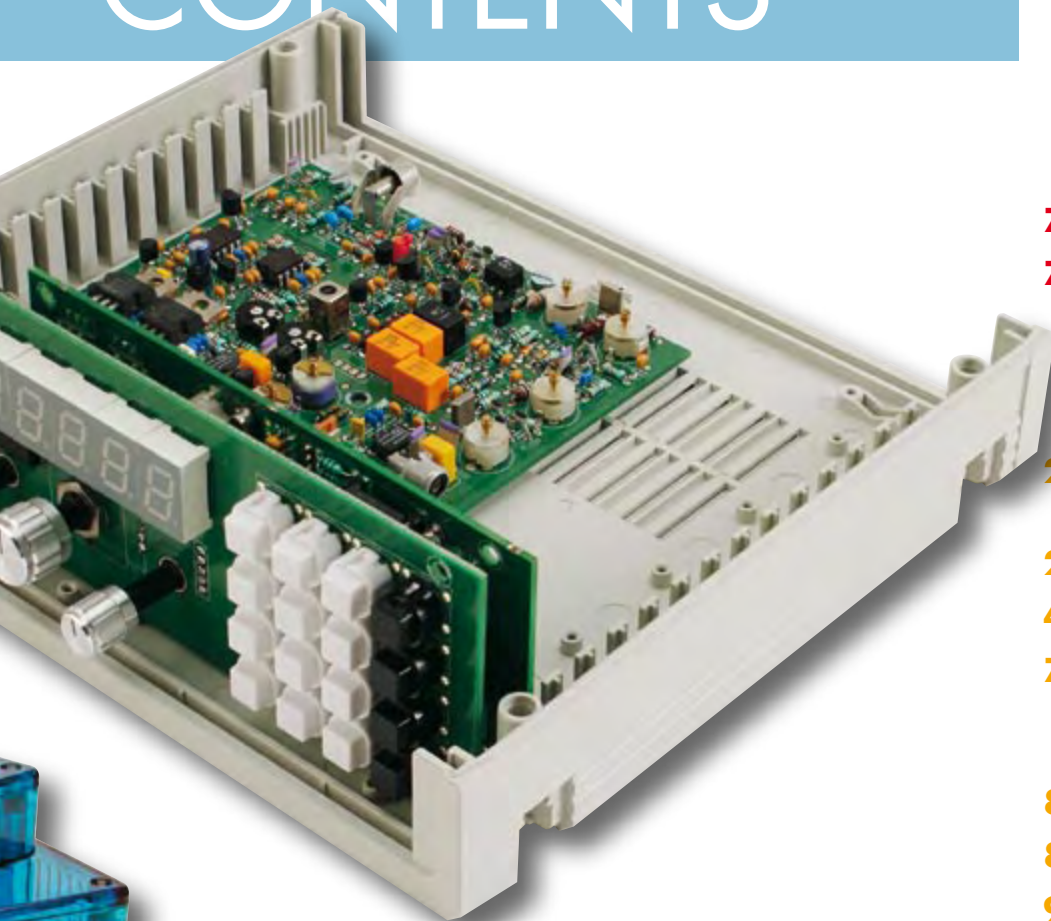

88 A New Flowcode



A new version of Flowcode for E-blocks has just been released — version 3. This is more than a simple upgrade: Flowcode has matured into a nice if not impressive development tool.

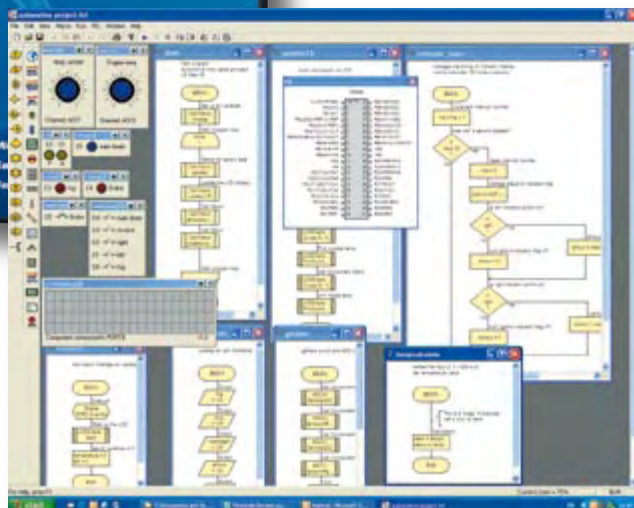

Volume 32
December 2006
no. 360

know-how

- 70** WLAN Antenna Design
- 76** Where am I — and Where are the Others?

hands-on

- 23** Multi-Purpose 3D Milling Machine (announcement)
- 24** Shortwave Capture
- 42** Go with the Flow
- 79** Design Tips
Client-server quizmaster
Pencil rubber cleans solder pads
- 84** FPGA Course (7)
- 88** A New Flowcode
- 92** Intelligent Voltmeter in a Plug
- 94** A Wire with Total Recall

technology

- 34** Spy Radio Stations
- 38** Wireless Key
- 80** Radio Control using WLAN ICs
- 96** Smaller is not Always Better

info & market

- 6** Colophon
- 8** Mailbox
- 10** News & New Products
- 20** Tightly Packed
- 108** Sneak Preview

infotainment

- 14** Christmas Presents
- 100** SSB Receiver for 20m and 80m (1987)
- 101** Hexadoku



Volume 32, Number 360, December 2006 ISSN 0268/4519

Elektor Electronics aims at inspiring people to master electronics at any personal level by presenting construction projects and spotting developments in electronics and information technology.

Publishers: Elektor Electronics (Publishing), Regus Brentford, 1000 Great West Road, Brentford TW8 9HH, England. Tel. (+44) 208 261 4509, fax: (+44) 208 261 4447 www.elektor.com

The magazine is available from newsagents, bookshops and electronics retail outlets, or on subscription. *Elektor Electronics* is published 11 times a year with a double issue for July & August.

Under the name *Elektor* and *Elektuur*, the magazine is also published in French, German and Dutch. Together with franchised editions the magazine is on circulation in more than 50 countries.

International Editor: Mat Heffels (m.heffels@segment.nl)

Editor: Jan Buiting (editor@elektor.com)

International editorial staff: Harry Baggen, Thijs Beckers, Ernst Krempelsauer, Jens Nickel, Guy Raedersdorf.

Design staff: Ton Giesberts, Paul Goossens, Luc Lemmens, Christiaan Vossen

Editorial secretariat: Hedwig Hennekens (secretariaat@segment.nl)

Graphic design / DTP: Giel Dols

Managing Director / Publisher: Paul Snakkers

Marketing: Carlo van Nistelrooy

Customer Services: Margriet Debeij (m.debeij@segment.nl)

Subscriptions: Elektor Electronics (Publishing), Regus Brentford, 1000 Great West Road, Brentford TW8 9HH, England. Tel. (+44) 208 261 4509, fax: (+44) 208 261 4447

Internet: www.elektor.com

Email: subscriptions@elektor.com

Rates and terms are given on the Subscription Order Form

Head Office: Segment b.v. P.O. Box 75 NL-6190-AB Beek The Netherlands Telephone: (+31) 46 4389444, Fax: (+31) 46 4370161

Distribution: Seymour, 2 East Poultry Street, London EC1A, England Telephone: +44 207 429 4073

UK Advertising: Huson International Media, Cambridge House, Gogmore Lane, Chertsey, Surrey KT16 9AP England.

Telephone: +44 1932 564999, Fax: +44 1932 564998

Email: r.elgar@husonmedia.com

Internet: www.husonmedia.com

Advertising rates and terms available on request.

International Advertising: Frank van de Raadt, address as Head Office Email: advertenties@elektuur.nl

Advertising rates and terms available on request.

Copyright Notice

The circuits described in this magazine are for domestic use only. All drawings, photographs, printed circuit board layouts, programmed integrated circuits, disks, CD-ROMs, software carriers and article texts published in our books and magazines (other than third-party advertisements) are copyright Segment. b.v. and may not be reproduced or transmitted in any form or by any means, including photocopying, scanning or recording, in whole or in part without prior written permission from the Publishers. Such written permission must also be obtained before any part of this publication is stored in a retrieval system of any nature. Patent protection may exist in respect of circuits, devices, components etc. described in this magazine. The Publisher does not accept responsibility for failing to identify such patent(s) or other protection. The submission of designs or articles implies permission to the Publishers to alter the text and design, and to use the contents in other Segment publications and activities. The Publishers cannot guarantee to return any material submitted to them.

Disclaimer

Prices and descriptions of publication-related items subject to change. Errors and omissions excluded.

© Segment b.v. 2006

Printed in the Netherlands

Your price conscious PCB supplier



Interested? Contact us: +44 2088 167 005
E-mail: euro@eurocircuits.com
www.eurocircuits.com

Online price calculation
Online ordering
Online order tracking
Online 24/24H and 7/7D

Verified

- pooling for standard boards
- up to 6 layers
- from 1 to 1000 pieces
- from 3 working days onwards


A la carte

- technology at the right price
- up to 8 layers
- from 1 to 1000 pieces
- from 3 working days onwards

On demand

- your board, our challenge
- up to 20 layers
- from 1 piece onwards
- from 2 working days onwards

All Major Credit Cards Accepted!




ElmScan 5 USB Scan Tool

- Diagnose any car with EOBD
- 9600 or 38400 baud
- Based on the ELM327 IC
- Supported by more software than any other OBD interface
- Supports all EOBD and OBD-II protocols
- Inexpensive
- ✓ ISO15765-4 (CAN)
 - ✓ ISO14230-4 (Keyword 2000)
 - ✓ ISO9141-2
 - ✓ J1850 VPW
 - ✓ J1850 PWM
- Full Speed USB 1.1
- Automatic protocol detection
- Package includes cables, software CD, and Quick Start Guide
- Buy from your local UK distributors!

www.ElmScan5.com/elektor

PicoScope 3000 Series PC Oscilloscopes

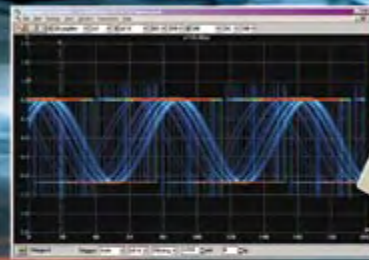The PicoScope 3000 series oscilloscopes are the latest offerings from the market leader in PC oscilloscopes combining high bandwidths with large buffer memories. Using the latest advances in electronics, the oscilloscopes connect to the USB port of any modern PC, making full use of the PCs' processing capabilities, large screens and familiar graphical user interfaces.



- High performance: 10GS/s sampling rate & 200MHz bandwidth
- 1MB buffer memory
- High speed USB 2.0 interface
- Advanced display & trigger modes
- Compact & portable
- Supplied with PicoScope & PicoLog software

PicoScope	3204	3205	3206
Bandwidth	50MHz	100MHz	200MHz
Sampling rate (sequential)	2.5GS/s	5GS/s	10GS/s
Sampling rate (single shot)	50MS/s	100MS/s	200MS/s
Channels	2+Ext trigger	2+Ext trigger/50 ps	2+Ext trigger/50 ps
Oscilloscope timebases	5ns/div to 50ns/div	2ns/div to 50ns/div	1ns/div to 50ns/div
Timebase accuracy	50ppm	50ppm	50ppm
Spectrum range	0 to 25MHz	0 to 50MHz	0 to 100MHz
Buffer memory size	256KB	512KB	1MB
Resolution / accuracy	8 bits / 3%		
Range	±100mV to ±20V		
PC Connection	USB2.0 (USB1.1 compatible)		

Tel: 01480 396395

www.picotech.com/scope374

pico
Technology Limited

PCB-POOL®
SERVICING YOUR COMPLETE PROTOTYPE NEEDS

Price Example: 16 Sq-Inches
(double sided pth)

2 Days: €123 (incl vat)

8 Days: €31 (incl vat)

Standard PCB-Pool Service

SIMPLY SEND YOUR FILES AND ORDER ONLINE!

New Service:




Save vital time on design errors in advance of receiving your Prototype. View high resolution photographic images of your PCB during each production stage. Be one step ahead, use our realtime PCB monitoring service.

WWW.PCB-POOL.COM

DOWNLOAD OUR FREE PCB SOFTWARE
www.free-pcb-software.com



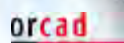Free Phone: 0800 389 8560
sales@beta-layout.com




Poor man's VGA Tester

Hi Elektor people — I attach a circuit diagram of a simple VGA Tester. The circuit is suitable for direct connection to a VGA display with a resolution of 480x640 pixels and generates a chessboard pattern. I designed the tester around a PIC12F508. It contains very few components and I believe the circuit speaks for itself. Jumper JP1 permits the colour selection between red, green and blue. By replacing it with three diodes (1N4148), the test picture goes black and white. The video output level is adjustable with preset P1.

The software I wrote for the tester is also simplicity itself. In principle, a loop is executed in which the image is built up bit by bit. The listing contains information regarding the pulse timing, which should enable users to adapt the program to suit other resolutions.

I designed the circuit with the help of MPLAB IDE v7.20 and Eagle 4.16.

Hans Kooij (Netherlands)

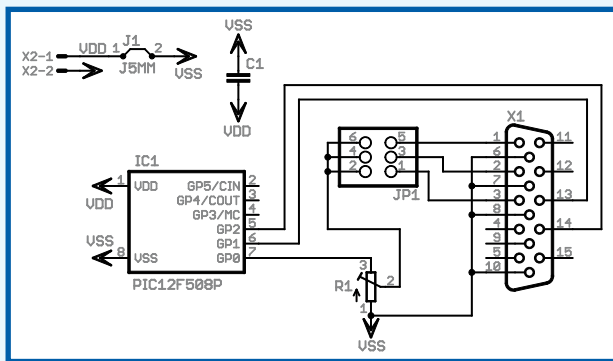

Thanks Hans, we agree that your circuit is hard to beat in terms of component count. The signal is composed entirely by the PIC and with some dexterity the tester could be built into a VGA plug. The source code is available for free downloading from our website — the file number is 060215-11.zip.

Phono Splitter — some points to note

Dear Editor — I write to mention a few small errors that apparently have kept in my project 'Phono Splitter' published in the July/August 2006 issue.

- Compensation capacitor C4 should have a value of 47 pF, not 470 pF.
- T1 should be a BC560C like T2 and T3.
- In my prototype, diodes D2 and D3 were types 1N4448, mainly because of their tighter specifications in respect of forward



bias voltage. I would expect 1N4148s to work equally well, though.


Thanks for publishing my design and hope a few readers benefit from it.

Marcel van de Gevel (Netherlands)

Thanks Marcel, and our apologies for the errors in reproducing your design. With over 100 article files being produced in four languages within a period of about four weeks, the production of our Summer Circuits edition is a tour de force where errors can not be ruled out entirely, particularly when making the drawings.

Apple-01 Replica computer

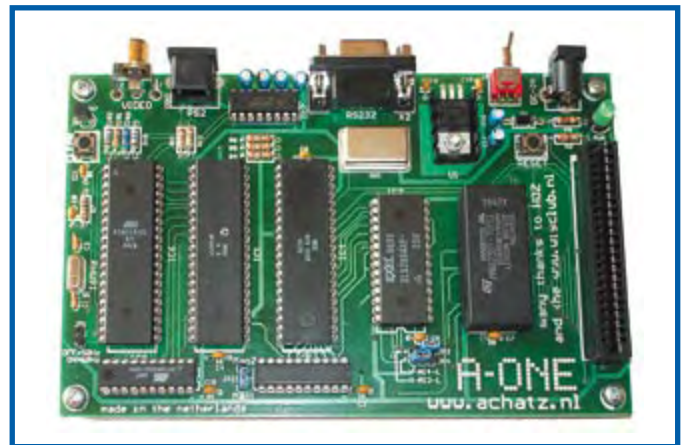Dear Jan — just to say that I built a replica of the 30 year old Apple-1 computer (see photo) for a personal 'OK' from Steve



Wozniak to reuse his A1 firmware on my replica computer which I dubbed 'A-ONE'.

The A-ONE works fine as far as I can check. Here are some data:

- 6502 at 1 MHz
- 6821 PIA
- 32 kB RAM
- EPROM with WOZ-Mon and WOZ BASIC
- GAL for address decoding etc.
- TINY2313 for PS2 keyboard and RS232 (reception)
- MEGA32 for video and

- RS232 (transmission)
- 2 x 22 pin A1 compatible slot

A nice change, I would say, from all that new fangled stuff around.

Franz Achatz (Germany)

Free e-SIM DVD

Dear Jan — I believe 754C1 is the answer to Hexadoku, October 2006 (correct! Ed.). I was looking for something to read at the shop, and found your magazine which I subscribed to in my student days, some twenty years ago. I have already tried some of the programs on the e-SIM DVD, thanks for bringing me back to the days of PCBs and simulations!

Magnus R. Berg (Norway)

Welcome back Magnus, you're in good company here.

RFID Quest extended

To give readers more time to read out the number stored on the free RFID card they got with their September 2006 issue (using a home built reader unit or one of the designs published in the same issue), the period for reporting winning card numbers has been extended to 15 December 2006. See also the RFID pages at www.elektor.com



galvanometers, standards and precision potentiometers. The workmanship is incredibly high and part of our heritage we should all be proud of.

John Price (UK)

Indeed we should, John. Thanks for letting us know about the origins of the Pontavi-Thomson bridge. Photograph reproduced courtesy of Kenyon College, Ohio (quite a distance from Kelvin Way Bridge, Glasgow).

MailBox Terms

- Publication of reader's correspondence is at the discretion of the Editor.
- Viewpoints expressed by correspondents are not necessarily those of the Editor or Publisher.
- Correspondence may be translated or edited for length, clarity and style.
- When replying to Mailbox correspondence, please quote Issue number.
- Please send your Mailbox correspondence to:

editor@elektor-electronics.co.uk
or
Elektor Electronics, The Editor,
1000 Great West Road,
Brentford TW8 9HH, England.

More power from the High-End Power Amp

Dear Editor — I believe the relatively low output power of the High-End Power Amplifier from the March 2005 issue is mostly owing to the enclosure used. In other words, if a larger cabinet is used, more space is available to step up the power supplied by the amp. For example, the transformer voltage can be increased from 18 V to 25 V. After rectification, this results in about 31 VDC. The modifications I carried out at the component level are:

Power supply:


225 VA toroidal transformer,
2x22 V
C5, C6, etc.: 10,000 μ F 35 V
Fuses: 1.5 A
Two NTCs in series with the mains voltage

Amplifier board:

R18: 10k
R42: 220k
R45: 220 Ω
D14;D15: 12V
Heatsink: 2 x Fischer SK 155, 75 mm (0.9 K/W)

Indicator board:

R16;R17;R33;R34: 330 Ω
R5;R22: 820 Ω

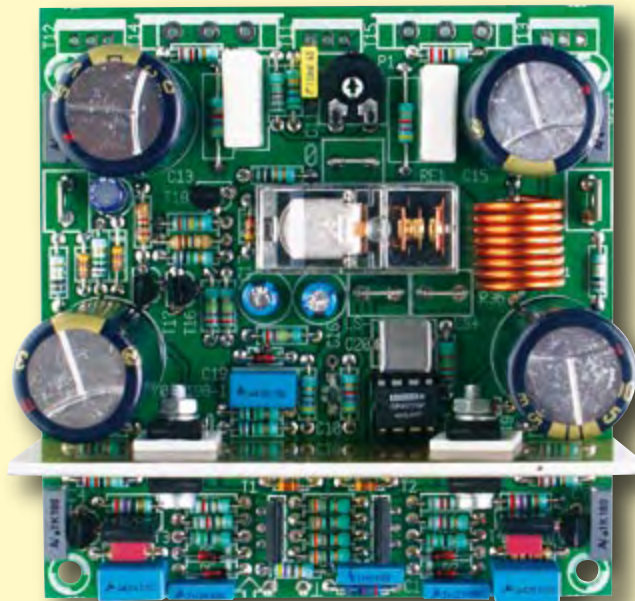

R6;R23: 10k

P1 and P2 allow the gain of the indicator board to be adjusted between 9 and about 13.7 times. I selected the Monacor (Monarch) type UC-204/SW case which has a size of 437x82x235 mm. Because of the larger output power, the indicator board is no longer required, hence I did not fit the LEDs on the front panel. Because the feedback is reduced, I fear the distortion goes up while damping is reduced. Lacking high-end test equipment I am unable to say if my modifications reduce the amplifier's performance in any way.
P. Kempenaar (Netherlands)

Our audio design specialist Ton Giesberts confirms that his High-End Power Amplifier design has potential for higher output power. The supply voltage may be increased to 35 V maximum, but not without major surgery to the existing design. For example, a larger heatsink must be used on the driver stage, and the resistor with the relay (R45) has to be adapted, as you have done. The sensitivity also requires adapting — it is now fairly low at 1.5 V for full drive. We confirm that it can be done by using 10 k Ω for R18, but stress that the modification modifies the carefully designed feedback response, which is likely to result in instability. This part of the modification really calls for a re-design. We recommend the use of an oscilloscope and a protected power supply if you want to stay on top of any tendency to oscillation.

The OPA177 has a maximum supply voltage spec of 22 V, hence is hard pushed in the original design already. Zener diodes of at least 12 V (D14; D15) are recommended at the suggested supply level of 31 VDC. At a supply voltage of 35 V, the zener diodes should be exchanged for 15-V types.

Regarding the output power, at a supply voltage of 31 V, about 50 watts can be delivered into 8 ohms, while the minimum load impedance goes up to about 3 ohms to keep the power transistors within their safe operating area.

Single-cell 1-A Li-Ion / Li-polymer charge management controllers

Microchip announces the MCP73833 and MCP73834 single-cell, high current (1 amp), Li-Ion/Li-Polymer linear charge-management controllers. These fully integrated devices combine several key charge-management and safety features in a single chip for reliable charging of high-capacity single-cell Li-Ion and Li-Polymer batteries.

By including a pass transistor, current-sense and reverse-discharge protection on a single chip, the MCP73833/4 charge-management controllers eliminate the need for external components. Multiple combinations of key charging parameters, including pre-conditioning current threshold and ratio, charge-termination threshold and recharge threshold ratio are available, meaning the devices provide standard product support for a variety of high-current Li-Ion/Li-Polymer charging applications. In addition, with a high charging current of up to 1 A and support for



multiple regulated output voltages (4.2 V, 4.35 V, 4.4 V and 4.5 V), the devices can be used with various generations of Lithium battery technology.

Safety features on the new devices to prevent overcharging and overheating include charge timers, battery-temperature feedback and thermal-current regulation. The charge timer shuts the charger off

if a charge is not terminated before timeout is reached. The battery-temperature feedback reduces the charge current if the battery's temperature reaches the limit of safety and the thermal-current regulation feature decreases the charge current if the charge-controller itself reaches its thermal limits.

Device-specific features include a power-good output on the

MCP73833 and a timer-enable input on the MCP73834. Both devices also offer a low dropout regulator (LDO) test mode that enables application system test even in the absence of a battery; and both feature two status outputs to provide the user with additional information about the state of the charge-controller.

To support development, Microchip offers the MCP73833 Evaluation Board (Part # MCP73833EV). The board is available today at www.microchipdirect.com.

The MCP73833/4 charge-management controllers are available in 10-pin MSOP and thermally efficient 3 x 3 mm DFN packages. They are available for sampling at sample.microchip.com and for volume ordering at www.microchipdirect.com.

For more information, visit Microchip's website at www.microchip.com/MCP73833.

(067227-VII)

Are you CO sure?

If you have a Carbon Monoxide (CO) concern and need to know more, Lascar Electronics' EL-USB-CO carbon monoxide data logger could help in determining the nature of the problem.

Carbon Monoxide (CO) is a poisonous gas which is both odourless and colourless. It is produced by equipment/machinery that isn't working correctly and can be found anywhere from construction sites and furnace rooms to office blocks and homes. Lascar's EL-USB-CO data logger monitors and records CO levels in an environment over a period of time.

This can help the user to determine where and when peak levels of CO occur, allowing corrective action to be carried out to remedy the problem.

The EL-USB-CO stores over 32,000 readings and can record CO levels from 0 to 1000 ppm. Setup of the data logger is completed using the supplied EL-USB software, with the EL-USB-CO plugging directly into the USB port of a PC. Here the user can assign the logger a name, choose a sample rate (from a choice of once every: 10 secs, 30 secs, 1 mins, 5 mins), as well as determining a high-alarm



level. Once setup is complete the EL-USB-CO should be left in the environment where the study is to take place.

The EL-USB-CO is available for pur-

chase at £49.00 from the Lascar website (www.lascarelectronics.com).

(067227-III)

DAB/FM radio module

Frontier Silicon announces the launch of Naples FS2011, an integrated standalone dual-band DAB/FM radio module. The unit is a complete DAB module operating in both master and slave modes and incorporating Frontier Silicon's Apollo RF front-end, Chorus DAB baseband processor and NXP Semiconductor's TEA 5764 FM radio IC. The module is meas-

uring 35mm x 38mm x 2.7mm on a single-sided PCB.

The DAB signal processing functions and protocol stack are implemented in firmware running on the Chorus processor, which also runs the control interface to Naples. In a master configuration the module requires a power source, antenna, LCD and keypad to create a fully featured digital radio. Alternative-

ly, the module can be controlled by an existing microcontroller as a slave module via a serial port or SCB (serial control bus) compliant device allowing it to be integrated into larger audio systems. The module also supports various software features such as DAB dynamic DLS radio service text, 256 kbps decode capacity, stored presets and manual tuning when con-



figured in system applications.

www.frontier-silicon.com

(067227-I)

Mid-power 24-Vin maxi modules

Vicor announces the addition of eight mid-power Maxi DC-DC converters to the 24 Vdc input family: a 3.3-Vout, 200-W model and 300-W models at 5, 12, 15, 24, 28, 36, and 48-Vout. The modules — which incorporate Vicor's patented low-noise Zero-Current and Zero-Voltage Switching (ZCS/ZVS) topology — are appropriate for industrial or process control, distributed power, medical, ATE, communications, defence, and aerospace applications. With switching frequencies up to 1MHz, the 24Vdc family provides rapid transient response well suited for RF applications. The new products provide design-

ers who do not need the full-power capability of a 24V Maxi module with a mid-power option, with all of the functionality and configurability of the high power models. In addition, low-noise ZCS/ZVS greatly reduces the design effort and filtering costs required for power converters to meet agency conducted emissions requirements. The modules, which are available in RoHS compliant models, are a compact 117 x 56 x 12.7 mm in size, with a height above board of 10.9 mm. With these new models, the 24 Vin Maxi family now comprises 16 models with output voltages from



3.3 to 48 Vdc and power levels from 200 to 400 W. The converters operate from 24 V nominal input, with an input range of 18 V to 36 V. Efficiencies range up to 88% for the higher output voltages. These models are available in five different environmental grades, with six different pin options and three choices of baseplate. They

can be configured in any combination in Vicor's Custom Module Design System. A datasheet is available on: www.vicorpower.com/library/technical_documentation/datasheets/2nd_gen/.

www.vicoreurope.com

(067227-V)

8-bit microcontrollers with integrated Ethernet peripheral

Microchip announces a family of the world's smallest 8-bit microcontrollers with an integrated IEEE 802.3-compliant Ethernet communications peripheral. The PIC18F97J60 family is optimized for embedded applications, and has an on-chip Medium Access Controller (MAC) and Physical Layer Device (PHY).

By integrating a 10BASE-T Ethernet controller onto a 10 MIPS PIC18 microcontroller with up to 128 kBytes of Flash program memory, Microchip is providing embedded systems designers with a simple, cost-effective single-chip remote-communication solution for a wide range of applications. Microchip also offers a free TCP/IP software stack to reduce development time. Ethernet is the leading networking technology for local area networks (LANs), and it can be used to connect embedded devices through a LAN to the Internet. Ethernet's infrastructure, performance, interoperability, scalability and ease of development have made it a standard choice for such embedded communications.


Any embedded application that requires Ethernet connectivity can take advantage of the new nine-member PIC18F97J60 microcontroller family. Such applications can include Industrial Automation (e.g. industrial control, power-supply monitoring, network/server



monitoring and environmental monitoring); Building Automation (e.g. fire & safety, access control, security panels, lighting control

and VoIP intercoms). Key features of the new family include:

- Seamless Migration: add Eth-

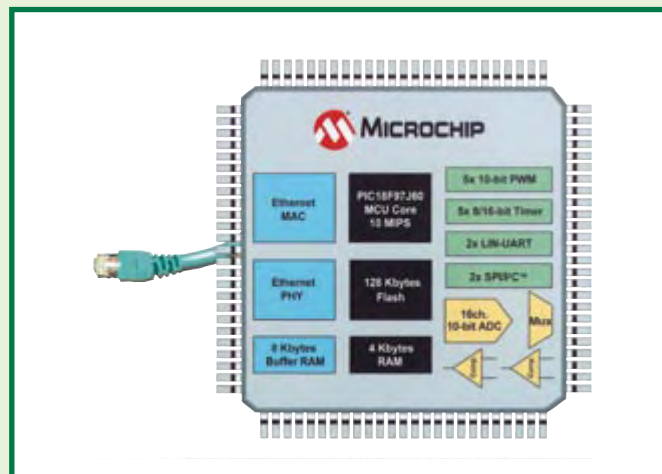

ernet to existing PIC18 designs with minimal cost and development time.

- IEEE 802.3-Compliant: on-chip 10BASE-T MAC and PHY provide reliable packet-data transmission and reception.
- Dedicated 8-kByte Ethernet Buffer: enables efficient packet storage, retrieval and modification, and reduces the demand on the integrated microcontroller.
- 128 kBytes of Flash and 4 Kbytes SRAM: to accommodate the TCP/IP stack and Web server, leaving ample space for application code.

The PIC18F97J60 PICDEM.net™ 2 Development Board (part # DM163024) has been created specifically to assist development with these new integrated devices. In addition, the latest version of Microchip's free PIC18 TCP/IP Ethernet Stack can be downloaded at www.microchip.com/tcpip. The new family is also supported by Microchip's suite of development tools, including the MPLAB® VDI Visual Device Initializer, Application Maestro™ software, MPLAB C18 C compiler and the MPLAB ICD 2 in-circuit debugger. The new PIC devices are all offered in RoHS-compliant TQFP packages.

www.microchip.com/ethernet

(067227-II)

Special Christmas Offer

3 Elektor Books/CD-ROMs

for just **£ 27.50 | \$ 52.50**

Offer valid until 1 January 2007

Excl. P&P

PC Interfaces under Windows

PC Interfaces can be used for more than just the printer, mouse, modem and joystick! While it was relatively easy to directly access PC interfaces using a DOS computer, under Windows things are not all that simple. This book (CD-ROM incl.) shows you how it can be done.

265 pages
£ 25.95
US\$ 52.00



Build your own High-end Audio Equipment

For those who cannot, or will not, pay high prices for high end equipment, a solution is offered in this book: build your own at considerable cost savings.


262 pages
£ 15.55 | US\$ 31.00



Designing Audio Circuits

How does speech, music, or, indeed, any sound get from the record, CD, or cassette tape to the loudspeaker? This book endeavours to give a comprehensible answer.


350 pages
£ 20.75 | US\$ 42.00

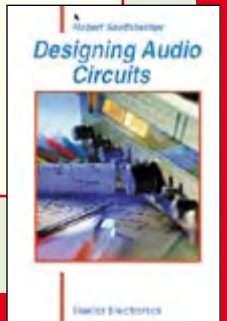

Lasers: Theory and Practice

A valuable book on the practical use of lasers. It consists of two main parts. The first deals with the fundamentals of lasers, including such topics as types of laser, modes of laser operation, wavelengths, chopping, scanning and applications. The second part contains a number of practical circuits and experiments.

180 pages
£ 20.75 | US\$ 42.00

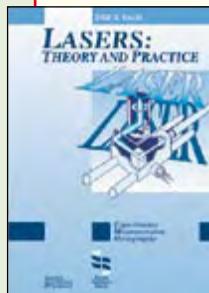

Faultfinding in Computers and Digital Circuits



Faultfinding in Computers and Digital Circuits


This book covers faultfinding not just in microprocessor systems, microcontrollers and industrial PCs, but also in consumer items such as personal computers, multimedia devices, digital television and so on.

625 pages | £ 31.15 | US\$ 63.00

Handbook for Sound Technicians

This book contains chapters on basic theory; microphones and musical instruments; various types of amplifier; loudspeakers; effects equipment; recording techniques; lighting equipment; the rehearsal room; and faultfinding and small repairs.


276 pages
£ 20.75
US\$ 42.00

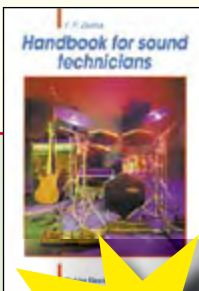

PC Service and Repair

This book provides the information you need to be able to deal with computer system faults whenever they occur. With the aid of this book, you can tackle faultfinding at various levels, ranging from the replacement of complete cards or assemblies to the identification of a single faulty component.

479 pages
£ 31.15 | US\$ 63.00

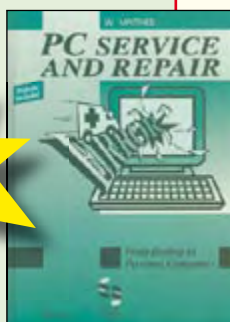

make your choice

CD-ROM Audio Collection 1 + 2

Two must-haves for the true audio lover. Each CD-ROM contains no fewer than 75 audio designs from Elektor Electronics. Using the included Acrobat Reader you are able to browse the articles on your computer, as well as print texts, circuit diagrams and PCB layouts.

£ 12.05
US\$ 21.25



Bestseller

Save £££'s

CD-ROM **Software Toolbox 2**

This CD-ROM contains software tools for, and information about, microcontrollers. Toolbox 2 gives specific attention to technical documentation about protocols, field buses, as well as modern information carriers which find increasing use. The hardware side of things is not forgotten either.



£ 12.05 | US\$ 21.25

CD-ROM **Robotics**

A large collection of datasheets, software tools, tips en tricks, addresses, Internet links to assorted robot constructions and general technical information. All aspects of modern robotics are covered, from sensors to motors, mechanical parts to microcontrollers, not forgetting matching programming tools and libraries for signal processing.


£ 12.05
US\$ 21.25



CD-ROM **ECD Edition 3**

Elektor's Components Database gives you easy access to design data for over 5,000 ICs, more than 35,000 transistors, FETs, thyristors and triacs, just under 25,000 diodes and 1,800 optocouplers. All databank applications are fully interactive, allowing the user to add, edit and complete component data.


£ 14.95 | US\$ 26.50

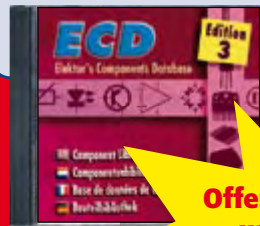

CD-ROM **Digital Circuit Library 1-2-3**

Each CD-ROM contains over 300 circuits complete with diagram and text. Zoom and print module. Fast search facility. Error-tolerant index search system. Many printed-circuit board layouts.

£ 12.05 | US\$ 21.25

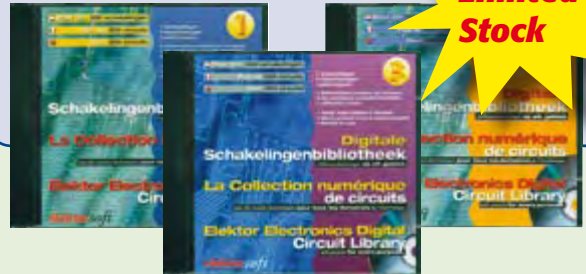

Limited Stock

CD-ROM **Elektor Electronics 2001 + 2004**

These Elektor Electronics annual CD-ROMs contain all editorial articles published in Elektor Electronics magazine volume 2001 and 2004.

The CD-ROMs are packed with features including a powerful search engine and the possibility to edit PCB layouts with a graphics program, or printing hard copy at printer resolution.

£ 16.25 | US\$ 28.75



Offer valid until 1 January 2007

No Order Form here?

No problem, you can still benefit from our offer.

Please contact us:

Elektor Electronics (Publishing)

Regus Brentford | 1000 Great West Road

Brentford TW8 9HH | United Kingdom

Telephone +44 208 261 4509 | Fax +44 208 261 4447

Email: sales@elektor.com

Christmas Presents

For the electronics hobbyist who has everything already

Do you still need help choosing gifts for others (or for yourself)? We'd like to lend you a hand with a variegated selection of interesting, fun, handy, gadget-like or simply unusual gifts. It also includes several items that people with no special interest in electronics will enjoy.



Time on the fly

The XP3 clock is a programmable digital clock that displays the time and messages hovering in the air. A set of LEDs fitted to a rod that swings back and forth at a tidy 16-Hz rate flash on and off at just the right times to create visible messages. Each message appears in a different form. You can program four individual messages, each with a maximum of 200 characters. They can be combined with the date and time

display in all sorts of ways. There are also several preprogrammed messages, in English of course.

Seen at: www.gadgethouse.nl

Hovering football

We must admit that this 'hovering football' isn't actually round. However, it's a nice alternative to the real thing for a spot of football in the living room without doing too much damage to the furniture. This is a genuine hovercraft in the form of a flattened ball. It floats on a cushion of air blown out at the bottom, so it can hover over the floor and move easily. It doesn't have any electronics – just a battery-powered motor.

Seen at: <http://smm.de>



T-shirt with graphic analyser

You're bound to attract attention if you wear this T-shirt to a disco or café. An illuminated panel in the form of a graphic analyser is fitted into the front of the T-shirt. The accompanying microphone and electronics pick up ambient sound and drive the bars of the graphic display accordingly. The analyser is powered by a detachable battery pack. The T-shirt is available in two sizes. Unfortunately, it can only be washed by hand, so you have to be prepared to handle it with TLC.

Seen at: www.bestel.nl



Solar-powered headphone radio

With this set of headphones, you have music with you wherever you go – all without batteries. An FM receiver is built into the ear shells, and it is powered by a set of rechargeable AAA cells. The cells are charged by a solar panel fitted on top of the headband. One hour of sunlight is enough for 1 to 3 hours of pleasant listening.

The headband, which also includes an integrated antenna, can easily be adjusted to fit any head size.

Seen at: www.paramountzone.com



Mini drum set

Who doesn't occasionally get the urge to have a go at being a drummer? But how many of us have a drum set at home? And of course, you have to remember the neighbours... Now there's a solution for the weekend drummer: an affordable electronic mini drum set. Several drums,

and even a cymbal, are located on a surface with the dimensions of a mouse pad. You can drum on these instruments with your fingers. Of course, it takes a bit of practice to get the hang of it. There are also several control knobs behind the drums. This way you don't have to worry about complaints from the neighbours – as long as you can resist the temptation to connect the drum set to your stereo system!

Seen at: www.megagadgets.nl





Talking toilet paper holder

This gadget is just the thing for surprising your friends and acquaintances. It generates a spoken message each time some pulls

toilet paper off the roll. You can record your own message, either serious or humorous. For instance, you could use it to remind your children to wash their hands when they're finished, or to remind adults to close the lid before they leave. As for humorous messages, that's something we'll leave up to you! The toilet roll holder has a spring-loaded middle piece, so it can be used with nearly every standard holder.

Seen at: www.bestel.nl

Flexible keyboard

With this unusual keyboard, which is not only flexible and waterproof but also features trendy blue illumination, you're immune to just about everything. It simply shrugs off coffee, bread crumbs and tobacco residues. An occasional rinse under the tap is enough to keep it looking as good as new. It will last for years if you take good care of it, and it's great with a laptop – just roll it up and pack it away.

Seen at: www.usbgeek.com



Mini UFO

If you always wanted to pilot a UFO, here's your chance. The X-UFO consists of a thin frame with four propellers, along with the control and receiver electronics you need to operate it. It is gyroscopically stabilised in flight.

The X-UFO is made from ultra-lightweight carbon fibre and EPP foam. Four LEDs (one red and three blue) not only help you keep track of the X-UFO, but also give it an unworldly appearance. The X-UFO comes with a four-channel proportional R/C unit.

Seen at: www.gadgethouse.nl



Remote-controlled golf ball

Just when you thought you'd seen it all! You may wonder how anyone came up with the idea of a remotely controlled golf ball, but it's mainly intended as a sort of practical joke. Suppose you're golfing with a friend, and he suddenly sees his golf ball making strange lurching motions. You know the answer: you swapped a remotely controlled ball for his real ball.

You can use the remote control to cause the ball to swing to the right or left while it's rolling. Just the thing for golfers with a healthy sense of humour!

Seen at: www.iwantoneofthose.com



Illuminated toilet seat

Are you always irritated by the dim lighting in the WC when you have to use it in the wee hours? And does your wife always complain that you leave the toilet seat up after you use it at night?

The intelligent LavNav toilet light puts an end to all these problems. After you fit this tiny light to the bottom of the toilet lid, it automatically illuminates the toilet bowl discreetly when you approach the toilet. And so you don't forget whether the toilet seat is raised or lowered, the lamp has two different colours. green means it's OK to sit down, while red means watch out, the seat's still up!

Seen at: www.gadgets.co.uk




Colourful loudspeakers


The Lightwave loudspeakers are small spherical loudspeakers made from transparent plastic that change colour in rhythm with the music. They also have beat detection. Listeners can choose from three different colour patterns or a specific constant colour, or they can let the colours respond to the music.

The speakers are approximately 10 cm in diameter, and the built-in amplifier delivers 5 W PMPO. They are an ideal complement to an MP3 player or a portable CD player.

Seen at: www.gadgets.uk

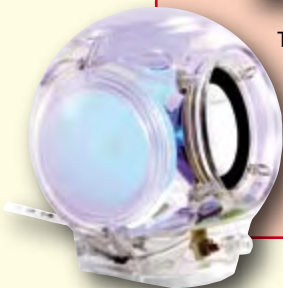

Shake those numbers!
 You're probably already familiar with pocket torches that you shake to generate the necessary energy. The same principle has now been applied to pocket calculators. The little calculator shown here has a small tube at the top with a magnet inside that can move back and forth. When you shake the calculator, a coil surrounding the tube generates enough electrical energy from the moving magnet to power the calculator for a short while. That's naturally something else than a calculator that runs on solar cells or uses water as a source of energy.
 Seen at: www.gadgets.co.uk

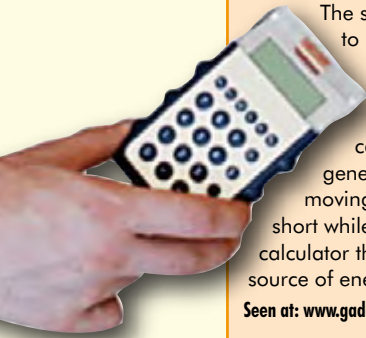

USB rocket launcher
 This article is full of all sorts of gadgets with USB interfaces, but this is really the best of the lot. This miniature rocket launcher has a rocket holder with three foam-rubber rockets. You can use the included software (Mac and PC versions) to aim the rockets horizontally and vertically and then fire them. The propulsive force is provided by several springs in the rocket holder, and the range is approximately 3 metres.
 This rocket launcher has become so popular that hackers have already developed modified software for it. Several successor models have also been sighted already.
 Seen at: www.gadgets.co.uk



Hovering globe
 It's still something special to see a metal globe hovering in the air thanks to a magnetic field. Here a bit of electronics and a coil are used to attract the globe just enough to keep it hovering in the air. Various models are available. Last year we had a very modern one, and this time we chose an 'antique' model with a nice 20-cm globe. The base of the copper-coloured frame houses a full-fledged microcontroller that adjusts the magnetic field 16,000 times per second.
 Seen at: www.gadgets.co.uk



Roll-up keyboard
 This keyboard (the musical kind) has 49 keys and a USB port (which is where it draws its operating power) along with another convenient feature: you can roll it up. That's something keyboard players who are familiar with normal 'hardcase' keyboards will certainly appreciate. Especially since this flexible USB keyboard can hold its own against its space-gobbling cousins. The keyboard features eight percussion instruments, demo songs, vibrato and other effects, a metronome, and much more. You can also compose your own rhythms if you want. The beat can be adjusted from a sedate 40 beats per minute to a nerve-wracking 208.
 Seen at: www.usbgeek.com




USB slippers
 If you often sit in front of your computer until the wee hours, it can get pretty uncomfortable sometimes, especially during the cold season. However, you can avoid cold feet with these USB-powered electric slippers. These fluffy slippers can be connected to any computer with a USB port (PC or Mac) or even a game console. The heating element is washable, and it warms the slippers to a maximum temperature of 48 °C. Now that's comfort! One caution: make sure your computer has enough USB ports and a hefty power supply, since otherwise it probably won't be able to handle all these USB gadgets.
 Seen at: www.usbgeek.com



High-tech ballpoint pen
 This is something we all need! Now you don't have to chew on your pencil during a drawn-out press conference. Instead, you can listen to relaxing music with this high-tech MP3 ballpoint pen. Thanks to its generous storage capacity of 512 MB or 1 GB, the pen is also suitable for long meetings. After you've listened to all the music, you can simply switch on the built-in FM radio. If somebody happens to say something interesting, the built-in microphone will pick it up nicely for you, so you don't have to miss anything. The rechargeable lithium-ion battery is good for 7 hours of operation.
 Seen at: www.usbgeek.com

Electronic Lederhose
 This pair of electronic Lederhose (leather shorts) comes from the Bavarian clothing manufacturer Lodenfrey. This traditional south-German garment is fitted with an MP3 player with 512 MB of memory and a built-in (or should we say sewn-in) control panel. It also has a handsfree function for your mobile phone. Now you can slap your thighs, listen to music and make phone calls all at the same time.
 Seen at: www.lodenfrey.de



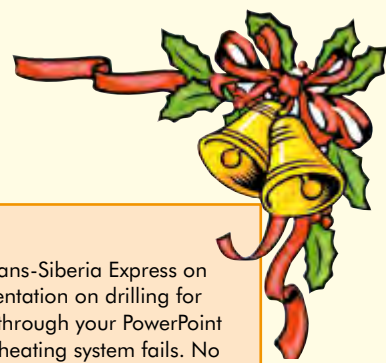

Pleasant scents

You know the type: glued to the computer day and night while churning out code at the rate of several pages a minute. This talent is often accompanied by sleep deficiency, personal hygiene that leaves something to be desired, and a penetrating musty odour. To help camouflage the aroma of canned cola and ambulant pizza leftovers, we recommend this USB-powered aroma dispenser as a suitable gift. Citronella and anise, camphor and orange-peel oil are mind-expanding, so they help with debugging.

Seen at: www.usbgeek.com



Heated gloves

Suppose you're sitting in the Trans-Siberia Express on your way to an important presentation on drilling for oil. Just when you want to run through your PowerPoint presentation again, the train's heating system fails. No problem – you simply slip on these USB-powered heated gloves and carry on. Incidentally, they match nicely with the USB slippers described in this article. However, in this case we recommend that you at least purchase a reserve battery, since otherwise you could easily find yourself sitting with cold feet, cold hands, and a blank screen.

Seen at: www.usbgeek.com



Overclock your brain

Overclocking CPUs is old news by now – the new rage is overclocking the grey matter between your ears. This gadget provides especially intensive training of your grey nerve cells. With this device and a bit of practice, you can significantly boost the 'clock frequency' of your brain. It trains your assimilation speed. We've heard that our boss has already ordered a thousand or so.

Seen at: <http://shop.elv.de>

Water-powered calculator

Following in the steps of pocket calculators powered by AC adapters, batteries and solar cells comes the most ecologically responsible model yet. It doesn't run on alcohol, but instead on water, which explains its name: H₂O. It goes for several weeks on just a few drops. When it doesn't want to work any more, just fill it up under the tap and you're all set for several more weeks. Handy, ecological, and economical – and above all a lot of fun!

Seen at: www.ledindon.com



Binary clock

Seen enough of those omnipresent LCD clocks that show the time in hours and minutes with painstaking precision? How about a clock that displays the time using blue LEDs, and what's more in binary form? That makes checking the time a mental exercise, since the six columns correspond to hours, minutes and seconds, each in the form of tens and units. The time displayed by the clock in the photo is 12 hours, 1 minute and 47 seconds. The LED brightness can be set to three different levels. Of course, as an electronics whiz you'll master this new way of telling time in only a couple of minutes.

Seen at: <http://www.bestel.nl>



Cubite speaker and USB hub

We'd be lost without USB in this world, and USB hubs are at least equally indispensable. The Cubite Speaker USB hub is a stylishly fashioned box that houses not only an excellent speaker for your PC, but also a USB hub with ports for your webcam, MP3 player, memory stick and digital camera. The speaker has a large volume knob and two smaller knobs to adjust the treble and bass. It is powered from the USB port, so it doesn't need an external power supply (or any additional software).



Seen at: www.iwantoneofthose.com

H Racer: a hydrogen-powered car

The first car fully powered by hydrogen: that's the technology of the future! Unfortunately, this model is rather small, but the 21st century is still young. The H Racer is a full-fledged demonstration of a hydrogen propulsion system. A solar cell supplies the energy to produce the hydrogen (H), and the transparent housing lets you easily see what happens: blue LEDs illuminate the tiny bubbles of oxygen (O₂) that are expelled from the water reservoir.

Seen at: www.latestbuy.com.au



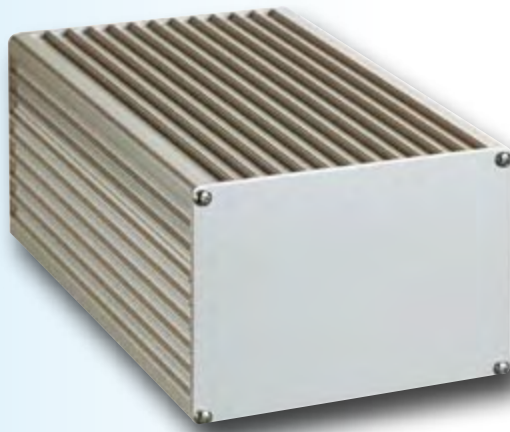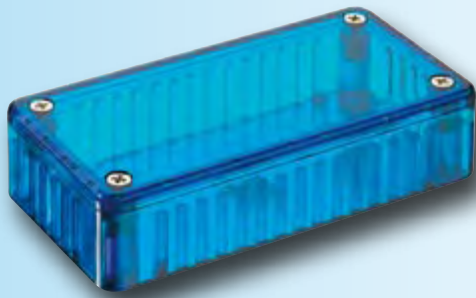

Tightly Packed

Enclosures and front panels

Thijs Beckers

There are an incredible number of options these days for the safe 'packing up' of electronic circuits. Open any catalogue from any well-known mail-order company and you will get an impression of the extensive range on offer. This article gives an overview of the different types with their particular characteristics and provides hints as to how you can make a professional looking front panel yourself.

From an economic and marketing perspective, the enclosure, including the front panel, of commercial equipment is very important for the manufacturer. Equipment that does not look attractive will sell poorly, of course, and is nearly impossible to extol its virtues in advertisements. So it is logical that much time and effort is spent on the design of these enclosures. An additional consideration is the ergonomics of equipment that has many operating controls. The design of the enclosure is then already taken into account during the development of the circuit.

This is usually not the case for prototypes, small (hand-made) production runs and home-built circuits. Of course, the marketing aspect is not a consideration here either. Specific characteristics, such as extra heavy-duty waterproof and explosion resistant boxes, are a little bit over the top for the average home project. A standard box is usually good enough. But that does not distract from the fact that appearance and function certainly also do play a role in your own circuits. With a little bit of searching for a nice and appropriate enclosure and a little bit of ef-

fort for a front panel you can definitely make a nice looking piece of equipment that would not look out of place when displayed in the average electronics shop window. With a clean design and your own logo on the front panel it will look like the real thing.

Making a choice

For prototypes you usually choose from a few types of enclosures that may optionally conform to some standard, (see inset *Industrial Enclosures*). For each design you will look at what type of enclosure suits best. There are a number of different types of enclosures that may be categorised as follows:

1. 19-inch enclosures, which can be easily built into, or removed from, a standard rack or industrial box.
2. Enclosures that are deliberately sized for the common 'Euro format' PCB.



3. Console enclosures with a tailored front panel or (sloping) top for control or mixing panels.

4. Small enclosures with a built-in mains plug, which plugs into a power point just like a mains power adapter.

5. Enclosures for handheld applications, such as multimeters.

6. Enclosures for DIN rail systems, which are commonly used in an industrial environment.

A few of the factors that are important for the type of enclosure are of course the size, safety, construction material, method of mounting and – mainly important in industrial applications – the NEMA and/or IP classification [1].

The size obviously depends on the components that have to fit in the enclosure, together with the connection and mounting options, internal and external access, thermal conditions and potential future extensions. The material selected needs to be able to withstand the conditions that the enclosure will be subjected to at the location at which it will be used. Considerations are corrosion resistance and rigidity requirements. The NEMA and/or IP classification is an industrial standard for the protective characteristics of an enclosure. **Tables 1** and **2** in the inset *Industrial Enclosures* give an overview of these two common protection classifications.

Machining

The internal electronics will, in all likelihood, be connected to the outside world via cables and plugs. This requires a number of plugs and contact points, which usually requires some machining of the enclosure.

In addition, the operating buttons need to be given a logical position, generally on the front panel. The front panel usually demands the most attention. To make an attractive aluminium front panel, complete with labelling, requires a fair amount of equipment (drills, routers, screen printer, sander, etc.) and the process is not easy. Also, if you only need to do these things every once in a while it is not worthwhile to invest in the required equipment. There are a number of companies that specialise in the manufacture of front panels, such as the German company Schaeffer [2], the American Internet company eMachineShop [3], the English company CTL-Components [4], the international company Elma [5] and the Dutch company Antronics [6]. Schaeffer and eMachineShop even offer their own (free!) software, which makes it easy to draw your own design. This design can then be sent to the manufacturer who will then machine and

screen print the front panel. In this way you can obtain a professional looking front panel.

Do it yourself

The specialist equipment that is required for this machining has its price, of course. This is often clearly noticed from the amount of money you have hand over for a custom manufactured front panel. A cheaper solution is the self-adhesive, transparent film that can be printed with a laser printer. This film gives only limited protection from scratches and gives a somewhat dull result. The latter can be improved with some plastic spray.

In addition to the special film for laser printers there is also the overhead transparency for inkjet printers. This

Case manufacturers

Manufacturer	Website
ABB	www.abb.nl
APW	www.apw.com
Bernstein	www.bernstein-ag.de
Bopla	www.bopla.de
Boss	www.boss-enclosures.co.uk
Box	www.boxenclosures.com
Cooper	www.b-line.com
Deltron Emcon	www.deltron-emcon.com
Dold	www.dold.com
Erni	www.erni.com
Eurobox	www.euroboxenclosures.com
Fibox	www.fibox.nl
Himel	www.himelenclosures.com
Hammond Manufacturing	www.hammfmg.com
Lawtronics	www.lawtronics.co.uk
Monacor	www.monacor.nl
Moeller	benelux.moeller.net/nl
OKW	www.okw.com
Pactec	www.pactecenclosures.com
Retex	www.retex.es
Rittal	www.rittal.nl
Rolec	www.rolec.de
ROSE Systemtechnik	www.rose-pw.de
Sarel	www.sarel.nl
Schroff	www.schroff.co.uk
Serpac	www.serpac.com
Spelsberg	www.spelsberg.nl
TEKO	www.tekoenclosures.com
VERO	www.vero-electronics.com
Weidmüller	www.weidmuller.nl

Table 1: Description degrees of protection to DIN EN 60529 (VDE 0470) (IP-type)

Number	Degrees of protection for people and solid objects (first number)	Degrees of protection against water (second number)
0	No protection	No protection
1	Protection against solid objects greater than 50 mm diameter	Vertically falling drops of water do not cause damage
2	Protection against solid objects greater than 12 mm diameter	Drops of water with up to 15° from vertical do not cause any damage
3	Protection against solid objects greater than 2.5 mm diameter	Drops of water with up to 60° from vertical do not cause any damage
4	Protection against solid objects greater than 1 mm diameter	Splashing water from any direction does not cause any damage.
5	Completely protected against accidental touch, partially against dust	Low pressure water jets from any direction do not cause any damage
6	Completely protected against accidental touch and against dust	Strong jets of water do not cause any damage
7	-	Water does not cause any damage if the enclosure is submerged by 0.15-1 m
8	-	Water does not cause any damage if the enclosure is submerged by a specified amount
9	-	Water under high pressure from any angle does not cause any damage

Table 2: NEMA standard for enclosures

NEMA standard	Description
NEMA 1	Enclosures constructed for indoor use to provide a degree of protection to personnel against incidental contact with the enclosed equipment and to provide a degree of protection against falling dirt.
NEMA 2	As NEMA 1, and to provide a degree of protection against dripping and light splashing of liquids.
NEMA 3	Enclosures constructed for either indoor or outdoor use to provide a degree of protection to personnel against incidental contact with the enclosed equipment; to provide a degree of protection against falling dirt, rain, sleet, snow, and windblown dust; and that will be undamaged by the external formation of ice on the enclosure.
NEMA 3R	As NEMA 3, except no protection against dust
NEMA 3S	As NEMA 3, and in which the external mechanism(s) remain operable when ice laden
NEMA 4	As NEMA 3, and hose-directed water and that will be undamaged by the external formation of ice on the enclosure
NEMA 4X	As NEMA 4, and protected against corrosion
NEMA 5	As NEMA 2, but protection against airborne dust, lint, fibers
NEMA 6	As NEMA 4, and protected against water during occasional temporary submersion at a limited depth
NEMA 6P	As NEMA 6, but protected against water during prolonged submersion at a limited depth
NEMA 7	Enclosure for indoor use at locations specified as Class I, Group A, B, C and D (refer National Electrical Code, NEC) withstands pressure caused by internal explosion and prevents the ignition if explosive gasses. Also internal heat does not cause danger to the environment
NEMA 8	As NEMA 7, enclosure submerged in oil
NEMA 9	Enclosures for indoor use at locations specified as Class II, Group E, F en G (refer NEC). Protected against dust, internal
NEMA 10	over-heating does not create an explosion hazard for surrounding gasses
NEMA 11	Suitable for use in corrosive environments, enclosure submerged in oil
NEMA 12	As NEMA 5, for industrial use
NEMA 12K	As NEMA 12, with knock-outs
NEMA 13	As NEMA 5, also protected against oil and non-corroding cooling fluids

film is printed on the reverse side. First stick clear, double-sided adhesive foil (available in stationery shops) to the front panel and then the mirror-printed film. In this way the ink is also protected against scratches. In colour and using at least 300 dpi it will also look good and is not expensive.

Before sticking the film to the front panel, you first have to make the holes in it. Tip: it is better to deburr the front side of small holes once the film is in place. The opening in the film will then have the correct diameter at the same time. You can easily cut square or large openings in the film with a sharp knife.

On (ugly) plastic front panels you can use the standard sticker sheets for the front panel layout. Or alternatively, you can use standard paper and the above-mentioned double-sided adhesive foil. The colour of the paper will obviously determine the colour of the front of the enclosure.

Tip: a 'membrane keyboard' can be made quite easily with an additional printed film between the front panel and the adhesive foil. Behind the printed keyboard is an opening in the front panel that could contain miniature pushbuttons. The front panel can be made from cheap materials, of course.

Drilling

To drill small round holes, twist drills are obviously the best choice. A good drill stand is very handy and a drill press is ideal. If you mark the locations of the holes with a centre punch then the tip of the drill will not wander if you are drilling free-hand. Large, round holes are best made by first drilling a smaller hole and then enlarging it with a reamer.

Rectangular openings are a little harder. With simple tools it is best to proceed as follows: drill, within the cutout, a hole that's large enough for the saw blade of a hacksaw. Now cut the material to within about 0.5 to 1 mm of the desired opening. Remove the last little bit with a file. If you are using thin sheet for the enclosure it is better to use a jigsaw for this, instead of a hacksaw. Sandwich the thin sheet with thin plywood or something similar, that you cut at the same time. In this way the thin sheet will not bend. Leave the plywood in place also when filing.



For very narrow openings (for slide potentiometers, for example), drill a number of small holes next to each other (with a good drill press and a short drill these holes can even overlap). With a little key file you can then remove the remaining unwanted material.

A nice result

Both in industry as well as for your own applications, the purpose of the enclosure is mainly to protect the electronics components from permanent damage caused by moisture, chemicals and dust. At the same time it provides a protective function for the environment. This can be protection to prevent the accidental touching of hazardous voltages but also for EMI.

A second good reason to package a circuit is to make it look more attractive. The average user is not fascinated with a collection of components on a circuit board. A good front panel layout will also make it immediately obvious what each operating button does and how to use the equipment.

In industry there is often great emphasis on the physical appearance. That is why specifically designed enclosures are often used, that are evaluated at an early stage of the


Industrial enclosures

The material from which an enclosure is made determines its physical properties for the most part. Plastic is usually chosen for portable applications, because of its weight and wear resistance. In other applications other factors such as mechanical strength, electrical and thermal resistance and fire resistance are more important. **Tables 1 and 2** show the protection classification that an enclosure can offer for two common standards.

To provide protection against EMI, the enclosures can be coated with, for example, carbon, aluminium or copper. This is very important, in particular for sensitive electronics, if the circuit is to operate without problems. Up to 1 MHz you can use electronic filters and metal screens. Above that frequency a decent Faraday cage is required. To also keep out magnetic fields, an aluminium or steel sheet enclosure is inadequate. This application requires special μ -metal.

A number of common materials for plastic enclosures are polycarbonate, polystyrene, polypropylene and ABS. Some enclosures are transparent for IR. This is very handy for remote controls, for example. And there are many more special properties along these lines.

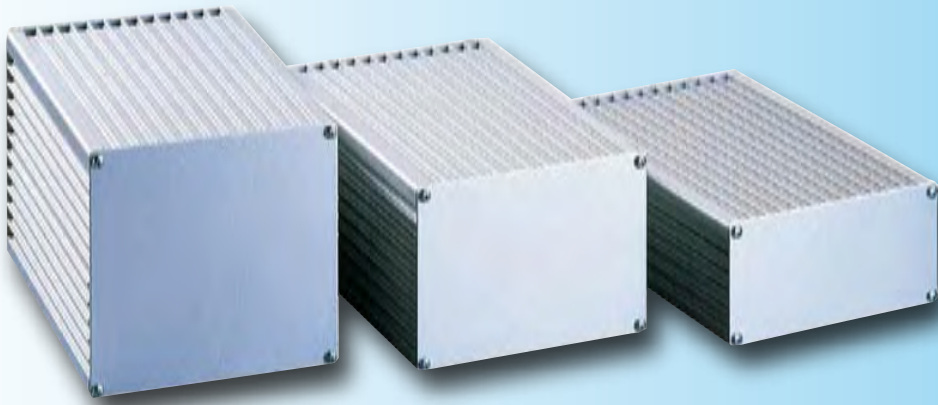If we select a metal enclosure, we can make a distinction between aluminium, galvanised steel sheet, stainless steel and a number of other materials. A metal enclosure has the advantage that it will largely block electric fields, of course.



overall design. The initial costs of a newly designed enclosure may be quite high, but large numbers reduce the price per enclosure considerable. Buying large numbers of standard enclosures would be much more expensive in the end, because the various holes still need to be machined.

If you are working with prototypes then the considerations are completely different of course. It is often the case that the circuit is already finished and you only need an enclosure that will fit everything. With the directions given above, it is entirely possible to make a front panel that does not have to look inferior to that of a professional piece of equipment.

(060298-1)

All photographs: Conrad Electronics.

Weblinks:

- [1] www.nema.org
- [2] www.schaeffer-ag.de
- [3] www.emachineshop.com
- [4] www.cfl-components.com
- [5] www.elma.de
- [6] www.supermoduul.nl

GLOSSARY

- ABS:** Acrylonitrile Butadiene-Styrene. Rigid man-made fibre with very little tendency to shrink.
- EMI:** Electromagnetic Interference. Undesired interference from electromagnetic fields.
- NEMA:** National Electronic Manufacturers Association, American association which represents the designers and manufacturers of electronic equipment.
- IP:** Ingress Protection, protection against access or touch.
- Stainless Steel:** alloy of iron, chromium and carbon which forms a layer of chromium-oxide on the outside so that the material does not corrode any further.
- μ-metal (mu-metal):** Nickel-iron alloy with 2% copper and molybdenum with a very high magnetic permeability. As a result it is very suitable for blocking magnetic fields.

Advertisement

PCBs in 24 hours from £30.00

www.PCBTrain.com

Tel: 01635 40347
 Fax: 01635 36143
 e-mail: circuits@newbury.com.co.uk

Newbury Electronics Ltd
 Faraday Road Newbury Berks RG14 2AD
www.newburyelectronics.co.uk

Approvals: ISO 9002/UL

ANDRE LAMOTHE'S
XGAMESTATION
 LEARN STEP-BY-STEP HOW TO BUILD AND DESIGN YOUR OWN VIDEO GAME CONSOLE!

Designs Inspired by the Atari 800/2600, Sinclair ZX Spectrum, Apple II & Commodore 64!

Parallax SX Key Compatible

INCLUDES:

- Tools, Demos & Utilities!
- Great for Hobbyists AND Students!
- The Fun Way to Learn Embedded Systems!
- Fully Assembled XGS Micro Edition Unit!
- Complete Software Development KIT!
- eBook on Designing the XGS Console!
- Cables and Power Supply included!

WWW.XGAMESTATION.COM
 PH: 925.736-2098 | SUPPORT@NURVE.NET

NURVE NETWORKS LLC
 2032 CAMINO ARROYO WEST
 DANVILLE, CA 94506 USA

NEXT MONTH IN ELEKTOR ELECTRONICS

Multi-Purpose 3D Milling Machine

Ready to go kit specially for Elektor readers

In next month's issue, Elektor – in cooperation with a renowned manufacturer – presents an extraordinary project many readers have eagerly awaited for many years: a real 3D milling machine for home construction from a kit.

taining all metal parts (see photograph), the stepper motors, two ready-assembled circuit boards for the drive electronics, a spindle motor with the associated clamping device and a base plate. The kit comes with special control software that's remarkable for its user-friendliness and general structure. All this is supplied to you no less than 700 pounds (approx. 1,000 euros) cheaper than a comparable instrument. Thanks to the article in the January 2007 issue and the supplied manual, construction of the Elektor Milling Machine is straightforward. Our serious advice is not to miss this unique project in next month's issue!

(060232-a)

Although we can't go into details right now, we also can't resist printing a photograph of all metal parts that go into building the **Elektor 3D Milling Machine**. Tell us if we're wrong when claiming that this is the first affordable tabletop milling machine for anyone doing precision mechanical work, be it for electronics, electromechanical applications or modelling. The machine is versatile in that it can be used not just for the production of front panels and 3D models, but also to mill your own PCBs at home, at incredible precision. The net X-Y working surface of the milling machine is 300x400 mm, while the Z (vertical) range is specified as 100 mm.

A complete kit

The Elektor 3D Milling Machine comes as a comprehensive kit con-



Shortwave Cap

0-30 MHz SSB/CW/FM/AM/DRM based on DDS and RISC

Gert Baars

As a special treat for all radio amateurs we present a general-coverage AM/FM/SSB receiver with a wide range of features, which uses a DDS chip in the VFO section and also has a DRM output that can be fed into a computer. The receiver is controlled by a modern 8-bit Atmel RISC processor. The frequency readout is on a clearly legible 7-segment LED display.

This receiver can be seen as the successor to the receiver published in January 1999. The experience gained with this predecessor (which, incidentally, has given a lot of listening enjoyment to many constructors), has been used to develop a more advanced RF receiver.

The best parts of the original design have been kept, such as the Intermediate Frequency (IF) and double conversion superheterodyne sections. This new receiver also has some new functions up its sleeve. For example, there is a DRM output that can be fed to a PC for decoding. The tuning resolution has also been improved to provide better fine-tuning, for example for SSB reception. This makes the frequency readout more precise and a BFO is no longer necessary.

Some thought has also gone into the aerial input stage, where an active input circuit makes the need for a long wire aerial superfluous.

We've also used a number of contemporary components, such as a DDS chip that is used as a VFO; the receiver is controlled by a modern 8-bit Atmel RISC processor.

In the design our preference went to 7-segment LED displays for the frequen-

cy readout, which look better and are easier to read than a standard LCD.

This receiver has three switchable bandwidths, each of which is optimised for use with one of the possible reception modes (AM, FM, USB, LSB or DRM).

The sensitivity and the ability to deal with large input signals have been improved for the reception bands of this receiver, largely through the use of a diode-ring mixer as the first mixer.

The receiver itself generates very little noise. This can be clearly heard when you aren't tuned into a station and connect an aerial: the noise then increases markedly.

A sensitivity better than 1 μV makes little sense at lower frequencies (roughly below 7 MHz), since it isn't the weak signals that make reception difficult, but rather the strong signals that swamp the others. A higher gain just doesn't make sense under these circumstances. Furthermore, you should find that most signals in that frequency range are strong enough to be picked up, even with a telescopic aerial.

In a nutshell, this is a receiver that is suitable to pick up all broadcast and amateur bands between 0 and 30 MHz. The ease of operation, its various functions and its performance are guaran-

teed to provide you with many hours of listening enjoyment.

Block diagram

The block diagram (**Figure 1**) starts with the aerials. The internal aerial is followed by a high impedance amplifier with adjustable gain. This amplifier isn't required for an external aerial. Directly after the aerial switch is a low-pass filter with a corner frequency of 30MHz. This suppresses any possible image frequencies and other unwanted signals. Following this is the first mixer. Its purpose is to convert the range of 0 to 30 MHz into 45 MHz. For this we require a VFO frequency of 45 to 75 MHz. A first IF of 45 MHz is a good choice because the first image frequencies are 90 MHz away, which make them easy to suppress.

The VFO signal is produced by a DDS generator. More details on its operation can be found in the DDS RF Signal Generator article that was published in the October 2003 issue. The reference frequency for this DDS is obtained by multiplying the 10 MHz crystal oscillator frequency by a factor of three to obtain 30 MHz. Inside the DDS a PLL multiplies this signal a further 6 times, so that the internal reference frequency

ture



becomes 180 MHz. Normally the maximum output frequency of the DDS should be around 40% of this reference frequency. But if we add a better band-pass filter at the output it is possible to increase this figure somewhat.


The DDS can now produce frequencies in 0.04 Hz steps. The required 100 Hz resolution therefore isn't a problem. The DDS is controlled by a microcontroller that also takes care of driving the frequency readout, the scanning of the keypad and a rotary controller for tuning.

A number of extra I/O lines take care of the selection of the audio bandwidth and reception mode (FM/AM/LSB/USB).


After the first mixer is the first IF filter, which has a bandwidth of 15 kHz. This bandwidth determines the maximum possible bandwidth of the receiver. This filter suppresses the image frequencies of the second mixer. It also removes any other unwanted by-products from the output of the first mixer. The signal now arrives at the second mixer. This converts the signal into an IF of 455 kHz. It does this using a fixed local oscillator frequency of 44.545 MHz. A frequency of 455 kHz was chosen because this low frequency can be easily amplified, and also because

Specifications

- Double conversion superheterodyne receiver - first IF 45 MHz, second IF 455 kHz
- Microcontroller control of the DDS generator and other functions
- Tuning range of 0 to 30 MHz in steps of 1 kHz or 100 Hz
- DRM output, suitable for connection to a PC soundcard
- Audio bandwidth of 3, 6 or 15 kHz, dependent on the reception mode
- Keypad with 16 keys for inputting the frequency, mode and bandwidth
- Memory for 64 frequencies, including bandwidth and mode
- Synchronous detector for AM
- Quadrature detector for FM
- Product detector for SSB
- Built-in adjustable input amplifier for a telescopic aerial
- Approximate sensitivity of 1 to 2 μV (without preamp)
- Supply voltage of 13 to 15 V, max. 650 mA

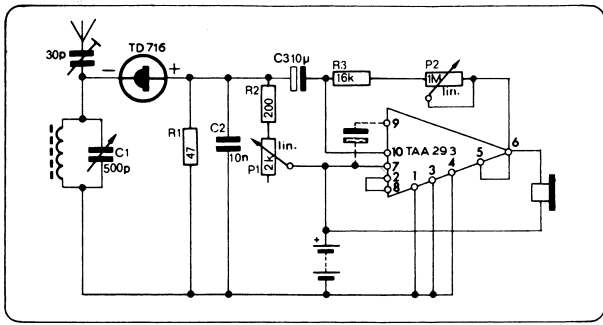

Back in time

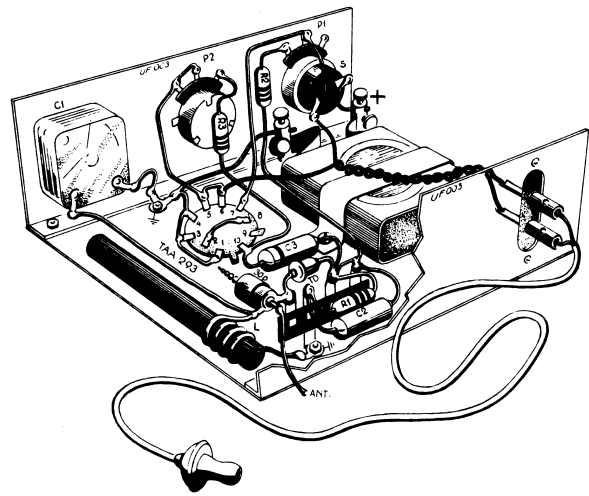

In the early days of Elektor Electronics many types of receivers were published on a regular basis. Due to the relatively high cost of semiconductors in those days these receivers were usually fairly simple designs. As a comparison we'll show you a shortwave receiver that was published almost 40 years ago in *Elektuur* magazine. The use of a tunnel diode in this design is of particular interest because it was an unusual component at the time. The construction method was nothing like what we expect these days: some soldering pins and wires were used to connect all the components together because it was quite difficult at the time to produce a PCB.

(Note: referring article not available in English)

there are many inexpensive but good-quality filters available for this much-used frequency.

The gain of the second mixer can be adjusted automatically or manually. To prevent overloading the receiver when very strong SW signals are picked up via a wire aerial we had to add a type of AGC circuit. Manually reducing the gain can improve the clarity of SSB signals in the amateur bands, because this reduces the QRM.

After buffering the signal it reaches three switches that select one of three filters, each with a different bandwidth. These switches are controlled by the microcontroller.

The three bandwidths in question are 3, 6 and 15 KHz. 3 kHz is suitable for SSB, 6 kHz for AM and 15 kHz for FM and DRM.

After another buffer is the IF amplifier. This actually consists of two amplifiers, each with an adjustable gain. This combination can provide a variable gain up to 80 dB, which is sufficient to keep the output signal level of the IF amplifier constant for both weak and strong signals. An AGC circuit is used to adjust this gain automatically. This adjustment follows the signal fairly quickly, for example to suppress the fading of AM signals. But for SSB reception it is made to react more slowly. The fast 'attack' and slow 'decay' of this AGC circuit improves the audio quality of SSB and CW signals.

The DRM detector takes the IF signal before it reaches the IF amplifier. This is because we don't need much amplification of the signal for this output. The DRM transmitters are powerful enough to produce a few hundred

mV_{pp} before the IF amplifier. This also avoids any noise from being introduced by the extra amplifiers.

The DRM detector consists of a product detector with a local oscillator of 467 kHz. The difference between this and 455 kHz is 12 kHz, which is filtered before being made available at the DRM output. The 10 kHz wide signal now covers frequencies between 7 and 17 kHz, which is exactly what is required by the DRM program, Dream. An AGC circuit is not really necessary for DRM because the soundcard and the Dream program can cope with widely varying signal strengths.

Following the IF amplifier are the AM, FM and SSB detectors. The AM demodulator used here is a variation on the well-known synchronous detector. The principle of operation is that the AM signal is multiplied by an unmodu-

Internal and external aerial

This receiver has the facility to accept two different aerials, each of which is suitable for different frequency bands.

Since even a suspended 20-metre length of wire has a higher impedance at low frequencies, an external aerial will work better than an internal one down to about 500 kHz. For lower frequencies it is better to switch to a telescopic aerial, which also has a high impedance, but is only very lightly loaded by the pre-amplifier.

The external aerial can be a 10 to 20 metre length of wire, suspended between 2 isolators, which in turn should be half a metre away from their mounting points. These isolators can be easily made from a length of PVC tubing. Two pieces around 20 cm long, with holes drilled at the ends are perfectly suitable. There is nothing special about the wire used for the aerial, as long as it can withstand strong winds and heavy rain.

We would advise against connecting an aerial longer than about 1 metre to the pre-amplifier. This can result in distortion and other interference. You would also pick up a lot of noise. A telescopic aerial or a 50 cm length of wire works perfectly well.

lated signal with exactly the same frequency and phase. This signal can be extracted using a PLL with a slow control loop, which keeps the frequency and phase intact should the AM signal momentarily fade. This results in less distortion than would otherwise occur when the signal fades. It is however also possible to extract the mix signal directly from the input signal as long as the modulation components are removed first. This is easily done with the help of a limiter. This limiter provides a mix signal with a constant amplitude. This results in good quality AM reception and provides better resistance to distortion caused by fading (which occurs in diode detectors). We have used a quadrature detector for

FM signal is multiplied by the same signal, but with a phase shift. This phase shift is exactly 90 degrees at the IF, but increases/decreases for an increase/decrease in the input frequency. The multiplier has a corresponding increase/decrease in its output voltage. A balanced multiplier is in fact very similar to an EXOR phase detector. The SSB detector is a product detector. If we multiply the USB or LSB signal with another signal that differs in frequency by 1.5 kHz we obtain the audio signal. Note that the first mixer creates a mirror image of the spectrum because we're using high-side injection, so USB becomes LSB and vice versa. The local oscillator used here is controlled via the microcontroller to

This comes in very useful when receiving SSB and CW signals. The corner frequency can be adjusted from about 500 to 3500 Hz.

To reduce interference from hum and other low-frequency noise a high-pass filter is also included, with a corner frequency of 300 Hz.

The last stage is an audio power amplifier. This has sufficient output power to drive a 2 W loudspeaker.

Schematic

We should now be familiar with the general design of the receiver. This makes it a lot easier to interpret the circuit diagrams in **Figures 2, 3 and 4**, and not be alarmed by the large

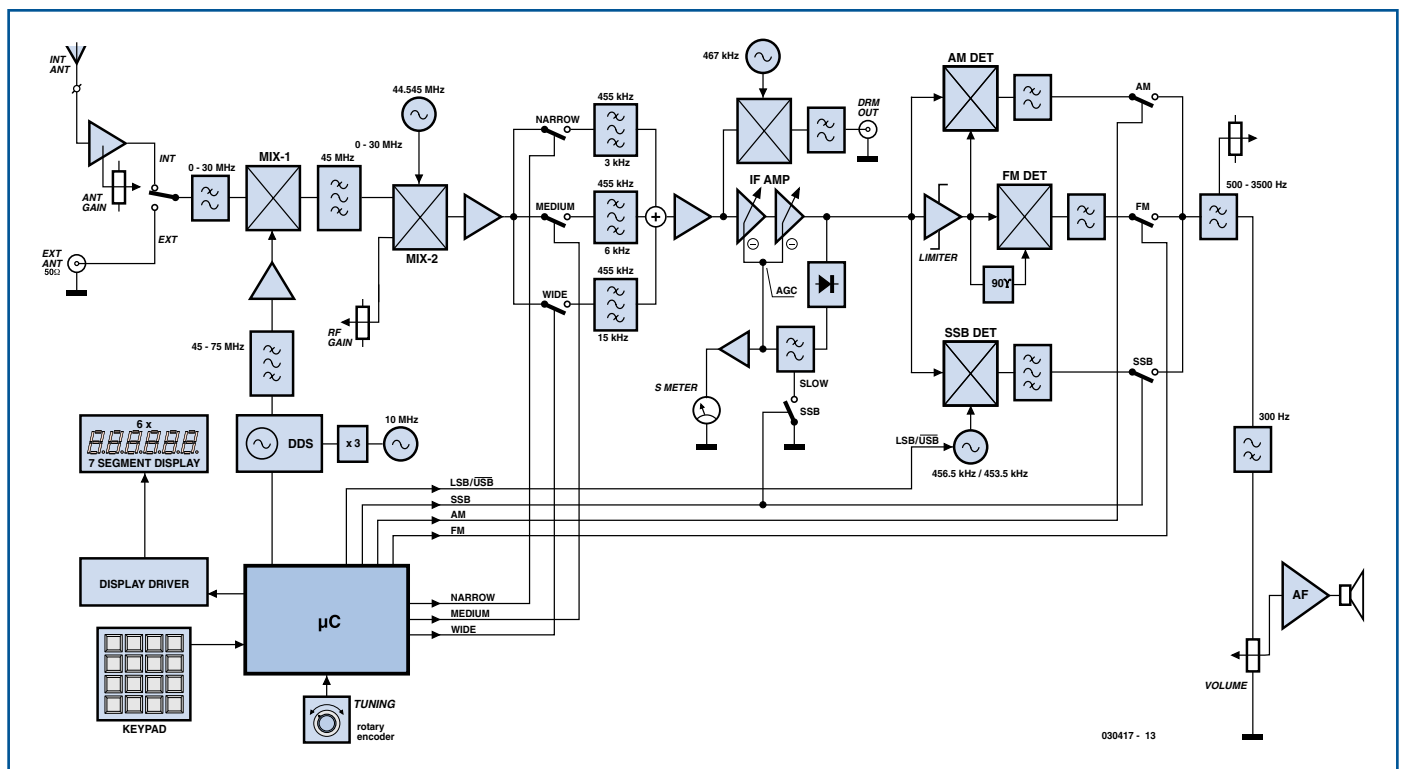


Figure 1. The block diagram for the shortwave receiver is fairly elaborate. At the bottom-left you can see the DDS generator and the microcontroller.


the FM demodulator. This type of detector is well known for the good quality audio it produces. The limiter used in the AM section is also used to supply a constant amplitude signal to the FM demodulator. This helps to avoid distortion caused by very strong input signals. It also suppresses AM noise components, which could overload the detector if their amplitude was too large. The overall result is a much better signal to noise ratio. The actual operation of the quadrature detector is quite straightforward. The

produce either 456.5 or 453.5 kHz. This way the selection can be made via the keypad.

The microcontroller selects the required mode with the help of analogue switches that follow each of the detectors. Since the microcontroller controls both the mode and the bandwidth it can automatically select the appropriate bandwidth for each mode. After the switches is an adjustable low-pass filter with a steep cut-off. This suppresses whistles and other interference caused by nearby stations.

number of components. The blocks shown in Figure 1 can be found in the diagrams quite easily.

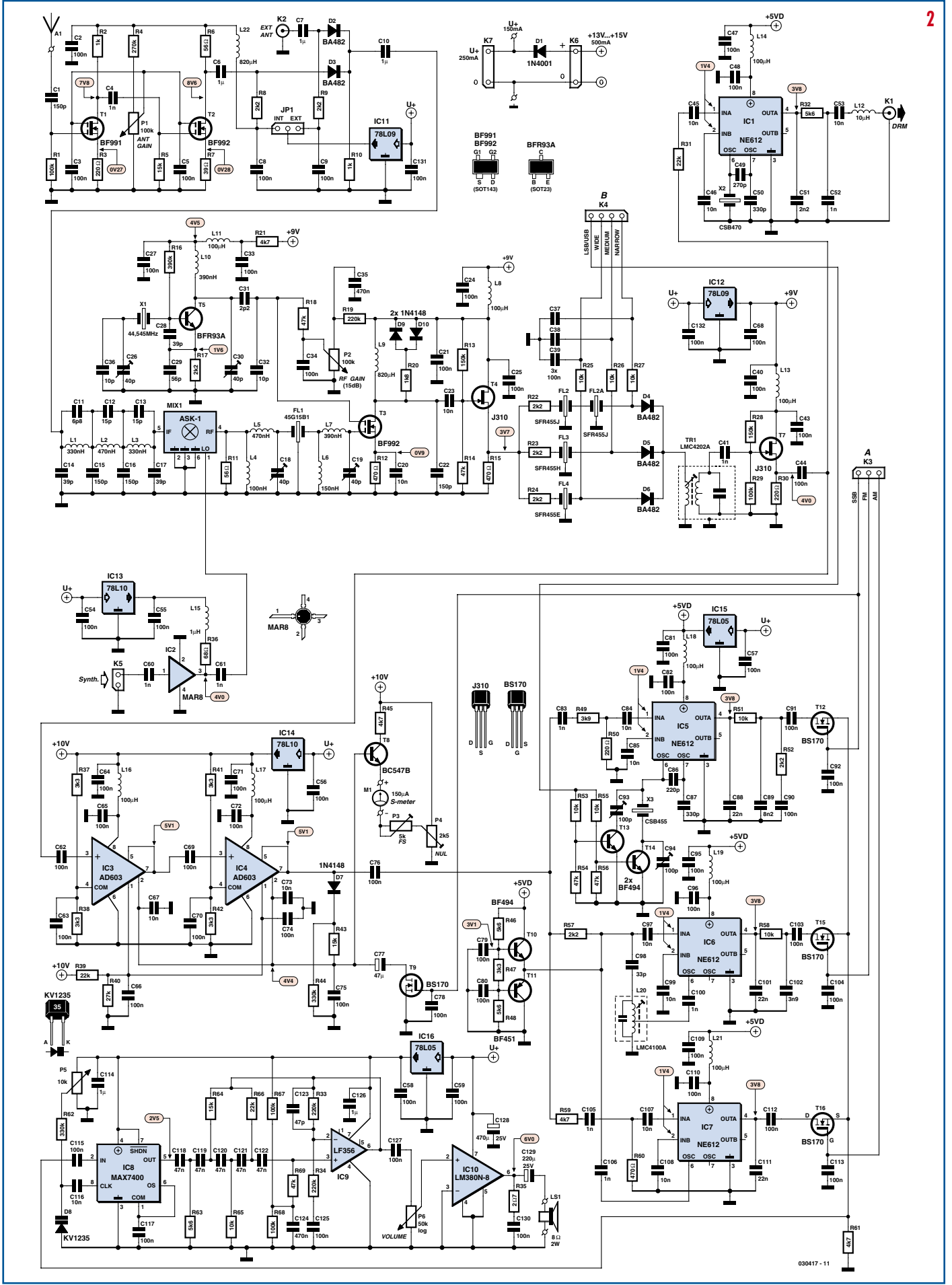We start with descriptions of the principal parts in the receiver section of **Figure 2**. At the top-left is the pre-amplifier for the telescopic aerial. This consists of a two-stage configuration using low-noise DG MOSFETs (T1/T2). The first stage provides a high-impedance input and some gain, the second stage functions as a 50 Ω driver. The gain can be adjusted from about +6 to -20 dB.



3

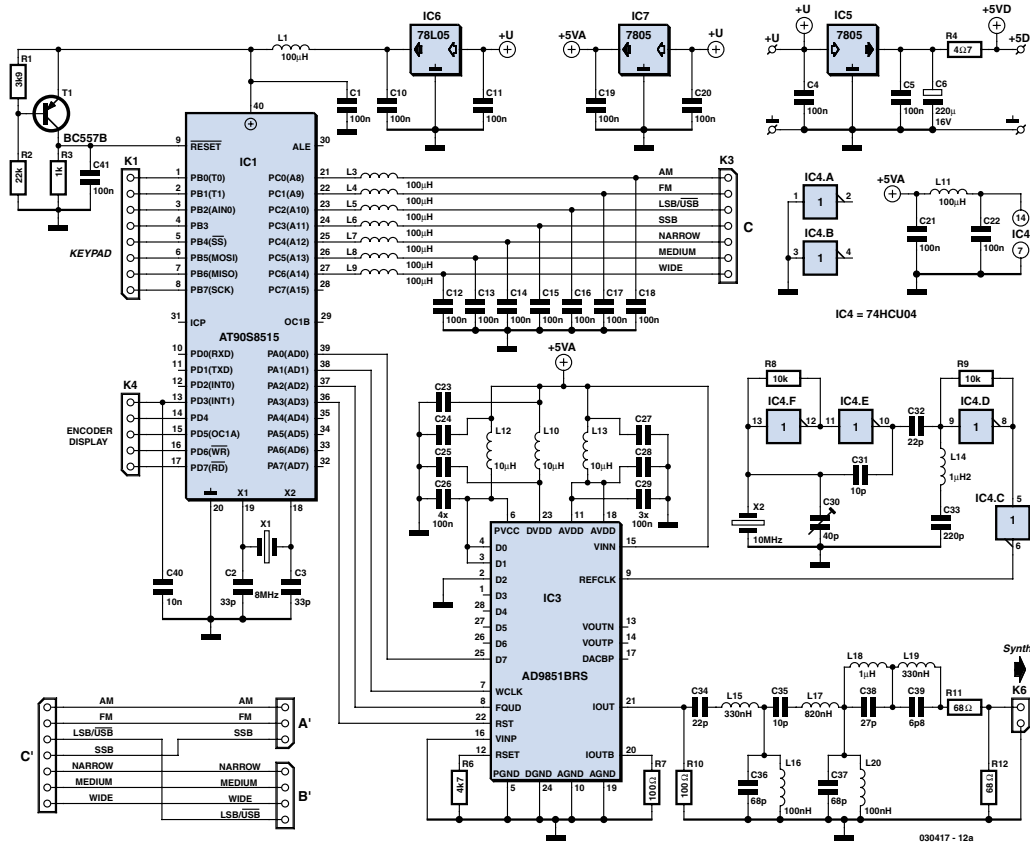


Figure 2. Schematic for the receiver section. There is a heap of components, but with the help of the block diagram you should be able to recognise the different sections.

Figure 3. The electronics for the microcontroller board. The wiring diagram at the bottom-left shows how K3 and K4 on the receiver board should be connected to K3 on the microcontroller board.


Figure 4. This part is on the display board: display driver, six-digit 7-segment display, rotary encoder and a keypad with 16 keys.

Two BA482 switching diodes (D2 and D3) have been used to switch between the pre-amplifier and the input for an external aerial. This type of diode has a very low AC resistance when a certain forward current flows through it.

From the aerial switch the signal is fed into a low-pass filter consisting of inductors L1 to L3 and capacitors C11 to C17. These form a Causer-like filter, which cuts off steeply at 30 MHz and which has a fairly flat transfer function

from 0 Hz onwards. The input and output impedance of this filter is 50 Ω. Following this input filter is the first mixer (MIX1). We have used an ASK-1 diode-ring mixer made by Mini-Circuits Labs because of its ability to handle

4

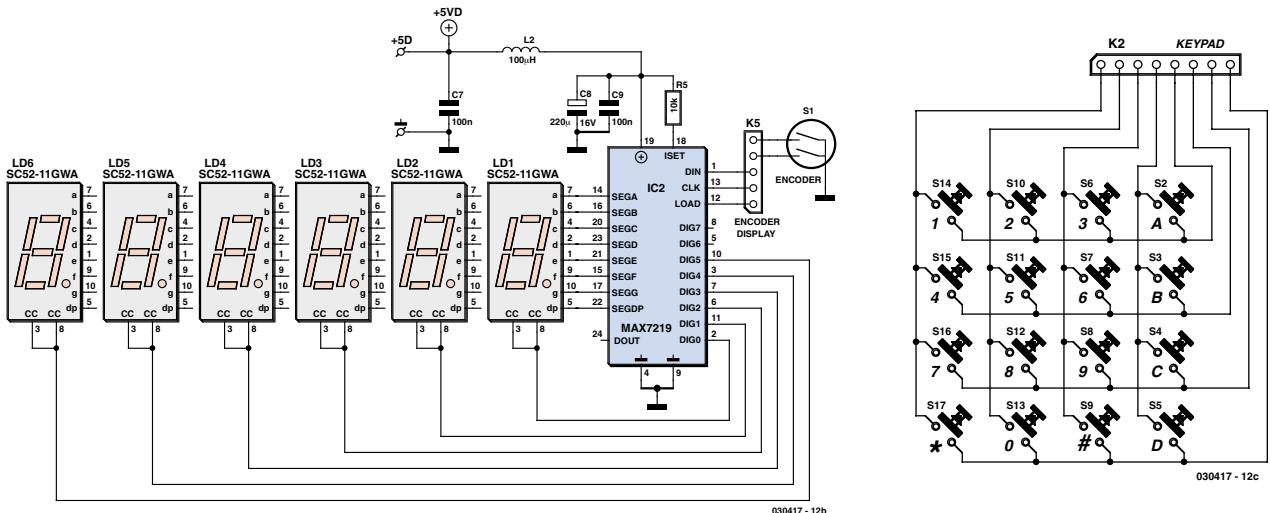



large input signals. Eagle-eyed readers will have noticed that we've swapped the input (RF) and output (IF) of this mixer. The mixer still works well in this configuration, but it has the advantage that the input frequency can be a lot lower (almost down to 0 Hz, which is exactly what we require).

At the output of this mixer is a filter (FL1) that suppresses unwanted by-products and the image frequencies of the second mixer. An LC network at the output of the filter is used to match the impedances.

We now come to the second mixer, which is built around T3. Again we've chosen a low-noise BF992 DG MOS-FET, which has a somewhat better gain than most of its equivalents. As far as large signals are concerned, we don't demand as much from this mixer as from the first one because we're only really dealing with one frequency here.

The purpose of the second mixer is to convert the first IF (45 MHz) to the second IF (455 kHz). Specifically designed crystals with a frequency of 44.545 MHz are available for this.

The local oscillator signal for the first mixer is supplied by a VFO. This signal should have a frequency range from 45 to 75 MHz, with a resolution of 100 Hz. We have chosen an AD9851 DDS made by Analog Devices (IC3 in **Figure 3**), which provides a stable output that can be accurately programmed in small frequency steps. The frequency range is just about wide enough for use in our application.

At the output of the DDS is a band-pass filter (C34 to C39, L15 to L20) with a pass-band of 45 to 75 MHz. The impedance of this filter is about 100 Ω. The impedance is lowered to 50 Ω using resistors R11 and R12. The resulting signal is then fed into a MAR8 (IC2 in **Figure 2**). This IC (made by Mini-Circuits) is a wide-band amplifier with an

output impedance of 50 Ω. It also has enough output power to provide a good signal to the first mixer.

After buffer T4 come the three IF-filters. These can be individually turned on using BA482 switch diodes (using the same principle as for the aerial switch). In this way the processor can switch between bandwidths of 3, 6 or 15 kHz. The IF transformer (TR1) provides a load to the filters that is equal to their characteristic impedance (about 2 kΩ).

Following buffer stage T7 we end up at the IF amplifier consisting of two AD603 ICs made by Analog Devices (IC3/IC4). The gain of each IC can be adjusted over a range of 40 dB using a control voltage. This gives us a total AGC range of 80 dB. The AGC voltage is also used to drive the S-meter (M1) via T8.

The detector for DRM signals has been placed straight after the IF filters. The IF amplifier is therefore not used for DRM signals, as we saw from the block diagram.

The DRM signal is decoded using a product detector that mixes the input signal with a fixed frequency signal. The mixer chosen for this job, an NE612 (IC1), has an internal Colpitts oscillator. This can be set up in such a way that it will oscillate at a slightly lower frequency than the resonant frequency (470 kHz) of the CSB470 resonator used here. In this case we require 467 kHz, which is used to convert the 455 kHz signal into an audio signal with a centre frequency of 12 kHz and a bandwidth of 10 kHz.

We've now arrived at the detection stages for AM/FM/SSB. Each of the three stages has been built around an NE612 mixer IC.

The SSB detector is a product detector, as is usual for SSB detection. The internal oscillator of IC5 has been configured in such a way that only one resonator is required for USB as well as LSB operation. The trick used here is that transistors T13 and T14 switch a trimmer capacitor either in series or parallel with the resonator.

The quadrature detector for FM demodulation is built around IC6. This detector is very suitable for demodulating narrow-band FM, which is normally used in the 11-metre CB band. Because this type of demodulator is somewhat sensitive to AM components, the signal is first fed through a limiter. This consists of a push-pull transistor pair (T10/T11). With the val-

ues for the base resistors as shown, the signal fed to the NE612 will be limited to about 250 mV_{pp} .

The simplest way of demodulating AM is with an ordinary diode. A disadvantage of this method is that distortion is introduced when the signal weakens. This is particularly a nuisance when the signal fades, which happens fairly often in the shortwave bands. A synchronous detector (IC7) is more resistant to these occurrences. For this we use the signal from the limiter in the FM demodulator as the mix signal. The amplitude of this signal is virtually constant, even when the signal strength varies a lot.

There are now three available audio signals, which can be selected by the microcontroller with the help of three BS170 FETs that are used here as analogue switches.

The receiver is equipped with an effective audio filter. This is an adjustable low-pass filter built around IC8, which is a switched capacitor filter. The MAX7400 contains a very steep 8th-order elliptic filter where the corner frequency can be set with a capacitor. If a varicap (D8) is used for this capacitor then the corner frequency can easily be adjusted using a potentiometer.

An active fifth-order high-pass filter built around opamp IC9 then filters out all frequencies below 300 Hz, thereby suppressing hum and other low-frequency noise.

The final stage is an audio power amplifier, for which we've chosen an LM380N8. This 8-pin IC is capable of delivering 2.5 W of audio power when supplied with a high enough voltage. In this case we supply the IC with the maximum permitted 15 V, which means it can output 1.7 Watts into 8Ω . That should provide enough volume in even somewhat noisy environments.

At the heart of the control section is an AT90S8515, a microcontroller made by Atmel (IC1, **Figure 2**). One of its many tasks is to provide the DDS chip (IC3) with the correct data. This happens serially, which requires fewer I/O lines. For each change in frequency the microcontroller sends a string of 40 bits to the DDS. This happens extremely quickly so you won't experience any delays when changing the frequency. A rotary encoder (S1 in **Figure 4**) is used for tuning purposes, which supplies 24 pulses per turn to the microcontroller. The encoder output is con-

nected to an interrupt line, so not a single pulse will be missed by the software. In this way you can tune through 24 kHz per complete turn at 1 kHz resolution, which is sufficient for AM and FM. The resolution can also be set to 100 Hz (via the D key on the keypad), which results in 2.4 kHz per turn. This is more suitable for tuning to a SSB station on the amateur bands. It would be nice if the encoder could provide more pulses per turn, so that you could always tune with a resolution of 100 Hz. In this case you would need to replace it with an optical encoder.

The keypad is another input device that is read by the microcontroller. This consists of 16 keys arranged in a 4x4 matrix. In this configuration you only need eight I/O lines to scan the keypad. The scanning is fast enough never to miss a key press.

Apart from the 10 digits there are four extra keys on this keypad (A, B, C and D), which are used as function keys. This reduces the number of switches required on the front panel, which makes the operation of the receiver easier and clearer.

Three I/O lines from IC1 provide the display driver (IC2, a MAX7219) with data. This display driver can drive a maximum of eight 7-segment displays. This IC also has the ability to control the segments of each digit individually. In this application we've made use of this to display an L for LSB mode, a U for USB mode, an F for FM and an A for AM, followed by the bandwidth of either 3, 6 or 15.

And last but not least, the microcontroller also controls the settings for the bandwidth and modes. This is implemented very simply using seven I/O lines, which are set high or low by the software as required.

The software for the microcontroller was written in assembly language and consists of about 1800 lines. The program has 21 subroutines, a reset routine, two interrupt routines (encoder, timer) and a main program loop.

A programmed microcontroller can be ordered from Elektor Electronics using order code **030417-41**. In contrast with other Elektor Electronics projects we can't provide you with the source and hex files.

Each of the boards for the receiver has been provided with a liberal number of voltage regulators, suppression chokes and capacitors. The supply voltage of 13 to 15 V (0.5 A) is provided by a mains adapter.

Construction

The electronics for the whole receiver have been divided across three boards: a receiver board, a microcontroller board and a display board. Due to a lack of space we can only show you photos of the completed boards in this article. All PCB layouts, component overlays and the accompanying parts lists can be downloaded free of charge from <http://www.elektor.com/> (look in magazine/December 2006/Shortwave Capture). Ready-made circuit boards are available from Elektor's business partner 'The PCBShop' (Eurocircuits). In a radio receiver you obviously have to use several special RF components. The best places to buy these are specialist electronics firms, such as internationally operating Barend Hendriksen (www.xs4all.nl/~barendh) or HaJé Electronics (www.haje.nl).

A reasonably experienced electronics hobbyist shouldn't have many problems with the construction. There is only one component that is difficult to solder: the DDS chip, which comes in an SSOP package!


There are two parts lists: one for the receiver board (-1) and one for the microcontroller and display boards (-2). Take care not to mix up the part numbers between -1 and -2.

The receiver board (030417-1) has been made very compact. Because of this, the space for resistors is smaller than usual and the leads have to be bent closer to the body. All SMD FETs and SMD transistors have to be soldered on the underside of the board. The MAR8 can be soldered either way up, since its connections are symmetrical. Do take care that the lead with the indicator dot is soldered to the correct pad.

We decided to make JP1 (aerial input selection) a header with a jumper, but if you intend to change the aerial input on a regular basis then it will be much easier if you add another switch to the front panel instead.

As we mentioned earlier, the soldering of IC3 and its associated components on the microcontroller board requires very delicate work. The decoupling capacitors are also SMD; these should preferably be 0805 types, but 1206 ones fit as well. You should first solder two decoupling caps (C24, C27) underneath (!) L12 and L13.

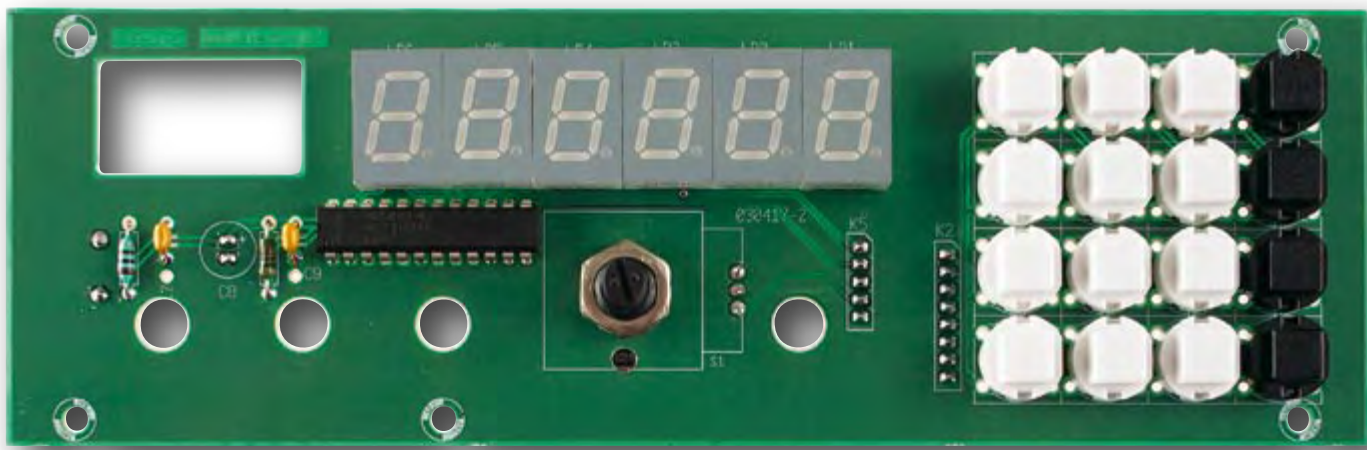The headers for K3, K6 and the supply are soldered onto the solder-side of the microcontroller board (assuming that you don't want to solder the con-



nection leads straight onto the board). The voltage regulators (IC5 and IC7) are also found here. These should be provided with a heatsink, otherwise they could overheat when the case is screwed shut. On the display board the following components are mounted on the underside of the board: the rotary encoder S1 (so the spindle sticks out through the front), the headers (if required) for K2, K5 and the supply, and electrolytic capacitor C8.

It is best to use flexible wire for the connections between the boards. If you have plugs at one end it will be easier if you ever need to separate the boards in the future. The cables should be kept away from the receiver board as much as possible, otherwise you're asking for trouble (unwanted oscillations etc.). Route the cables directly away from the board and only then bend them towards the other boards. Keep in mind that the order of the pins on K3 and K4 on the receiver board is different to that on K3 on the microcontroller board. We've added a wiring di-

agram in Figure 3 to remind you. You should use a short length of thin 50 Ω coax cable like RG174 for the synthesiser connection.

The supply for boards -1 and -2 loops from one to the other, which is why there are two connectors for the power supply. On the receiver board you could use K6 for the incoming +13 V for example, and use K7 to link it to the microcontroller board and display board. To avoid buying many different types of plugs we have used only 5 or 8-way types and just removed the unwanted pins when necessary.

The dimensions of the boards are such that they all fit in a standard case made by Bopla. The receiver board is mounted flat on the bottom of the case and the other two boards are mounted vertically behind each other (display board at the front). The spindles of the potentiometers of the receiver board fit through the holes in the other two boards.

The potentiometers should therefore have long spindles so they can stick through the front panel. When you use the recommended Bopla case, the receiver board can be fitted using a few

M2.5 bolts.

It won't do any harm if you put some aluminium foil on the bottom inside the case and connect it to ground. This provides some extra shielding, which improves the stability of the receiver. An unetched piece of PCB is also suitable. We don't want any short-circuits, so the PCB should be placed with the copper side down, or if you used aluminium foil you should cover it with insulation tape.

The microcontroller and the display boards are mounted vertically inside the case. Although there are slots on the left and right-hand side of the case for this purpose, we didn't use them because the boards wouldn't fit. Luckily the boards can also fit on either side of the slots. The 7-segment display ends up just behind the front panel and there is also enough room for the microcontroller board this way.

At the back of the case is a connector for the supply, a feed-through for the telescopic aerial and a hole for a phono-socket for connecting an external aerial.



Adjustments

There are nine trim points in this receiver. To start with it is best to set all trimmers at their halfway position. Before you continue, make sure that an aerial is connected and selected.

Select the AM mode using the A key on the keypad. Next you should type in the frequency of a strong medium wave transmitter. If you use an internal aerial you should set the gain to its maximum; this also applies to the RF gain. Set the audio volume control to halfway. If necessary, use the rotary encoder until you hear a medium wave station. First set trimmer C30 in the collector of the local oscillator of

mers should again be adjusted to get the maximum S-meter-reading.

In a double conversion superheterodyne receiver there are two oscillators that determine the accuracy of the reception frequency: the reference oscillator for the DDS and the local oscillator for the second mixer. You will need a frequency counter to set these correctly. First type in a frequency of 30.000.0 MHz. Then adjust the trimmer of the 10 MHz reference oscillator (C30 on the microcontroller board) until the frequency at the output of the MAR8 (IC2) is 75.000.000 MHz. The frequency counter should now be connected to the second gate of the second mixer (T3). Use trimmer C26 near

AM station, for example in the medium wave. Then use the B key to select LSB, and adjust C94 until you have a beat frequency of 0 Hz. Now use the B key to select USB, and adjust C93 until you have a beat frequency of 0 Hz.

The receiver is now ready for use and the case can be put together.

DRM use

In order to process DRM signals you have to connect the DRM output of the receiver to the line input of a soundcard in a PC. Next you have to start a program called Dream. The bandwidth of the receiver has to be set to 15 kHz using the C key. The mode doesn't mat-

Operation

Overview of all keypad functions:

- 0 to 9** numerical input of frequency
 - D** 'Enter' after inputting the frequency
 - A** AM(6)/FM(15) mode
 - B** LSB(3)/USB(3) mode
 - C** select 3, 6 or 15 kHz bandwidth, independent of the current mode
 - D** select 100 Hz or 1 kHz tuning resolution
 - *** store the frequency, mode and bandwidth into memory
 - *mm** store into memory entry mm (mm = 00 t/m 63)
 - #** recall the frequency, mode and bandwidth from memory
 - #mm** recall memory entry mm (mm = 00 to 63)
- (When the receiver is turned on, memory entry 00 is used by default.)

The display for the frequency readout consists of 6 digits and has a resolution of 100 Hz. This also means that when you input a frequency via the keypad you have to enter it down to the last 100 Hz. For most stations you'll find that you have to input the frequency in kHz followed by an extra zero. But to receive the DCF time signal on 77.5 kHz you just type in 775 and D.

There are two fixed decimal points on the display. So for channel 14 in the 27 MHz band for example, the display will show 27.125.0. When the A or B keys are used to change the reception mode, the display will show the selected mode for several seconds. For example, after pressing the A key it will show A-6, which means AM mode with a 6 kHz bandwidth. Pressing the A key again will show F-15 (FM mode, 15 kHz bandwidth).

Pressing the B key changes the display to L-3 (LSB mode, 3 kHz bandwidth). Pressing the B key again shows U-3 (USB mode, 3 kHz bandwidth).

Repeatedly pressing the C key doesn't change the mode, but rather the bandwidth. Again, the display will show the last selected setting.

When none of the A, B or C keys has been pressed for a period of 2 seconds the display will automatically revert back to the frequency readout.

the second mixer to obtain maximum volume.

Next you should set the trimmers of the first IF (C18 and C19) to obtain maximum volume.

The full-scale trimmer (P3) and the null-trimmer (P4) for the S-meter should now be adjusted. The rest of the settings can now be completed with the help of the S-meter reading.

If a very strong signal is received you should reduce the aerial gain a little.

Adjust the core of the IF transformer following the IF filters (TR1) to get the maximum S-meter-reading.

When the sensitivity of the receiver improves you can try tuning to a weaker station. The previously mentioned trim-

mers should again be adjusted to get the maximum S-meter-reading.

Once all these settings have been completed we can start with adjusting the FM demodulator. For this we need to tune in to an FM transmission in the 27 MHz band. We then need to adjust the core of the IF transformer (L20) in the FM demodulator. (Make sure that you have selected the FM mode with a 15 kHz bandwidth, using the A key.) As an alternative, you could adjust it for minimum audio output when receiving an AM station in FM mode, which is actually a bit more precise.

The last trimmers to be adjusted are the two trimmer capacitors in the SSB product detector. Tune in to a known

ter, but if you select AM you may be able to tell via the loudspeaker if there is any interference in the DRM signal. After setting up the soundcard on a PC (this is described in the March 2004 issue of *Elektor Electronics*) the receiver can be tuned to a DRM transmitter. Many DRM stations don't transmit continuously, but according to a certain schedule. You can check via the loudspeaker of the receiver whether you've tuned into a DRM transmission. A harsh noise should come out of the loudspeaker. You can then turn down the volume on the receiver. Finally, you use the recording control on the PC to set the required level.

(030417-1)

Spy Number St

Curious short wave transmissions...

Jochen Schäfer

Their programme content is not what you would describe as entertaining but these strange broadcasts have not only attracted the attention of shortwave enthusiasts but also songwriters and filmmakers... not forgetting government counter-intelligence departments.

Those of you who choose to do a spot of short wave surfing during their idle moments will no doubt have hit upon one or two stations where the programme content is made up entirely of someone (usually female) monotonously reading out a series of numbers. Your first assumption may be that you have gate crashed a pirate radio version of Bingo until you notice that some of the numbers are repeated and grouped either in fours or fives.

The enigmatic nature of these broadcasts is further enhanced by the station identification which can take the form of a repeated short extract of music played on what sounds like a Stylophone. Once you add in ionospheric distortion and fading the overall effect is quite spooky. Recording artists have exploited this aspect of the transmissions and used sampling and mixing to produce interesting effects. The film 'vanilla sky' also features them in the soundtrack. Directional antennas have been used to pin-point the sources of these transmissions but they do not appear on any official broadcast schedule and when the authorities have been asked what the transmissions actually represent their explanation seems to favour 'meteorological data'.

Emerging Patterns

Transmissions from the number stations conform to a regular pattern: They begin (usually on the hour or half hour) with an interval signal (tone sequence, melody or call sign), followed by a three number ID (usually), a count value corresponding to the number of code groups in the transmission followed by transmission of the code groups. The former West German BND transmissions were always terminated by a combination of two characters from the NATO alphabet (over 80 different

combinations were used) followed by a tone burst.

The 'Lincolnshire Poacher' is an active station purported to emanate from the RAF base at Akrotiri in Cyprus. Each transmission begins on the hour and lasts for 45 minutes. Transmission starts with the first 15 notes of the English folk tune repeated 12 times followed by a 5 figure ID repeated six times and two notes from a glockenspiel. The message follows and is always composed of 200 groups of five numbers (the last number in each group is pronounced with a rising terminal). The message ends with six repeats of the poacher tune.

Number Stations do not exclusively use voice transmission; Morse is also used as well as tone signalling where each tone represents a different number. These 'polytone' stations are thought to be operated by the Russian authorities.

Some irregularities

Not all the stations retain their original identity; take for example a German speaking station which had been broadcasting for over 30 years from a site in Poland. Its station identification was an extract of the 'Swedish Rhapsody' by Mantovani played on a music-box chime or 'ice cream van' as it became more affectionately known. The station closed after the catastrophic floods of 1997 but today it is again in operation, at the same site and frequency but this time thought to be run by the British SIS. The mechanised voice which popped up on this station was instantly recognised by Number Station listeners as belonging to 'Cynthia' who they had heard before on a station thought to be used by the American security department.

The American security department ceased all Number Stations activity in October 2003 but up until then they



ations



were thought to be operating (like the Russian security services) in Europe, transmitting in many languages including English, German and Spanish. Up until a few years ago there was also an Arabic speaking station. It has never been established which government was responsible for the 'Swedish Rhapsody' transmissions and some stations are not always what they first appear; a recent example was heard broadcasting from the Indian subcontinent in July 2005 and given the designation 'E22', the transmissions bore the hallmarks of a Number Station but it was finally identified in December 2005 as test transmissions by 'All India Radio' for a new transmitter site. The station has since become fully operational and reclassified as a broadcast station. More details of the transmissions can be found at [1] under the heading 'E22 private room and study page'.

Current activity

Number Stations first appeared at a time when there were no alternative paths available to relay messages worldwide. Today we have a number of options which offer global coverage including satellite communication and the Internet which you might reasonably assume would eventually supplant radio broadcasts but in recent months shortwave activity has actually grown more intense. Among the organisations thought to be making use of these stations are the British Secret Intelligence Service (formerly MI6) The Israeli intelligence agency (a.k.a. Mossad) and the Russian Federal Security Service (FSB) together with other organisations broadcasting from Chechnya, Cuba, Korea and two English speaking stations in Egypt.

Their continued use by many countries highlights the advantages of this form of broadcast which includes low

Tools of the trade

One of the advantages of communicating via Number Stations is that no specialised equipment is needed to pick up the message, just a regular travel or 'world band' radio which can be purchased on the high street (some stations use upper side band). The operative just needs patience and an undisturbed period of time to take down the numbers. Communication is only one-way of course but small portable two-way HF radios have also been developed for use in the field.

An example of this type of radio equipment is the SP-15 short wave set developed in the late 50s by Wandel & Goltermann together with Pfitzner. The receiver was fully transistorised while the transmitter used valves. The entire kit including aerial, headphones, Morse key, fast code generator, crystals, NiCd batteries and mains charger are all contained in a neat briefcase which enables the set to be ready for use in a very short time. A notable design feature is the simple superhet receiver covering 2.5 to 24 MHz in two ranges with a BFO. For its time it had an extremely good specification with a sensitivity of $22 \mu\text{V}$ at 10 dB S/N. Current consumption is just 8 mA. It was used by the German secret service 'Gehlen' (later the BND) and also by the German armed forces for military reconnaissance. The excellent receiver design also saw service in other NATO roles.

An example of a similar piece of kit 'from the other side' is the Soviet built R-353 set, the transmitter and receiver are housed in a light metal case together with the power supply. In contrast to the SP-15 the R-353 receiver is a valve double superhet. An interesting feature of this unit is the programmable magnetic band cassette shown attached to the front of the radio. Number sequences can be recorded onto the tape using a 10-way dial and then sent very quickly in a short transmission burst. This dramatically reduces the risk of the transmitter being discovered by direction finding.

(EK)



The West German SP-15 (Photo: Max O. Altmann)



Its Eastern Block rival: The R-353 (Photo: Max O. Altmann)

Table		
Frequency (kHz)	Enigma Identity	Details
6959/ 9251/ 11545	E03	Thought to be used by the British Secret Intelligence Service. Transmissions begin on the hour. Mode: USB (J3E). Station ident: A repeated keyboard rendition of a phrase from the 'The Lincolnshire Poacher'.
3150/4270, 4461, 6840/9130/ 11565/ 13533	E10	Thought to be used by the Israeli Mossad. Letter groups are used instead of number groups. Transmissions begin on the hour and half hour. Mode: Mostly AM (A3E). Station ident: A three letter sequence.

cost, low tech equipment (the signals can be picked up on a relatively inexpensive 'world band' type of radio), broad coverage (assuming the signals are not subject to Electronic Counter Measures) and excellent message security.

The stations usually operate at frequencies between the recognised shortwave bands, using either AM (Amplitude Modulation) or USB (Upper Side Band). They can be located by sweeping these frequencies on the hour and half hour. The table gives details of two stations which are currently active. The 'E03' refers to the station identity assigned by ENIGMA.

Those of you interested in exploring this subject in more depth are recommended to pay a visit to the website of Simon Mason [2] it contains many fascinating curiosities. A popular American site is also included [3] — it has a link to the 'FRS Commander Bunny' transmissions complete with an attempt at decoding.

The Usergroup

The Number Station broadcasts have fascinated listeners for decades. Since the end of the 1990s there has been a European mailing list covering this subject from a Yahoo group with the name ENIGMA 2000 (European Number Information Gathering and Monitoring Association) which evolved from the earlier ENIGMA group. This organisation has catalogued and classified all the known Number Stations and given them the designations E = English speaking, G = German speaking, M = Morse transmissions, S = Slavic speaking (Russian, Polish etc.), V = various for transmissions in other languages and X = transmissions using special types of modulation (e.g. polytones as already mentioned). The mailing list for ENIGMA 2000 has currently grown to around 700 subscribers.

Securing the information

It's a sobering thought that while most radio programmes are designed to capture the greatest number of listeners this must be one of the few examples where the intended audience for an international broadcast may be just a single listener who alone possesses the key to unlock the message. When transmitting cipher text to what is potentially an entire global audience it is vital that the encryption method employed is absolutely bullet proof otherwise government counter intelligence departments with their vast computational resources will surely resolve (eventually) any encryption scheme based upon a mathematical algorithm. One such cipher which has

proved to be perfectly secure is the Vernam cipher or 'one time pad'. The encryption key is a series of random numbers each of which are added to each character in the plain text message. The resulting cipher text is transmitted and the receiver subtracts the key on their 'one time pad' to recover the plain text message. Even with knowledge of some part of the message it does not help to decipher the rest of the message provided truly random keys are used. The weakness of this method is that a 'one time pad' containing the keys must be carried securely by the operator and then destroyed (by both sender and receiver) after use, if it is stolen or copied security will be jeopardised.

Over the years many agents working in foreign lands (both east and west) have been found in possession of tiny 'one time' pads sometimes concealed in a hollowed out soap bar, sometimes inside the shell of a walnut (the most literal form of code cracking?). Governments are obliged to remain silent on matters of national security and have never acknowledged the existence of Number Stations or their possible role in espionage, the identical nature of sequences transmitted by Number Stations and those found on agent's one time pads may of course prove to be purely coincidental.

Without any hard evidence we are forced to accept the official account that the transmissions are in fact reporting snow fall levels in the Mediterranean but if you find that explanation too difficult to swallow then maybe that thought about pirate radio Bingo (at the tax payer's expense) really is the only plausible alternative.

(060229-1)

[1] <http://mysite.wanadoo-members.co.uk/thesecondsiteofmike>

[2] www.simonmason.karoo.net/page30.html

[3] www.spynumbers.com

Further interesting links:

<http://home.freeuk.com/spook007>

<http://www.irdial.com/conet.htm>

http://en.wikipedia.org/wiki/Numbers_station

The Author

Jochen Schäfer is 34 years old and has been blind from birth. He works as a documentation assistant at the German Blind Studies Institute (Blista) in Marburg. He has been tuning into Number Stations in his free time since 1977 when he first started listening to short wave. His archive contains more than 1000 cassettes documenting Number Station broadcasts; he is a subscriber to the ENIGMA 2000 mailing list and one of four site moderators. In his capacity as Germany's leading Number Stations specialist he has made contributions to many publications on the subject.

His Email address is (the_kopf@yahoo.com). He is keen to get in touch with anyone who has any recordings of earlier broadcasts (from the 60's to the 80's) to add to his collection, he has particular interest in broadcasts made by West German BND stations with a two-letter call sign.



EzPCB, Easy Way To PCB

Features:

- UL Proved High Quality
- ISO 9000 Certificated
- Accept Orders From 3pcs to 1M Pcs

Capabilities:

- Up to 40 Layers
- 2.5mil Track/Space
- 0.1mm Hole Size
- Blind And Buried Vias
- RoHs, WEEE Compliant

Prices:

- Only \$50 For 5pcs 4" x 4" 2L
- Only \$188 For 3pcs 4" x 4" 4L
- Only \$288 For 3pcs 4" x 4" 6L
- Free Solder Mask & Silkscreen
- Very Competitive Price For Bulk Orders



Http://www.ezpcb.com
sales@ezpcb.com

www.Lichfield Electronics.co.uk

LED/Light Kits	
6 LED V.U. Meter	£3.99
10 LED V.U. Meter	£4.99
Wireless V.U. Meter	£12.99
2 LED Flasher	£3.99
3 LED Running Light	£4.49
5 LED Flasher	£4.99
10 LED Running Light	£4.99
1CH 700W AC Flasher	£5.99
2CH 1400W AC Flasher	£7.99
10 LED Running Light, S	£8.99
10 LED Running Light, C	£8.99
Two Way Chasing Light	£8.99
Circular Casing Light	£10.99
12V Xenon Tube Flasher	£8.99
Super Electronic Roulette	£24.99
Mini Roulette wheel	£9.99
Heads or Tails Game	£4.99
Deluxe Electronic Dice	£10.99
Dancing Light 3CH	£19.99
LED Flasher 2 colour	£3.99
Priority Machine	£5.99
Xenon Tube Flasher	£15.99
Super Bright Flasher	£5.99
Robot LED Flasher	£5.99
Fire Fly Light:	£3.99
6 Prog chasing light kit	£15.99
11 LED Star Flasher	£6.99
25 LED Star Burst	£16.99
4 Way Traffic Light	£9.99
21 LED Chasing Arrow	£9.99
Atom Chasing light	£4.99
Two Way Chasing Light	£7.99
Triangle Flasher 6 LED	£4.99
Electronic Windmill	£9.99
Electronic Sand Glass	£14.99

Radio Kits	
FM Wireless Mic 3V	£6.99
FM Wireless Mic 9V	£6.99
Easy FM Radio:	£14.99
Easy AM Radio:	£7.99
Walky Talky Kit:	£34.99
Advanced AM Radio Kit:	£13.99
Advanced AM/FM Radio	£16.99
IC Shortwave Receiver	£9.99
MK484/ZN141 AM Radio	£9.99

We would like to wish all the readers of Elektor a very merry Christmas and a happy new year!

Free postage on any kits ordered above £10 to the UK from now until Jan 1st 2007.

Orders below £10 add £1 P&P
Outside UK: £1.50 per item

To order simply visit
www.lichfieldelectronics.co.uk
By Phone: (01543) 256684
By e-mail: sales@lichfieldelectronics.co.uk

Or by post to:
Lichfield Electronics, Conduit Street
Lichfield, Staffordshire, WS13 6JU

Other Kits	
TV transmitter	£27.99
Sound Reversing Car	£14.99
DIY Digital Multimeter	£16.99
Electric Shock Machine	£5.99
300mA 6-9-12V PSU kit	£8.99
0-30V 3A DC Regulator	£15.99
0-30V 1A DC Regulator	£7.99
Emergency Light circuit	£5.99
Rat/Cockroach Banisher	£8.99

Other Kits	
Muscle Massage equipment	£12.99
PIR Sensor with 7A relay	£27.99
Human to Robot Voice	12.99
Raining Alarm & speaker	£6.99
Stereo Simulator Kit	£14.99
Low Battery Alarm 12V	£6.99
0-12V 500mA Regulator	£4.99
Digital Counter 2 digit.	£12.99
Transistor Checker	£6.99

Noisy Kits	
Steady Hand Game	£7.99
Ambulance Siren	£5.99
Fire Siren Kit	£4.99
Police Siren Kit	£5.99
Two Tone Door Bell	£5.99
Christmas Tune Generator	£3.99
13 Tone Mini Organ	£4.99
25 Tone Mini Organ	£8.99
Car Reversing Alarm	£4.99

Telephone Kits	
Recorder Starter:	£9.99
Telephone Amplifier	£9.99
10W Speaker ringer	£9.99
Phone Eavesdropper	£8.99
Dual Station Intercom	£10.99
Telephone In-Use display	£2.99
Privacy Protector	£7.99
FM Telephone Transmitter	£8.99
Ring Controlled Relay:	£12.99
Do-It-Yourself Phone:	£28.99

Switching Kits	
Light Activated Switch	£7.99
Light Controlled Switch	£8.99
Touch Switch	£8.99
Timer Switch 0-3hr	£9.99
Fimer Switch 0-10hr	£16.99
Voice Activated Delay off	£9.99
Voice Control Switch	£9.99
25ft Infrared Remote Relay	£18.99
2CH 50ft IR Remote Relay	£29.99
Light Dimmer 500W	£5.99
Electronic Code Switch	£14.99
Water Level Control	£9.99


Other Kits	
Intruder Alarm	£9.99
Visitors Chime	£7.99
Magnetic switch Alarm	£16.99
Infra Red Alarm	£24.99
50V 30W Mono Amp OTL	£14.99
12V 15W Stereo Amp BTL	£24.99
8W 12V Sterep Amp	£13.99
2W 9-12V Stereo Amp	£9.99
Stereo Tone Control kit 15V	£22.99

Wireless Key

Compact and secure

Gert Baars

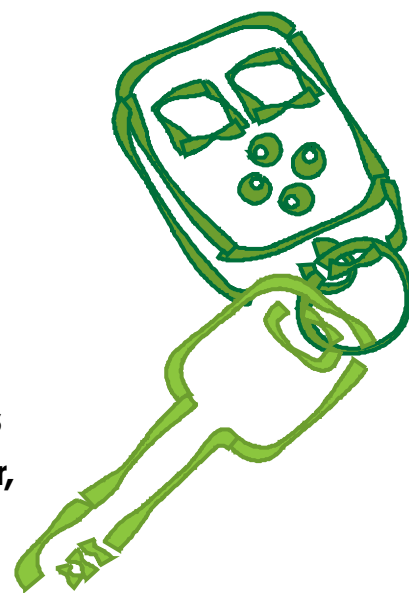Secure wireless switching can be useful in a variety of applications, such as activating or deactivating an alarm system, operating a garage door opener, or operating an anti-start device in your car. The circuit described here is compact and quite secure, and it operates in the 433-MHz ISM band.



The circuit described here consists of a transmitter and a receiver operating on a frequency in the 433-MHz ISM band. Frequencies in this band can be used without a licence if the transmitter power does not exceed 10 mW (10 dBm). The transmitter is small enough to be fitted in a key fob, and it is powered by a 3-V lithium cell. The transmitter only emits RF signals in short bursts, so the current consumption is no more than 8 mA. As the battery has a capacity of more than 200 mAh, it will last for several years.

The receiver operates from a supply voltage of 5 V and can be powered from a simple AC adapter. If it is used with a car battery, a 78L05 must be connected between the battery and the circuit. In the case of a 6-V battery (such as is used with motorcycles and scooters), a low-drop 5-V regulator must be used.

A 24-bit code is used to ensure that the receiver only responds to the proper key transmitter. More than 16 million combinations are possible with such a code. To give you an idea of how big this number is, with a burst length of 300 ms for each transmitted code the transmitter would have to transmit an uninterrupted series of sequential codes for two months in order to work through all possible combinations.

Microcontrollers are used in both units (transmitter and receiver) to encode and decode the key.

Transmitter

The actual transmitter consists of a Maxim MAX1472 (Figure 1). This tiny 8-pin IC contains a crystal-controlled

ASK transmitter for frequencies in the 300–450 MHz range. It includes a fixed-ratio PLL and a crystal reference oscillator. This type of design is more precise and more stable than an ISM transmitter based on a SAW filter.

The frequency selected for this project is 433.920 MHz. It results from the fact that the PLL multiplies the crystal frequency by 32. Due to the narrow tolerances of crystals, the match between the transmitter and the receiver is always adequate without any need for tweaking, in part because the receiver has a relatively large bandwidth.

The crystal has a frequency of 13.560 MHz. It comes from Hong Kong X'tals [1]. The coil in series with the crystal ensures that the circuit oscillates at the series frequency of the crystal.

The transmitter IC has a 10-mW output stage, which is good for a range of at least 10 metres indoors (the author only tested the unit in his house). A loop antenna etched on the circuit board is often used in such applications, but a dipole antenna (too short for the actual frequency) proves to give better results. Two radiating elements, each approximately 4 cm long and 0.04" thick are fitted to the transmitter board for this purpose.

The transmitter IC has a data input for ASK modulation. Although it can be modulated at up to 100 Kb/s, we have to point out that the reliability of the system is better at lower rates. As only a relatively small amount of data must be transmitted, a bit rate of 100 b/s can be used. It takes only 240 ms to send 24 bits at this rate.

The total burst length is 300 ms,

including the preamble and start bit.

This burst is transmitted when the transmit button is pressed, with a total current consumption of around 8 mA. The microcontroller switches the transmitter off immediately after the burst has been sent and then enters a power-down mode, with the result that the total current consumption drops to less than 2 mA as long as the button is held pressed. This reduces the battery consumption to a minimum. In practice, it means the transmit button must be held down for approximately half a second to transmit all the data.

A microcontroller is used to generate the code key and transmit it by modulating the transmitter IC. The selected microcontroller is the Atmel ATtiny15L, which is available in an 8-pin DIP package. This microcontroller has an internal RC clock generator that runs at 1.6 MHz, and it can be set within a tolerance of 1% using a calibration byte. After the flash code memory has been programmed, the calibration byte must read from the internal 'signature space' using the programming software and then written to location 1023 (\$3FF) of the flash memory. This only has to be done once when the microcontroller is programmed. Each time the microcontroller starts up, it reads the calibration byte from the flash memory and then writes it to the oscillator calibration register to optimise the accuracy of the internal processor clock.

Receiver

The receiver is also a Maxim IC (Figure 2). In this case it is a MAX1473, which

contains a complete superheterodyne receiver. Here again the reference frequency, in this case the local oscillator frequency, is provided by a PLL oscillator. As the PLL multiplication factor is 32 and the IF is 10.7 MHz, the crystal frequency must be 13.2256 MHz (see [1]). A remarkable feature of this IC is the integrated image rejection mixer, which effectively means that the mixer stage also provides adequate image frequency suppression, so there is no need for a preselection filter at the input. As a result, the required number of external components can be reduced to around 20.

The receiver does not have to be tuned, and it boasts a sensitivity of better than approximately 1 μ V. The receiver IC also has an audio filter that is intended to reduce noise and interference. A 'data slicer' after the filter provides automatic operating point adjustment to provide data that is as reliable as possible even under weak signal conditions. The receiver unit is also fitted with an ATtiny15L microcontroller. The data slicer output of the receiver IC is connected to an input of the microcontroller, which decodes the burst signals from the transmitter. If the decoded data contains the correct key, it activates two outputs. Here OUT1 provides a 1-second pulse if the correct key is received. It is intended to be used to drive a mechanical latch opener, which is usually fitted with a solenoid. The second output (OUT2) is an alternate-action switch. OUT2

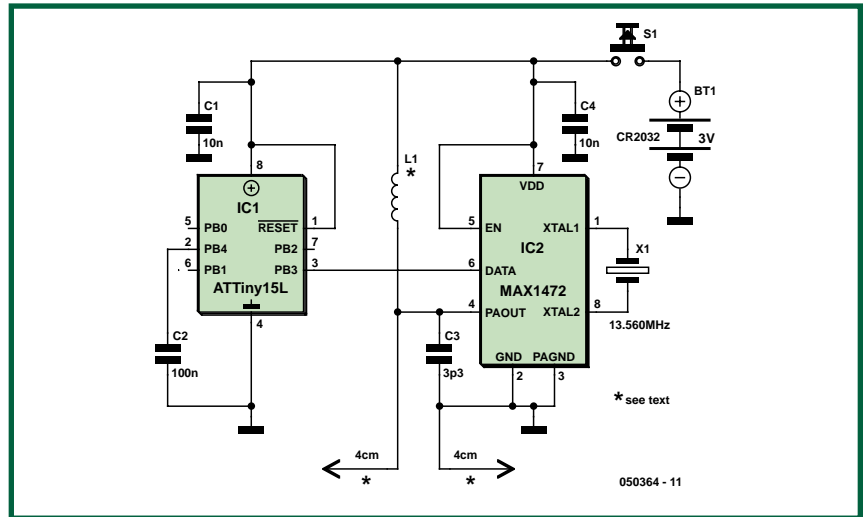


Figure 1. The transmitter consists of only two ICs and can be built in a very compact form.

switches to +5 V when the key is received once and then toggles to 0 V the next time it is received. It can thus be used to switch something on or off, such the control unit of an alarm system or an anti-start device in a car.

Software

The software consists of two separate programs – one for the transmitter and one for the receiver. At somewhat more than 400 lines each, these programs are fairly modest in size. At the transmitter end, after starting up the software looks for a particular value (a 'signature') in the EEPROM of

the microcontroller to see whether a valid key has already been generated. If it hasn't, the software immediately generates a 24-bit code and stores it in the EEPROM memory along with the signature so it will not have to generate a new key the next time. A random number generator that provides an arbitrary 24-bit value is needed to generate the key. This is implemented using a capacitor connected to pin 2 of the microcontroller. The algorithm used for this purpose is based on timing. Pin 2 is first configured as an output and held low for a certain length of time to discharge the capacitor. After that the pin is config-

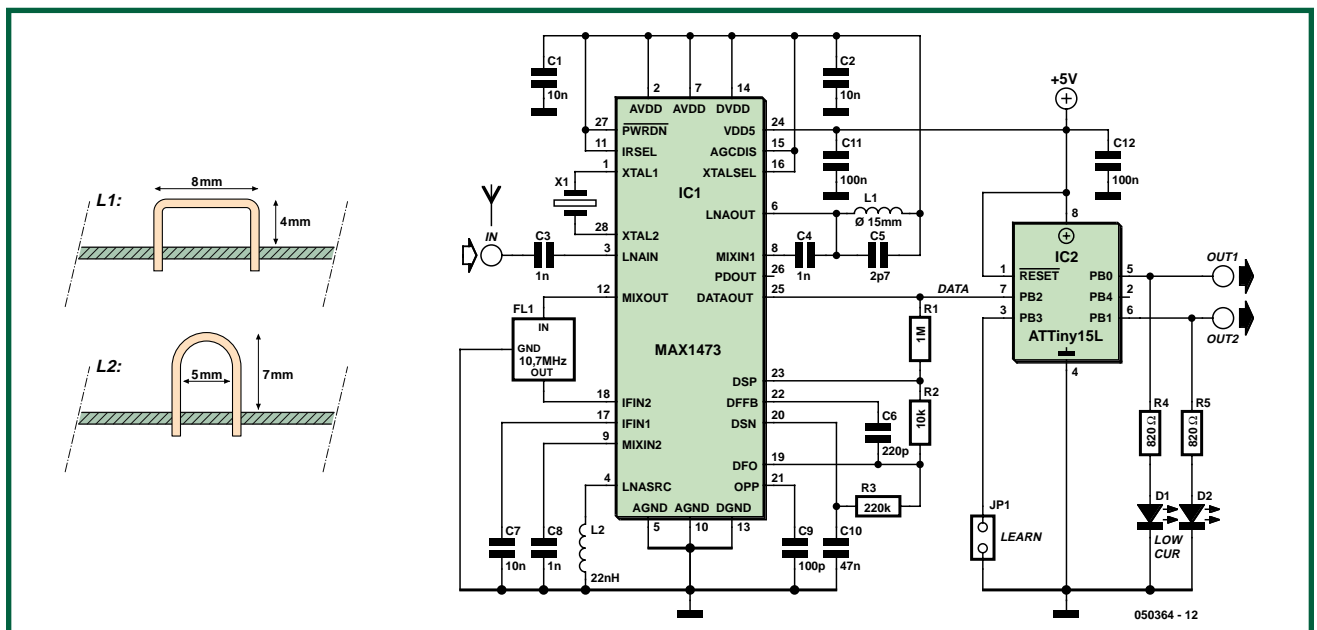


Figure 2. The receiver is somewhat larger, primarily due to the extensive circuitry around the MAX1473.

ured as an input, which also means that an internal pull-up resistor is connected to the pin. The capacitor is charged via this resistor, but the charging time constant is much longer than the processor speed. During the interval when the input is still low, the value of the key is changed in rapid succession by a certain algorithm. This continues until the capacitor is fully charged. The input read as a '1' at this point, at which time the key value stops changing. This results in a key with a random value.

The randomness arises from the fact that the charging process is slow relative to the processor speed. The charging time corresponds to approximately 10,000 processor cycles. Tests have shown that the charging time is not entirely constant. A 0.01-percent change in the charging time is sufficient to yield a different result. This also shows that two different transmitters will never generate the same key, especially because most capacitors have a tolerance of around 5%.

With a normal start-up process (switching on power), the transmitter first reads the key present in memory, but it cannot be transmitted just like that. A preamble with a duty cycle of exactly 50% is transmitted first to allow the operating point of the data slicer to be adjusted. The transitions in the preamble also serve to synchronise the timing at the receiver end with the timing at the transmitter end. A start bit is transmitted after the preamble to indicate that the key will be transmitted next. The 'real' data is only sent after the start bit, after which the transmitter is switched off immediately and the microcontroller enters the power-down mode to minimise battery consumption.

A different program is naturally necessary at the receiver end. In contrast to the transmitter, the receiver is always on. In this case the microcontroller listens to see whether anything is being received. If it is, it checks whether the received data stream has the correct format, which includes checking whether the start bit synchronisation is valid. After this it reads the key and compares it with the value of the key stored in its EEPROM memory.

The microcontroller has a jumper that enables it to read the key. If the jumper is fitted, the receiver is in 'learn mode'. If a key is received in this mode, it is stored in the EEPROM. This means that the first time the receiver is switched on, the jumper must be fitted

and the code transmitted using the key transmitter so the key can be stored in the receiver's memory. After the jumper is removed, the receiver should switch its outputs when the key transmitter is activated. It may be necessary to disconnect the receiver antenna for this procedure and activate the transmitter close to the receiver. This will reduce the effect of any interference signals present at 433.92 MHz. The watchdog timer is also enabled in the microcontroller on the receiver end. If the program counter is affected by a noise pulse on the supply line, for instance, which can lead to a 'hung' system, the microcontroller will be reset automatically after approximately 1 second and the receiver will execute a normal start-up.

Data slicer and Manchester coding

The data slicer in the receiver is built around an opamp in the receiver IC that is intended to be used for this purpose. A data slicer is simply a comparator with a reference level that is automatically set when a data signal with a duty cycle of 50% is received. It is thus important that the duty cycle of the data signal is in fact 50%. Manchester coding is used to achieve this result. The circuit of the data slicer is shown in **Figure 3**. The time constant of R and C is large relative to the data bit rate that is used. As a result, the DC level at the inverting input is equal to the average value of the received signal. With a 50% duty cycle, it will thus be exactly halfway between the minimum and maximum values. However, a certain amount of hysteresis is desirable because the receiver also generates noise when no signal is present or the signal is relatively weak. This is provided by R1 and R2.

It is also necessary to have the transmitter send a preamble before the actual data. The preamble consists of a series of clock pulses with a duty cycle of 50% and a period that is much shorter than the RC time constant of the data slicer. This ensures that the operating point of the data slicer is set properly. Manchester coding must be used to achieve the required 50% duty cycle with the signal used here. This essentially amounts to EXORing the data with a clock signal having the same period as the bit interval. The original bit stream is then recovered in the same manner by EXORing

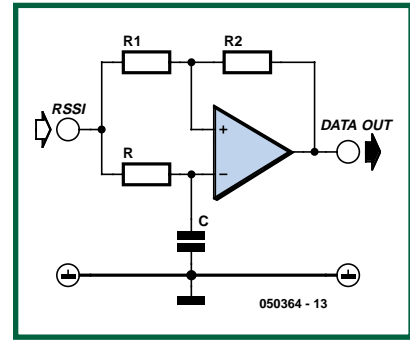


Figure 3. Design of the data slicer in the MAX1473.

the received data with a clock signal. A drawback of Manchester coding is that it increases the bandwidth of the transmitted signal by a factor of 2, but this is not a problem with the low bit rate used here.

In theory, the bytes output by the decoding logic when the clock is high are the same as the bytes output by the decoding logic when the clock is low. Both bytes are in fact decoded by the receiver software. The second byte should essentially be a copy of the first one. The correctness of the timing is monitored closely by comparing the two bytes after each set of eight decoded bits.

Timing

The most important aspect with regard to the algorithms used in the software at both ends (transmitter and receiver) is proper timing. The transmitter must generate a bit stream with a certain frequency, and the receiver must be able to recover it with sufficient accuracy. For this reason, the key transmitter sends the receiver a preamble consisting of clock pulses at the same frequency as the bit rate before it sends the coded 24-bit key. The preamble is followed by a start bit that enables the receiver to deduce that the preamble is finished and the actual data will follow. The ATtiny15L microcontrollers at each end run on their internal RC clocks. A calibration byte for the clock generator is programmed into each microcontroller by the manufacturer. However, this calibration value is intended to be used with a supply voltage of 5 V. As the transmitter operates at 3 V, its clock frequency is lower than it would be at 5 V. For this reason, an extra provision has been made in the software of the receiver. With the receiver in learn mode (as described below), the receiver

copies the timing of the transmitter as well as its 24-bit key. Both values are stored in the EEPROM of the microcontroller and used when the receiver is operating in the normal mode.

Programming settings

The code for the ATtiny microcontrollers in the transmitter and receiver is available free of charge on the *Elektor Electronics* website under item number **050364-11** (see month of publication). The microcontrollers must be programmed using a suitable programmer before they are fitted to the circuit boards.

When you program the microcontroller, don't forget to read the oscillator calibration byte from the signature memory of the microcontroller and reprogram it in flash memory location 1023 (\$3FF). It is also important to tick BOD as enabled and set the BOD level to 4.0 V for the receiver or 2.7 V for the transmitter. If BOD is not programmed, the content of the EEPROM memory (which contains the key code) can be affected when power is switched on or off, with the result that things may no longer work properly.

The 'very quickly rising power' fuse settings (CKSEL = 11) must also be programmed for the transmitter and the receiver. This is partly related to proper operation of the watchdog timer.

Initial use

After you have fully assembled the transmitter board, you must first activate it so it can generate and store a code. It's a good idea to do this a couple of times to be sure that a 24-bit code has been generated and stored. Next, fit J1 on the receiver board. Then switch on the receiver, but do not connect any antenna yet (to avoid picking up interference). Hold the transmitter close to the receiver board and activate it a couple of times. Now remove J1 while the receiver is still on and reset the receiver (by switching it off and on) without J1. The supply voltage must drop to nearly zero during this process, so watch out for the effects of any large capacitors in the power supply. If everything goes well, the LED connected to OUT1 of the receiver will now light up for around 1 second each time you press the transmit button. To be on the safe side, hold the transmit button of the receiver pressed for at least 1 second each time you activate the transmitter.

If everything is working the way it should, you can connect the receiver outputs to the device or circuit to be operated. Bear in mind that it may be necessary to connect a buffer stage or semiconductor relay between the receiver and the load.

(050364-1)

[1] Crystals used in this project:

www.hongkongcrystal.com

Tx: 9SMI356000E03FAFZ000

Rx: 9SMI322560E03FAFZ000

Coil data

L1 (transmitter): 3 turns 0.3 mm dia. silver-plated copper wire, coil diameter 2.5 mm, length 5 mm

L1 (receiver): see Figure 2.

L2 (receiver): see Figure 2

34 channel Logic Analyser only £210!*



Professional Features – Exceptional Price

34 Channels sampled at 500 MHz

Sophisticated Multi-level Triggering

Transitional Sampling / Timing and State

**Connect this indispensable tool to your PC's
USB I.1 or 2.0 port and watch it pay for itself within hours!**



**Economical
2-day
Shipping!**

- **500 MHz Max. Timing Mode** Sample Rate (internal clock)
- **200 MHz Max. Sample Rate** State Mode (external clock)
- **Multi-level Triggering** on Edge, Pattern, Event Count, Group Magnitude/Range, Duration etc.
- **Real-Time Hardware Sample Compression**
- **Qualified (Gated) State Mode Sampling**
- **Interpreters for I²C, SPI and RS232 included**
- **Integrated 300 MHz Frequency Counter**
- **+6V to -6V Adjustable Logic Threshold** supports virtually all logic families
- **Full version of software free to download**
- **Mictor adapter available**

www.pcTestInstruments.com

Visit our website for screenshots, specifications and to download the easy-to-use software.

Intronix Test Instruments, Inc.
16421 N. Tatum Blvd. Unit 130
Phoenix, Arizona 85032 USA
Tel: (001) 602 493-0674
Fax: (001) 602 493-2258
www.pcTestInstruments.com

*The amount of £210 was calculated at the time this ad was created. The actual price will depend upon the exchange rate at the time of purchase. Price does not include the UK VAT of 17.5% plus a small import fee of typically £5-10. These fees will be collected at the time of delivery (companies can claim a refund for the 17.5% VAT from HMRC). E&OE

Go with the Flow

Jürgen Maiß

In this day and age enjoying constant hot water should not be an expensive luxury. All the same, the way some households squander energy to provide this on tap makes you wonder. Our novel circuit saves both your bank balance and the environment!

The circulation pump in a heating system is the device that makes possible the accustomed luxury of having hot water at the turn of the tap. Unavoidable heat losses in the plumbing system and the constant operation of the circulation pump lead to profligate waste of energy, however. In fact, according to Oxford University's Environmental Change Institute, the pump consumes as much energy as lighting or the fridge in most households, and a pan-European drive is now underway to find ways of saving costs for what is one of the most ignored electrical devices in the home. To cut power consumption we need to lag all pipes well and reduce the amount of time that the pump operates to only when hot water is actually required.

There are already a variety of control systems on the market for managing circulation pumps. One of these relies on flow sensors, which react adequately fast but are hardly simple to install (they require plumbing into the pipe system). Other devices observe

temperature variations. These determine the temperature difference between the hot water and circulation pipes, using any variation from the desired value as the trigger. The systems are both reliable and very simple to install, since no 'invasive action' is necessary to the plumbing. Unfortunately the sluggish action of the temperature sensors means they do not operate very rapidly. One feature that both systems share is their relatively high purchase cost. Our approach here takes a rather different route. A simple, readily available piezo sounder used as an acoustic emission sensor detects the sound of flowing water in the plumbing system. This is what we use as the switching trigger.

Piezoelectric effect

Piezoelectric sounders, also known as electronic buzzers, are used in many electronic circuits as audible transducers or 'bleepers'. Easy to use, they also take up little space and are extremely affordable. A change in the voltage



Piezoelectric transducer controls domestic water system

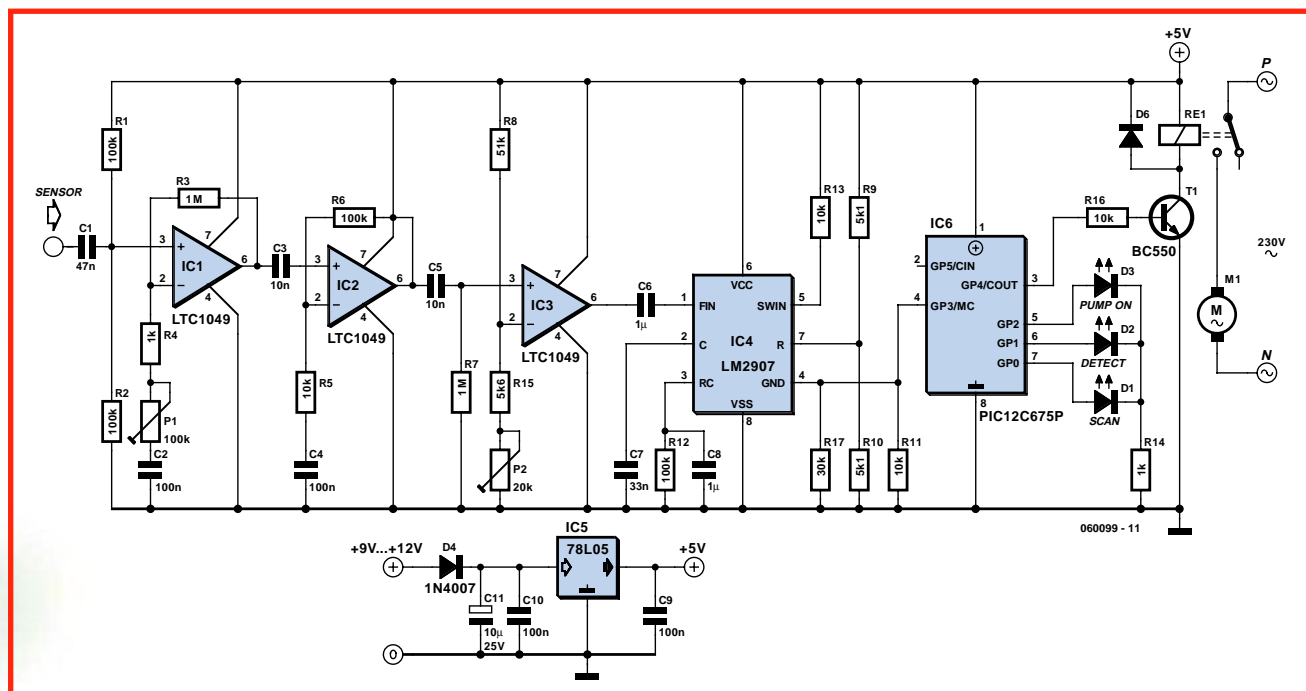


Figure 1. The pump control comprises five capacitor-coupled stages.

applied to the piezo crystal in the sounder deforms it slightly, an effect that is used to generate sound. The principle is reversible too, enabling the transducer to work as a highly sensitive 'microphone' as well. The variations in voltage charge resulting from altered mechanical stress on the crystal structure can be registered electronically and processed further. Piezoelectric sensors are widely used today in workshop tools, for automotive applications and in technical setups as pressure, power and dynamic accelerometer devices.

The pump control system shown in **Figure 1** comprises several modules, each with their own function.

- The first is a **preamplifier stage** with an amplification factor of from 10 to 1,000. The signal coming from the sensor has a value in the region of 100 to 300 μV and is delivered via coupling capacitor C1 to the non-inverting input of IC1. The amplification of this stage is set by trimpot P1. The

extremely low-noise precision amplifier LTC1049 (from Linear Technology) functions not only as an amplifier but also as an impedance adapter with a high-Z input resistor to avoid loading the sensor signal. Coupling capacitor C3 takes the now boosted sensor signal to a second amplifier (once more type LTC1049 with an amplification factor of 10). Total amplification is defined as $A = [(R3 / (R4 + P1)) + 1] \times [(R6 / R5) + 1]$.

- The signal, now amplified to around 1.0 V is fed via C5 to a **comparator stage**. The switching threshold for IC3 (yet again a LTC1049) is set in the region of around 0.5 to 1.55 V by R8, R15 and trimpot P2. If the sensor detects a flow signal, a squarewave output voltage of approximately 1 kHz appears at the output of IC3.

- This squarewave signal is taken via C6 to the **frequency-to-voltage converter** LM2907 (IC4). This module operates in 'speed switch-mode' and above the frequency set as $f = 1 / (2$

C7R12) delivers a High output level, which —

- provides the trigger signal for the PIC16F675 *microcontroller* that follows.

As each of the switching elements is connected by coupling capacitors, they can all be modified easily for other applications too. The amplifier circuitry would, for instance, make a magnificent microphone amplifier, ultrasonic amplifier or ground motion detector (geophone). Linear Technology provides for its own modules a free and easy-to-use simulation tool called SwitcherCadIII. A simulation program for this project is contained in our Project Software archive file **060099-11.zip** which can be downloaded free of charge from www.elektor.com.

Soft- and hardware

The software controlling the pump is relatively straightforward; the program can be modified according to requirements and the particular circuit appli-

cation. After applying supply voltage the system is initialised, with all three LEDs activated sequentially. The flashing of SCAN indicator LED on Pin 7 of the Controller indicates that monitoring is in progress. A High output produced by the analogue signal processing section is recognised by the microcontroller at pin 4 and activates the FLOW DETECT indicator LED on pin 6. False triggering is excluded to a large extent automatically as the Controller waits about three seconds for the High signal to be repeated. If this is the case, then the FLOW DETECT and PUMP ON indicator LEDs are activated for 50 s, together with circuit's output pin 3 and consequently the relay as well. Turning on the hot water tap briefly (3 s) is sufficient to put the circulation pump into operation. Switching times should be adjusted in the software according to the length and other characteristics of the plumbing. To facilitate this, the Project Software includes the source code in BASIC as well as the HEX data for programming the Controller.

Construction and installation

As the header photo shows, the author built the hardware using SMD technology, to enable everything to fit inside a small case. However, this is not absolutely necessary, after all the microcontroller comes in a normal DIL enclosure for easy reprogramming. Transparent silicon rubber (as used around sinks and showers) is ideal for fixing the sensor to the back of the enclosure, three or four small fixing pads on the edge of the sensor being entirely adequate. **Figure 2** indicates how the little device can be clamped to the hot water pipe with a couple of cable ties.

The Controller switches the circulation pump on and off using a transistor driver stage and a suitable relay. The relay is connected (looped) into the Live (L) wire of the pump as shown. Since we are dealing with mains voltage here all connections to the relay must be protected from accidental touch contact and installed according to the IEE Wiring Regulations, which are the national standard to which all domestic and industrial wiring must conform in Britain.

Both potentiometers should be adjusted to their middle setting the first time the circuit is installed, so as to give an amplification factor A of around 500 (trimpot P1) and a signal switching threshold of around 1.0 V



Figure 2. Two cable ties clamp the enclosure and sensor (glued onto it) to the hot water pipe.

(trimpot P2) for the signal amplitude. The final task is to turn on the hot water tap and adjust the overall signal amplification factor of the system at P1 so that the circuitry recognises the noise of water flowing reliably (maximum amplification with the trimpot turned fully to the left). If required, the amplitude switching threshold can also be increased or reduced.

(060099-1)

Links:

Data sheet LTC 1049:

www.linear.com/pc/downloadDocument.do?navId=H0,C1,C1154,C1009,C1

027,P1189,D3403

Simulation program:

<http://ltspace.linear.com/software/swcadiii.exe>

Data sheet LM2907:


www.national.com/pf/LM/LM2907.html#Datasheet

University of Oxford/European Union SAVE II project:

www.eci.ox.ac.uk/lowercf/eusave_circulation.html

IEE Wiring Regulations:

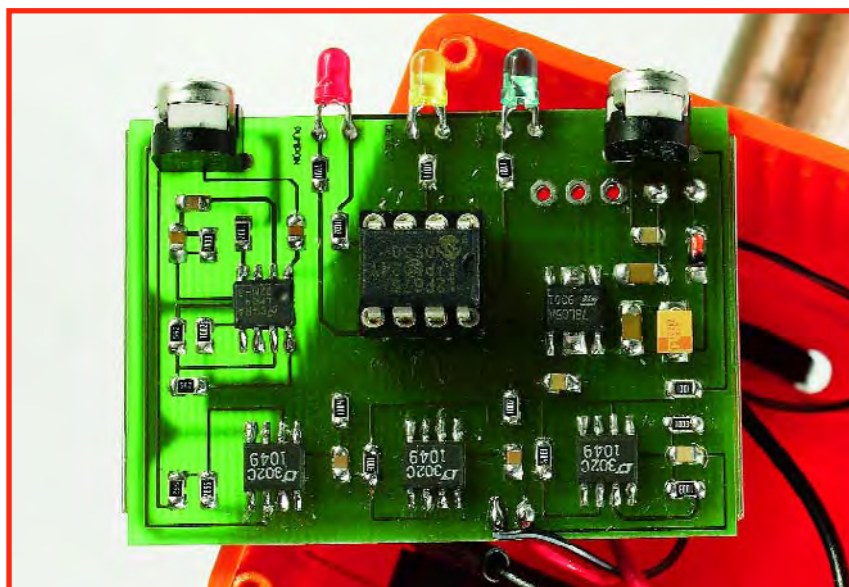[http://en.wikipedia.org/wiki/Electrical_wiring_\(UK\)](http://en.wikipedia.org/wiki/Electrical_wiring_(UK)) and www.iee.org/Publish/WireRegs



i-TRIXX


collection

- Did some-one ring?
- A touch more bling, perhaps?
- Empty battery? Lord and master!
- Battery saver? Battery saver for the caravan!
- When the siren sounds... Temperature-controlled switch
- Check your contacts
- Check Out Your LEDs
- It's Wet! Dicing with LEDs
- Surf simulator
- Save Your Ears
- Electronic poltergeist
- Pump it up: MP3 booster
- Musical saw
- Luminous house number
- Applause generator

i-trixx is powered by



www.elektor.com

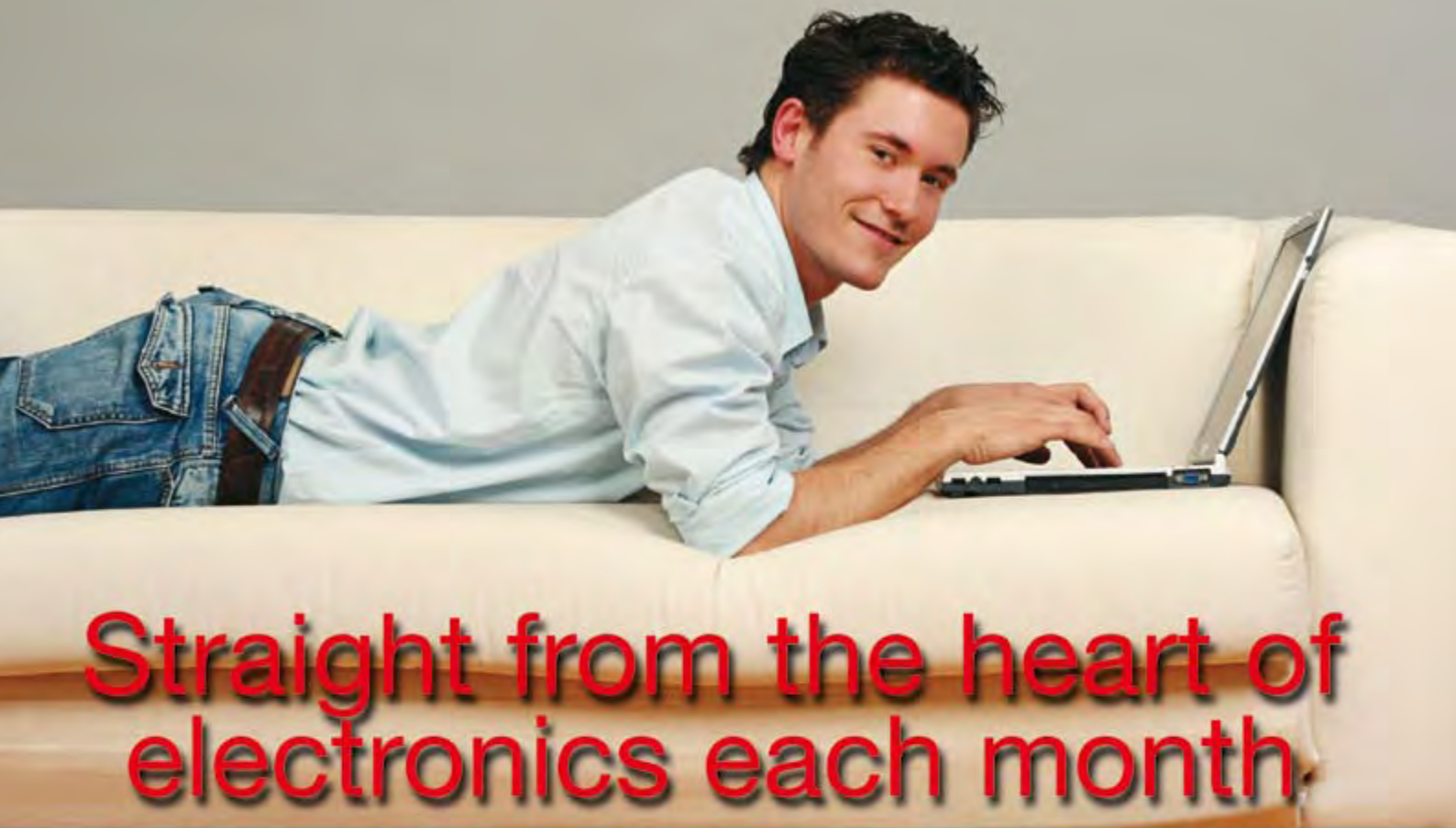

Straight from the heart of electronics each month

This Issue:

24-PAGE 'E-TRIXX' SUPPLEMENT

escaped from the Elektor kitchen

Next Issue:

FREE CD-ROM FROM MICROCHIP/LABCENTER/ELEKTOR

MPLAB — C30 Compiler — EXPLORER-16 — Proteus VSM for PICs



Want to know everything each month?

SELECT YOUR OWN ANNUAL SUBSCRIPTION

AND RECEIVE A FREE 1W LUXEON LED TORCHLIGHT*

Fill out the Order Form with this issue today!

elektor
lectronics

Subscription rates and conditions may be found at the back of this issue.

* Offer available to Subscribers who have not held a subscription to Elektor Electronics during the last 12 months. Offer subject to availability.

CONTENTS

Did someone ring?	4
A touch more bling, perhaps?	5
Empty battery?	6
Lord and master!	7
Battery saver circuit	7
Battery indicator for the caravan	8
When the siren sounds...	9
Temperature-controlled switch	10
Check your contacts	11
Check Out Your LEDs	12
It's Wet!	13
Dicing with LEDs	14
Surf simulator	15
Save Your Ears	17
Electronic poltergeist	18
Pump it up: MP3 booster	19
Musical saw	20
Luminous house number	22
Applause generator	23

i-TRIXX

collection

Circuits Allsorts

This December 2006 issue of *Elektor Electronics* comes with a free collection of simple yet useful and sometimes playful circuits for home construction. The circuits, we hope and expect, are easily understood and reproducible and should appeal to the less advanced electronics enthusiast, although more experienced readers are also bound to find interesting bits and bobs to help them through the dark winter evenings in a pleasant and educational way. A deafening siren that will make burglars run off — electronic dice adds fun to games — a lighting house number helps your friends and acquaintances find your home more easily in the dark. Do you want to stand out from the crowd in the local disco, or encourage annoying visitors to leave early, with a bit of help from an electronic poltergeist? All these, and more, circuits may be found in this 24-page i-TRIXX supplement, which is offered to you free of charge.

All i-TRIXX circuits in this supplement originate from the Elektor labs and are spin-offs from larger projects, scribbblings on the back of envelopes, dead-bug fiddling, 'quick and dirty' solutions, or even design ideas that eventually became so intriguing the designer just had to develop it out for enthusiasm, curiosity and technical satisfaction — all at the same time in not a few cases. In this respect, i-TRIXX are truly 'tricks of the trade' that got pencilled down and eventually — with the help of our editorial team — made it to this publication in print instead of just ending up in a drawer or the more contemporary Windows Recycle Bin.

From over 30 years experience in publishing for electronics enthusiasts all over the world we know that the Christmas holidays are a great time for fun circuits that cost next to nothing to build, often from parts found in the junkbox (*now's a good time to clean it out!*). Especially newcomers to the hobby will find i-TRIXX useful to learn about the process that begins with the ability to 'read' a circuit diagram and culminates in powering up a fully working prototype.

Have fun with the i-TRIXX collection!

Jan Buiting, Editor



Did someone ring?

If you're expecting an important visitor but you just have to step out for a moment, an electronic doorbell memory can come in handy so you can see whether someone rang while you were out. Of course, you can't tell whether it was the visitor you were expecting who dropped by then, but a call to the mobile phone of the person concerned can quickly answer that question. A doorbell memory can also save you the trouble of going to the front door (if you live upstairs) when you think you heard the bell but aren't sure. And if you can't buy one, then of course you can build one yourself! Read on to find out how.


Doorbell memory

It takes only a handful of electronic components to build a handy tale-tale with an LED that indicates whether someone pressed the button of your doorbell. How many times have you thought you heard your doorbell while watching television in the evening? The sound of the well-known 'ding-dong' chimes occurs all too often, especially during the many commercials that nowadays remind us at the most inconvenient times that the gripping film we're watching is only a fantasy. A glance at the LED of the doorbell memory will tell you whether you have to go to the door or can try to escape the ads by zapping to a different channel. Or if you're expecting someone but have to make a quick trip to the neighbours to borrow a few beers for the occasion, it can be handy to be able to see whether your visitor already arrived while you were out. If so, you can always call him or her on the mobile to confess that you hadn't properly prepared for the expected visit.

The circuit is as simple as it is effective. It is connected in parallel with the bell and powered by a 3-V supply formed by two 1.5-V penlight batteries connected in series. The doorbell memory draws so little current that a set of batteries will last several years in normal use. The circuit works as follows. When the supply voltage is switched on with switch S1, capacitor C1 (initially uncharged) prevents transistors T1 and T2 from conducting. LED D2 is off,

and the memory is armed. When the doorbell button is pressed, the memory circuit receives an AC or DC voltage via diode D1, depending on the type of doorbell. It can handle either type. Transistor T1 thus receives a base current, so it starts conducting and drives T2 into conduction. The LED lights up as an indication that the doorbell has rung (i.e. was energised). The combination of transistor T2 and resistor R3 keeps T1 conducting after the bell voltage goes away (when the button is no longer pressed). The memory remains in this state until switch S1 is opened. This switch thus acts as a reset switch as well as a power switch.

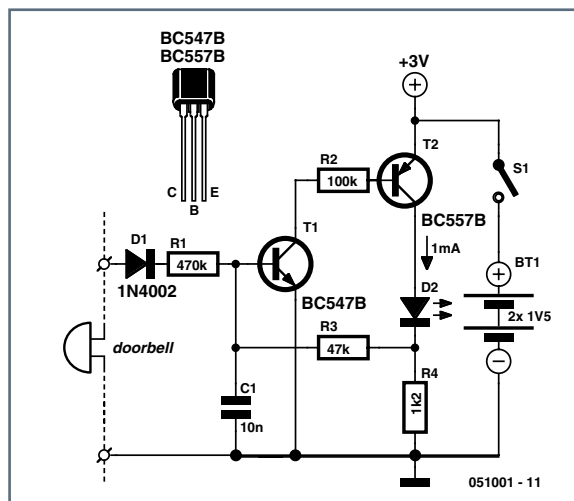The circuit can be assembled compactly on a small piece of perforated prototyping board, so it can be fitted into just about any model of doorbell. The transistors can be replaced by other, equivalent types as long as you use a combination of NPN and PNP types.



i-TRIXX

Electronics inside out!

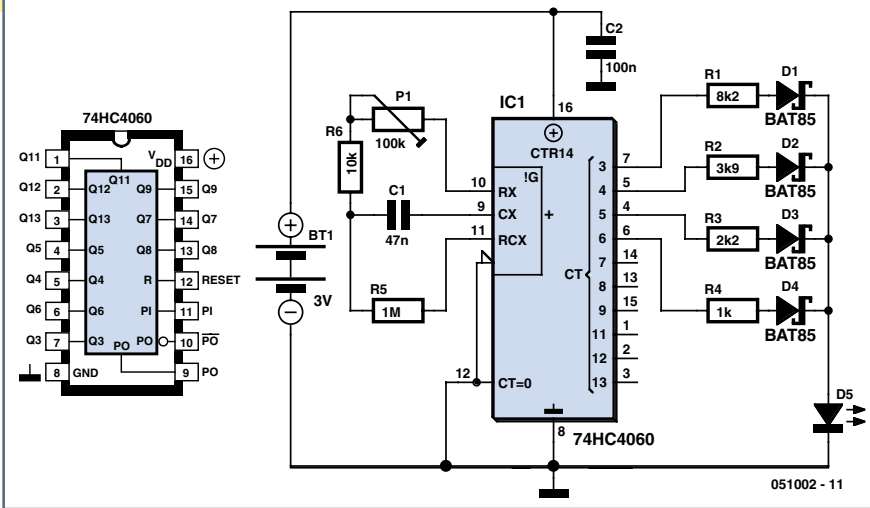


Figure 1. A binary counter (IC1) raises the current through LED D5 from zero to the maximum value in 16 steps.

Want to attract attention at bling-bling parties? That's not so easy, since all the party animals there are doing their best to grab attention. The more bling, the more looks you get. An electronic disco brooch with a cool skin as an eyecatcher can certainly help. If you make it yourself, your chances of success lie entirely in your own hands. And it's certainly not all that difficult!

A touch more bling, perhaps?

Disco brooch

The disco brooch described here is a small but attention-getting bit of electronic circuitry. It lights up a LED in steps until it reaches maximum brightness and then goes out, after which the entire process repeats itself, so you can attract attention at discos and parties. If you solder all the components on a small piece of perforated prototyping board, possibly along with a small battery, you can keep the whole thing nice and compact. We'll come back to that later.

First let's have a brief look at how the circuit works. It is built around IC1 (see **Figure 1**), which is a binary counter chip. A digital pattern of ones and zeros appears at its outputs. Only the outputs on pins 4 to 7 are used in this particular case. They thus generate a count from 0 (binary 0000) to 15 (binary 1111). All outputs are zero at the start, and the LED is dark. Resistors R1–R4 are dimensioned such that the current flowing through LED D5 increases in steps to its maximum value during the following 15 states of the counter. This all happens at a rate that is controlled by the RC network connected to pins 9–11 of the IC. At the end of the cycle, the counter goes back to zero and the LED goes dark. You can use trimpot P1 to adjust the duration of each of the steps. The maximum length of the full step cycle is 1.5 seconds, and the minimum

length is 0.14 seconds. At the minimum time setting, it appears that the LED just blinks.

Diodes D1–D4 isolate the individual outputs of IC1 so they do not interfere with each other. They are Schottky diodes, which have a lower forward voltage drop than normal diodes. As a result, there will be enough voltage to provide adequate current through resistors R1–R4 (and thus through the LED) even when the battery voltage is low. Of course, the brightness of the LED still depends on the battery voltage. In practice, a battery voltage of 3 V gives very nice results. This voltage can be provided by a button cell, since the maximum current at this supply voltage is only around 2 mA. If you use a suitable battery holder designed for PCB mounting, you can tuck the button cell away nicely on the circuit board (see **Figure 2**).

Of course, you also have to be able to switch the brooch on and off. You can use a safety pin for this purpose, and at the same time it can do what it is designed for, which is to attach the brooch to your clothing. To prepare the safety pin for this purpose, cut a piece out of the fixed leg. That represents the opened switch. The easiest way to do this is to first solder the pin in the proper position on the circuit board (see **Figure 3**). Use a bit of sandpaper to roughen the surface of the pin first so the solder will stick better. After the pin is soldered securely in place, cut out a piece in the middle and your DIY switch is ready to use.

Figure 2. Fit the components as close together as possible on a piece of perforated circuit board to keep the finished circuit compact.

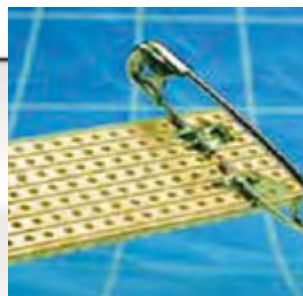


Figure 3. You can make an on/off switch from a safety pin, which also serves to pin the brooch to your clothing.





Empty battery?

Photo: www.energizer.com

Is the battery empty, or is there something wrong with the device? That's always a difficult question when your walkman or some other battery-powered device appears to be dead when you switch it on. Before you take it to the shop for servicing, the first thing you should do is to test the battery or batteries. Of course, this means you need a reliable battery tester, but it also means you can limit the damage to the cost of a battery or two and a one-time investment of time and money in building a suitable tester.

Battery tester


Many commercial battery testers consist of nothing more than a resistor, a simple little meter and a pushbutton. Some manufacturers include an even simpler tester with a set of batteries, consisting of a strip of plastic with a layer of some sort of electrically conductive material that changes colour when a current flows through it. If you press this strip over the battery between the positive and negative terminals, a fully charged battery will cause a more intense change in colour than a partially discharged battery. Naturally, tests of this sort do not provide especially reliable or accurate results.

The idea behind the circuit described here is to load a single battery, a set of batteries connected in series, a rechargeable battery, or even a small button cell with a reasonably constant current and use a separate multimeter or voltmeter module (M1) to check the voltage. A quickly decreasing voltage indicates that the battery or batteries will have to be replaced soon.

If a constant-current circuit is used for the load, the current can never too be large and there is no need to make an adjustment for the number of cells. The constant-current circuit is specially designed to work with a voltage as low as 0.9 V. It's quite difficult to make a circuit work at even lower voltages with normal transistors.

The active constant-current element is transistor T1. The current through it is held constant by comparing the voltage across resistor R1 in its collector path with a relatively constant reference voltage across diode D1. This comparison is provided by differential amplifier T3/T4. The voltage across diode D1 (a Schottky type) is reasonably constant by nature, but it is also stabilised by using FET T5 as a simple constant-current sink. T5 also limits the current at relatively high voltages (with several batteries in series). The constant voltage across D1 is transferred to resistor R12 by differential amplifier T1/T2, so a constant current flows through R1 from the battery or batteries being tested. R1 has a relatively low resistance, so this current is larger than the current drawn by the rest of the circuit. The quiescent current, which incidentally is also reasonably constant, is thus negligible. The test current thus remains reasonably constant while the battery or batteries is/are being tested.

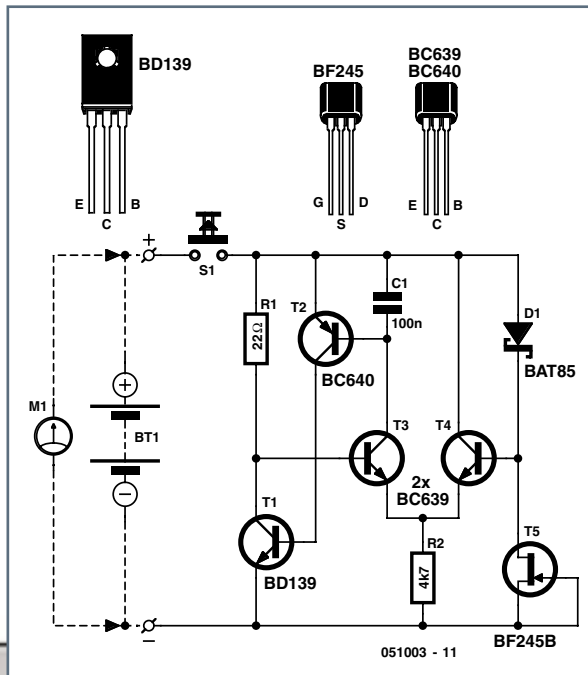
The maximum battery voltage that the tester can handle is set by T5, and here it is 30 V. To ensure that T1 does not get too warm at high battery voltages, keep the test as short as possible. Use a pushbutton switch as a test switch so the battery being tested cannot be left under load by accident.



In these days of environmental awareness it has become desirable to use batteries as efficiently as possible. A lot of battery powered electronic devices do not switch themselves off automatically, such as multimeters. Forgetting to turn these off isn't just a nuisance (since you'll find that you don't have a spare battery at the crucial moment), but you're also unnecessarily reducing the lifespan of the batteries and causing extra pollution. And it isn't really necessary for those electronic thermometers to display the temperature day and night. As a skilful and environmentally aware i-TRIXXer you should make one or more of these small battery saver circuits.

i-TRIXX

Electronics inside out !

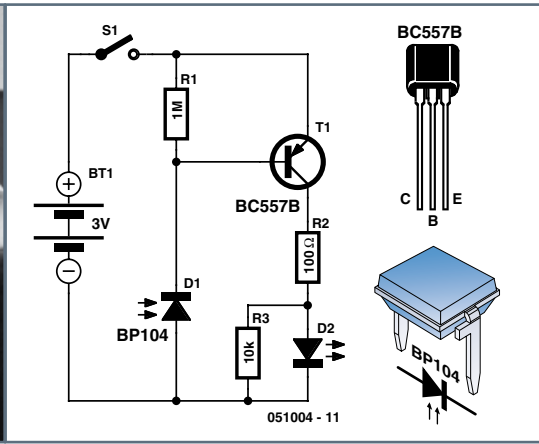

Lord and master!


Men in particular enjoy the convenience of television remote controls – often to the annoyance of their female partners. Men apparently want to know what they're missing when the TV is tuned to a particular programme, so they like to keep zapping to other channels. With the remote control in their hands, they feel like they are the lord and master of the TV set. They are thus completely at a loss if the remote control doesn't work properly. There are many reasons why a remote control unit can malfunction, such as defective IR receiver in the TV set, a defect in the remote control, or empty batteries. Here a tester that can determine whether the remote control unit still emits an IR signal can come in handy. If you want to keep the IR reins firmly in hand, you can build your own IR detector.

IR detector

If you have a few remote control units around the house, you'll appreciate this little circuit. The LED clearly indicates whether the remote control unit actually emits an IR signal when you press one of the buttons on the unit.

The circuit uses a photodiode (D1) to sense the infrared light emitted by the remote control unit (if it is working properly). The plastic package of this diode acts as an IR filter that is only transparent to invisible light with a wavelength of 950 nm. Although there are probably some remote control units that use IR diodes operating at a different wavelength, the circuit has enough sensitivity to detect them as well.

If enough light falls on photodiode D1, an electrical current will flow through the diode. In fact, what happens is that the leakage current increases, since photodiodes are usually operated in reverse-biased mode (as is the case here). If the current is large enough, transistor T1 conducts and causes LED D2 to light up. If LED D2 remains dark, this means the remote control unit is not producing any IR light. This can be due to an empty battery (or batteries) or a fault in the internal circuitry. Pay careful attention to the polarisation of the photodiode when wiring it into the circuit. The cathode is clearly marked by a special pin. For LED D2, use a low-current type that can handle a current of at least 7 mA. The detector can be powered by a pair of 1.5-V penlight cells connected in series.

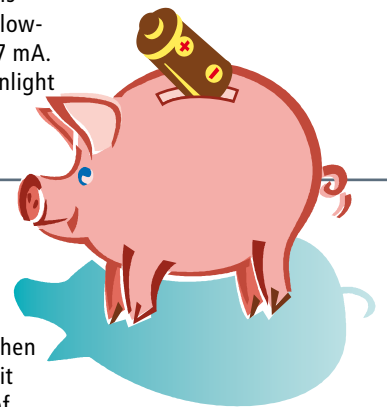


Battery saver circuit

i-TRIXX presents a small electronic switch that connects a battery to the equipment for a certain amount of time when a push-button is momentarily pressed. And we have also taken the ambient light level into account; when it is dark you won't be able to read the display so it is only logical to turn the switch off, even if the time delay hasn't passed yet.

The circuit is quite straightforward. For the actual switch we're using a well-known mosfet, the BS170. A mosfet (T2 in the circuit) used in this configuration doesn't need a current to make it conduct (just a

voltage), which makes the circuit very efficient. When the battery is connected to the battery saver circuit for the first time, capacitor C2 provides the gate of the mosfet with a positive voltage, which causes T2 to conduct and hence connect the load (on the 9 V output) to the battery (BT1). C2 is slowly charged up via R3 (i.e. the voltage across C2 increases). This causes the voltage at the gate to drop and eventually it becomes so low that T2 can no longer conduct, removing the supply voltage to the load. In this state the battery saver circuit draws a very small current of about 1 μ A. If you now press S1, C2 will discharge

Battery indicator for the caravan

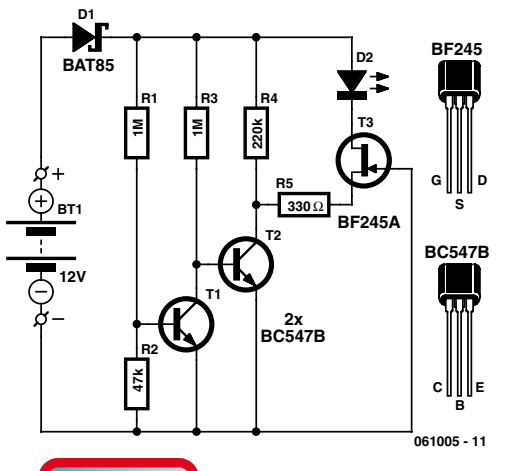

This i-TRIXX circuit can prevent a whole lot of trouble for those of you who go on holiday in a caravan. It would be a significant damper on your holiday spirit when you are ready to leave the camping and discover that you have used your battery too much and that you are now unable to start the car. This annoyance can be avoided if you were warned early enough by an illuminated LED when the charge in the battery threatens to become too low. A quiet, out of the way, in the countryside camping is what modern people look for to be able to unwind. However, we do not want to be completely deprived of all our creature comforts. We don't cope very long without electric light or a TV! And in the absence of a mains power outlet the car battery has to function as energy source, with the risk that later on there will be too little left to start the engine. The little circuit presented here gives you an early warning when the battery voltage (and therefore its stored energy) threatens to become too low.




The setting of T1 and T2 determines whether LED D2 will light up when the battery voltage drops below a certain level. Junction FET T3 is used as a current source in order to try to keep the current through the LED as constant as possible. In this way the indicator remains lit even when the battery is in a state of very deep discharge (< 4 volt). The LED is a good low-current type that is still very bright at a very small current (1 to 2 mA). Voltage divider R1 and R2 has been calculated such that T1 will start to conduct when the voltage of the battery is greater than 12 V. If you think this threshold is too high (or: if you think that you can still start your car with a lower battery voltage), then you can reduce the value of R2 or replace it with a 50-k preset (connected as an adjustable resistor). When T1 conducts, the base current to T2 is interrupted and the collector of T2 will become high through R4. In this state T3 does not conduct and the LED is off. When the battery voltage drops below 12 V, T1 will block and T2 will start to conduct. R5 is now connected to ground via T2 which turns T3 into a current source of about 2 mA that drives the LED. There is, of course, a transition region during which

the current through the LED slowly increases; after all, T1 and T2 do not switch with infinite gain! In our prototype the LED changed from fully off to fully on at a voltage variation from 12 to 11 V. As a bonus, a partially illuminated LED gives a rough indication as to how much the voltage actually is. Diode D1 prevents the circuit from inadvertently giving up the ghost if the circuit is connected incorrectly to the battery (reverse polarity). In practice, because of variations in the specifications of the transistors, the threshold and the current level through the LED can be different. Test the circuit thoroughly before using it. If you want a brighter indicator, you can increase the current through the LED by replacing T3 with a BF245B or BF245C. When the LED is off, the current through the circuit is barely 30 μ A at a battery voltage of 14.4 V. With the LED is on and at a battery voltage of about 10 V, the current consumption is about 2 mA. Even with an illuminated LED, the circuit is not likely to be the cause of a flat battery. Even a good quality battery will have a selfdischarge rate which is many times greater than the maximum current consumption of this circuit!

and the circuit returns to its initial state, with a new turn-off delay. Resistor R5 is used to limit the discharge current through the switch for a few hundredths of a second to fully discharge C2. In our prototype, connected between a 9 V battery and a load that drew about 5 mA, the output voltage started to drop after about 26 minutes. After 30 minutes the voltage had dropped to 2.4 V. You should use a good quality capacitor for C2 (one that has a very low leakage current), otherwise you could have to wait a very long time before the switch turns off!

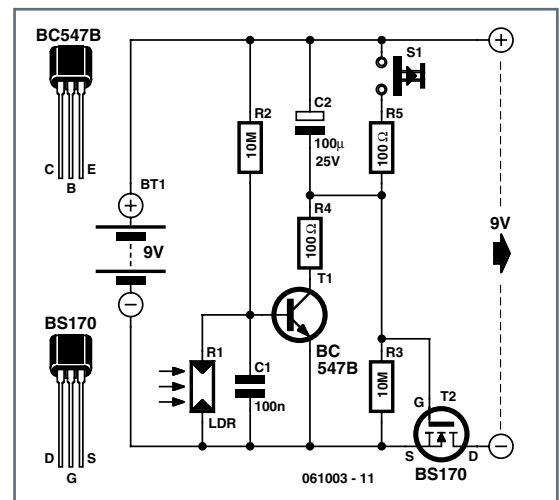The ambient light level is detected using an LDR (R1). An LDR is a type of light sensor that reduces in resistance when the light level increases. We recommend that you use an FW150, obtainable from



When the siren sounds...

In Greek mythology, a siren was a demonic being (half bird, half woman). Later on this idea was transformed in art into a mermaid: a combination of a fish and a woman. Mechanical and electromechanical versions were invented even later, and electronic models were developed in the last century. Sirens are characterised by their ability to produce sounds that attract attention. With the exception of the flesh-and-blood models, they are thus used to warn people in a particular area of impending danger. The electronic versions are the most suitable for DIY construction.

Siren

There are lots of different ways to make an electronic siren. Here we use a binary counter (IC1) and an analogue multiplexer (IC2, which is a digitally configurable switch). The counter is a type 4060, which has an integrated oscillator. The oscillator generates the tone of the siren. The frequency of this tone depends on the resistance between pin 10 of IC1 and the junction of C1 and R9.

The trick here is that the analogue multiplexer adjusts the clock rate of the counter depending on the state of the counter. The frequency of the oscillator decreases as the resistance between pin 10 of IC1 and the junction of C1 and R9 increases, and the lower the frequency of the oscillator, the longer the counter remains in its current state. This means that high frequencies present on pin 9 are generated for shorter times than low frequencies.

The values of resistors R1–R8 increase in uniform steps of approximately 10 k Ω , with the result that the output on pin 9 is a series of eight decreasing frequencies, and this series is constantly repeated in cyclical fashion. Transistor T1 (BD139) and resistor R10 are included to boost the signal from pin 9 to a level suitable for

e.g. Conrad as part number 183547-89. When there is too little light its resistance increases and potential divider R1/R2 causes transistor T1 to conduct. T1 then charges up C2 very quickly through R4, which limits the current to a safe level. This stops T2 from conducting and the load is turned off. The choice of value for R2 determines how dark it has to be before T1 starts to conduct.

The battery saver circuit can be added to devices that use 6 or 9 volt batteries and which don't draw more than 100 mA. The circuit can be built on a piece of experimenter's board and should be made as compact as possible so that it can be built into the battery powered device.



driving a loudspeaker. The sound produced by this circuit may be familiar to some of our readers (especially if their memories extend back to older types of pinball and arcade game machines).

You can also adjust the characteristics of the sound, since this circuit is primarily an invitation to experiment with the component values – in particular R1–R8 (10 k Ω minimum), but also C1. The values of R1–R8 do not have to follow a strictly increasing series; they can also be selected randomly.

The current consumption is primarily determined by resistor R10 and the loudspeaker (in our case an 8- Ω type). The siren circuit draws approximately 33 mA at a supply voltage of 9 V. The supply current is 11 mA at the minimum supply voltage of 4 V, and it increases to 60 mA at the maximum supply voltage of 15 V.



National Archaeological Museum of Athens

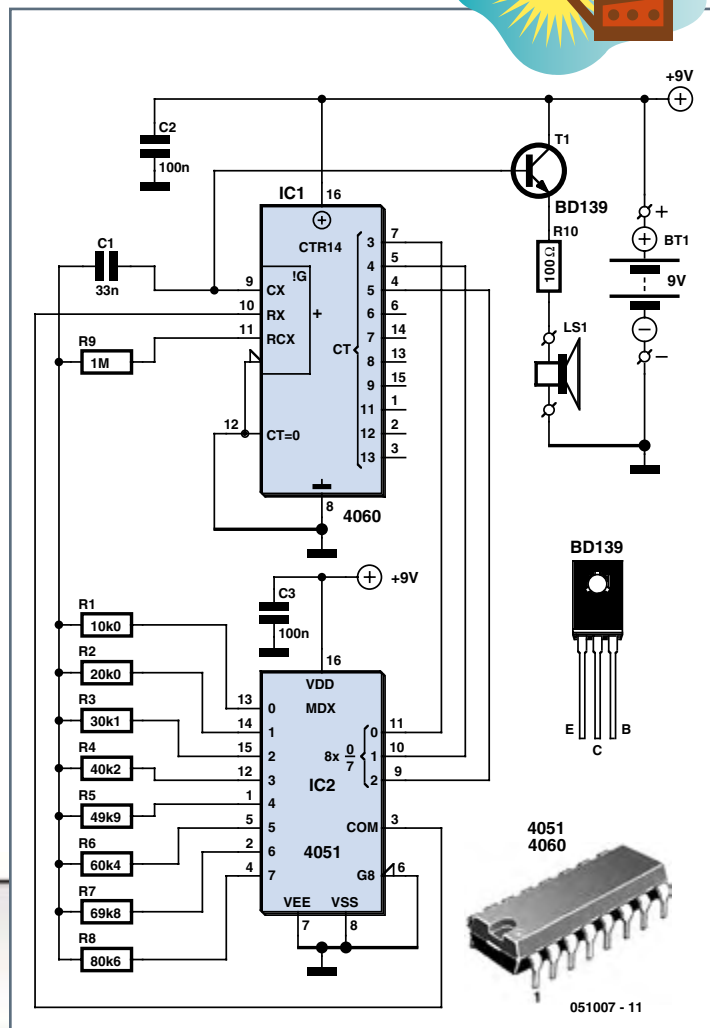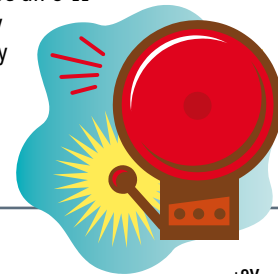

Temperature-controlled switch

It sounds rather mysterious: a switch that is controlled by its ambient temperature. All without the touch of a human hand, except for when you're building this sort of electronic thermostat.

There are a lot of handy uses for a thermally controlled switch. If the temperature inside your PC gets too high sometimes, the circuit can switch on an extra fan. You can also use to switch on an electric heater automatically if the room temperature is too low. There are innumerable potential applications for the thermostat described here.


There are lots of ways to measure the temperature of an object. One very simple way is to use a semiconductor sensor, such as the National Semiconductor LM35 IC.

This sensor is accurate to within 0.5 °C at 25 °C, and few other sensors can do better or even come close to this level of accuracy. In the circuit described here, the sensor (IC2) generates an output voltage of 10 mV/°C, so the minimum temperature that can be measured is 0 °C. At 25 °C, the output voltage of the sensor is (25 °C × 10 mV/°C) = 0.25 V.

The circuit uses a TLC271 opamp as a comparator. It compares the voltage from the temperature sensor, which is connected to its non-inverting input (pin 3), with the voltage on its inverting input (pin 2). The latter voltage can be set with potentiometer P1. If the voltage from the sensor rises above the reference value set by P1 (which represents the desired temperature), the output of the comparator toggles to the full supply voltage level. The output is fed to transistor T1, which acts as a switch so the output can handle more current. This makes it possible to energise a relay in order to switch a heavy load or a higher voltage. The transistor also supplies current to LED D1, which indicates whether the temperature is above the reference value. The reference value can be adjusted by P1 over the range of 18–30 °C with the indicated component values. Of course, you can adjust the range to suit your needs by modifying the value of R1 and/or R2. To prevent instability in the vicinity

of the reference value, a small amount of hysteresis is provided by resistor R4 so the temperature will have to continue rising or falling by a small amount (approximately 0.5 °C) before the output state changes.

The LM35 is available in several different versions. All versions have a rated temperature range of at least 0–100 °C. One thing you may have to take into account is that the sensor has a relatively long response time. According to the datasheet, the sensor takes 3 minutes to reach nearly 100% of its final value in still air. The opamp has very low drift relative to its input voltages, and in the low-power mode used here it draws very little current. The sensor also draws very little current, so the total current consumption is less than 80 µA when LED D1 is off. The advantage of low current consumption is that the circuit can be powered by a battery if necessary (6 V, 9 V or 12 V). The sensor has a rated operating voltage range of 4–30 V, and the TLC271 is rated for a supply voltage of 3–16 V. The circuit can thus work very well with a 12-V supply voltage, which means you can also use it for car applications (at 14.4 V). In that case, you must give additional attention to filtering out interference on the supply voltage.

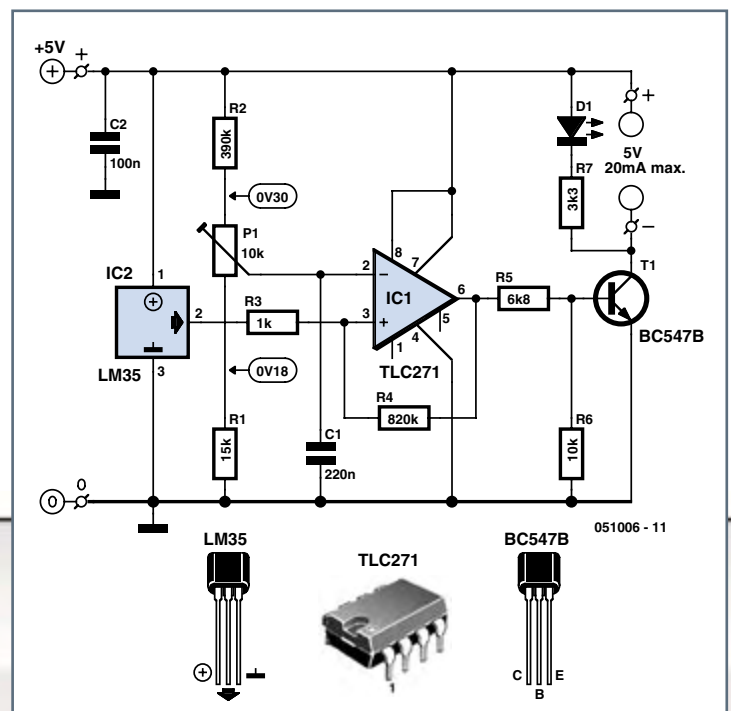

i-TRIXX

Electronics inside out!

Check your contacts

Having good contacts is important – not only in your daily life, but also in electronics. In contrast to social contacts, the reliability of electrical contacts can be checked quickly and easily. Various types of continuity testers are commercially available for this purpose. Most multimeters also have a continuity test function for electrical connections. A simple beep helps you tell good contacts from bad ones. However, in some cases the tester doesn't produce a beep because it won't accept contact resistances that are somewhat higher than usual. Also, poorly conducting (and thus bad) connections are sometimes indicated to be good. Here e-trix comes to your aid with a design for a DIY continuity tester that helps you separate the wheat from the chaff.



Photo: Hirschmann Electronics BV

Continuity tester

Many multimeters have a built-in continuity test function. However, in many cases the resistance necessary to activate the beeper when you are looking for bad connections is just a bit too high. It can also happen that the beeper sounds even though the resistance of the connection is unacceptably high. This circuit lets you adjust the threshold between bad and good contacts to suit your needs.


The circuit is built around an operational amplifier (IC1) wired as a comparator. The opamp compares the voltage on its inverting input (pin 2) with the voltage on its non-inverting input (pin 3). The voltage on pin 3 can be set using potentiometer P1, so you can set the threshold between good and bad connections. When test probes TP1 and TP2 are placed on either side of a connection or contact to be tested, a voltage is generated across the probes by the current flowing through resistors R1 and R3, and it appears on pin 2 of the opamp. This voltage depends on the resistance between the probe tips. If the voltage on pin 2 is lower than the reference voltage on pin 3, the difference

is amplified so strongly by the opamp that its output (pin 6) is practically the same as the supply voltage. This causes transistor T1 to conduct, which in turn causes DC buzzer BZ1 to sound. This means that the resistance of the connection being tested is less than the threshold value set by P1, and thus that the connection is OK.

By contrast, a bad connection will cause the relationship between the voltages on the inputs of the opamp to be the opposite, with the result that its output will be at ground level. The transistor will not conduct, and the buzzer will remain still.

To ensure that the opamp 'toggles' properly (which means that its output goes to ground level or the supply voltage level) when the difference voltage is sufficiently large and does not oscillate during the transition interval due to small fluctuations in the difference voltage produced by interference, its output is coupled back to its non-inverting input (pin 3) by resistor R4. This causes any change on the output to be passed back to this input in amplified form, with the result that the detected difference voltage is amplified (and thus boosted).

Diodes D1, D2 and D3 protect the circuit against excessive positive and negative input voltages that may come from the connections or contacts being tested. They also ensure that the continuity tester does not inject excessively high voltages into the item under test. Capacitor C1 suppresses high-frequency interference. The circuit draws only a small supply current, so it can easily be powered by a 9-V battery.

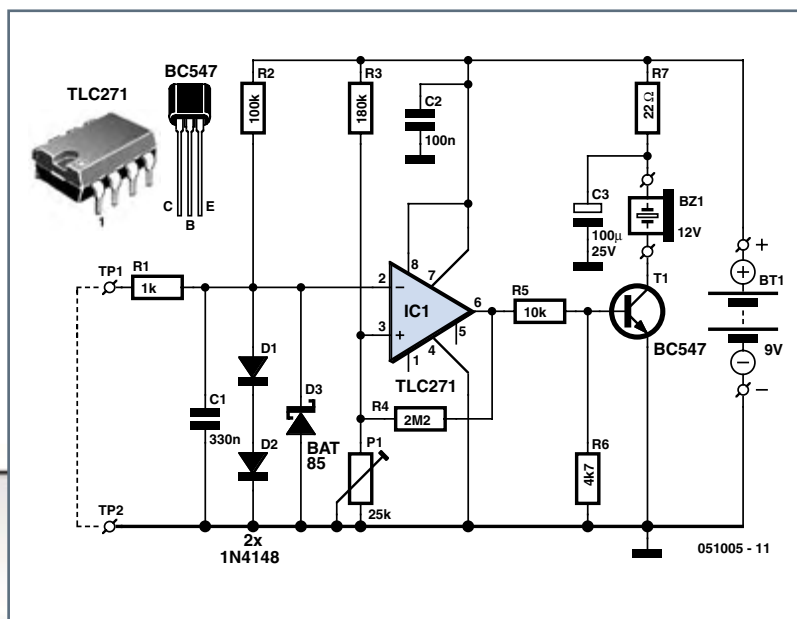



Check Out Your LEDs

You have to admit that these tiny electronic lamps are handy, and they last almost forever. Around 40 years after Nick Holonyak developed the first LED, they have become just about indispensable. Any self-respecting electronics hobbyist always has a few in his junk box. But before you use LEDs, it's a good idea to check them out. With a LED tester, you can even do it in the dark!


LED tester

LEDs are available nowadays in all shapes and colours. There are types with clear, colourless packages, while others have coloured plastic packages. Many modern types of LEDs need less current than older types. Some of them provide quite a puddle of light if you give them a decent amount of current.

When you're working with used LEDs from the junk box, there's a good chance that you can't tell which lead is which any more. (If the leads haven't been trimmed, the short lead is always the cathode lead and the long lead is the anode lead.) If you use several LEDs in a display where they all have the same current, you naturally want all the LEDs to have the same brightness. But that's not always the case, even with LEDs of the same type. To save yourself unnecessary soldering work, it's a good idea to check the LEDs out first. That's the job of the LED tester described here.

This circuit can be used to test up to three LEDs at once, connected in series. You can easily increase that number by using a higher supply voltage. If you do so, you should allow 2.7 V for each additional LED. The Zener diodes are included in the circuit so it can also be used to test one or two LEDs. Another benefit of the Zeners is that even if one or more of the LEDs are defective or connected with reverse polarity, the remaining ones will light up normally. That makes it easy to spot suspect LEDs. If you extend the tester to handle more LEDs, you must add another Zener diode for each LED position.

The test current that flows through the LEDs is held reasonably constant by FET T1, independent of the number of LEDs being tested. The FET is used as a constant-current source to keep the circuit as simple as possible. The drawback of this approach is that the tolerance range of FET characteristics is especially large. The type used here even has three versions: A, B and C. We used the B version here so the current through the LEDs can be adjusted using

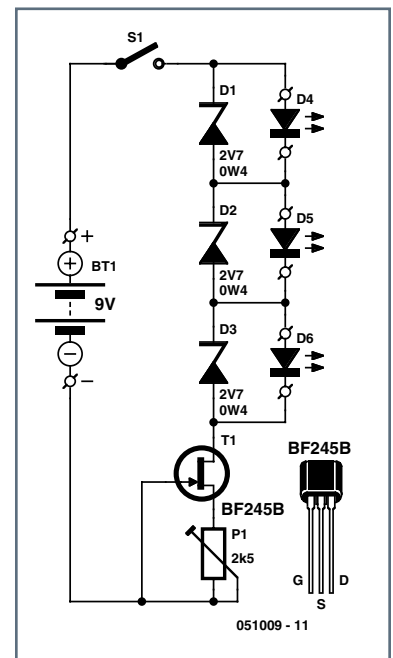

potentiometer P1 over the range of 1–7 mA. If you need more current, you can use a BF254C instead, but then you will also need a higher supply voltage. For example, you can connect two 9-V batteries in series or power the circuit from a mains adapter. However, some LEDs have a maximum rated current of only 5 mA. You should thus always start testing at the lowest current by setting P1 to maximum resistance. You can easily see from the brightness whether you need more current. If an LED does not light up, it may be defective or connected the wrong way round. Reduce the current to the minimum level before reversing or replacing any LEDs.

If you label the polarity of the terminals on the LED tester, you can easily mark the cathode and anode leads of the tested LEDs. To make it easy to swap the LEDs, you can use an IC socket as a test socket. The selected Zener diodes were chosen to make the tester suitable for red, yellow and green LEDs. Red LEDs have a forward voltage of 1.6 V to 1.8 V. The value for yellow LEDs is around 1.9 V, and with green LEDs the forward voltage can be as high as 2 V. If you also want to test modern blue or white LEDs, you will have to replace the Zener diodes with types having a voltage of 4.7 V or 5.1 V. The supply voltage will also have to be increased accordingly – for example, by connecting two 9-V batteries in series.



i-TRIXX

Electronics inside out!

It's Wet!



Have you ever seen the stairs to one of the upper stories in your house turn into a waterfall? Or maybe you've come home to find your aquarium fish trying to swim across the carpet? For your sake, we hope not, because the consequences are usually fairly dramatic. With a handful of electronic components, you can at least ensure that you will be warned before you have to put on your waders.

Water alarm

It's better to prevent water problems than to have to correct them. But no how many precautions you take, an occasional leak can still happen. A burst water supply hose for the washing machine, a bath tap that someone forgot to turn off, a broken aquarium wall, or a leaking boiler or central heating tank – anything is possible. In such cases, it's nice to be warned as quickly as possible, for example by an acoustic water alarm. Then you can at least limit the damage. If you're handy with a soldering iron and know the difference between an IC and a PC, you'll no doubt enjoy building the electronic water alarm described here.

The circuit takes advantage of the fact that 'normal' water is always slightly contaminated, even if only slightly, and thus conducts electricity to a certain extent. It is built around an popular IC from the somewhat antiquated 4000-series logic family: the 4093. This IC contains four inverted-output AND gates (NAND gates) with Schmitt-trigger inputs. If water is detected between the probes, it emits an intermittent and rather irritating beeping tone. The conductivity of the water is used to active the circuit built around IC1a. The two electrodes (probes) are fitted at the lowest point where water will come to stand. They can be two tinned copper wires, but you can also use two pieces of circuit board with the copper surface coated with solder. The combination of IC1a, resistor R2 and capacitor C2 forms a simple oscillator that produces the intermittent (on/off) effect of the alarm. If no water is present between the

probes, the input of IC1a is held low by R1 and the output of IC1b is also low. The oscillator is not active in this state. If moisture is sensed, the supply voltage pulls input 1 of gate IC1a high via the conductive water, causing the gate to start oscillating. Whenever the output of IC1b is high, the tone generator built around IC1c is enabled, and in turn it energises buzzer BZ1. The net result is a periodic, intermittent beeping tone.


You can adjust the intermittent effect of the sound produced by the water alarm to suit your taste by simply adjusting the value of R2 or C2. You can also set the pitch of the sound with P1. The closer the pitch is to the resonant frequency of buzzer BZ1, the louder the tone will be. You should set the sound to the most irritating level possible.

Gate IC1d is used to boost the amount of power than can be pumped into the buzzer. It inverts the output signal from IC1c to double the voltage applied to the buzzer.

Naturally, the circuit of the alarm must be fitted somewhere that will remain high and dry. Use a pair of thin twisted wires to connect the electrodes (probes) to the board. Naturally, you should use insulated, flexible wire for this purpose. Twisting the wires together makes the relatively long connection between the probes and the circuit less sensitive to false alarms due to external electromagnetic interference.

The current consumption is very low (less than 0.1 μA) when everything is dry. When the buzzer is energised, the current consumption can rise to around 2 mA. We measured 3 mA with the frequency set to the maximum

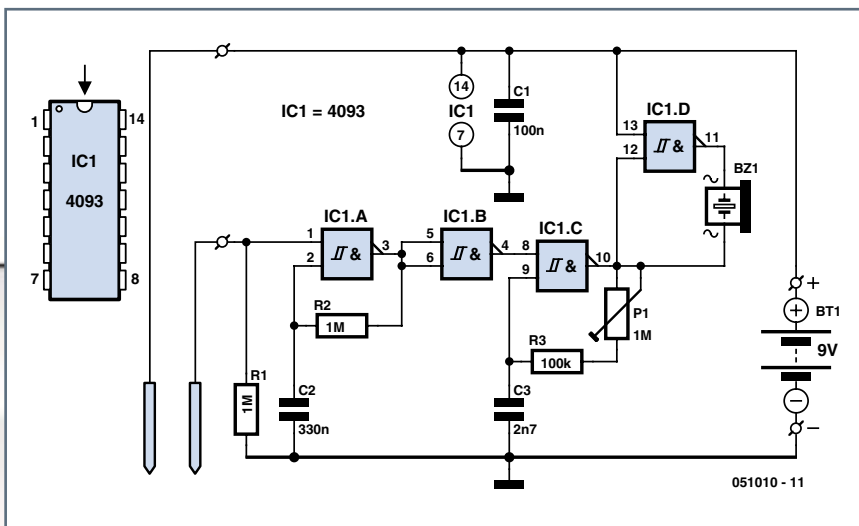value. The battery will thus last for several years as long as no water is detected. Of course, you should bear in mind that the battery might start leaking after a while...



Dicing with LEDs



Every self-respecting DIYer makes his own electronic dice with LEDs as spots. Then you don't have to throw the dice anymore – just push the button. The electronics also ensures that nobody can try to improve his luck by fiddling with the dice. Too bad for sore losers!

This circuit proves that an electronic die built using standard components can be made quite compact. The key component of here is a type 4060 digital counter (IC1). This IC has an integrated oscillator stage, so only two resistors (R7 and R8) and a capacitor (C7) are necessary to generate the clock signal. The clock signal is divided by various factors by the internal digital circuitry of the IC. The division factors are designated by 'CT' in the IC drawing symbol. For instance, the signal on the CT3 output (pin 7) is a square wave with a frequency equal to the clock frequency divided by 2^3 (8). The clock signal is divided by 2^4 (16) on the CT4 output, by 2^5 (32) on the CT5 output, and so on. This means the output signals form a binary number that

counts upwards, which is naturally what a counter does.


Of course, a die has only six possible values marked on the six sides of a cube. This means that at least three bits (the first three outputs) of the counter are necessary to drive a display. Eight different counter states (2^3) can be represented with three bits, but in this case the counter must be restricted to six states. To make sure this happens, D11, D12 and R6 are used to reset the counter to its initial state when it reaches the seventh state, which means when it reaches a binary count of 110. When this happens, pins 4 and 5 of the IC are both logic '1' (high level), which causes a logic '1' to be applied to pin 12 via resistor R6. This causes the counter to be reset, which is what we want.

The display consists of seven LEDs arranged in the same pattern as the usual markings on a normal die. This arrangement is shown in the schematic diagram. Before you begin thinking about the proper logical connections between the LEDs and the counter outputs, you can start by noting that except for the '1' state there will always be two LEDs lit up at the same time. This means that only four distinct indications are necessary, instead of seven (with a total of seven LEDs). Another advantage of this is that the current consumption can be reduced by connecting pairs of LEDs in series.

Resistors R1–R4 limit the current through the LEDs to approximately 2 mA. This means you have to use low-current LEDs. They are nice and bright at a current of 2 mA. Resistor R3 has a higher value because only one LED is driven via it.

For convenience, the circuit is dimensioned based on using a 9-V battery. The current consumption of the circuit depends on the number of LEDs that are illuminated, and with our prototype it varied over a range of approximately 2.5 mA to 6.5 mA. The LEDs still produce enough light even when the supply voltage is as low as 6 V, but this depends strongly on the characteristics of the low-current LEDs used in the circuit.

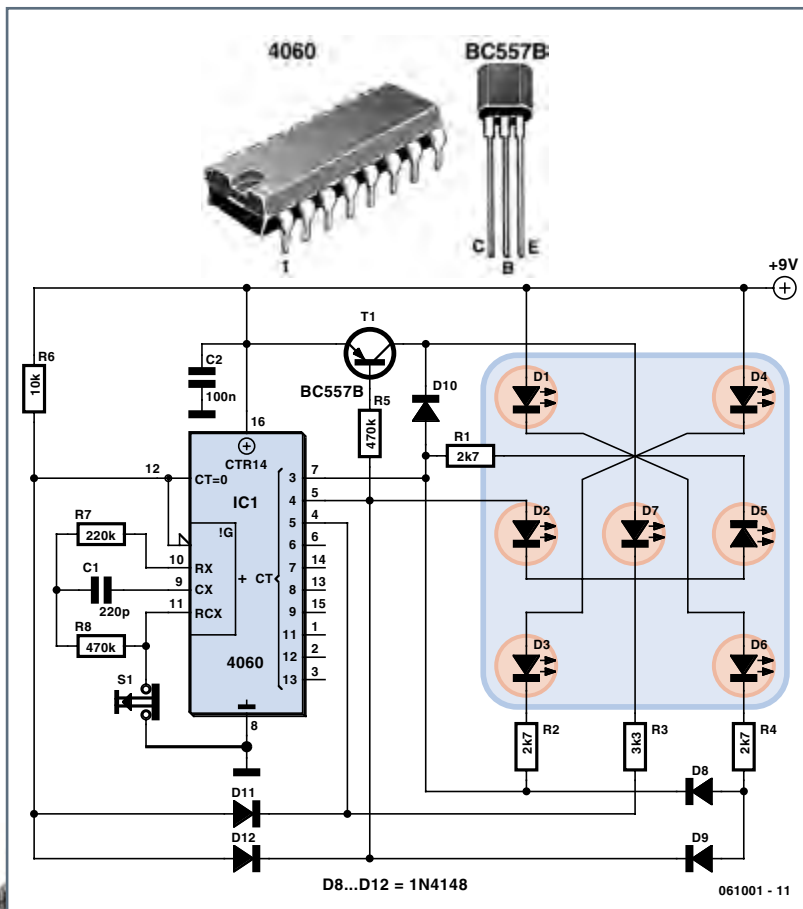Diodes D8–D10 and transistor T1 are necessary to enable all the states of a normal die to be shown. By that, we primarily mean the states with two or three spots, which must be located diagonally.



state	binary	LEDs 'on'	spots
1	000	1, 3, 4, 6, 7	5
2	001	1, 6, 7	3
3	010	1, 2, 3, 4, 5, 6	6
4	011	7	1
5	100	1, 3, 4, 6	4
6	101	1, 6	2

i-TRIXX

Electronics inside out !

Surf simulator



For readers who want to delve more deeply into the design, the following table shows the six different binary states, which LEDs are lit up for each state, and the number of spots shown by the die.

The die is operated by switch S1. In the quiescent state, the break contact of S1 is closed and the oscillator is stopped because the input of the oscillator stage is connected to ground via the switch. When S1 is pressed, the oscillator starts running and causes the states of the LEDs to change at a rate of 1 kHz, which is too fast to follow with the naked eye. This high frequency ensures that the state of the die is purely random when S1 is released, so there is no regularity or pattern in the results.


The circuit can be assembled on a small piece of perforated prototyping board. Fit the LEDs in exactly the same pattern as shown in the schematic diagram, since otherwise the spot patterns will not correspond to a real die. When you have assembled the circuit board, fit it in a plastic enclosure along with a 9-V battery to provide power.

Do you long for a beach holiday on a tropical island, but you don't have the necessary wherewithal? We've got just the answer: build the i-TRIXX surf simulator, put on your headphones, and dream yourself away from this dreary realm. Let the rhythmic rush of the waves transport you to a sun-drenched beach with gently swaying palm trees, and relax for a while before returning to a chilly confrontation with reality. That's the ultimate in low-budget travel. Book now!

Isn't it great to relax on the snow-white sand of a tropical beach with a cool drink in your hand? To enjoy the magnificent of earthly creation while letting your thoughts drift on the hypnotic mantra of the breaking surf? No relaxant brewed by human hands can possibly compete with it! But when you start thinking about how much it all costs, you'll reach for the headache pills instead. Fortunately, there's a less expensive way to relax — with a bit of electronics that imitates the soothing sound of the sea. You'll have to imagine the corresponding surroundings on your own. A sunlamp and a few scoops of sand may help...

This circuit uses more components than most of the i-TRIXX do it yourself projects, but this doesn't make it harder to understand how it works. We have also designed a PCB layout for the circuit, which makes DIY construction that much easier.

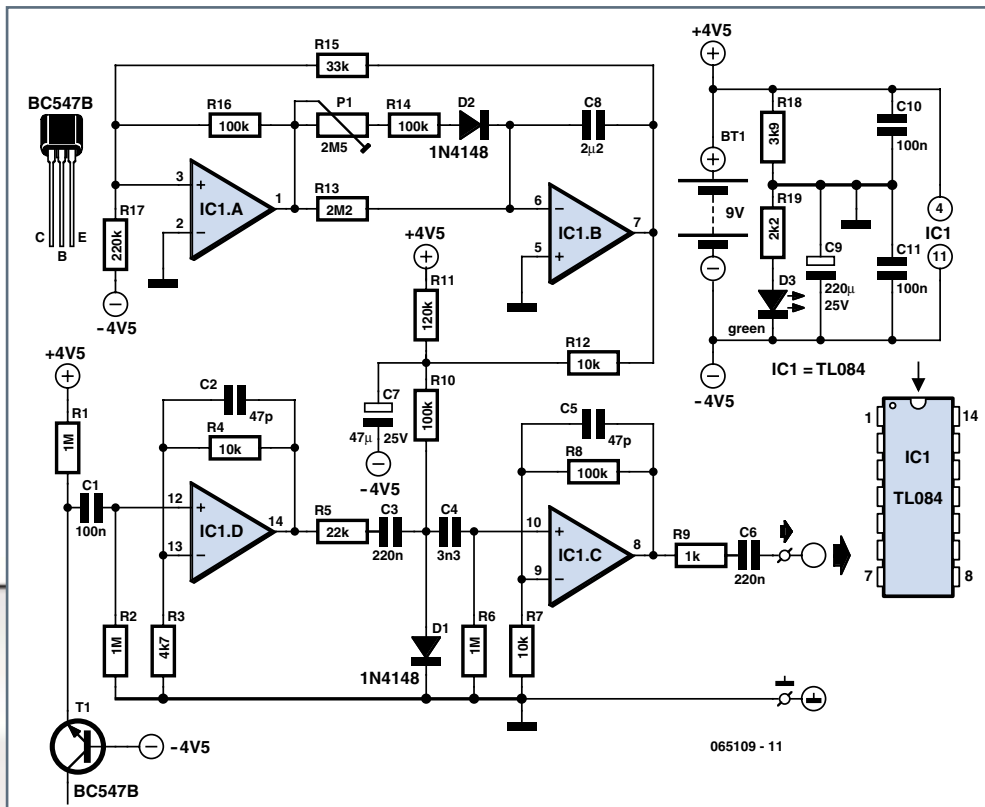Noise is usually the last thing you want in any sort of audio circuitry. Noise is generated in semiconductor



devices (transistors and diodes) as an undesirable by-product. However, in our surf simulator we just can't get enough of it! Noise forms the basis for imitating the sound of breaking surf. We take advantage of the fact that a reverse-biased base-emitter junction of a transistor generates noise like the devil if the voltage is high enough. The noise source in the schematic diagram is transistor T1. The base-emitter junction of this transistor breaks down at approximately 7 V (depending on the specific transistor). R1 limits the current to a level that avoids destroying the transistor.

T1 generates a constant noise signal, which doesn't resemble the sound of breaking surf. If you listen carefully to the sound of real surf, you'll notice that it resembles a noise signal that increases rapidly in volume (as the wave rolls up the beach) and then slowly dies down. This means the noise must rise and decay in a sawtooth waveform. To achieve this effect, we make use of the AC impedance of a normal diode (D1 in the schematic diagram), which depends on the amount of DC current flowing through the diode. The higher the current through the diode, the lower its AC impedance (and thus its impedance to the noise signal). The voltage across R10 determines how much current flows through diode D1. The noise signal is amplified by IC1d and applied to the diode, and the voltage across the diode is further amplified by IC1c to the output level. As already mentioned, the amplitude of the noise signal depends on the DC current through diode D1. What we have to do now is make the current through D1 (or in other words, the voltage across R10) vary in a sawtooth pattern. This job is handled by amplifiers IC1a and IC1b. You can use P1 to adjust the form of the sawtooth (and thus how the noise grows and decays) according to your taste.

The circuit works best with a clean 9-V supply voltage, so an AC mains adapter with a stabilised 9-V output is the preferred choice as a power source. A balanced supply voltage is required for proper operation of the circuit, so a virtual ground is necessary. This is created in a simple manner by a voltage divider (R18 and R19). To reduce the current consumption (in case you want to power the circuit from a battery), it also provides a 'power on' indication. The current consumption of the circuit is approximately 9 mA, which means the battery would have to be replaced already after two days of continuous use if it is powered by a battery, so using an AC mains adapter is certainly advisable.

We designed a PCB layout for this project to make it easier to assemble, since it is a bit more complex than most of the i-TRIXX circuits. If you follow the illustrated component layout, you shouldn't have any trouble at all. The idea here is that you print the copper layout at actual size (52 × 52 mm) on transparent film. The easiest way to do this is to use the supplied pdf file which you can open with Adobe Reader. You can then use the film to expose a circuit board, develop it, and then etch it. Alternatively, you can take the film to your local electronics shop and have them make a board for you.

If you need a real holiday before tackling this, visit your local travel agent!

Resistors

R1,R2,R6 = 1 M Ω
 R3 = 4k Ω
 R4,R8,R10,R14,R16 = 100 k Ω
 R5 = 22 k Ω
 R7,R12 = 10 k Ω
 R9 = 1 k Ω
 R11 = 120 k Ω
 R13 = 2M Ω
 R15 = 33 k Ω
 R17 = 220 k Ω
 R18 = 3k Ω
 R19 = 2k Ω
 P1 = 2M Ω 5 preset

Capacitors



C1,C10,C11 = 100 nF
 C2,C5 = 47 pF
 C3,C6 = 220 nF
 C4 = 3nF3
 C7 = 47 μ F/25V radial
 C8 = 2 μ 2 MKT lead pitch 5 or 7.5mm
 C9 = 220 μ F/25V radial

Semiconductors

D1,D2 = 1N4148
 D3 = LED, 3mm, green, low current
 T1 = BC547B
 IC1 = TL084

Miscellaneous

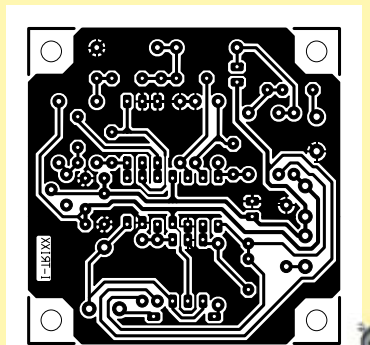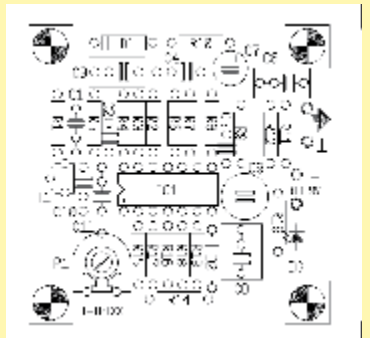6 PCB solder pins
 BT1 = 9V battery with clip-on leads (however 9 V battery eliminator preferred)



i-TRIXX

Electronics inside out!

Save Your Ears

'Hello... HELLO! Are you deaf? Do you have disco ears?' If people ask you this and you're still well below 80, you may be suffering from hearing loss, which can come from (prolonged) listening to very loud music. You won't notice how bad it is until it's too late, and after that you won't be able to hear your favourite music the way it really is – so an expensive sound system is no longer a sound investment. To avoid all this, use the i-trixx sound meter to save your ears (and your neighbours' ears!).



Noise meter

With just a handful of components, you can build a simple but effective sound level meter for your sound system. This sort of circuit is also called a VU meter. The abbreviation 'VU' stands for 'volume unit', which is used to express the average value of a music signal over a short time. The VU meter described here is what is called a 'passive' type. This means it does not need a separate power supply, since the power is provided by the input signal. This makes it easy to use: just connect it to the loudspeaker terminals (the polarity doesn't matter) and you're all set. The more LEDs that light up while the music is playing, the more you should be asking yourself how well you are treating your ears (and your neighbours' ears).

Of course, this isn't an accurately calibrated meter. The circuit design is too simple (and too inexpensive) for that. However, you can have a non-disco type (or your neighbours) tell you when the music is really too loud, and the maximum number of LED lit up at that time can serve you as a good reference for the maximum tolerable sound level.


Although this is a passive VU meter, it contains active components in the form of two transistors and six FETs. Seven LEDs light up in steps to show how much power is being pumped into the loudspeaker. The steps correspond to the power levels shown in the schematic for a sine-wave signal into an 8-ohm load. LED D1 lights up first at low loudspeaker voltages. As the music power increases, the following LEDs (D2, D3, and so on) light up as well. The LEDs thus dance to the rhythm of the music (especially the bass notes).

This circuit can easily be assembled on a small piece of prototyping board. Use low-current types for the LEDs. They have a low forward voltage and are fairly bright at current levels as low as 1 mA. Connect the VU meter to the loudspeaker you want to monitor. If LED D2 never lights up (it remains dark even when LED D3 lights up), reverse the polarity of diode D8 (we have more to say about this later on). In addition, bear in mind that the sound from the speaker will have to be fairly loud before the LEDs will start lighting up.

If you want to know more about the technical details of this VU meter, keep on reading.

Each LED is driven by its own current source so it will not be overloaded with too much current when the input voltage increases. The current sources also ensure that the final amplifier is not loaded any more than necessary. The current sources for LEDs D1–D6 are formed by FET circuits. A FET can be made to supply a fixed current by simply connecting a resistor to the source lead (resistors R1–R6 in this case). With a resistance of 1 k Ω , the current is theoretically limited to 1 mA. However, in practice FETs have a especially broad tolerance range. The actual current level with our prototype ranged from 0.65 mA to 0.98 mA.

To ensure that each LED only lights up starting at a defined voltage, a Zener diode (D8–D13) is connected in series with each LED starting with D2. The Zener voltage must be approximately 3 V less than the voltage necessary for the indicated power level. The 3-V offset is a consequence of the voltage losses resulting from the LED, the FET, the rectifier, and the overvoltage protection. The overvoltage protection

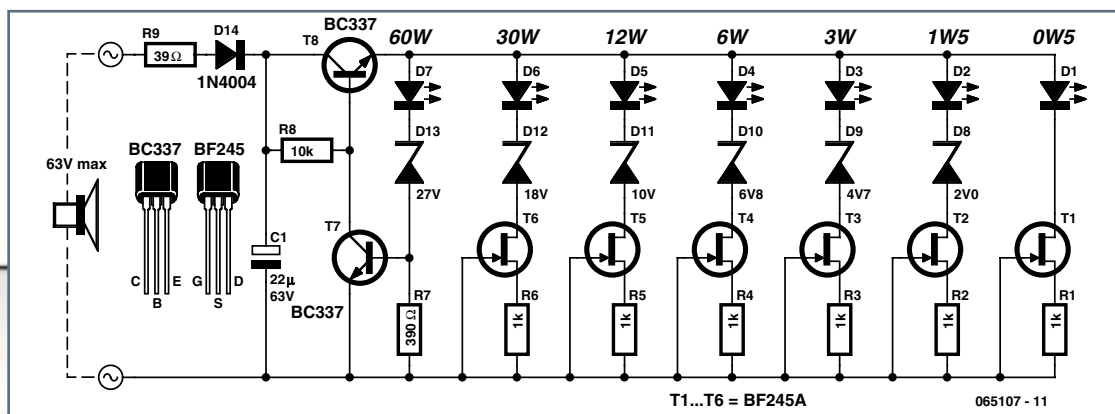



Electronic

is combined with the current source for LED D7. One problem with using FETs as current sources is that the maximum rated drain-source voltage of the types used here is only 30 V. If you want to use the circuit with an especially powerful final amplifier, a maximum input level of slightly more than 30 V is much too low. We thus decided to double the limit. This job is handled by T7 and T8. If the amplitude of the applied signal is less than 30 V, T8 buffers the rectified voltage on C1. This means that when only the first LED is lit, the additional voltage drop of the overvoltage protection circuit is primarily determined by the base-emitter voltage of T8. The maximum worst-case voltage drop across R8 is 0.7 V when all the LEDs are on, but it has increasingly less effect as the input voltage rises. R8 is necessary so the base voltage can be regulated. R7 is fitted in series with LED D7 and Zener diode D13, and the voltage drop across R7 is used to cause transistor T7 to conduct. This voltage may be around 0.3 V at very low current levels, but with a current of a few milliampères it can be assumed to be 0.6 V. Transistor T7 starts conducting if the input voltage rises above the threshold voltage of D7 and D13, and this reduces the voltage on the base of T8. This negative feedback stabilises the supply voltage for the LEDs at a level of around 30 V. With a value of 390 Ω for R7, the current through LED D7 will be slightly more than 1 mA. This has been done intentionally so D7 will be a bit brighter than the other LEDs when the signal level is above 30 V. When the voltage is higher than 30 V, the circuit draws additional current due to the voltage drop across R8. The AC voltage on the loudspeaker terminals is half-wave rectified by diode D14. This standard diode can handle 1 A at 400 V. The peak current level can be considerably higher, but don't forget that the current still has to be provided by the final amplifier. Resistor R9 is included in series with the input to keep the additional load on the final amplifier within safe bounds and limit the interference or distortion that may result from this load. The peak current can never exceed 1.5 A (the charging current of C1), even when the circuit is connected directly to an AC voltage with an amplitude of 60 V. C1 also determines how long the LEDs stay lit. This brings us to an important aspect of the circuit, which you may wish to experiment with in combination with the current through the LEDs. An important consideration in the circuit design is to keep the load on the final amplifier to a minimum. However, the combination of R9 and C1 causes an averaging of the complex music signal. The peak signal levels in the music are higher (or even much higher) than the average value. Tests made under actual conditions show that the applied peak power can easily be a factor of 2 to 4 greater than what is indicated by this

How about an amusing (although your victims may not agree) circuit that you can use to play a trick on your friends or family, or to get rid of your mother-in-law? A handful of electronic components can create a cricket-like chirping sound every few minutes or so. You should hide this electronic poltergeist such that it's difficult to find, but can still be heard clearly. It is guaranteed to drive people mad! i-TRIXX shows you how to build this irritating circuit. Read on...

- Did you hear that? - What? - That chirping noise.
- Chirping noise? - Yes, I think there's a cricket somewhere in the room. - I didn't hear anything!
- Well, it's stopped now!

A bit later: - There it is again! Did you hear it? - I heard nothing, go back to sleep! - I'm not going mad am I? I'm sure there's a cricket around somewhere! We have to get rid of it, otherwise I won't be able to sleep!

This could be a possible conversation in the bedroom where you've hidden the electronic poltergeist. But before you can create all this mischief you'll have to use your soldering iron. You'll be pleased to hear that the construction of this circuit won't give you sleepless nights, as long as you work carefully.

At the heart of the circuit is an old favourite IC, the 4093. This chip contains four NAND gates, each of which has two inputs. These NAND gates have Schmitt triggered inputs (more on this later) and are ideal for use in this particular application. Three of the gates are used as oscillators. The oscillator built around IC1A produces a high-pitched sound similar to that made by crickets when they rub their wings together. A second

VU meter. This amounts to 240 W or more with an 8- Ω loudspeaker. You can reduce the value of C1 to make the circuit respond more quickly (and thus more accurately) to peak signal levels.

Now a few comments on D8. You may receive a stabistor (for example, from the Philips BZV86 series or the like) for D8. Unlike a Zener diode, a stabistor must be connected in the forward-biased direction. A stabistor actually consists of a set of PN junctions in series (or ordinary forward-biased diodes). Check this carefully: if D2 does not light up when D8 is fitted as a normal Zener diode, then D8 quite likely a stabistor, so you should fit it the other way round.



i-TRIXX

Electronics inside out!

poltergeist


oscillator (IC1B) is used to interrupt this noise at regular intervals. The third oscillator (IC1C) is used to turn on the chirping noises for a short while, with a few minutes silence in between.

So how do these oscillators work? We'll take IC1A as an example. The output of this binary NAND gate will only be a logic low (virtually equal to 0 Volts) when both inputs are at a logic high level (typically just over half the supply voltage). Each input has a Schmitt trigger circuit so that slowly changing input signals can be also be dealt with. The Schmitt trigger makes the gate switch state suddenly when the input is slowly increasing and reaches the point where it could be considered at a logic high state. Inputs that are hesitating somewhere between low and high are effectively given a helping hand upwards. When the supply voltage (a 9 V battery) is first connected to the circuit, the input at pin 2 is at a logic low level (since capacitor C2 has not yet charged up). This means that the output of the NAND gate at pin 3 will be at a logic high level. Capacitor C2 is now charged up via the output at pin 3 and resistor R3 until the Schmitt trigger decides that the voltage level at pin 2 has increased enough for it to be at a logic high level. The output of the gate now switches over to a logic low level, assuming that the input at pin 1 is at a logic high level. Capacitor C2 will now be discharged by the output at pin 3 via R3, which causes the input at pin 2 to become low again, and the whole cycle repeats itself. The speed (frequency) at which this charging and discharging takes place depends on the values of R3 and C2.

The oscillator built around IC1C works in a slightly differently way. In this case a diode (D1) causes capacitor C1 to charge via both R1 and R2, which is much quicker than when C1 discharges via R2 only. This causes the poltergeist to be quiet for three minutes (the slow discharge) and only make a noise for a second or so (the fast charge).

The fourth gate (IC1D) is used to combine the two oscillators (IC1A, which makes the high-pitched sound of the wings rubbing together and IC1B, which imitates the periodic movement of the wings) and drive the sounder. It is possible to change the frequencies at which gates IC1A to IC1C operate by varying the values of resistors R1 to R4. A lower value results in a higher frequency, and a higher value lowers it. You could also consider reducing the volume of the sounder by increasing the value of R5; this will make it even more difficult to find the circuit.

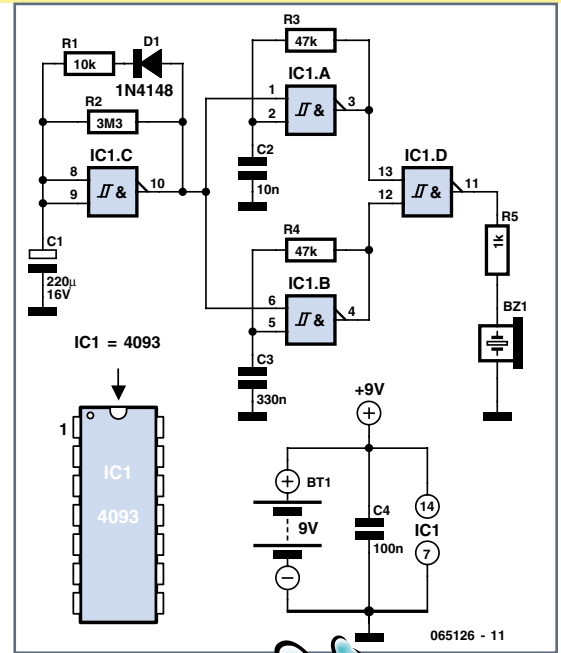The current consumption of our prototype was under 300 μ A during the time it was silent, which rose to about 1.3 mA when the circuit was producing sounds (this only lasts 1 second). With an ordinary 9 V battery this circuit can operate for several (irritating) months, and there won't be many people who could put up with that!



Pump it up: MP3 booster

MP3 players are all the rage these days. The smaller ones in memory-stick format are particularly easy to take with you; your very own 'personal sound system' on the move! It's when you want others to share your taste in music that you find these players to have a lack of power. You can get round this problem with the help of the i-TRIXX MP3 booster, a small amplifier that can be used to connect your MP3 player directly to your Hi-Fi. When you next invite your friends to a party you can ask them to bring their 'personal music' as well as the usual drinks! But first we have to build this booster!

The small battery-powered players have an output signal that is more than sufficient to drive a set

of 32 Ohm headphones. You'll often find that with an output of 1 mW the sound pressure level (SPL) produced can reach up to 90 dB. This would be sufficient to cause permanent damage to your hearing after only one hour! The maximum output voltage will then be around 200 mV. This, however, is insufficient to fully drive a power amplifier. For this you'll need an extra circuit that boosts the output voltage. Power amps usually require 1 V for maximum output, hence the signal has to be amplified by a factor of five. We will also have to bear in mind that quieter recordings may need to be amplified even more. We've used a simple method here to select the gain, which avoids the use of potentiometers. After all, the MP3 player already has its own volume control. We decided to have two gain settings on the booster, one of three times and the other ten times.

Musical saw

Usually it's the person who sings when the sawing goes well. But the saw itself can also be made to produce musical sounds by drawing a bow across its edge. By bending the saw in different ways an experienced saw player is able to extract a musical melody from the saw. If you don't have a spare saw and bow to hand you could always build this electronic version. At least with this instrument you'll never cut yourself! So warm up your soldering iron and get cracking!

Everybody who has sawn some wood will be aware that the saw can sometimes produce musical sounds, especially when the sawing isn't going very smoothly. There are even professional musicians who use specially manufactured saws as musical instruments. You'll only appreciate their skills if you happen to like this style of music though. As a dedicated electronics hobbyist you'd rather build an electronic version, of course, and we've designed a simple circuit for you. The circuit diagram may appear a bit complex at first, but don't let it worry you. We have also designed a printed circuit board for this circuit, which makes the construction a lot easier than if you had to use experimenter's board. The complete circuit is built around a single IC, a TL084, which contains four opamps. These opamps have been configured as oscillators in this circuit, and together they produce sounds similar to that of a musical saw.

The circuit consists mainly of three, almost identical, adjustable oscillators built round IC1B, IC1C and IC1D. The frequencies can be adjusted via potentiometers P1 to P3, with a slight overlap in the frequency range between the oscillators. A fourth (similar) oscillator, which produces the final output, is modulated by the first three oscillators, which creates a varying frequency that quite closely resembles the sounds produced

Amplifiers IC1A and IC1B (for the right and left channels) are housed in a single package, a TS922IN. The output signal of the MP3 player is fed via a stereo cable and socket K1 to the inputs of the amplifiers. The gain depends on the relationship between resistors R2 and R1 (R6 and R5 for the other channel) and is equal to ten times. When you add jumper JP1 (JP2), resistor R3 (R7) will be connected in parallel with the negative feedback resistor R1 (R6), which causes the gain to be reduced to about three. When you start using the booster you can decide which gain setting works best for you.

Resistor R4 (R8) takes the amplified MP3 signal to the output socket K2 (K3). A cable then connects these phono sockets to the input of your power amplifier. The resistors connected in series with the output (R4 and R8) are there to keep the booster stable when a long cable is connected to its output. Cables have an unwelcome, parasitic capacitance. This capacitive effect could (due to phase shifts of the signal) affect the negative feedback of the booster in such a way


by a saw. Oscillator IC1B creates a type of vibrato effect (this is a quick variation of the frequency, and is comparable to the effect produced when you use your hand to rapidly change the amount of bending of the saw). Oscillators IC1C and IC1D, which oscillate at lower frequencies, create an arbitrary variation of the frequency (melody) of the electronic saw (corresponding to small changes in the level of bending of the saw). The oscillators operate as astable multivibrators with a Schmitt trigger. We'll take the oscillator built round IC1B to explain how it works. When power is first applied, capacitor C1 will be completely discharged and a voltage of -9 Volts will appear at the inverting input (pin 6) of IC1B. Since the non-inverting input (pin 5) will be at a higher potential (via R1 and R2), the output (pin 7) will be at a high level (virtually equal to the supply voltage of +9 Volts). This output will now charge capacitor C1 via P1 and R3, until such time that the voltage at pin 6 rises above that of pin 5. At that moment the output of the opamp switches over to -9 Volts (the negative supply voltage). This causes capacitor C1 to discharge via P1 and R3, until the voltage at the inverting input falls below that of the non-inverting input, when the whole process repeats itself. The output of the oscillator is therefore a square wave. Resistor R4 and capacitor C4 smooth the sharp


that a positive feedback occurs, with the result that the booster oscillates and possibly damages the power amplifier! The resistors (R4 and R8) effectively isolate the output of the booster from the parasitic capacitance of the output cable. They also protect the booster outputs from short circuits.

We've used a TS922IN opamp in this booster because it can operate at very low supply voltages (the maximum is only 12 V!), but can still output a reasonable current (80 mA max.).

For the supply we've used rechargeable batteries (e.g. NiCd or NiMH cells) so that we don't need a mains supply. To keep the number of cells required as small as possible, we've chosen a supply voltage of 5 volt; this can be supplied by four rechargeable batteries. It is also possible to use four ordinary, non-rechargeable batteries; it's true that the supply voltage then becomes a bit higher (6 Volts), but that won't cause any harm.

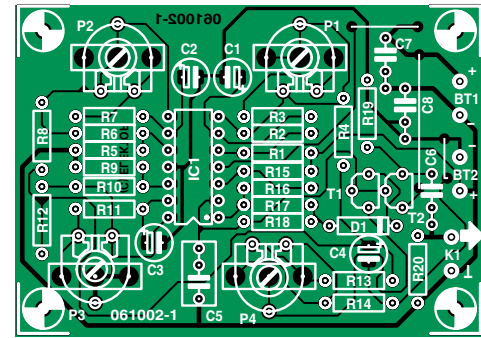Since we've used a symmetrical supply for the booster (2 x 2 batteries), it will be easiest if you use two separate



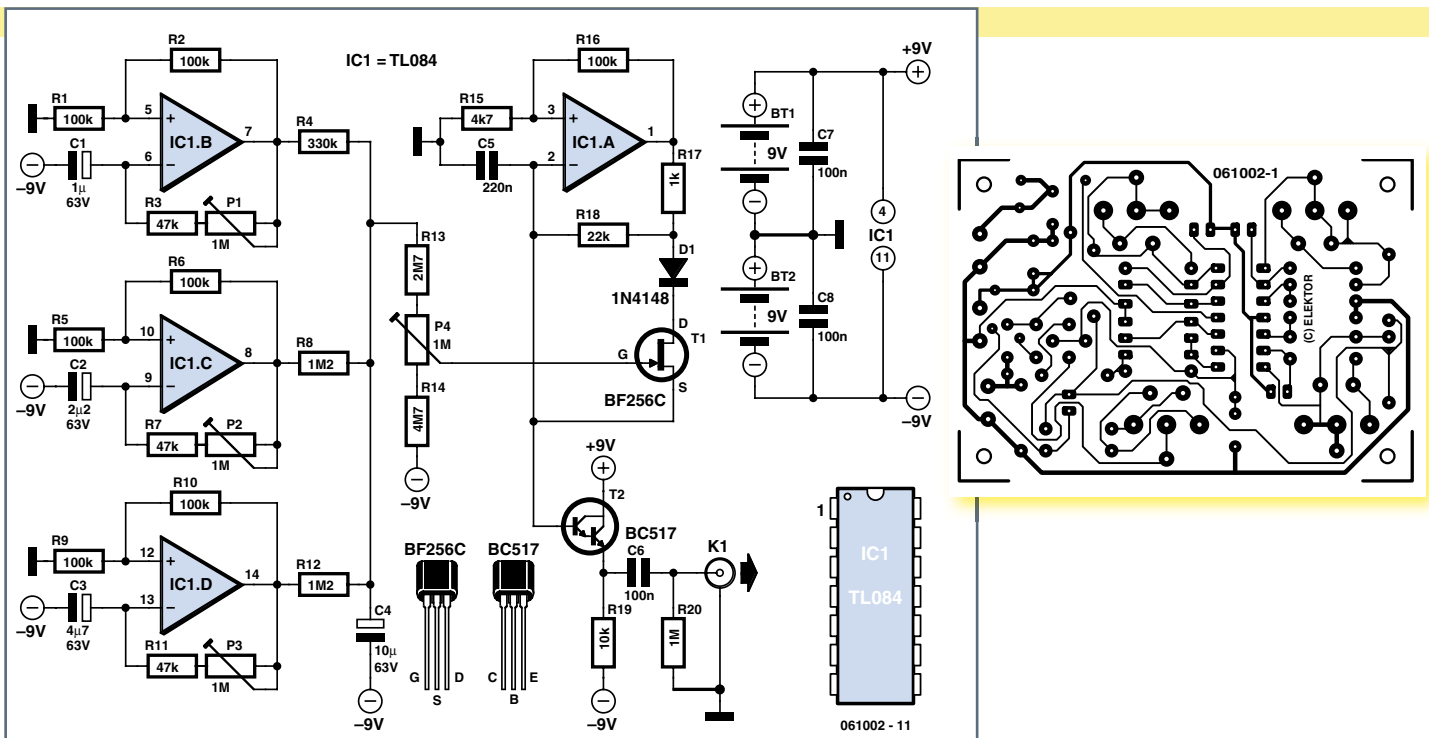


edges of this square wave, which produces a more pleasing sound when it is fed into the final oscillator (IC1A). The outputs of the other two oscillators (IC1C and IC1D) are also added to this modulation signal. P4 is used to adjust the level of modulation that is presented to the input of FET T1. This FET is connected in parallel with resistor R18 and determines the frequency (pitch) of oscillator IC1A. This oscillator also produces a square wave output (on pin 1). However, the output is taken from pin 2, which is a more rounded signal and therefore won't sound so harsh. This signal is first buffered by Darlington transistor T2 so that the frequency isn't affected when you connect a load to the output. The electronic musical saw can also be played by hand. In that case you should replace presets P1 to P3 with slider potentiometers, which can be easily and quickly adjusted by hand.


battery holders, each with two AA cells. The two holders are connected in series. Make sure that the batteries are connected the right way round; the positive of one always has to be connected to the negative of the next. This also applies to the connection between the two battery holders. S1A/B is a double pole switch, which is used to turn both halves of the battery supply on or off simultaneously.

If you can't find the (dual) opamp we've used (or an equivalent), you could always use standard opamps such as the NE5532, TL082 or TL072. These do need a higher supply voltage to operate properly. In these cases you should use two 9 V batteries and replace resistor R9 with a 15 kΩ one. Do take care when you connect the circuit to your power amplifier because the output signal can be a lot larger and you could overload the power amplifier. (Although you're more likely to damage the loudspeakers, rather than the amplifier!) (Please note that these two 9 V batteries can't be used as a supply for the TS922IN!)


The current consumption of the circuit is on average +/- 8 mA. When you use two 9 V batteries they can provide the circuit with many hours of (musical?) power. To make the construction of this circuit a lot easier we have designed a PCB layout. Since we have also included the component layout there's not much that could go wrong with the construction. You should copy the track layout at its true size (70 x 50 mm) to a sheet of transparent plastic. That is easiest if you download the PDF file supplied for this project and use Adobe Acrobat Reader to print it out. You can use this to expose, develop and etch your own PCB. Alternatively, you could take it to a local electronics shop who may be able to produce the PCB for you.

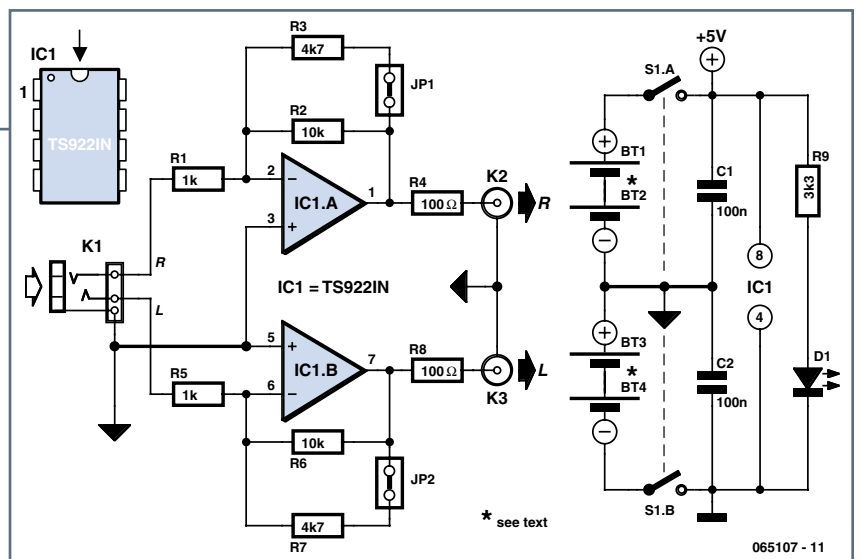

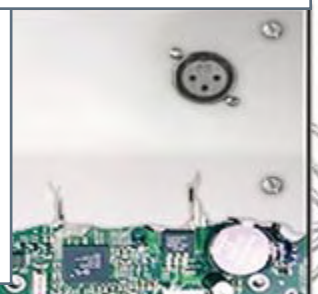In our circuit we've used a stereo jack socket for the input and phono sockets for the output because these are the most compatible with MP3 players and power amplifiers respectively. If you wanted to, you could solder shielded cables directly to the circuit instead, with the correct plugs on the ends. You'll never find yourself without the correct connection leads in that case!



Luminous house number

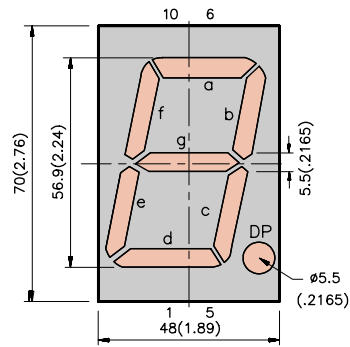

During the dark autumn and winter months in particular you'll find that ordinary house numbers are more difficult to read, especially if your home is further back from the road. If you want to avoid that your family, friends and deliverymen drive past your home, you should build this electronic version. At the same time you can show the world that you're an avid electronics hobbyist! It can easily be put together during a rainy weekend.

For a change this isn't a hi-tech circuit, but instead is quite straightforward and it comes in useful too. House numbers can sometimes be difficult to read. In this article we show you how to build a luminous version that uses large 7-segment displays made by Kingbright, which have digits with a height of 57 mm. There are of course other manufactures that produce similar displays and it is not essential that you use the same displays that we've used here. You do have to keep an eye on the number of LEDs used to make up each segment (7 in total) and on the forward voltage drop when the segments are lit, so that you don't exceed the maximum current through the LEDs, but more on this later.

The required segments of the display are connected to the supply via resistors. When you connect all segments you obtain the digit 8, for a 0, 6 or 9 one of the segments is disconnected and a 1 for example only needs two segments lit. In this way you can display all of the digits from 0 to 9. Each segment in the display consists of a number of LEDs connected in series (in our module this is 4). In the display used by us the anodes of the first LED in every segment are connected together, hence the term 'common anode display'.

The common anode obviously has to be connected to the positive supply. The 'free' ends of the segments that have to be lit are connected via a resistor to the negative supply (ground). The current through the segments and hence their brightness is dependent on the value of the resistors.

For the power supply we can use a doorbell transformer, which is often already present and which generally supplies 8 Volts AC. The alternating voltage of the doorbell transformer is rectified so that the peak current through the LEDs doesn't exceed their limits. The rectifier circuit consists of a standard bridge rectifier followed by a smoothing capacitor. These can supply the right voltage for a one or two-digit house number. For house numbers of three digits or


more you will have to experiment with the resistors to find what values give the correct current through the segments. But for house numbers like 88, 80 or 90 (many segments will be lit) this also applies. For every extra segment that is lit the current consumption increases, which causes the supply voltage to drop by an amount dependent on the quality of the doorbell transformer. It is therefore difficult to give an exact figure for the value of the current limiting resistors in the circuit; the 47 Ω mentioned here should be taken as a guideline to give a current of about 22 mA (which is a safe value for the type of display we used) when an 8 Volt doorbell transformer is used. If you want to be sure that you're not exceeding the current limit you should place an ammeter in series with the supply and divide the measured current by the number of segments that are lit. If the result is greater than 22 mA you should increase the values of the resistors, and reduce their value if the result is less than 22 mA. To determine what current flows through a segment you could of course measure the voltage across the resistor connected to it and use Ohm's law to calculate the current.

For the installation it's best to split the circuit into two parts: the bridge rectifier (B1) and the smoothing capacitor (C1) near the transformer and the display and resistors in a weather proof box next to the front door. When your house number consists of two digits you should build two display modules (shown in the circuit diagram inside the dotted lines). The display section should be connected to the power supply section using a twin-cored cable such as loudspeaker cable. Try to use a cable with reasonably thick cores, especially if a lot of segments are lit. For '88' the current requirement is 0.3 A!

The house number also has to be legible in strong sunlight. To achieve a better contrast you can place a piece of transparent plastic (with the same colour as the LEDs) in front of the display, or you could stick transparent tape over the segments (using the right colour). In the latter case you should only cover the active segments so that you can still see the number without an applied voltage.

The table below shows you which resistors need to be soldered to produce each digit:

0	R1,R2,R3,R4,R5,R6 R2,R3
1	R1,R2,R4,R5,R7
2	R1,R2,R3,R4,R7
3	R2,R3,R6,R7
4	R1,R3,R4,R6,R7
5	R1,R3,R4,R5,R6,R7
6	R1,R2,R3
7	R1,R2,R3,R4,R5,R6,R7
8	R1,R2,R3,R4,R6,R7
9	R1,R2,R3,R4,R6,R7

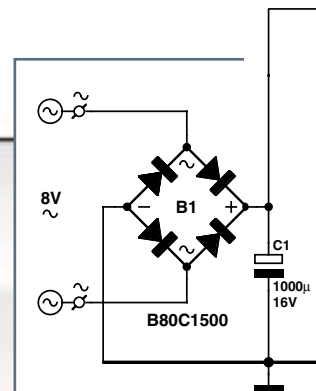

i-TRIXX

Electronics inside out!

Applause generator



No, the performance of our national team during the 2006 World Cup Soccer Tournament did not deserve any applause. Better occasions come to mind where a resounding applause is much more appropriate. And to prevent injury to your hands when this occasion does present itself, we developed an electronic applause generator. In this way you can avoid being the only one applauding in a busy hall and prevent both yourself as well as the receiver from feeling uncomfortable.

Applause from a large crowd sounds very similar to noise. Noise is therefore also the source signal in this circuit. A proven method for the generation of noise is to 'zener' the base-emitter junction of a transistor. That is what T1 and R1 are for. The base-emitter junction is wired as a diode in the reverse biased direction and connected via R1 to the power supply voltage of 9 volts. Because of this relatively high voltage, the base-emitter diode will break down, but the high resistance value of R1 prevents the junction from failing because of excessive current. The voltage across the base-emitter diode is relatively constant; this diode acts like a zener diode. The noise that is produced is very small however and is considerably amplified by opamp IC1 first, before any further processing. The opamp is set to half the supply voltage by R2 and R3. The noise signal is applied to the input of the opamp via C1. This capacitor ensures the separation of the high DC voltage (the 'zener voltage') at the emitter of T1 and the half-power-supply-voltage at pin 3 of the opamp. In our prototype this zener voltage amounted to 8.3 V. It can happen that this voltage is greater than 9 V. In that case you will have to either increase the power supply voltage or pick another transistor for T1 that has a lower zener voltage. This is just a case of swapping the transistor and repeating the measurement.

Because of the presence of C2 and C3, the opamp amplifies mostly the low-frequency part of the noise. This results in the best approximation of real applause. The transistor stage that follows provides the clapping sound.



The noise is presented to the base of T2 via C5. C6 is charged slowly via R5 after the power supply is switched on and this causes T2, via R6, to progressively conduct more and more. As a result the noise signal at the collector of T2 will grow to a maximum.

The emitter voltage is set by R7 and R8 to half of the power supply voltage. T2 comes out of conduction for part of the time because of the size of the noise signal. There is therefore a switching effect with the noise that gives a strong impression of applause. The signal is available at the output via C7.

If you object to the lower frequencies then you can pick a smaller value for C7. D1 ensures that C6 is discharged quickly when the circuit is switched off so that when it is switched back on again the same delay and growth of applause results. If you like experimenting, you can change the values of C2, C3 and R4 or choose a different opamp and try to make the sound even more realistic. If you would also like the applause to decay slowly, you can connect R5 alternately to the positive and negative of the power supply, for example with the aid of a change-over switch (D1 is omitted in this case). A smaller value of C6 accelerates the effect.

The current consumption of the circuit is only 4 mA; a 9-V battery is therefore eminently suitable as the power supply. If you plan to put the circuit in a box then do not forget the on/off switch.

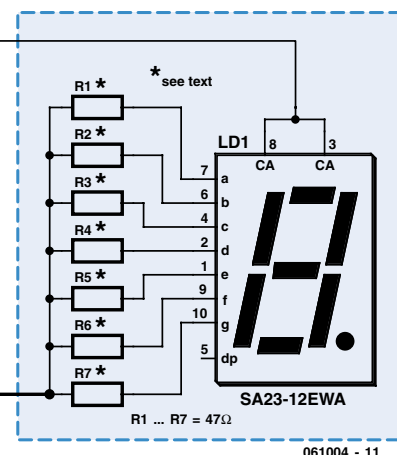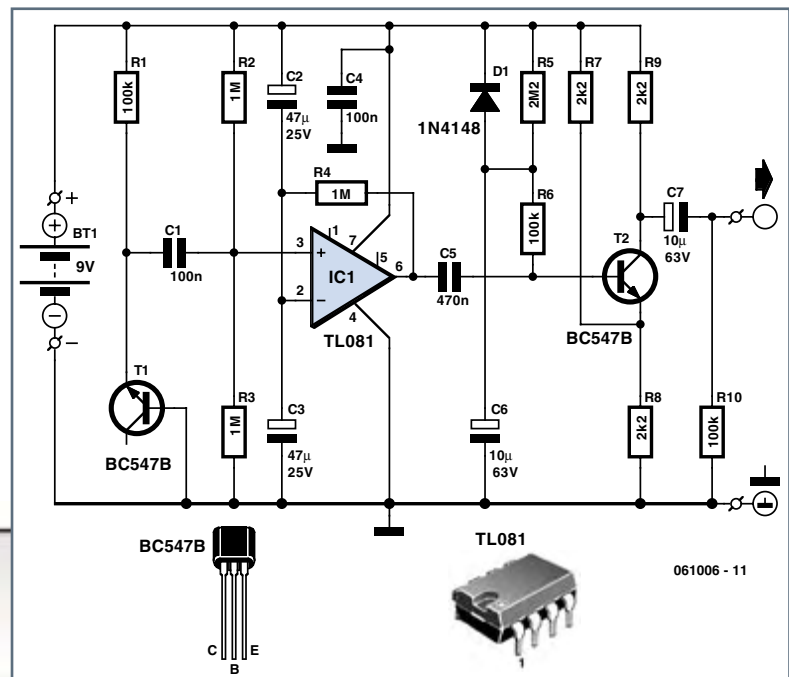Once you've got the circuit to work, the first applause is naturally for yourself!





velleman[®]
INSTRUMENTS

£ 399,99




TWO-CHANNEL USB PC OSCILLOSCOPE

The PCSU1000 digital storage oscilloscope uses the power of your PC to visualize electrical signals. High sensitive resolution, down to 0.15mV.

1Gs/s
2x60MHz

USB

PCSU1000

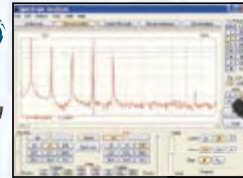

THREE-IN-ONE LAB UNIT

Contents: 1 multimeter, 1 power supply & 1 soldering iron. This unit covers 99% of your home lab needs. Perfect solution for starters or schools.




LAB1

£ 89,99

10MS/s PERSONAL POCKET SCOPE

World's most portable oscilloscope.

PC CONNECTION
RS232

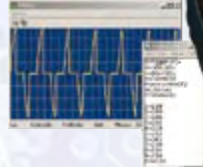

£ 154,99



PPS10

velleman[®]-kit HIGH-Q



£ 79,99

K8077

SUBWOOFER KIT

Complete kit, just add wood. Kit includes: amplifier and filter circuit, two 16cm woofers, alu rear panel, bass-reflex tube, small hardware and assembly instructions for both amp circuit and enclosure.


200W

velleman[®]
MODULES

ASSEMBLED PRODUCTS

8-CHANNEL RF REMOTE CONTROL SET

8-channel RF remote control set. Latching or momentary mode for each output.

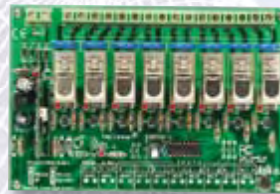

VM118

£ 69,99



USB

EXTENDED USB INTERFACE BOARD

universal I/O card with USB™ interface. Safe, optically isolated communication between all the I/O's and your PC.



K8061



£ 65,99

2 MODULAR DIGITS WITH SERIAL INTERFACE

Bright, red, jumbo-sized 7-segment displays (57mm). Complete with snap-in enclosure. Multiple units can be linked in an easy way to create larger readouts for e.g. score-keeping, timing, counting, ... Easy platform-independent control via RS232 three-wire interface. Sold per pair.



K8063

£ 29,99

200W POWER AMPLIFIER MODULE

Excellent value for money. Fully discrete design. Overload and short-circuit protection.



VM100

£ 39,99



ULTRASONIC RADAR MODULE

Buzzer output: fast / slow / continuous. Distance indication with 3-LED-bar. Adjustable alarm distance. LED alarm indicator. Dry contact NO/NC relay. Applications: robot projects, object detection, distance measuring, parking aid, security systems.



£ 19,99



VM125



MINI KIT

SOUND STAR VU METER



MK172

FLASHING YELLOW LED STAR




MK169Y

FLASHING RED LED STAR




MK169R

ELECTRONIC CHRISTMAS TREE

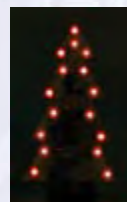


MK100

DE LUXE XMAS TREE

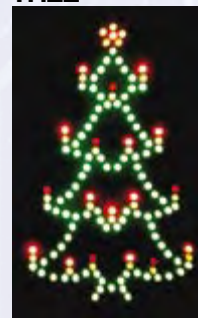

MK117

60-LED MULTI-EFFECT STAR

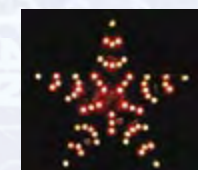

MK170

RIDING SANTA



MK116

ALL THESE KITS HAVE LED ANIMATIONS

For more information and dealers, see www.vellemanprojects.com

Suggested retail prices VAT included

www.velleman.eu

DON'T LOSE YOUR TEMPER

Before phoning us - if you are looking for a hard-to-find part. We have over 20,000 items in stock - including obsolete and up-to-date parts.




WHY NOT VISIT OUR WEBSITE
www.cricklewoodelectronics.com

2N 2SA 2SB 2SC 2SD 2P 2SJ 2SK 3N 3SK 4N 6N 17 40 AD
 ADC AN AM AY BA BC BD BDT BDV BDW BDX BF
 BFR BFS BFT BFX BFY BLX BS BR BRX BRY BS
 BSS BSV BSW BSX BT BTA BTB BRW BU BUK BUT BUV
 BUW BUX BUY BUZ CA CD CX CXA DAC DG DM DS
 DTA DTC GL GM HA HCF HD HEF ICL ICM IRF J KA
 KIA L LA LB LC LD LF LM M M5M MA MAB MAX MB
 MC MDAJ MJE MJF MM MN MPS MPSA MPSH MPSU
 MRF NJM NE OM OP PA PAL PIC PN RC S SAA SAB
 SAD SAJ SAS SDA SG SI SL SN SO STA STK STR STRD
 STRM STRS SV1 T TA TAA TAG TBA TC TCA TDA TDB
 TEA TIC TIP TIPL TEA TL TLC TMP TMS TPU U UA
 UAA UC UDN ULN UM UPA UPC UPD VN X XR Z ZN
 ZTX + many others

We accept Mail, telephone & email orders.

Callers welcome.

Opening hours Mon-Sat 9:30 - 6:00

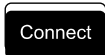

Cricklewood Electronics Ltd

40-42 Cricklewood Broadway London NW2 3ET

Tel: 020 8452 0161 Fax: 020 8208 1441

sales@cricklewoodelectronics.com

ByVac Electronics

Control hardware using simple text commands

Making complex tasks simple:

Using a two letter text command, control LCD displays, Analogue to digital converters, motors, keypads, LED matrix displays. All products work by serial connection.

This is just a small selection
 visit the web site for hints tips
 and free software

Connect using a PC RS232 or Microcontroller UART

*** All controlled with 2 wire serial bus ***	BV4103		<ul style="list-style-type: none"> Scrolling Text Backlight and contrast control Binary to text display Much more... 	LCD Display £22.90
	BV4108		<ul style="list-style-type: none"> Control any compatible LCD Up to 4 lines by 20 characters Scrolling text Much more... 	LCD Controller £11.00
	BV4102		<ul style="list-style-type: none"> 8 x 8 Bit Colour Red/Green Brightness control User defined bit patterns Switch on "splash screen" 	Dot Matrix £14.95
	BV4106		<ul style="list-style-type: none"> 4 x Analogue to digital 4 x digital input or output Pulse width modulation Trigger control 	A/D Control £11.00
	BV4107		<ul style="list-style-type: none"> 4 x 4 matrix keypad controller 16 key buffer Row, column configurable Additional digital input 	Keypad Control £11.00
	BV305		<ul style="list-style-type: none"> 8052-89S132 based No programmer needed Includes Tiny BASIC On board power supply 	Microcontroller £14.95 KIT £4.50 RBT

HOWEY BACK GUARANTEE:

If you are not completely satisfied, return the goods within 30 days for a full refund.

Purchase Options: On-Line at www.byvac.co.uk • Telephone 07905 734 348 •

email sales@byvac.com • Cheque or Postal Order to: ByVac, PO BOX 4049,

Penistone, SHEFFIELD, S36 6WP

Post and packing UK £2.50 World Wide £3.50

www.byvac.co.uk



Number One Systems

Easy-PC for Windows

The World Beating PCB design software



Easy-PC version 10 sets another milestone

Winning accolades the world over, Easy-PC for Windows V10 is another major milestone in the evolution of this extremely popular software tool. Try a demonstration copy of Easy-PC and prepare to be amazed at the power, versatility and remarkable value for money.

STILL FROM ONLY
£247
 PLUS VAT

Fully integrated Schematics & PCB layout in a single application complete with forward and back annotation. Design and rules checks at all stages ensure integrity at all times. Professional manufacturing outputs allow you to finish the design process with ease.

Version 10 features

- Intelligent Gerber Import option
- Track/Shape 'Hug' Mode Routing
- Text Callouts
- Layer & Via Stack Previews
- Blind & Buried Via Support
- Teardrop Pads
- Draw Spacing Clearances
- Spiral Tracks & Shapes
- Plus many more exciting features.....

Stop press... Stop press... Stop press... Stop press...

Easy-PC imports Eagle files as well as Tsien Boardmaker 2 files

call for a brochure, prices & CD on +44 (0)1684 773662

or e-mail sales@numberone.com

you can also download a demo from

www.numberone.com

Oak Lane, Bredon, Tewkesbury, Glos. GL20 7LR, United Kingdom



WLAN Antenna Desi

Increased range the easy way

Stefan Tauschek and Thomas Scherer

The domestic use of WLANs has grown rapidly as DSL routers with built-in wireless Ethernet have become available, and now it is easy to use a notebook PC to surf the Internet wirelessly from the comfort of one's sofa. However, things get trickier if a reinforced concrete wall stands in the way, or if a neighbour happens to be using the same frequency..

The enormous popularity of WLANs (wireless local area networks) is easy to understand: not everyone has their desk situated next to a telephone socket. Even in the case of desktop PCs it is now easier to provide a fast Internet connection via the ether rather than by installing fixed cables. Unfortunately, things do not always go perfectly smoothly in practice: sometimes it can be difficult to set up a reliable connection between two devices even just a short distance apart in the same building.

The problems and their causes

The frequency used for WLAN communications according to IEEE 802.11b or 802.11g is around 2.4 GHz. At this frequency radio waves propagate quasi-optically and are considerably attenuated by moisture in walls. Reinforced concrete and limestone block the waves to an even greater extent because of their high metal content. A further limitation is that in Europe transmit power in this band is limited to 100 mW.

Often also corners are cut in the interests of cost reductions. A WLAN router with a price tag of a few tens of pounds will make a few compromises in performance: a typical device will have inside a mini-PCI WLAN card,

just as a laptop might. Such cards often only output around 50 mW rather than 100 mW, and poor matching to the antenna often accounts for a few more dB of loss. The overall effective transmit power might only be around 10 mW or 20 mW.


A straightforward way to recoup some of this loss is to use a special antenna that offers gain. And that is what this article is about: how to build a DIY directional WLAN antenna which focuses the available transmit power in the desired direction, providing a gain of several dB over a conventional omnidirectional antenna. Furthermore, a directional antenna does not just provide gain in the transmit path; signals received from sources within the antenna's beam are amplified by the same factor. Since the WLAN connection is bidirectional, this means that a directional antenna can give us a considerable increase in range without the need for complex RF electronics.

The solutions

When faced with a poorly-performing WLAN, it is wise to pause before reaching for the soldering iron. A couple of aspects should be considered before deciding to make or buy a directional antenna.

First it is worth noting that the best

Ethernet connection is a wired one. A wired connection is both faster and more reliable. If this is not an option for any reason, or if (because connection is to be made to a notebook) it is not convenient, then there are a few things one can do to improve the performance of a wireless network. The first step is to try moving the router a few feet closer to the computer. Another option is to splash out a few tens of pounds on a repeater, which can add five to ten metres of range within a building. Even better is to deactivate the WLAN part of the router and, for a similar sum, purchase an access point (see **Figure 1**). This is a box of electronics which takes an Ethernet connection on one side and provides a WLAN connection on the other. The device can be connected to the router using an Ethernet cable. Because the device is dedicated to the one function, we might reasonably hope that it would provide better RF performance. A more significant advantage is that multifunction devices that combine a DSL modem with WLAN router and switch functions do not normally have a usable RF connector, and so it is hard to connect an external antenna. The small stub antenna usually provided is connected by a fixed wire to a sub-miniature connector on the internal WLAN card. This connector is not designed for repeated

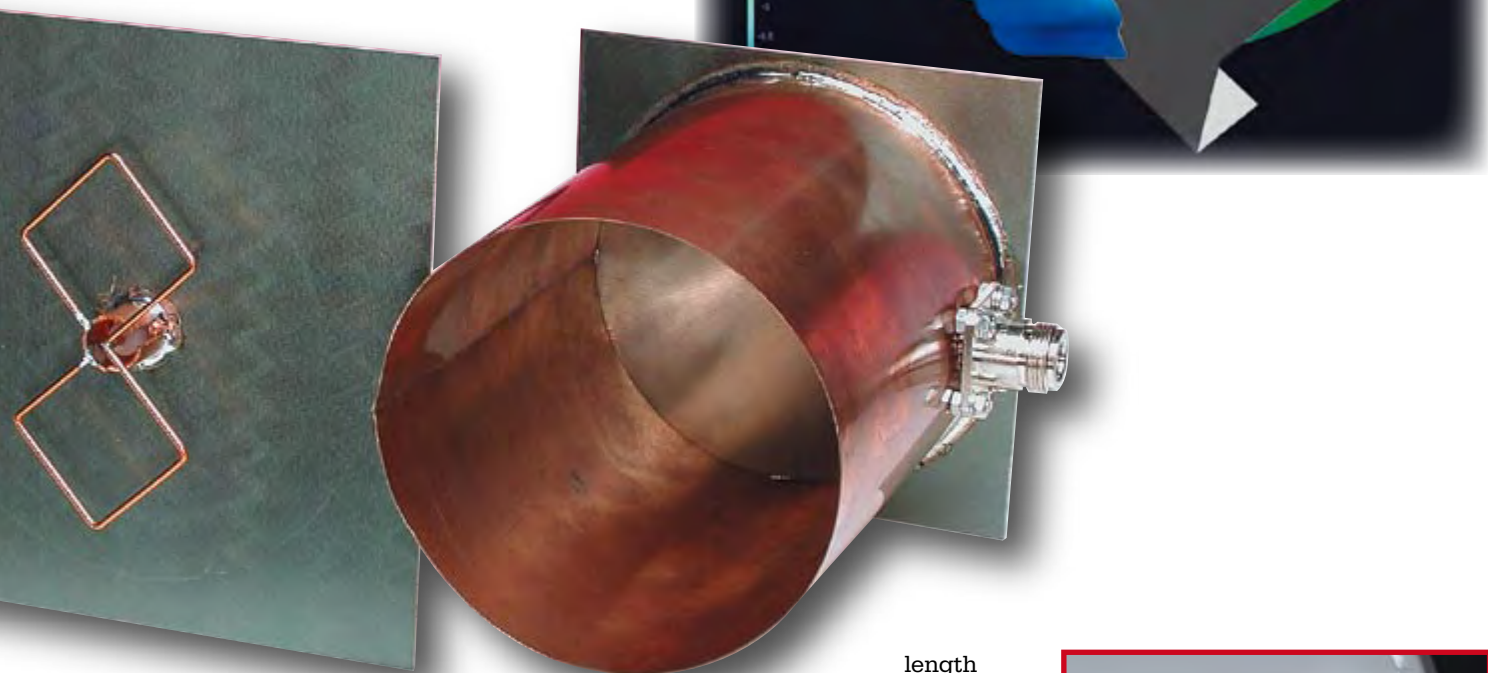

plugging and unplugging and is unmanageably tiny. Access points, however, are available with common-or-garden SMA connectors (see **Figure 2**), making it easy to connect an external purchased or home-made directional antenna.

One further piece of advice: it is preferable to use a longer Ethernet cable rather than a longer antenna cable. It is easy to achieve data transfer rates of 100 Mbit/s over 50 m or more of CAT5 cable; but the losses in 50 m of antenna cable could easily cancel out the benefits of a directional antenna.

Antenna types

In the following discussion we shall not consider WLAN routers that employ several antennas and MIMO (multiple input multiple output) technology. Commercially-available access points (such as the one shown in **Figure 1**) are usually fitted with a so-called quarter-wavelength stub antenna, or monopole (see **Figure 3**). Sometimes the stub can be entirely inside the enclosure (as long as it is made of plastic). The antenna consists of a piece of wire with

length $\lambda / 4$. At 2.44 GHz, this is a quarter of $300 \times 10^6 / 2.44 \times 10^9$ metres, or slightly more than 3 cm.

At the other end of the spectrum from this simple antenna is the parabolic reflector, which can have a diameter of several metres. This can offer a gain of up to 60 dB over the simple quarter-wavelength monopole. European regulations only allow such antennas to be fed at a very low power. Experiments in the USA with specially-constructed (and expensive) antennas of this type have achieved ranges of up to 200 km.

A wide range of directional antenna designs between these two extremes have been tried for WLAN applications. Two designs have proved most successful, offering good gain and simple construction. The first type takes the form of a waveguide and goes by the catchy name of 'cantenna' (see left-hand half of **Figure 4**). The second type consists of specially-arranged diamond-shaped sections in front of a reflector, and is called a 'biquad' (see right-hand half of **Figure 4**). The lat-



Figure 1. SMA connector on the rear panel of an access point.



Figure 2. A typical access point: sometimes these are used to help reduce the length of antenna cable needed.



Figure 3. Quarter-wavelength stub antenna suitable for a WLAN router or access point.



Figure 4. Prototype antenna and biquad antenna constructed in the Elektor Electronics laboratory.

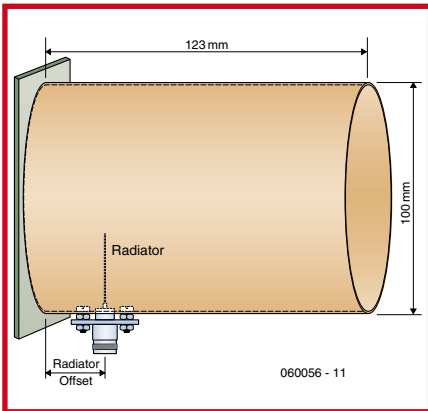


Figure 5. Construction drawing for the antenna.

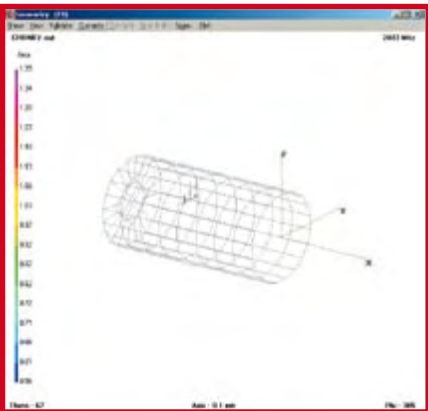


Figure 6. Three-dimensional model of the antenna plotted by 4NEC2.

ter type can in theory offer a gain of around 12 dB (although as we shall see later, practice can deviate from theory!), somewhat more than the 10 dB that the antenna can provide. Both types give considerable improvements over typical integrated antennas, and we shall now go on to look at them both in more detail.

The antenna

As mentioned above, the antenna operates as a kind of waveguide. The theory of such antennas is far from trivial; those interested can find a good introduction at [1]. As can be seen from Figure 4 and the drawing in Figure 5, the antenna consists of a can of certain specified dimensions and a carefully-arranged feed.

There is a wide range of guides available to constructing antennas of various dimensions [2]. The following suggestions have the advantage that they have been tested by simulation, carried out by Stefan Tauschek using a software package called 4NEC2, available for free download from [3]. The program is based on the so-called boundary element method [4]: the idea is to convert Maxwell's equations into a system of linear algebraic equations, which are then stepwise integrated to calculate the current distribution in the antenna. The 'NEC' in the program name stands for 'numerical electromagnetic code'. Although their derivation is complicated, the results themselves are simple: Figure 6 shows the three-dimensional model of the Antenna in 4NEC2 and Figure 7 the calculated radiation pattern. The directional nature of the antenna is clear.

To make an accurate antenna the can must be exactly one wavelength long. At 2.44 GHz this is very nearly 123 mm. The internal diameter is approximately 100 mm, slightly more than $4/5 \lambda$. The feed stub, shown as a radiator, should be approximately $\lambda/5$, or 25 mm, long. Ideally this is a wedge-shaped or tapered piece of metal, with the thicker end pointing to the middle of the can. The distance from the base of the can, the 'radiator offset', is the rather odd multiple of $7/32$ times the wavelength, or 27 mm.

It is difficult to find ready-made cans with these dimensions. A reasonably accurate version can be made by hand from copper sheet as shown in Fig-

When we had constructed prototypes in our laboratory we naturally wanted to test them immediately. The test equipment comprised an ordinary laptop and a PC as the fixed station to which the various antennas were connected. The walls of the laboratory building are built using a type of brick that absorbs RF of this frequency very well. The layout of the building is a chain of rooms in a slightly staggered arrangement. There are many PCs and other electronic devices in the laboratory and in the editorial offices, producing a high level of electromagnetic interference.

We tested the ranges of four antennas: an ordinary $\lambda/4$ stub, the biquad, the antenna, and a commercial model (the HA-O14SD from Hawking Technology: see Figure 12) costing around fifty pounds, with a quoted gain of at least 14 dB. In each case the antenna was connected to the WLAN card in the



ure 4; deviations of up to 10 % from the nominal dimensions should be tolerable for ordinary use. Of course, there is plenty of scope for experimentation. The trickiest part of construction is connecting to the radiator. We can start from a commercially-available N-type RF connector. Figure 8 shows an example of this type of connector with a radiator (sometimes called 'exciter') soldered to it. A suitable hole must be made in the can to fit the connector. Washers should be used when fitting the connector to avoid damage to the can. The antenna is now ready for use. If it is to be used outside it is worth considering waterproofing the connection to the radiator.

Adaptor cables from N-type connectors to SMA connectors or other types are available ready made; alternatively, it is easy, as well as cheaper, to make up a suitable cable oneself. As noted above, the antenna cable should be no

Web links

[1] **Waveguide theory:**
http://en.wikipedia.org/wiki/Waveguide_%28electromagnetism%29

[2] **Various antenna designs:**
<http://qdg.sorbs.net/qdgant.htm>

PC using an RF cable three metres long.

We achieved the following results:

- 1) Stub: 10 m
- 2) HAO14SD: 20 m
- 3) Biquad: 21 m
- 4) Antenna: 26 m

Here again the antenna comes out on top. The performance of the commercial antenna teaches us two things: first, one should not always believe in a manufacturer's sometimes rather optimistic gain figures (the antenna is delivering an estimated gain of around 6 dB rather than 14 dB); and second, the DIY approach often pays off!



Figure 12.
The commercial directional WLAN antenna used for comparison tests.

longer than necessary in order to get the most benefit from the gain of the antenna.

Biquad

An alternative design of antenna, which is also easy to construct, is the biquad. This takes the form of an angular figure-of-eight pattern of wire in front of and parallel to a reflector surface. The design has proved very popular on the Internet, where there are countless construction guides, no doubt because of its good theoretical performance and 'high-tech' appearance. The design described here has the advantage, shared with the antenna above, that it has been simulated and optimised by computer.

In essence the biquad is a folded multiple $\lambda/4$ dipole. As **Figure 9** shows, the resulting shape resembles a figure-of-eight. Each edge of the two squares

is $\lambda/4 = 30.5$ mm long. A suitable material is 1 mm copper wire. The feed connection is made between the point where the two squares meet and the open ends, which are connected to ground (the feed cable screen). **Figure 10** clearly shows the current distribution due to the individual antenna elements. Current nodes and antinodes can be seen at the corners of the square: the antenna is in resonance.

The figure-of-eight should be mounted approximately 15 mm to 17 mm in front of the reflector. Practical experiments have shown that it is possible to achieve an excellent SWR (standing-wave ratio) of 1:1.15.

It is recommended that the side of the reflector should be equal to one wavelength. In other words, the ideal reflector is a conducting square of metal measuring 123 mm on each side. Various materials are suitable: in the prototype we found copper-clad printed circuit board satisfactory. A reflector could also be made from a CD (the metallised part has diameter approximately 118 mm). The dimensions of the multi-dipole are unfortunately rather critical.

As shown in **Figure 4**, a suitable piece of copper pipe can be used to fix the biquad figure-of-eight. The pipe is soldered to the reflector and the RF coaxial cable passed through the pipe as the feed. The central conductor of the cable is then directly soldered to the middle of the figure-of-eight. Alternatively, an N-type connector can be used as with the antenna, the correct distance to the reflector being achieved using two pieces of copper wire of suitable length.

The figure at the beginning of the article shows the radiation pattern of a biquad antenna whose reflector is fitted with two plates, 30 mm high, on opposite sides to attenuate the rearwards-pointing lobes. Using this construction a gain of between 10 dB and 12 dB can be achieved. There are reports of laptops equipped with biquad antennas connecting to an access point (also with a specially-constructed antenna) 10 km away.

Miscellanea

Tall tales of spectacular results obtained by avid WLAN hunters abound, but it is true to say that there can be enormous differences in practically-achievable range depending on the local townscape or countryside, on

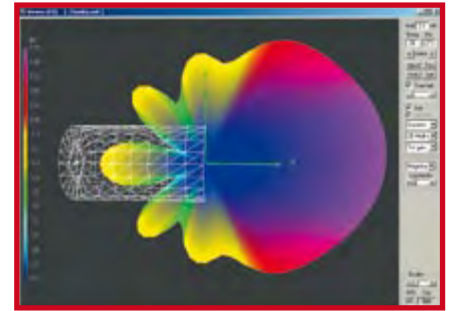


Figure 7. Radiation pattern of the antenna calculated using 4NEC2.



Figure 8. N-type connector with a tapered radiator made from copper sheet soldered to it.

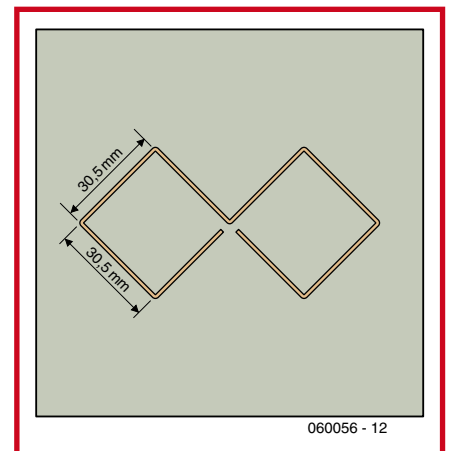


Figure 9. Construction drawing for the figure-of-eight biquad antenna.

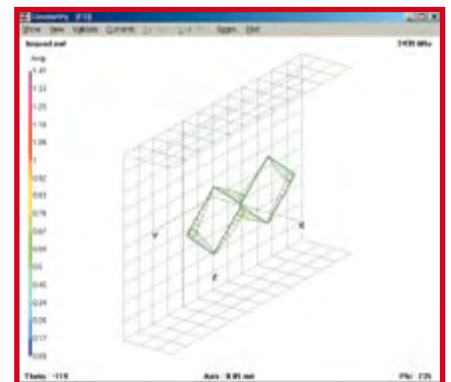


Figure 10. Current distribution for the biquad antenna calculated using 4NEC2.

[3] 4NEC2 software:

<http://home.ict.nl/~arivoors>

[4] Boundary element method:

http://en.wikipedia.org/wiki/Boundary_element_method

[5] Download page for NetStumbler:

<http://www.netstumbler.com/downloads>

Antennas in practice

The most detailed calculations and highest technical specifications count for nothing if good results are not achieved in practice. We therefore decided to take the antennas we built in the Elektor Electronics laboratory according to the designs calculated by Stefan Tauschek for a practical test. The most stringent test involved installing the various antennas at the home of Thomas Scherer in Frankfurt city centre and then using an ordinary Centrino laptop running NetStumbler to measure the signal strength in the street outside and determine over what range a connection could be achieved.

MAC	SSID	r	Speed	Vendor	Type	Enc.	SNR	Signal	Noise	SNR+
000C	Movada	1	54 Mbps	Gentek	AP		-52	-100	8	
000E	WLAN	1	54 Mbps		AP	13	-42	-100	18	
0004	IfPP Test Kanal 1	1*	54 Mbps	Fake!	AP	WEP	55	-45	-100	55
001E	FRITZ!Box Fon WLAN 7050	6	54 Mbps	Fake!	AP	WEP	-77	-100	23	
001E	FRITZ!Box Fon WLAN 7050	6	54 Mbps	Fake!	AP	WEP	-42	-100	18	
001E	Accor/WirelessLAN/Hgu	6	54 Mbps	Fake!	AP	WEP	-47	-100	13	
001E	Späder	6	54 Mbps	Fake!	AP	WEP	-60	-100	20	
001E	FRITZ!Box Fon WLAN 7170	6	54 Mbps	Fake!	AP	WEP	-42	-100	18	
001E	FRITZ!Box WLAN 3070	6	54 Mbps	Fake!	AP	WEP	-42	-100	38	
0004	FRITZ!Box Fon WLAN 7050	6	54 Mbps	Fake!	AP	WEP	-57	-100	43	
001E	IfPP Kanal 9	9	54 Mbps	Fake!	AP	WEP	-60	-100	20	
000C	level_one	10	22 Mbps	Secomem	AP	WEP	-65	-100	15	
000E	NETGEAR	11	54 Mbps	Netgear	AP	WEP	-52	-100	8	
001E	arjits	11	54 Mbps	Fake!	AP	WEP	-51	-100	9	
000E	knuscheinet	11	54 Mbps	AP	WEP	15	-60	-100	20	
000C	WLAN	11	54 Mbps	Accoton	AP	WEP	-52	-100	8	
000E	NETGEAR	11	54 Mbps	Netgear	AP	WEP	-64	-100	16	
000C	Movada	11	54 Mbps	Gentek	AP	WEP	-64	-100	16	
001E	StarbergerSee	11	54 Mbps	AP	WEP		-65	-100	15	
000C	WLAN	11	54 Mbps	Accoton	AP	WEP	-75	-100	25	
000C	mitsu	13	11 Mbps	Accoton	AP	WEP	23	-77	-100	23

Figure 11. List of WLANs found by NetStumbler.

The screendump in **Figure 11** was taken immediately outside the building. It shows that in this area there are many WLANs competing for the airwaves. The strongest signal, with SSID 'IfPP Test Kanal 1', is being produced by the access point shown in Figure 2 set up for this test.

Table 1. Typical antenna ranges in the city centre.

Distance	Antenna type		
	Stub	Biquad	Cantenna
20 m	-84 dB	-80 dB	-72 dB
30 m	-	-85 dB	-80 dB
40 m	-	-	-86 dB

The building is a five-storey reinforced concrete structure built in the 1980s. The walls screen radio signals so effectively that radio and digital television reception is difficult, even though the transmitter is

only 4 km away. The WLAN router is situated in a hallway on the third floor, surrounded by walls. Even just 5 m away, on the floor above, signal quality has dropped from 'excellent' to merely 'good'. Inside the building only four of the 21 WLANs shown in Figure 11 can be received. The building thus makes an excellent test location..

Table 1 shows how far the radio waves propagate along the street outside the building, after attenuation by one wall. The directional antennas were, of course, correctly aligned for the test. The first surprise is that the biquad is clearly outperformed by the cantenna. The reason for this disagreement with the theoretical results was not found: cable connections and the like were thoroughly checked. In the city (and with one wall interposed between transmitter and receiver) the cantenna offers approximately double the range of the ordinary stub antenna. The performance of the biquad antenna sits between the two: we eagerly await the comments of our expert readership in the Elektor Electronics online forum!

To see what a directional antenna is capable of, we need to get away from the electromagnetic smog of the city. To this end we moved the test setup to a house on the outskirts of a small village. The antenna, connected to an access point, was arranged to transmit from the (open) front door of the house over the fields beyond. The measurements therefore give the line-of-sight performance of the antennas. Besides the test WLAN, NetStumbler found two other WLANs in range, but both were at least six channels away from the test frequency.

Table 2. Ranges achieved in open countryside.

Distance	Antenna type		
	Stub	Biquad	Cantenna
40m	22 Mbit	48 Mbit	54 Mbit
60m	-	11 Mbit	54 Mbit
120m	-	-	5,5 Mbit

Table 2 shows that line-of-sight communication is possible over considerably greater distances than in the city. We have shown the communication rates achieved, as this is the most practically useful figure. Communication over 120 m using a tin can is not a bad achievement, we think! The tripling of range achieved using the cantenna, compared to the stub antenna, is in line with the theoretical gain figure of 10 dB.

If both access point and laptop are equipped with directional antennas, ranges under these conditions of over 200 m can easily be obtained. In this case the laptop must be used in conjunction with an external WLAN adapter (either a PCMCIA card or connected via USB) which has an RF connector, although this arrangement does make the laptop rather unwieldy!

house layout and construction material, and even on the neighbours! For example, in Frankfurt city centre where Thomas Scherer carried out his antenna field tests there is practically no point where a laptop cannot pick up signals from at least 15 WLANs, and the same would go for any other major European city. To this we can add interference from microwave ovens, mobile telephones and other transmitters, all in or near the frequency band we are interested in. Things are quieter (as yet) in the 5 GHz band used by

IEEE 802.11a WLANs. It is also worth noting that the channels available in Europe, numbered from 1 to 13 in the IEEE 802.11b and 802.11g standards, provide for only three non-overlapping channels. A powerful WLAN run by a neighbour can interfere with between three and six channels on either side.

If problems with signal quality are encountered, the first thing to check is what transmitters are active in the neighbourhood. The NetStumbler program [5], a favourite of 'wardrivers'

(people who drive around looking for WLANs using a laptop) is helpful here. It scans the radio frequencies in a configurable fashion and shows information about the various networks available, including their SSIDs and signal strengths. Depending on the WLAN hardware, the results might not always be perfectly accurate, but the relative values do usually give a good overview of the situation.

(060056-1)

In all mains-operated equipment certain important safety requirements must be met. The relevant standard for most sound equipment is Safety of Information Technology Equipment, including Electrical Business Equipment (European Harmonized British Standard BS EN 60950:1992). Electrical safety under this standard relates to protection from

- a hazardous voltage, that is, a voltage greater than 42.4 V peak or 60 V d.c.;
- a hazardous energy level, which is defined as a stored energy level of 20 Joules or more or an available continuous power level of 240 VA or more at a potential of 2 V or more;
- a single insulation fault which would cause a conductive part to become hazardous;
- the source of a hazardous voltage or energy level from primary power;
- secondary power (derived from internal circuitry which is supplied and isolated from any power source, including d.c.)

Protection against electric shock is achieved by two classes of equipment.

Class I equipment uses basic insulation; its conductive parts, which may become hazardous if this insulation fails, must be connected to the supply protective earth.

Class II equipment uses double or reinforced insulation for use where there is no provision for supply protective earth (rare in electronics – mainly applicable to power tools).

The use of a Class II insulated transformer is preferred, but note that when this is fitted in a Class I equipment, this does not, by itself, confer Class II status on the equipment.

Electrically conductive enclosures that are used to isolate and protect a hazardous supply voltage or energy level from user access must be protectively earthed regardless of whether the mains transformer is Class I or Class II.

Always keep the distance between mains-carrying parts and other parts as large as possible, but never less than required.

If at all possible, use an approved mains entry with integrated fuse holder and on/off switch. If this is not available, use a strain relief (Figure, note 2) on the mains cable at the point of entry. In this case, the mains fuse should be placed after the double-pole on/off switch unless it is a Touchproof® type or similar. Close to each and every fuse must be affixed a label stating the fuse rating and type.

The separate on/off switch (Figure, note 4), which is really a 'disconnect device', should be an approved double-pole type (to switch the phase and neutral conductors of a single-phase mains supply). In case of a three-phase supply, all phases and neutral (where used) must be switched simultaneously. A pluggable mains cable may be considered as a disconnect device. In an

approved switch, the contact gap in the off position is not smaller than 3 mm.

The on/off switch must be fitted by as short a cable as possible to the mains entry point. All components in the primary transformer circuit, including a separate mains fuse and separate mains filtering components, must be placed in the switched section of the primary circuit. Placing them before the on/off switch will leave them at a hazardous voltage level when the equipment is switched off.

If the equipment uses an open-construction power supply which is not separately protected by an earthed metal screen or insulated enclosure or otherwise guarded, all the conductive parts of the enclosure must be protectively earthed using green/yellow wire (green with a narrow yellow stripe – do not use yellow wire with a green stripe). The earth wire must not be daisy-chained from one part of the enclosure to another. Each conductive part must be protectively earthed by direct and separate wiring to the primary earth point which should be as close as possible to the mains connector or mains cable entry. This ensures that removal of the protective earth from a conductive part does not also remove the protective earth from other conductive parts.

Pay particular attention to the metal spindles of switches and potentiometers: if touchable, these must be protectively earthed. Note, however, that such components fitted with metal spindles and/or levers constructed to the relevant British Standard fully meet all insulation requirements.

The temperature of touchable parts must not be so high as to cause injury or to create a fire risk.

Most risks can be eliminated by the use of correct fuses, a sufficiently firm construction, correct choice and use of insulating materials and adequate cooling through heat sinks and by extractor fans.


The equipment must be sturdy: repeatedly dropping it on to a hard surface from a height of 50 mm must not cause damage. Greater impacts must not loosen the mains transformer, electrolytic capacitors and other important components.

Do not use dubious or flammable materials that emit poisonous gases.

Shorten screws that come too close to other components.

Keep mains-carrying parts and wires well away from ventilation holes, so that an intruding screwdriver or inward falling metal object cannot touch such parts.

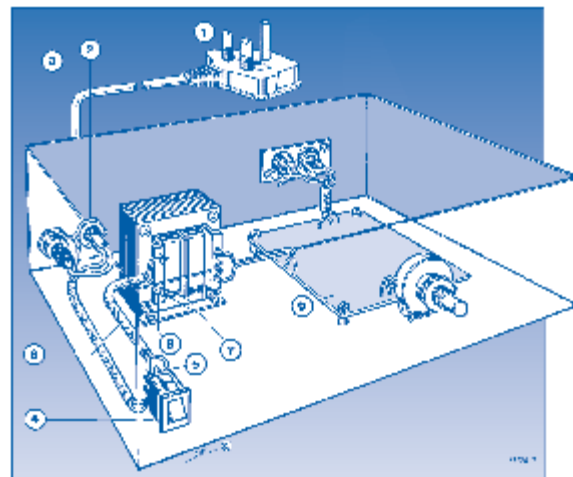As soon as you open an equipment, there are many potential dangers. Most of these can be eliminated by disconnecting the equipment from the mains before the unit is opened. But, since testing requires that it is plugged in again, it is good practice (and safe) to fit a residual current device (RCD)*, rated at not more than 30 mA to the



1. Use a mains cable with moulded-on plug.
2. Use a strain relief on the mains cable.
3. Affix a label at the outside of the enclosure near the mains entry stating the equipment type, the mains voltage or voltage range, the frequency or frequency range, and the current drain or current drain range.
4. Use an approved double-pole on/off switch, which is effectively the 'disconnect device'.
5. Push wires through eyelets before soldering them in place.
6. Use insulating sleeves for extra protection.
7. The distance between transformer terminals and core and other parts must be ≥ 6 mm.
8. Use the correct type, size and current-carrying capacity of cables and wires – see shaded table below.
9. A printed-circuit board like all other parts should be well secured. All joints and connections should be well made and soldered neatly so that they are mechanically and electrically sound. Never solder mains-carrying wires directly to the board: use solder tags. The use of crimp-on tags is also good practice.
10. Even when a Class II transformer is used, it remains the on/off switch whose function it is to isolate a hazardous voltage (i.e., mains input) from the primary circuit in the equipment. The primary-to-secondary isolation of the transformer does not and can not perform this function.

mains system (sometimes it is possible to fit this inside the mains outlet box or multiple socket).

* Sometimes called residual current breaker – RCB – or residual current current breaker –RCCB.

These guidelines have been drawn up with great care by the editorial staff of

this magazine. However, the publishers do not assume, and hereby disclaim, any liability for any loss or damage, direct or consequential, caused by errors or omissions in these guidelines, whether such errors or omissions result from negligence, accident or any other cause.

3-core mains cable to BS6500 1990 with three stranded conductors in thick PVC sheath

Max current	3 A	6 A	13 A
conductor size	16/0.2 mm	24/0.2 mm	40/0.2 mm
Nom cond area	0.5 mm²	0.75 mm²	1.25 mm²
overall cable dia.	5.6 mm	6.9 mm	7.5 mm

Insulated hook-up wire to DEF61-12

Max current	1.4 A	3 A	6 A
Max working voltage	1000 V rms	1000 V rms	1000 V rms
PVC sheath thickness	0.3 mm	0.3 mm	0.45 mm
conductor size	7/0.2 mm	16/0.2 mm	24/0.2 mm
Nom cond area	0.22 mm²	0.5 mm²	0.95 mm²
overall wire dia	1.2 mm	1.6 mm	2.05 mm


3-flat-pin mains plug to BS 1363A

Where am I – and Where am I going

Position determination using WLAN

Dennis Vredeveld

Wireless LAN (WLAN) has become incredibly popular in the last few years. Wireless internet has now become very common in a corporate environment as well as in public spaces and in our homes. But what not many people know, is that WLAN can also be put to excellent use for other applications, such as, for example, determining the position of devices on the wireless network. How this works you can read in this article.

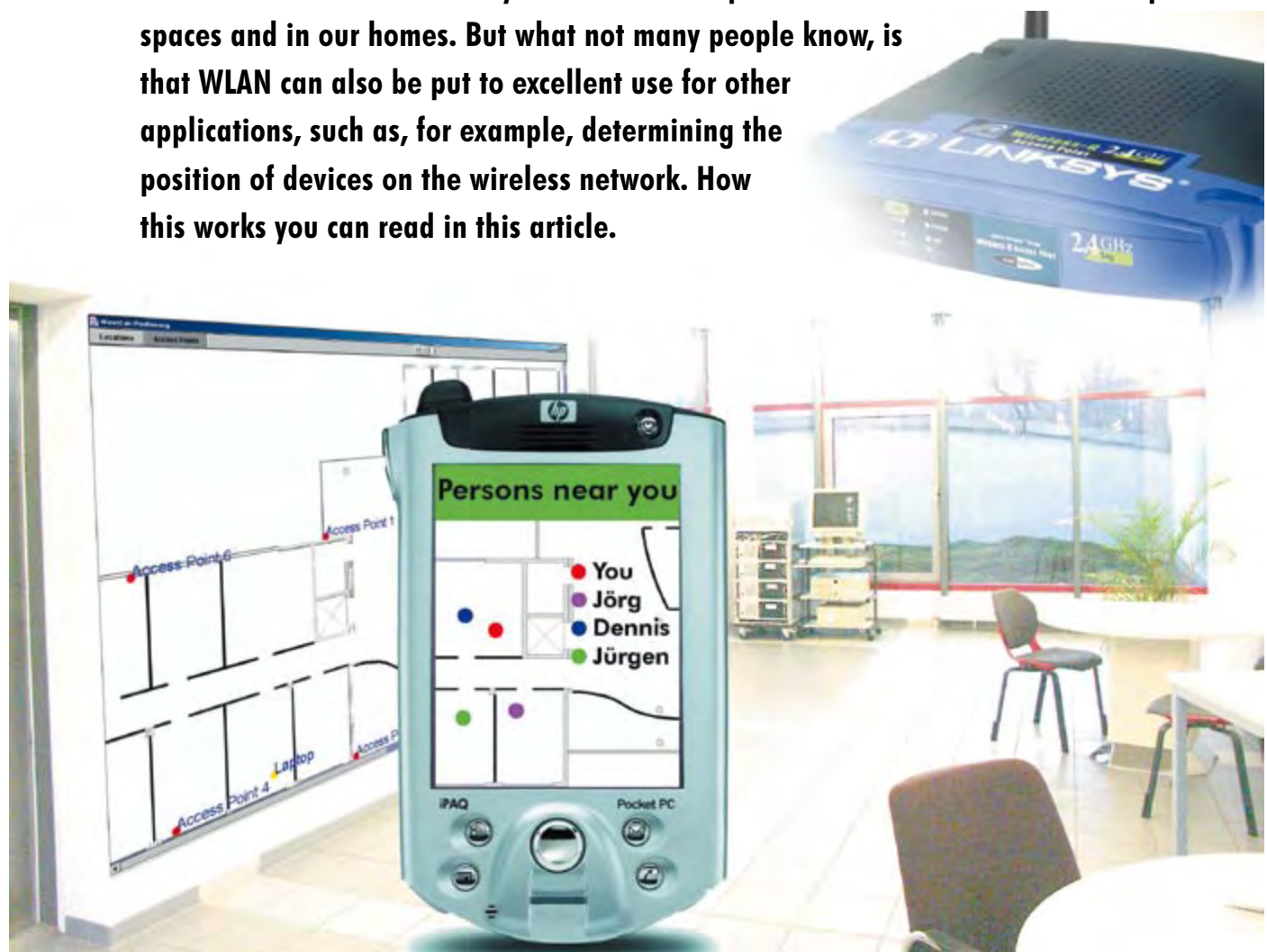

Position determination technology is the basis for the now universally known GPS (Global Positioning System). GPS operates relatively accurately in the city and motorways, but is not suitable for use inside buildings. The reason is that the reception of the GPS signals from the satellites are too weak inside buildings so that there is very little left of the original accuracy. An indoor equivalent of the GPS system is currently not available and there is not even the slightest sign of a possible standard. As a result we have to resort to other

systems, which, even though they were not developed for this purpose, still provide surprisingly good results in practice. Such as, for example, position determination using WLAN!

WLAN – how does it work?

Devices with WLAN functionality generally have an integrated WLAN card. This card maintains the connection with the base station, the so-called Access Point (AP).

here are the Others?

Wireless transfer of data can take place once a successful connection has been established. Because the quality of the connection can diminish – or even disappear completely – when the user moves, the card scans at regular intervals for other Access Points that may be within range. Based on different algorithms that are implemented by the manufacturer in the driver for the card, the card can decide to establish a connection with another AP and terminate the old connection. This is called a 'handover'. Which access point becomes the new connection depends on the signal strengths of the various APs. The signal strength is determined by the card based on data packets that are sent by the AP specifically for this purpose. The packets are called beacons and are transmitted by the AP at regular intervals (about 10 times per second). These beacons contain the unique MAC-address of the AP, as well as the name of the wireless network, the so-called SSID. Should the signal strength of the AP that the card is currently connected to become too weak then the card starts to search for better alternatives. This is only valid of course if we have the use of a network with multiple APs (refer to the example in **Figure 1**).

Relationship signal strength-position


The method described here implies that there is a relationship between the position of the user (or more accurately: of the WLAN card in the device that the user is carrying) and the measured signal strength of the beacons that are received from different APs. This relationship can also be used to locate the user within the WLAN network. In principle two different methods can be thought of to achieve this:

1. Simulation: We try to calculate the expected signal strength at each position in advance based on a model. Afterwards we compare the measured values and try to find out where the user is based on the results from the model.
2. Calibration: Instead of calculating the expected signal strength for each location, the signal strength is measured at different, predetermined locations. This information is stored and used as data for comparison for subsequent measurements when the user is in an unknown location.

Various tests have shown that the first method is not only significantly more complicated, but is also less accurate than the second. The reason for this is that the signal propagation in an indoor environment is so very complex that even very extensive models cannot take all existing factors into account.

Reading Signal strengths

The question now arises how we are going to obtain these seemingly very important signal strengths. Windows, after all, hides this information from us in the first instance by translating the received signal strengths into less accurate terms such as 'very strong' or 'weak'. The answer to this? NDIS! NDIS is a standard Win-



Mac	SSID	Ch	RSSI	Last Seen	First
00022D32D08F	ipos	3	75	060601-131440	060601-131440
001217CCC558	linksys	5	73	060601-131440	060601-131440
00022D2D1068	LiMoNet	6	73	060601-131440	060601-131440
001217CCC528	linksys	3	60	060601-131440	060601-131440
001217CCC52E	linksys	9	61	060601-131440	060601-131440
0016869523F9	IMST	8	61	060601-131440	060601-131440
00131A961850		11	73	060601-131440	060601-131440
00022D2D60EE	LiMoNet	11	93	060601-131439	060601-131440
00022D0F7ACA	LiMoNet	1	60	060601-131440	060601-131440
000D898C916E	IMST	10	77	060601-131440	060601-131440
000D89ACAE4	IMST	2	67	060601-131440	060601-131440
000F3D09C86A	IMST	7	77	060601-131440	060601-131440
00601D1D00C	LiMoNet	4	79	060601-131440	060601-131440
0016869C3A94	IMST	9	78	060601-131432	060601-131440
0016869C38C3	IMST	4	78	060601-131440	060601-131440

Figure 1. This signal strength information is normally hidden from us by Windows.

dows-API for communicating with network cards. In this way it is possible to obtain the necessary information from the WLAN-driver in a pre-defined manner, irrespective of the manufacturer. More information can be found at [1] and [2].

Performing the calibration

Before our positioning system can be used, we must first carry out the calibration. This consists of recording the

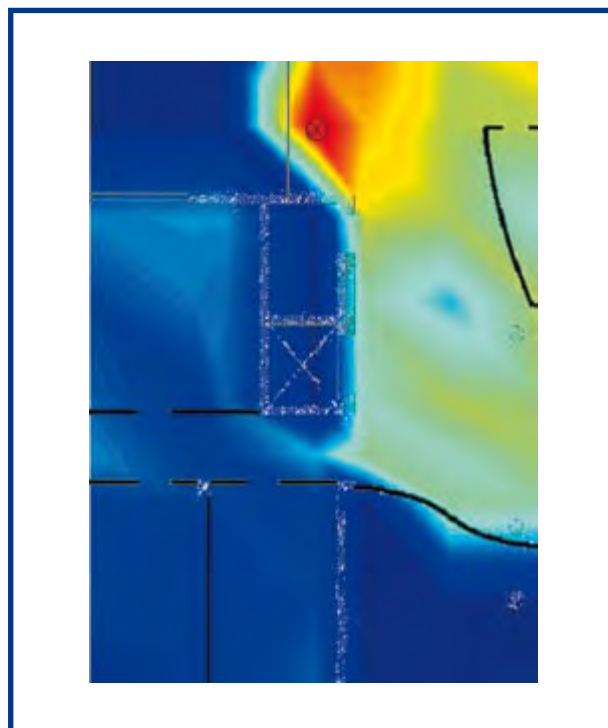


Figure 2. Visualisation of the signal strength of an AP, based on a simulation. Red means large signal strength, blue means weak signal strength.

signal strengths of all access points at different locations, scattered over the space that is covered by the LAN network. More points increase the accuracy, until the points are less than one meter apart. At every calibration location we measure the received signal strength in four different directions for a few seconds for all APs. This information is stored in a database. The different orientations are important because the human body has a measurable influence in the received signal strength. There is therefore a difference if we are facing the AP or if we are between the AP and the WLAN device.

Where am I?

Once this calibration has been completed, the actual position determination can begin. By measuring the signal strengths of all APs at regular intervals and comparing these with the calibrated locations, the most likely position can be calculated. Because we will not usually be at a calibration location, a weighted average is taken from the calibration positions that correspond best with the signal strength profile.

With additional mathematical tricks (such as calculating a running average of the recent locations) the accuracy of the system can be further improved. In this way we are able to achieve a resolution down to a few meters; sufficient to determine in which room or in which corner of a hall the user is located.

The smarter the algorithm, the better the position can be determined. The development of a real clever algorithm

The author

Dennis Vredeveld (vredeveld@imst.de) is a software-architect at IMST GmbH in Kamp-Lintfort, Germany, where, among other things, work is being done on a software-framework for several indoor position determination technologies, including WLAN.

More information can be found at www.imst.com and www.centrum21.de under the heading 'ipos'.

for determining the position is certainly no sinecure – we are curious for your solution. If you have developed a good method for this, then be sure to let us know!


(060269) Illustrations : IMST GmbH

Web links

- [1] www.ndis.com
- [2] <http://msdn.microsoft.com/library/default.asp?url=/library/en-us/wceddk40/html/cxconNDISDriverArchitecture.asp>

Advertisement

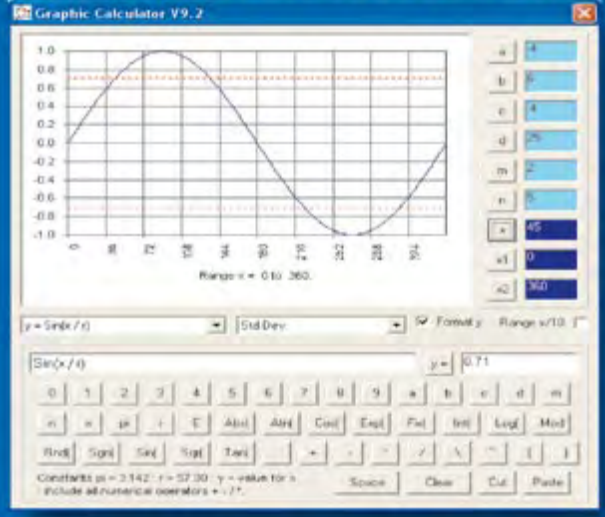FREE download
Graphic Calculator V9.2
 with Electronics, Mechanics and Maths Toolbox.



includes 'Technology, Hobbies and Education Store' software.

Principles V9.2 *Link your business to thousands of new educational and hobbies visitors every day via our software integrated browsers!*


Something for all the family!
installs to more than one computer

Home Study Pack

Principles V9.2! our top selling package for maths, computing, ICT, physics, CDT, electronics, electrical, mechanics, engineering, PICs, model railways, amateur radio, motor vehicle maintenance. GCSE, A-Level, HNC HND and Degree. Download and fully installed for less than 20p a day, you only pay for as long as you need it!

www.eptsoft.com

eptsoft limited, Glebe House, School Lane, East Keel, Spilsby, Lincolnshire PE23 4AU
 Tel: 01750 754037 email: info@eptsoft.com

Senior Power Engineer 

£35k - £55k **Cambridge, UK**


Splashpower Ltd develops wireless power technology for recharging portable consumer electronics devices. Having completed a major phase of R&D, they are preparing to license their technology to global OEM's. Based in the vibrant and Historic town of Cambridge, 40 miles North of London, it is the centre of new and emerging technology within the UK.

They are currently seeking a **Senior Power Engineer** to:

- Lead all Power circuit design and assessment from requirements analysis through to acceptance and certification, providing technical leadership to implementation teams
- Develop system level mapping, detail simulation tools and Design Methodology
- Assist in the capture, and preparation of, design specifications from primary requirements to the implementation of secondary requirements

If you have extensive experience in low power electronics (sub 100 Watt), with knowledge of batteries, charging, and/or power systems (e.g. SMPS), we'd like to talk to you.

If you want to work with some of Europe's brightest Engineers contact **Lisa Hart** on **+44 (0)1582 878827** or **Lhart@redlineplc.com**

Redline  **www.redlineplc.com** Luton: +44 (0)1582 450054
 Manchester: +44 (0)161 491 7830
 Scotland: +44 (0)1698 527120
 Recruiting Excellence **cv@Redlineplc.com**


Client-server quizmaster

Manuel Schreiner

This circuit is designed for use in quizzes involving several players. The situation is a familiar one: whoever presses (or, in practice, thumps) their button first lights their lamp and is given the opportunity to answer the question.

We have published a number of designs for such circuits over the years in *Elektor Electronics*, but admittedly none has been particularly straightforward, often using microcontrollers and even radio modules!

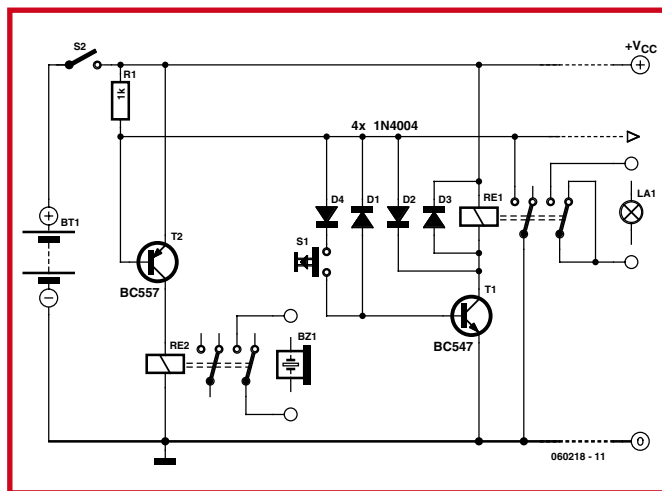This circuit demonstrates that we can do the job very simply, using just a couple of discrete (not to say antique!) components. Our terminology, on the other hand, is bang up-to-date: we have designed a client-server quiz system. The server (i.e., the quizmaster)



is shown on the left in the circuit diagram. It consists of a relay (K2), a pull-up resistor (R1) and a transistor. The relay is used to switch a buzzer or bell. Switch S2 is used to reset the system. The client systems are connected

to the server and to one another using a three-wire bus. Each client consists of a relay, a transistor and a couple of diodes. One of the jobs of the relay is to switch on the lamp on the contestant's desk.

The three bus wires carry V_{CC} , ground, and a blocking signal. A number of client systems, one per contestant, can be connected to the three wires. In the quiescent state the blocking signal carries the supply voltage V_{CC} . When one of the contestants' lamps is lit this drops to 0.7 V.

When a contestant presses his button (S1) relay K1 pulls in as a result of the voltage (the blocking signal minus 0.7 V) applied to the base of transistor Q1. If another contestant subsequently presses his own button nothing will happen: the voltage appearing at the base of his transistor will now be 0 V, and so it will not be turned on.

Relays with a working voltage of 6 V can be used, with a supply voltage not exceeding 9 V.


(060218-1)

Pencil rubber cleans solder pads

Luc Lemmens

Just in case you didn't know, from 1 July 2006 all new electronics equipment has to be RoHS-compliant. One of the implications of the new rules is that solder tin containing lead may no longer be used in newly produced equipment. Interestingly, exceptions are made for automotive electronics, medical and military equipment. Currently there are some doubts regarding the mechanical durability of the substances used to replace the lead/tin alloy we've been using for decades to solder our circuits. The use of lead/tin solder is also still allowed for repair work on older equipment. Consequently it will take a while before the 'old' type of solder tin has disappeared from electronics in general.

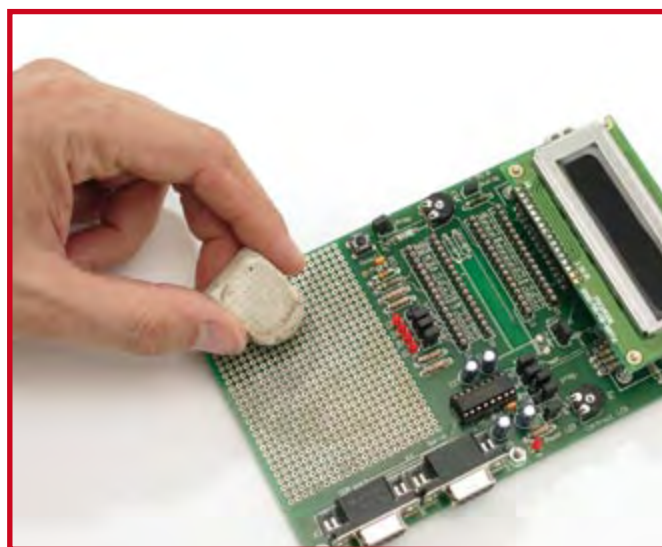Browsing the soldering and soldering tools section of just about any catalogue from a major electronics supplier, you'll soon be at a loss at what solder tin to choose, the choice of alloys and compounds being confusing to say the least. Still, 90% of all varieties have one thing in com-



mon: the lead component has been replaced by silver. Only the tin/silver ratio varies. In most cases, another metal has been added to optimise the chemical and thermal characteristics. Also, differences exist in the flux type and the amount of it added to the solder tin. Pre-tinned Elektor Electronics printed circuit boards, too, had to undergo a change in the pro-

duction process. Since a few months, our board suppliers apply chemical silver to cover copper surfaces and so comply with RoHs. It took us some getting used to when the first boards started to arrive in our lab — to us, it seemed as if the white component overlay was covering the solder pads! Still, the boards turned out to be perfectly solderable.

Now, silver has a nasty habit if oxidising quickly. Just as table silver, our boards seem to turn black and dull after a while, especially if touched by fingers. It is therefore recommended to use airtight packaging for circuit boards when in storage or transit. After all, solder tin will not flow very well on silver oxide.

If a circuit board shows black smudges, problems in soldering may be prevented by solving the silver oxide traces with a soft piece of pencil rubber, which some of you may remember from the days when a pencil was used to make notes and drawings. The silver-oxide spots and areas will disappear remarkably quickly and soldering will be a breeze afterwards. If you solder immediately after applying the pencil rubber, the problems are solved for good. So far, we have not observed significant oxidising in joints made using the latest silver/tin based solder, so 'polishing the silver' is unlikely to become a recurrent subject in this magazine.

(060230-11)

Radio Control using

Dieter Perkuhn

Model aircraft these days fly at lightning speed and with their backup systems can cost as much as a small car. If someone else's control system blocks yours, the results can be dearly fatal for both aircraft! A new broadband-based system could prove an ideal solution.



Foto: Weatronic [5]

Until recently it was no exaggeration to describe radio control (R/C) systems for plane, car and ship models as utterly 'stone age', at least from a communications technology point of view. Transmission techniques had not moved forward since amplitude modulation (AM) was generally ditched in favour of frequency modulation (FM), and that was several decades ago. The standards established at that time are largely still in use around the world. Key points of this standardisation include using the frequency bands 27, 35 and 40 MHz for control signal transmission. Across Europe 35 MHz is reserved exclusively for model aircraft control, whereas a multitude of other users have access to the 27 and 40 MHz bands. The frequency bands are divided into channels 10 kHz wide, making this a narrowband modulation system. With no guardbands between individual channels, it is technically simple for signals to bleed over into adjacent channels, requiring signals to be limited to 8 kHz bandwidth if interference is to be avoided. Most of today's R/C receivers use IF filters having a 3-dB bandwidth of around 6 kHz.

The simplest way of generating R/C transmissions is to code the signal using Time Division Multiplex (TDM) technology. To control between 4 (minimum) and 12 (maximum) servo functions, a corresponding number of pulses of variable width are generated sequentially with a repetition rate of around 20 ms, then used to modify the RF carrier using frequency modulation. For this kind of coding the term Pulse Position Modulation (PPM) has been defined. Over the years another system known as Pulse Code Modulation (PCM) has also been implemented and there is no single standard in use. Proprietary (manufacturer-specific) data compression systems reduce compatibility between PCM systems.

Since the signal structure does no more than distinguish between two different amplitude levels, the modulation of the RF carrier boils down to frequency switching between two fixed values. **Figure 1** shows a block diagram of a current model aircraft R/C receiver using double super-het technology. Its architecture conforms to the classic frequency conversion process using a first IF of 10.7 MHz and a second IF of 455 kHz. Signal processing is handled by a microprocessor.

Interference

Unfortunately the interference problem is as old as the remote control hobby itself. Interference in the airwaves is both frequent and destructive, arising from many causes but chiefly through use of the same radio channels by more than one user simultaneously. In severe cases propagation effects can lead to near total signal blocking for a moment or two, although total data loss over any extended period is rare.

Various measures can mitigate the problem of two users occupying the same channel simultaneously. Frequency band scanners built into the transmitters can prevent operation when it is detected that the selected channel is already occupied. This becomes a total solution only when every user's transmitter is equipped in this way, which is seldom the case. The scanner is of no value of course if another user cuts into the channel after the first owner's plane is already in flight.

A higher level of interference protection is achieved by using more than one control channel simultaneously, as in the case of a commercial system that uses one channel each in the 35 and 40 MHz bands at the same time. The possibility of simultaneous interference on both chan-

WLAN ICs

Broadband and DSSS technology for model aircraft

nels is more or less excluded, at the cost nevertheless of increased hardware costs and greater failure risk arising from the higher component count.

A broadband future?

With some model aircraft now using jet propulsion (the heading illustration is a replica of the Albatros L-39 military jet) costing the same as a small car and representing a significant safety risk with air speeds of well over 300 km/h, the desire for fully interference-resistant R/C systems is entirely comprehensible. Unfortunately, regulatory requirements and the need for backwards compatibility are hindering the introduction of any fundamentally new R/C technology. On the other hand practically proven communication techniques have existed for a long time that would adapt to model control extremely well. Examples taken from mobile radio include the DECT, WLAN, Bluetooth and ZigBee standards. In all these applications a multitude of point-to-point or user device-to-user device radio links are operated bi-directionally and simultaneously in the same frequency domain.

The American Paul Beard and his firm Spektrum have developed a radio R/C system for models that exploits modern communication techniques and takes full advantage of cheap, off-the-shelf chipsets [1]. The initial offering, for R/C car models only, was RF modules for three servo functions. This was a far cry from the latest product, a fully airworthy system covering six servo functions with the code number DX6. **Figure 2** shows the transmitter and receiver. The only restriction is that this control system is intended only for so-called parkflyers and micro helis. These craft have a range of 100 metres maximum.

The technology

Spektrum's R/C system operates in the 2.4 GHz ISM (industrial, scientific, medical) frequency band that is available for use without a user licence in most countries. Consequently it is used by a multitude of applications including WLANs, Bluetooth and ZigBee. The effect of these other applications is of minor significance to us, since in the vast majority of cases the physical distance or separation between these indoor users and our outdoor R/C systems will be large enough to cause no difficulty. The generous breadth of spectrum at our disposal, around 83 MHz (from 2.4 to 2.4835 GHz), enables modern digital modulation techniques to be used to their best advantage. Regulatory conditions lay down a spectral power density of 10 mW per MHz of bandwidth, capped at a maximum of 100 mW for the complete band. Depending on the bandwidth of the signal being radiated, transmit powers of between 10 and 100 mW are permissible. A purely theoretical calculation indicates a potential transmission range of over 10 km with 100 mW transmit power, -90 dBm receiver sensitivity and 6 dB antenna gain at transmitter and receiver—or 4 km using 10 mW. In a radio controlled aircraft context several conditions would have to be guaranteed to achieve this kind of range and experience with WLANs and Bluetooth indicates the dis-

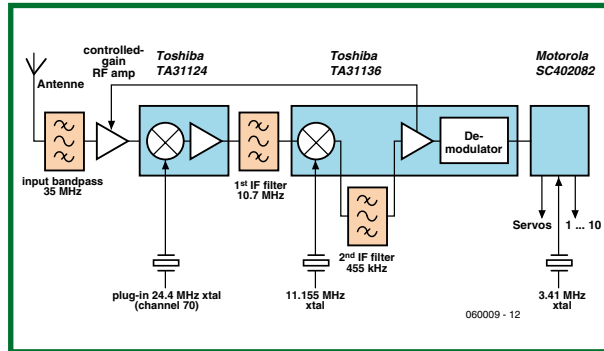


Figure 1. Block diagram of a conventional remote control receiver for model aircraft (Photo: author).



Figure 2. DX6 2.4 GHz model aircraft transmitter with receivers for six servo functions (Source: Graupner [6]).



Figure 3. Transmit RF module and receiver for remote control of model cars (Photo: author).

tances achieved in practice are frequently well below the theoretical values.

To establish what might be realistic results, range tests were carried out using transmit and receive modules made by Spektrum for radio-controlling model cars (**Figure 3**). In these tests the transmitter and receiver were positioned around 1.5 metres off the ground (flat landscape, ground covering damp, transmit and receive antennas in direct line of sight with around 800 m separation). Under these conditions the link was rock-solid, without any interference at all. However, as soon as either transmit or receive antenna were blocked by human bodies the link was lost altogether.

The Spektrum transmit module has an output power of 10 mW and thus conforms to specification ETS 300 328 for GSRDs (General Short Range Devices). By way of comparison, data sheets for commercial WLAN routers indicate they provide radiated power levels of 15 dBm (equivalent to 31.6 mW), as they occupy a greater bandwidth.

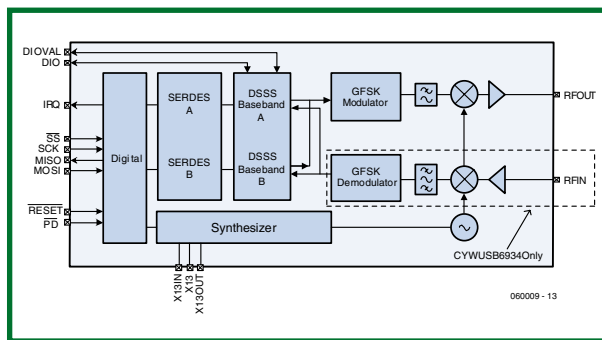


Figure 4.
Simplified block diagram of
the Cypress CYWUSB6934
transceiver
(Source: Cypress).

Chips with everything

At the heart of Spektrum's transmit and receive modules is the CYWUSB6934 transceiver made by the U.S semiconductor producer Cypress Semiconductor Corporation [2]. Receive sensitivity is -90 dBm ($7 \mu\text{V}$ into 50Ω) and transmit output power is 0 dBm (1 mW). Integrated with this is a 13 MHz reference oscillator for the internal frequency synthesiser. The oscillator is voltage-controlled so that it can cover the complete 2.4 -GHz ISM band. Its circuit architecture reveals a single superhet with low IF and integrated IF filter (**Figure 4** gives a simplified block diagram). According to the manufacturer the module is intended for cordless applications in PC mouse, keyboard and joystick applications, for game controllers, remote controllers, barcode scanners and toys. To achieve the output power of at least 10 dBm (10 mW) required for remote control of models, the transmit module uses an SE2526A power amplifier from SiGe Semiconductor [3] to boost the signal. This amplifier module is normally used in WLAN applications built according to IEEE 802.11b and g specifications that provide RF output levels up to 20 dBm (100 mW). The chip has an integrated low-pass filter and an antenna changeover switch that makes separate transmit and receive connections possible. The transmit antenna is well matched and is connected using $50\text{-}\Omega$ coax cable. Whether Spektrum actually limits the output to 10 dBm would need precision measurement to establish but the power is certainly appreciable. The

author's tests were confined to making relative measurements. In this process the transmitter was switched on and off many times at random so as to test occupancy of all possible 79 RF channels in the 2.4 GHz ISM band. The total frequency range covered was determined at around 84 MHz, which squares up well with the permitted bandwidth of 83 MHz. The band occupancy of the signal in use in one of the 79 RF channels was around 830 kHz, corresponding to the channel spacing of 1 MHz.

Construction and layout of transmitter and receiver printed circuit boards are shown in the following pictures. In **Figure 5** the transmit RF board can be seen together with the subminiature co-ax socket for the antenna connection. The track from the connector to power amplifier chip has an impedance close to 50Ω . Near the edge of the board is the 13 -MHz reference oscillator for the transceiver IC. **Figure 6** shows the transmit signal processing board with its microprocessor and clock oscillator, **Figure 7** illustrates the receiver RF board with the transceiver. The simple wire antenna, which is not impedance-matched, is taken direct to the receiver input with filtering. Finally in **Figure 8** we see the signal processing board for the receiver, complete with microprocessor and clock oscillator. With no adjustable filters used in either the transmit module or the receiver, construction is both straightforward and affordable. The VLSI chips used have a unit price of less than five dollars (in quantities of 100 upwards).

Management matters

Organisation of signal generation and processing is handled in both the transmit RF module and the receiver by a Cypress CY8C27443-24PVI microprocessor [2]. The Cypress transceiver is configured so that it operates in one of the 79 possible channels within the 83 MHz wide 2.4 -GHz ISM band. To achieve this, a scanning process is initiated when the device is powered up. This means that the Spektrum transmitter operates bi-directionally; the receiver associated with the transmitter scans the band and gives the go-ahead to the transmitter only when an unoccupied channel is found. To avoid mistakes the transmit/receive management system ensures that the devices do not transmit and receive simultaneously. Test measurements show that the transmit signal is pulsed with an 'on' time of just over 5 ms and 13 ms repetition rate.

The signal used to control the servo functions is not in fact modulated directly onto the RF carrier. Cypress makes use of a digital modulation system by the name of DSSS (Direct Sequence Spread Spectrum) [4]. This is one of two prominent digital modulation techniques, the other being FHSS (Frequency Hopping Spread Spectrum). DSSS is used in WLANs, ZigBee, GPS and UMTS, with FHSS employed by Bluetooth. Both techniques have their roots in the military field. The FHSS technique involves signal-hopping among the 79 channels of the ISM band $1,600$ times a second, following a fixed sequence determined individually between each transmitter and receiver.

Military origins

The remote control system that we are using employs DSSS. In the process the narrowband desired signal is first processed digitally so as to straddle a significantly broader bandwidth and is only then modulated onto the RF carrier. In this way the spectral power density is reduced to a level where the spread-out transmit signal dis-

appears into the general noise background and can no longer be detected using conventional methods (the military connection now becomes clear). The receiver, if provided with the same code, can reverse the spread process using what is called 'processing gain'. The gain here increases as the straddle code ('chipping sequence') becomes extended. Any transmitters using the 'wrong' code will be heard as noise and ignored. It's not all gain, however, and there are nevertheless limits that are set primarily by the limited processing power available. The bitrate change of the chipping sequence used by Spektrum for remote control amounts to 64 chips/bits corresponding to a calculated gain of $10\log_{10}(64) = 18$ dB. Various losses reduce this in practice to perhaps 16 dB. To achieve an acceptable signal-to-noise ratio of circa 10 dB and system losses of around 2 dB for good resistance to potential interference a signal processing gain of more than 30 dB would be required. In a situation like this the power of the interfering signal might be 20 dB stronger than the wanted signal. This, however, would imply a bitrate change or chipping code length of more than 1,000. It's easy to see how the system parameters for really good interference suppression run rapidly out of control. It's worth noting in addition that this process can work only when transmitter and receiver use the same code. With Spektrum's remote control the transmit code is made known to the receiver at the start of operation using the so-called 'binding process' (it's just conceivable that other receivers might be linked in too!).

Finally, here's an interesting thought to consider: for data transmission this new system employs one out of 79 channels each 1 MHz wide and prevents another user of the same system from sharing the same channel. Resilience to interference in the same channel is nevertheless minimal if a more powerful user employing another system appears. The WLAN system on the other hand employs three channels each 22 MHz broad and permits a limited number of devices using the same system within a single channel. And on account of the significantly greater channel bandwidth, WLAN is significantly more resistant to same-channel interference. It is nevertheless accepted that increasing user numbers in a channel reduces the data rate. This selfsame criterion is not acceptable for radio control, however; real-time response takes top priority. This is presumably the reason why Spektrum employs the system described, even though it is less interference-resistant. A further pointer in this direction is the fact that the new DX6 remote control for model aircraft actually occupies two out of the 79 channels simultaneously and the receiver is also built on a twin-channel basis (Figure 2). It would be fascinating to learn how remote control systems of this kind perform when several users are using the same type of equipment concurrently.

(060009-1)

Web links

- [1] www.spektrumrc.com
- [2] www.cypress.com
- [3] www.sige.com
- [4] http://en.wikipedia.org/wiki/Direct-sequence_spread_spectrum
- [5] www.weatronic.com
- [6] www.graupner.de

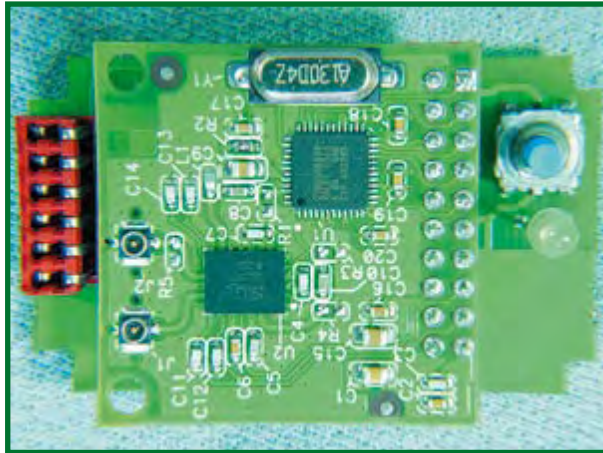


Figure 5. Transmitter RF board with miniature co-ax connector for antenna connection. The circuit track from the connector to the transceiver IC has an impedance close to 50 Ω (Photo: author).

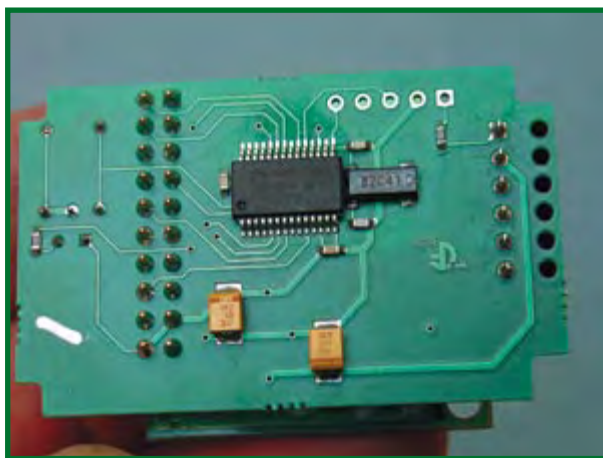


Figure 6. Transmitter signal processing board with microprocessor and clock oscillator.

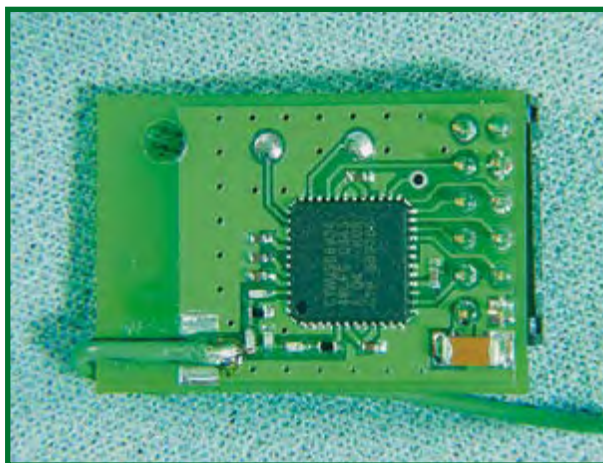


Figure 7. Receiver RF board with transceiver IC. The simple wire antenna, which is not impedance-matched, is connected direct to the receiver input without filtering.


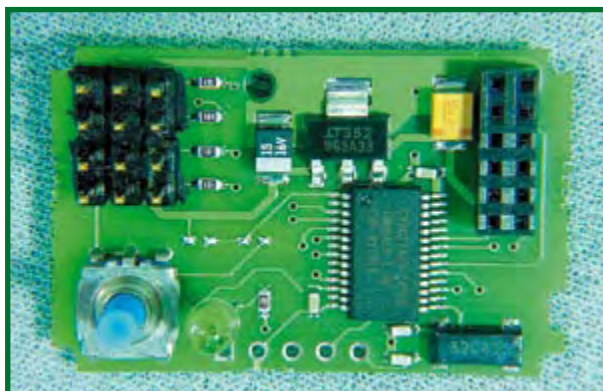


Figure 8. Receive-side signal processing board with microprocessor and clock oscillator.

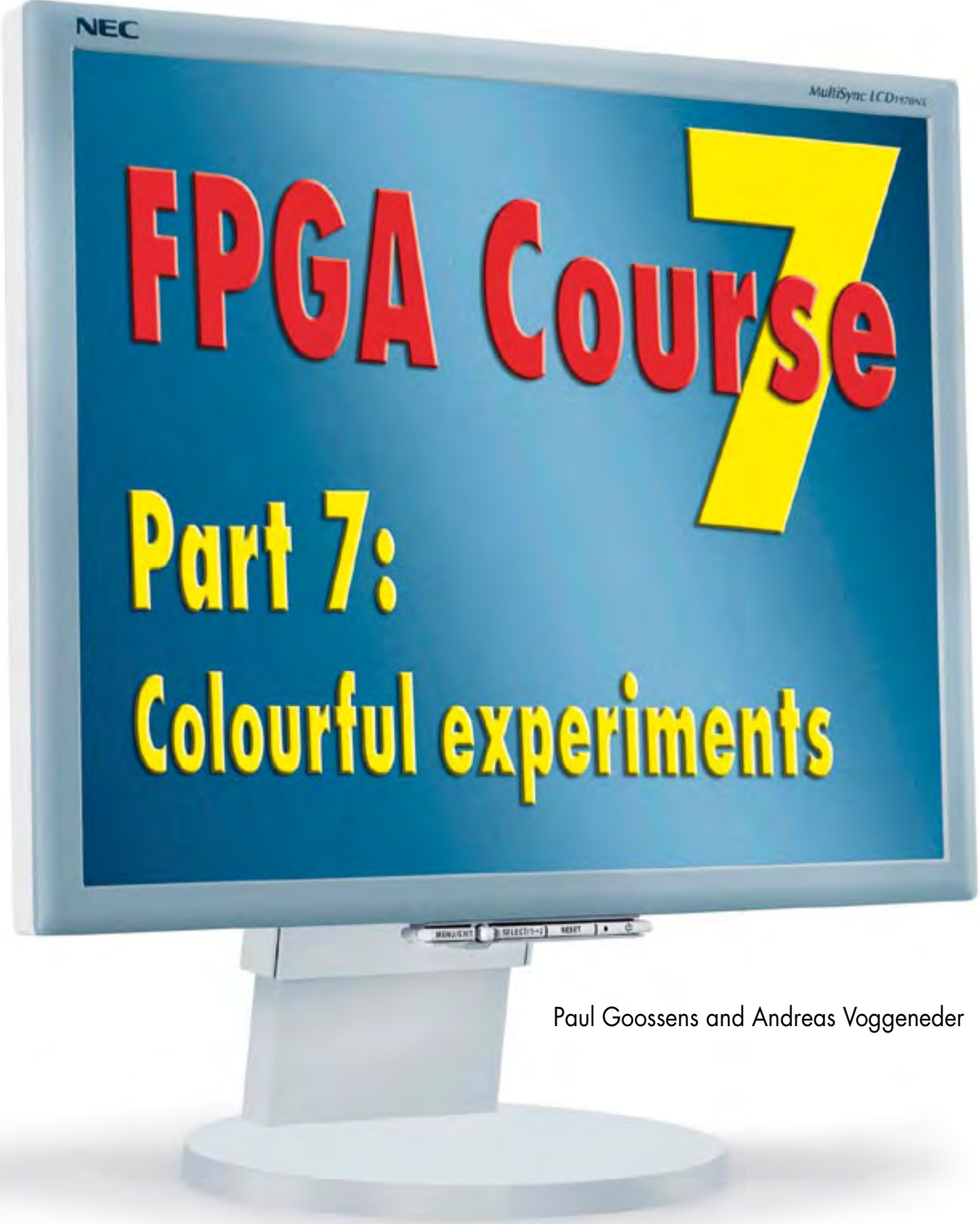

Paul Goossens and Andreas Voggeneder

A picture is worth a thousand words, which is probably why alphanumeric displays have given way to graphic displays in the latest mobile telephones. Although our FPGA prototyping board is not as small as a mobile phone, it can still generate video. That's why it has a VGA port.

As you have probably already guessed, the VGA port can be used to display video imagery on a VGA monitor. We've kept the VGA hardware on the prototyping board quite simple. Three D/A converters are implement-

ed using several resistors. Each converter has a resolution of 3 bits. They generate the red, green and blue (RGB) signals. The horizontal and vertical sync signals come straight from the FPGA.

VGA signals

Naturally, all five VGA signals are generated by the FPGA. Before you delve into the details of the implementation, you need to know how these signals ultimately create a video image.

Here we limit ourselves to generating an image with a resolution of 640×480 pixels and a frame rate of 60 Hz. Every VGA monitor can easily display this standard resolution.

Each frame consists of a number of lines of video information. A typical video line is shown in **Figure 1**. A video line can be decomposed into a certain number of pixel intervals. One image pixel can be generated in each pixel interval by the combined R, G and B signals.

The R, G and B signals must be low during the first 96 pixel intervals. The HSYNC signal is also low during this time. The monitor recognises the start of a new line from this set of signal states.

This is followed by 48 pixel intervals during which HSYNC is high while the colour signals (R, G and B) remain low.

The actual image line starts next. For each pixel interval, the R, G and B signals determine the colour and intensity of the associated pixel. As you might expect, this portion of the line consists of 640 pixel intervals – one for each pixel in a horizontal line. At the end of the line, there are another 16 pixel intervals during which the colour signals are all low. HSYNC remains high during this time. A single video line consists of 800 pixel intervals in total.

It takes another 479 video lines after this one to send all the pixels to the monitor. They are followed by ten video lines that are fully black (RGB = 0). These lines are followed by another two lines (also black) with the VSYNC signal low. This tells the monitor that the next frame is coming. Finally, there are another 33 black video lines with VSYNC high again. The total number of lines in a frame is thus 525.

Example 1

The pixel frequency (dot rate) in this VGA mode is 25.167 MHz. The length of one pixel interval is thus the inverse of this frequency, which is approximately 39.7 ns. For this example, we can round off the frequency to 25 MHz, which is easy to generate from the 50-MHz clock signal already present on the board. This dif-

VGA functions

Various low-level routines that make it easier to use the VGA interface are located in `fpga_lib.c`. The most important routines are:

Init_screen(): initialises the VGA controller

SetCurrentColor (Color):
sets the new foreground colour

SetCurrentBkColor (Color):
sets the new background colour

Gotoxy(x,y): places the cursor at the specified position

WriteScreen(Text): writes text to the screen starting at the current cursor position

Clrscr(): erases the screen

Several constants that can come in handy when you're programming are located in `infpga_lib.h` and `fpga_reg.h`. They include constants for the various colours.

fers from the desired frequency by approximately 0.7%, which is fairly small and lies within tolerance.

Example 19 (ex19) generates a VGA signal that produces a colourful image on the monitor.


The code in file `ex19.vhd` contains a process named `vid`, which generates the `VSYNC` and `HSYNC` signals. This process also keeps track of which column and line of the screen image is 'at bat'. This information is stored in the `Col` and `Line` registers.

`VidEn` indicates whether a pixel is being generated or the R, G and B signals must be set to 0. Note that the `Col` and `Line` signals are only valid when `VidEn` is set to 1.

The `qen` signal divides the 50-MHz clock signal by 2. The rest of this process is very simple. Try to figure out for yourself exactly how it works!

The `fractal` process uses the current coordinates (`Col` and `Line`) to determine the intensities of the red, green and blue signals. The algorithm used here is actually not significant – its only purpose is to generate a particular pattern on the monitor screen.

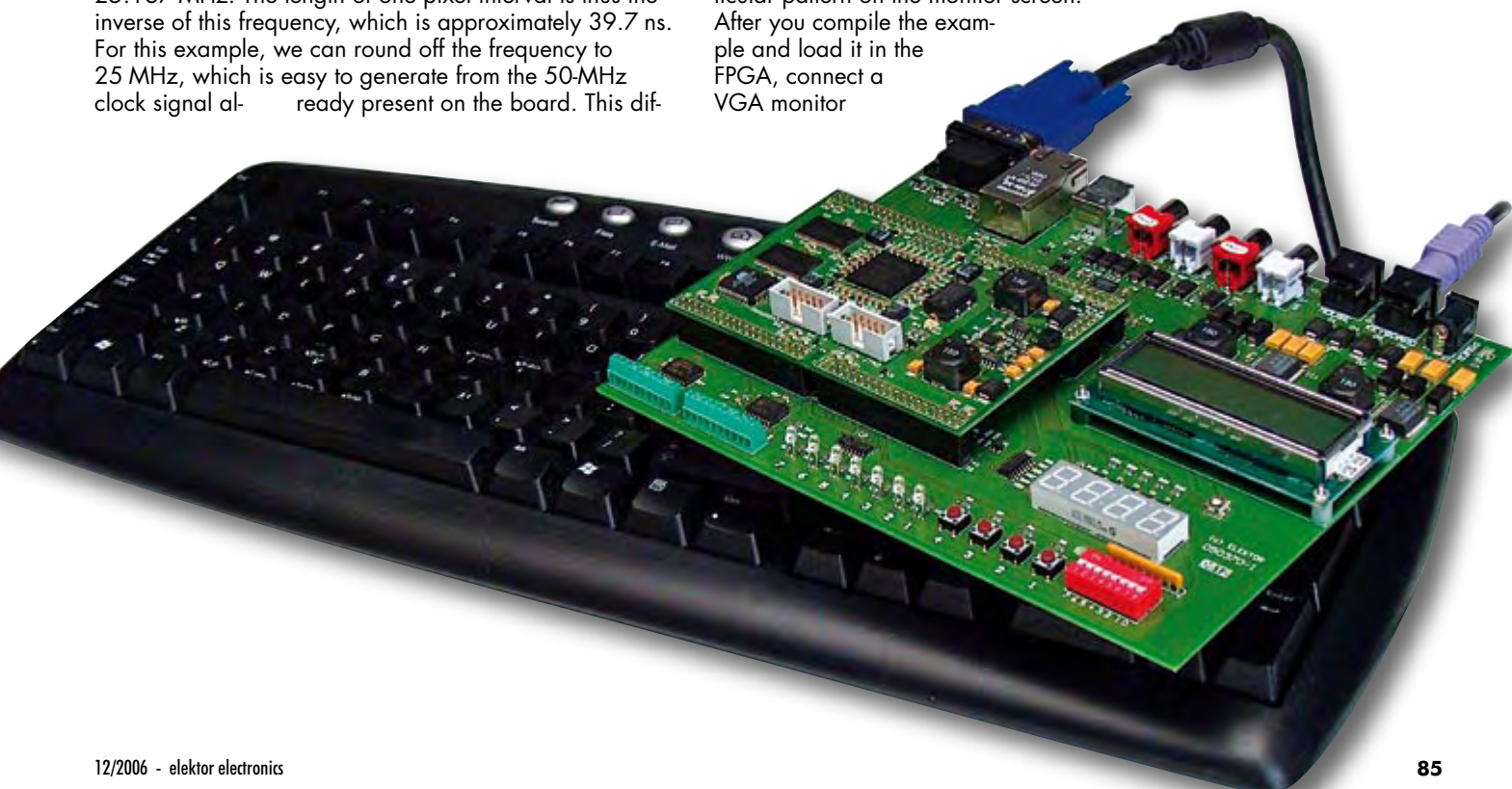After you compile the example and load it in the FPGA, connect a VGA monitor



DIY experiments

Example 19 forms a good basis for some simple DIY experimenting. Be sure to make a copy of the file first so you can restore things to the original situation.

To get you started, try making the following changes:

- Delete lines 147–149
- Replace the graph process with the following code:

```
graph : process (clk, clr)
begin
if clr = '1' then
  Red <="00";
  Blue <="00";
  Green <="00";
elsif (clk'event) and (clk = '1') then
  if qen = '1' then
    if VidEn = '1' then
```

```
if Col(3 downto 0)="1000" then
  Green<="11";
else
  Green<="00";
end if;
else
  Red <= "00";
  Green <= "00";
  Blue <= "00";
end if;
end if;
end process graph;
```

The above modification is quite simple. Now try making your own modification to add a blue horizontal line to the image. (Tip: the Line register keeps track of the currently active line.)

Once you've mastered this, how about generating a dashed line instead?

Timing

Signal timing is very important in digital circuit design. For instance, changes to a design can affect its maximum operating frequency.

Registers (flip-flops) are often used in digital designs. They impose timing requirements on the associated signals to ensure that they work properly. The most commonly used timing parameters are:

Tsu (setup): specifies how long the data must be valid at the input of the flip-flop before the clock pulse arrives

Tco (clock to output): indicates how long it takes for the data on the input to appear at the output after the clock pulse arrives

Th (hold): specifies how long the data on the input must remain unchanged after the clock pulse arrives

An operation of some sort (such as AND, OR or even addition) usually occurs between the output of one flip-flop and the input of the next one. These combinational circuits also have delays between their inputs and the outputs. The interconnects inside the FPGA also cause delays.

These delays and requirements have certain tolerance ranges. For example, a flip-flop with a specified Tco of 2 ns may be able to work even faster in practice. The longest possible time is called the 'worst-case time', and the best possible time is called the 'best-case time'.

After Quartus compiles a design, it analyses the timing of the design. This yields a figure for the maximum operating frequency of the design. To arrive at this result, the program calculates the maximum delay between the clock pulse and when the signal arrives at the flip-flop data input for each signal line. This delay is often called the 'arrival time'. The Tsu of the flip-flop concerned is included in this delay. Worst-case times are used for this calculation.

The longest delay determines how quickly successive clock pulses can follow each other. If you set a desired minimal clock rate in Quartus (refer to Quartus Help), it can determine whether the design meets your requirement.

Quartus also analyses the Th requirement of the flip-flops. Here again it calculates the delay between the clock pulse and when the data signal arrives at each flip-flop. The best-case times are used for this second analysis. They must always be greater than the Th requirement of the flip-flop concerned.

You can view the results of the timing analysis in Quartus in the Compilation Report. This report includes a section named 'Timing Analyzer', which provides detailed information about the timing of your design. The term 'slack' appears frequently in this report. Slack designates the difference between the calculated delay and the desired delay based on your desired clock frequency. A positive slack for Tsu indicates that the signal arrives at the data input of a flip-flop earlier than the required time (by the amount of the slack value). In the case of Th, the slack indicates how much longer the signal remains unchanged than the required (minimum) time. Positive slack is good news, and negative slack is bad news.

If your design is too slow, you have two options. The first option is to see whether Quartus can help you compile the design better. To do this, select 'Timing Optimization Advisor' under Advisors in the Tools menu. It will help you configure the Quartus compiler to produce a better result.

The second option is to examine the timing report to see which signals are slowing things down. Once you know this, you can try to modify your design to make these signals somewhat faster. You might find that using a different algorithm helps.

There are also techniques that can be used to adapt a design to a higher clock frequency, but that's a different subject!

to connector K9 on the prototyping board. If everything went right, you will be treated to a pretty design on the monitor.

Dynamic

Conjuring up a nice figure like this on your monitor is a lot of fun, but you'll get tired of looking at it after while. It would be better (and more useful) to be able to display information on the screen. If you combine this with a bit of intelligence, you might just have something.

This is the purpose of **Example 20** (ex20). Here the trusty T51 microcontroller has been extended to include the PS/2 interface described in the last instalment and a VGA interface. The VGA interface is linked to the microcontroller via the XRAM bus. From the perspective of the microcontroller, this interface is simply a block of memory starting at address 0x8000 and a set of eight memory locations starting at address 0xAA00.

As you can see from the size of the *Graffikkarte.a.vhd* file, this is a fairly sizeable design. For this reason, we don't intend to describe it in detail here. Based on what you've already learned from the previous instalments, you should be able to figure it out on your own.

However, it is good idea to say something about how the interface is driven by the software.

Driver

Thanks to the C files provided with the course, the driver routine that runs in the microcontroller is fairly simple. The first thing *ex20.c* does is to call *Initscreen()*. This causes the VGA controller to be configured properly so it is ready to be used.

Next, *SetCurrentColor* and *SetCurrentBkColor* set the image colours. Each character can be displayed in a different colour. These functions only change the colour that is used when the data is written to the screen.

Next, *Gotoxy(28, 1)* positions the (invisible) cursor to coordinates (28, 1).

Writescreen("text") places the first text on the screen.

Here the colour is determined by the previous *SetCurrentColor* and *SetCurrentBkColor* functions.

Finally, the *putchar2()* function displays individual characters on the screen. This function also uses the previous colour information.

Use

A welcome message will appear on the monitor after you configure the FPGA and connect a PS/2 keyboard. You can then use the keyboard to type in text, which will appear immediately on the monitor. You can use the function keys (F1 to F4) to change the colour of the text.

As an exercise to familiarise yourself with the VGA interface, you can experiment with modifying the software. For instance, try integrating the I²C interface described in one of the previous instalments so the output of the A/D converter can be displayed on the monitor. Another idea would be to display the scan codes received on the PS/2 interface instead of the decoded characters. If you can't get that to work, you can always ask other readers of *Elektor Electronics* for help via the Forum on our website.

Let's have fun!

After all this hard work, it's time for a bit of relaxation. As a special treat, we've developed a fun application for

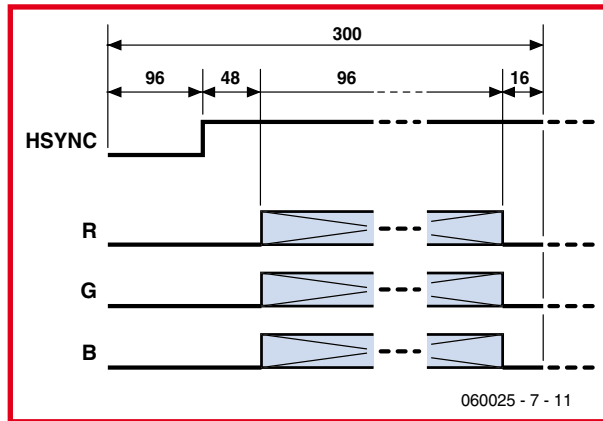


Figure 1. Structure of a video line.

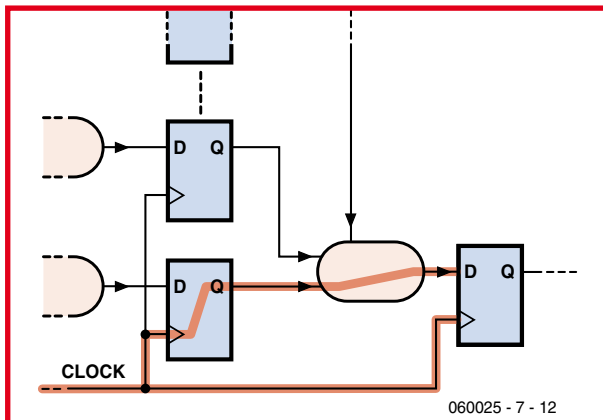


Figure 2. Signal flow for a timing analysis.

you. The hardware is exactly the same as for the previous example (ex20). The only difference is in the software, which has been modified 'slightly'. **Example 21** (ex21) implements the familiar 'four in a row' game, but this time entirely in the FPGA.

This example also shows how you can define your own characters – that is, if you can tear yourself away from the game long enough to have a look at the source code.

(060025-7)

Join the FPGA Course with the Elektor FPGA Package!


The basis of this course is an FPGA Module powered by an Altera Cyclone FPGA chip, installed on an FPGA Prototyping Board equipped with a wealth of I/O and two displays (see the March 2006 issue).

Both boards are available ready-populated and tested. Together they form a solid basis for you to try out the examples presented as part of the course and so build personal expertise and know-how in the field of FPGAs.

Further information may be found on the shop/kits & modules pages at www.elektor.com

A New Flowcode

Putting Flowcode 3 through its paces

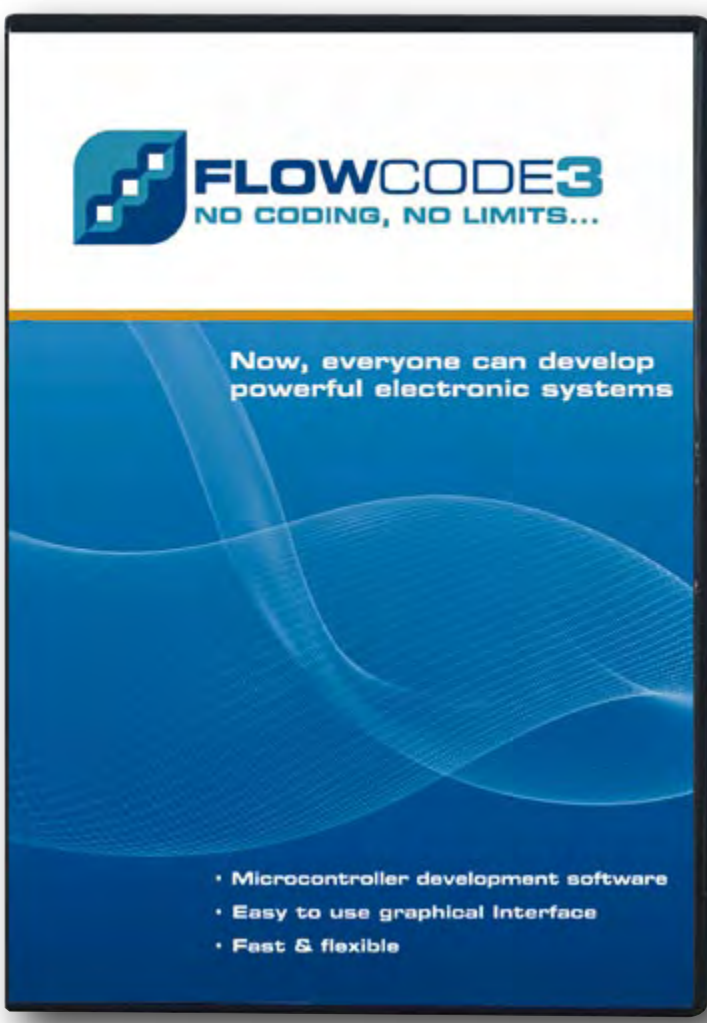

Jan Buiting

A new version of Flowcode for E-blocks has just been released — version 3. This is more than a simple upgrade: Flowcode has matured into a nice if not impressive development tool.

Many of our readers are now quite familiar with Flowcode, the software brains behind all E-blocks projects, with some having actually bought the product. A number of E-blocks tutorials, reports and application examples were published earlier this year.

Originally, Flowcode was designed to help College students develop electronic projects based on the popular PIC microcontroller. As time has passed, more and more features have been added to Flowcode, and the latest version 3 has actually turned out to be quite a nice development tool not just for the programmers starting out but also for professional engineers.

In this respect, my own position is that I have been an electronics enthusiast for 30-odd years and have occasionally worked with microcontrollers, specifically the CDP1802 (see *Retronics* in the October 2006 issue). Fortunately, thanks to contributing authors and colleagues in the Elektor lab I have never been out of touch with microcontrollers and related stuff like (E)PROMs and Flash devices. Although I can read PIC, 8051 and AVR assembly code and the odd piece of C and Visual Basic, I must admit that I am not *au fait* with the latest in microcontroller land when it comes to programming. So, when the new

Flowcode landed on my desk I thought I would see for myself whether it lived up to my expectation: microcontroller programming should be *easier* than 20 years ago.

On the desk and on the PC

To undertake the review I got hold of the 30-day demo copy of Flowcode 3, which is available as a free download from our website. At the time of writing I got Beta 5 — the final version will be on our website. I also got out a set of E-blocks modules comprising a PICmicro Multiprogrammer board, an LED board, a Switch board and an LCD board. The lot was connected up as shown in

Figure 1.

My colleagues in the lab having estimated my proficiency (“zero”) and general chances of success (“we’ll see”), gave me an 18-pin PIC16F88 device (worth £2.75) to insert in the Multiprogrammer. Somehow I surmised that this must be a low-end device but having looked up the datasheet on the Microchip website I discovered the device has 7 kB ROM, 368 bytes of RAM, seven 10-bit A to D channels, timers, a USART communication port and a host of other things I had never heard of (BOR? LVD?).

for E-blocks

Looks like things have moved on a little since I last used a microprocessor! I was happy with my 'low-end' 'F88 chip because its simple architecture would prevent me from attempting the impossible (yet).

Having installed Flowcode 3 and the associated PPP driver (which was a breeze) I thought I would see if I was in control of the hardware and software setup by getting a single LED to flash. I know the example is corny, but you have to walk before you run — writing that I²C bus driver or 8-level DMA demultiplexer will come later!

The sequence

Right. In Flowcode I started a new flowchart, dragged an Output icon onto the chart and clicked on it to get the properties up. I set bit 1 of PIC port A to go On and pressed the 'PLAY' button. The software simulated the 'program' and pin A0 on the PIC graphic faithfully went red to indicate a logic 1 had been placed on port A bit 0. After a little trial and error I very quickly had a program that flashed A0 on and off on the screen. No time wasted on editing assembly code, re-assembling the code, burning a new EPROM, stirring the coffee and finally relaunching the application, fingers crossed and praying for success. That was 20 years ago.

I learned a few things here: you need to slow Flowcode's simulator down so you can see what is going on in your program. Correspondingly I deduced you need to put delays in the program otherwise what I had hoped to be a slowly flashing light will just look like a slightly dim LED. You can see my first program in **Figure 2**. Not bad for 10 minutes work.

Flushed with success I then decided it was time to see this in action on a real PICmicro device. Simulation is great but I am only convinced by real-life electronics. To download a program to a microcontroller, in my case the lowly 16F88, you simply click on the small chip icon on the menu and off it goes.

Off it went — but nothing happened on my hardware. Time to read the Help file and the Getting Started guide, both of which can only be described as crisply produced, easy-going yet comprehensive documents with great educational value. Having gone through this I concluded that I needed to load the CHIP...CONFIGURE screen to set up the parameters for the real-life PIC: set the clock oscillator for a Crystal, turn off the watchdog timer, Brown Out Detection and Disable Low Voltage Programming. These settings, by the way, are now the number-1 problem experienced by readers having built an Elektor project based on a PIC, having burned their own PIC device and finding that it doesn't work. Check those PIC config words!

Then I pressed the Download to Chip icon again and I had my first program running on the real-life PIC. I looked at my watch — I started 30 minutes ago. For a relative newcomer who occasionally still gets nightmares in assembly code I did not think that was too bad.

Learning curve

Having read the Help file I discovered that Flowcode 3 is shipped with around 30 example files that demonstrate

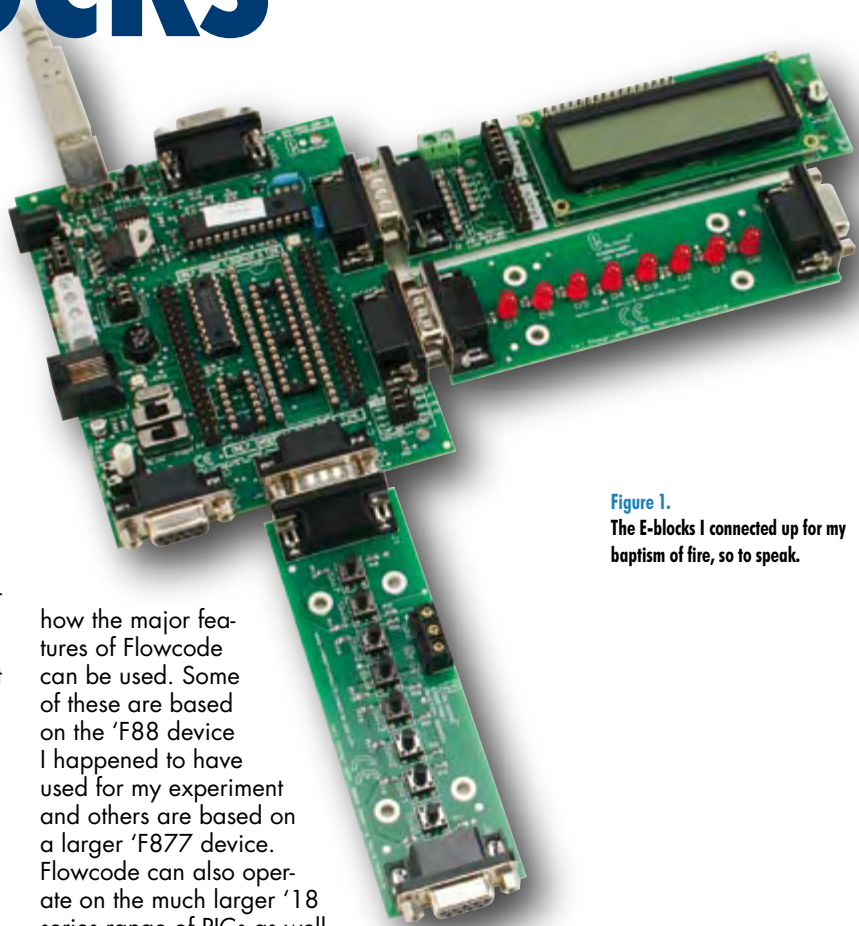


Figure 1. The E-blocks I connected up for my baptism of fire, so to speak.

how the major features of Flowcode can be used. Some of these are based on the 'F88 device I happened to have used for my experiment and others are based on a larger 'F877 device. Flowcode can also operate on the much larger '18 series range of PICs as well as the smaller '12 series. I then spent the next hour or so looking through the example files for the 'F88, downloading a number of them to my hardware and launching the applications.

Many only require the use of simple LEDs, switches and LEDs, but some call for more advanced components

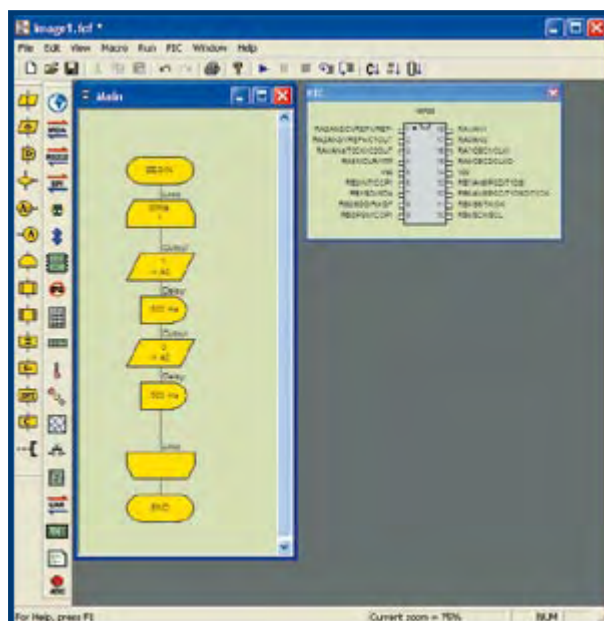


Figure 2. My first program.

What's new & better in Flowcode Version 3

Graphical User Interface improvements

- Zoom: Multiple zoom levels, zoom to fit
- Tiling: horizontal tile, vertical tile
- Smaller PICmicro MCU on-screen device
- Screen icons: new graphics, description now inside icons, better comments, more icons per screen viewable
- Screen appearance: user selected icon shading, and background colour
- Hardware and software macros now have separate icon graphics now known as: 'macro' and 'hardware macro'
- New: Print Preview and print to screen zoom setting
- Flowcharts can be exported to JPEG or BMP for incorporation into documents
- Tile horizontal and vertical and auto-arrange for multiple macro viewing

Improvements for migration to C

- All icons have bubble help to display icon function
- Icons can also produce equivalent C code of each icon as bubbles
- Students can view the C code equivalent of the whole program
- Students can view the Assembly code equivalent of the whole program
- Screen layout is preserved on save to allow educators to build more relevant examples
- Tutorial file descriptions now included
- Tutorial files exploit features such as labelled components to add context

Multilingual support

- Main program and Help file: English, French, Dutch, Finnish, German, Spanish
- Main program but not Help file: Chinese, Italian, Greek

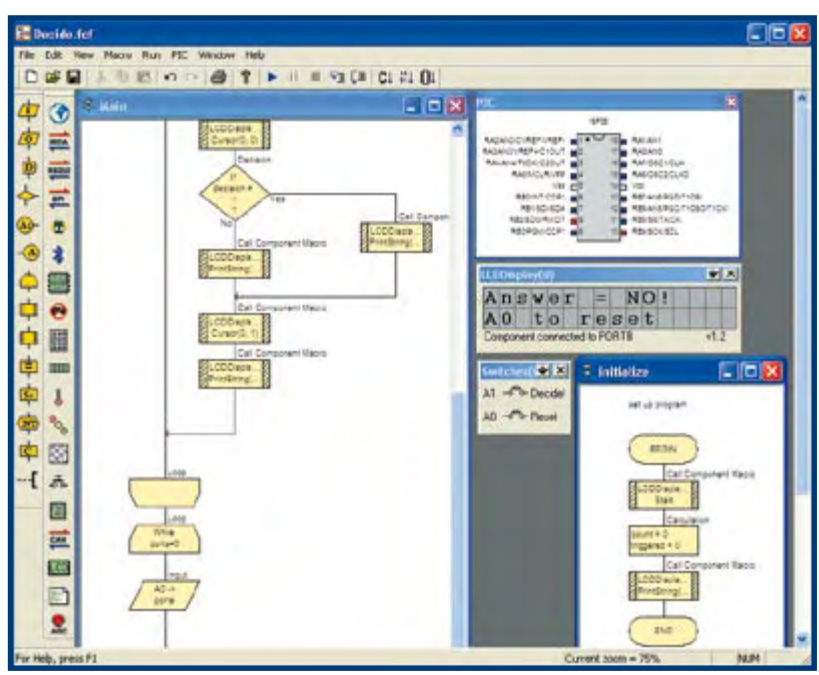


Figure 3. My final Decision Maker program.

(i.e. E-blocks) like keypads and sensors. When you look through these examples, Flowcode's two main strengths become clear. Firstly, it is a very good way for those that are not front line programmers, like myself, to understand how programs work and can be created in a short time. This in turn means that the learning curve for Flowcode itself is actually very steep. Secondly, it is not a toy. Whilst it is great for those starting out to program, it is also quite powerful, with fully supported interrupts and a range of communication protocols like SPI, RS232, CAN, Bluetooth and even TCP/IP supported — all of which I will grind my teeth on — in due course!

Earlier in this series

- *Electronic Building Blocks*, November 2005.
- *E-blocks and Flowcode*, December 2005.
- *E-blocks in Cyberspace*, January 2006.
- *E-blocks – now you CAN*, February 2006.
- *E-blocks Making Waves*, March 2006.
- *E-blocks Making Waves at C*, April 2006.

From 2 to 3

Those of you who are currently using Flowcode version 2 will want to know what improvements have been made to version 3. I have no experience of version 2 but looking in the Help file it states that major improvements have been made to the graphical user interface, there are new features to help learners, lots of functionality improvements such as 16-bit numbers, support for strings, better interrupt handling, improved macros, more components, and so on. A full list is given in the **inset**.

Flowcode flips the coin

So, having trained myself up it was time to get down to developing an application that, although serious in intention, is the tongue-in-cheek equivalent of flipping a coin: a PIC-assisted Yes/No decision maker. Some people, mostly managers, attribute great authority and powers of decision to PCs and microcontrollers, arguing that they are 100% digital hence have no 'grey areas' or room for 'discussion'. What I need to confirm these people in their beliefs (as well as making them forget the simple coin in their wallet) is a program where they could press a button and get a 'YES' or 'NO' decision to display on the LCD. So I set about making it — as an exercise, of course. You can see the final program in **Figure 3**. It took me about an hour in the end. I have put up the file 'Decide.

Software functionality improvements

- Better range of simulation speeds to check working program before downloading it to the PICmicro microcontroller
- Alter variables whilst simulation is paused
- Support for 16-bit numbers and arithmetic, choice of types includes CHAR, INT and STRING
- Support for hexadecimal and binary numbers in all dialogue boxes
- Full support for strings including string manipulation commands like ADD, LEFT, RIGHT
- Variables are now case sensitive
- New string process icon supports string manipulation
- Interrupt icon supports a larger range of interrupts as well as custom interrupt definition. Each interrupts run a macro of your choice.
- Improved Delay icon with a much greater range of delays
- While icon can operate for a defined number of times
- Subroutines can now have parameters passed to them, and returned
- Larger range of supported devices now includes 18 series PICmicro microcontrollers (technical specification for full list).

- Undo and Redo commands
- Improved C compiler

Component improvements

- LCD: range supported now includes 40-character 2-line; 20-character 4-line etc.
- Full LCD functions now supported with scroll and other features.
- Switches can now be labelled, options for display vertical and horizontal, left to right or right to left.
- LEDs can now be labelled, options for display vertical and horizontal, left to right or right to left.
- New PWM (Pulse Width modulation) component for motor control.
- Analogue components available now include thermometer, dial, or slider
- Target communications components now include RS232, I2C, Internet web server, Internet TCP/IP, Bluetooth, CAN bus and LIN bus

E-blocks for Prototyping, May 2006.

E-blocks and X-10, June 2006.

E-blocks Easy ARM Pack, September 2006.

Articles may be downloaded individually from www.elektor.com.

An overview of available E-blocks and software is available on the [SHOP](http://www.elektor.com) pages at www.elektor.com

fcf' for free downloading with this article — the file number is **065096-11.zip**.

Unfortunately Flowcode does not have a random number generator so I created a simple counter and then used the MOD feature in a calculation icon to detect whether the count was odd or even. This outcome was used to answer Yes or No to whatever weighty decision the user had in mind.

What impressed me is just how easy this was. The LCD was very easy to incorporate in the program and it really adds a lot of functionality to an electronic system.

The hardest part of the job was deciding how I was going to structure the program itself in terms of the logical flow and the variables I needed to track the status of the program. Once I had done this on paper, transferring it to Flowcode was quite painless. The thing that most impressed me was that once I had got the program working using Flowcode's simulation mode, when I transferred it to the hardware (this time having loaded the PIC config bits!) it worked just like the simulation did.

Conclusion

To a newcomer, Flowcode 3 'does what it says on the tin'. It was easy to get started and make a program, was intuitive to use, and produced code that worked. There are a few minor disappointments such as the lack of a random number generator, which I happened to stum-

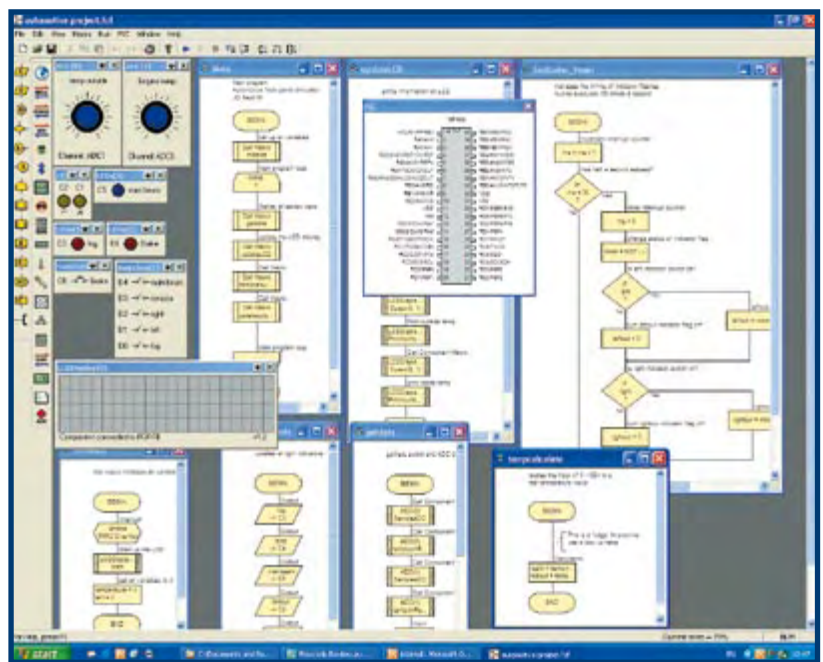


Figure 4. An example of a more advanced Flowcode program.

ble on for the *Decision Maker* program, and the fact that floating-point numbers are not supported as variables. It does however seem to have more features and capabilities than you could shake a stick at. I was also struck by the thought that it was more fun than the day job. Then I realized that this was my day job!

(065096-1)

A full featured but 30-day limited demo version of Flowcode 3 can be downloaded free of charge from www.elektor.com.

Follow: magazine → volumes → 2006 → december → A New Flowcode for E-blocks

Intelligent Voltmeter

Miniature 3-channel A/D converter

Jeroen Domburg & Thijs Beckers

This month we'll make use of the ATtiny13 again. This versatile microcontroller is used here in a practical, compact voltmeter with an RS232 link for use 'on the road'.

In this article we show you how to build a small device that wouldn't be out of place in the laptop case of an electronics fanatic. It is a three-channel A/D converter/voltmeter, connected via the serial port. Whether you want to measure transistor characteristics, battery discharge characteristics or just measure the voltage at a few points, this circuit can help you out as long as the voltages are between 0 and 5 V.

Description

One of the most important design criteria of this circuit is the amount of space it takes up. To keep this as small as possible we have left out as many components as we could. The final design consists of just five components, which were coaxed into a DB9 plug (see photos). The circuit uses RS232 for connecting to a PC, although the voltages don't fully comply with the standards, as this saves on the number of components required. There is one section that is conspicuous by its absence: the power supply. This is in fact drawn from the serial port.

The circuit diagram shows how simple this circuit is. The supply section consists of D1, IC1 and C1. When the serial port is in a ready state, the voltage on the DTR line is usually somewhere between 8 to 12 V. The circuit gratefully makes use of this. The 78L05 and the electrolytic capacitor ensure that IC2 is supplied with a stable 5 V. D1

protects the circuit from damage if the DTR line is somehow in the wrong state and outputs a negative voltage. At the heart of the circuit is an Atmel ATtiny13. This IC has the all-important 10-bit A/D converter and 1.1 V reference voltage integrated on the chip. The ATtiny13 is available in a DIP package as well as an SMD package. If there is a need for it, it's therefore possible to construct an even tinier version.

Interface

There is no UART present inside the chip, so we had to implement this in software. For this reason there is also no need to use a MAX232 or similar to invert the signals or convert them into 12 V. The latter has been done in the cheapest way possible: we've left it out altogether. The RS232 signal generated by the microcontroller is connected directly to the Rx/D line of the PC. Although this isn't according to the official specifications, in practice it seems to work most of the time.

To convert the ±12 V of the Tx/D line from the PC into a TTL level for the microcontroller we use a single 10 k resistor (R1). The internal ESD diodes of the GPIO pin of the microcontroller short signals above 5 V and below 0 V to the supply lines. R1 limits the current to a safe level. The UART is, as mentioned earlier, emulated inside the microcontroller. A UART normally requires a stable clock to



You only need five electronic parts, one DB9 connector & cover and some cable to build this project.



In this case a PCB would take up valuable space. Besides, it's much more fun to construct it like this.

r in a Plug

operate, such as a crystal. This component is also missing from the circuit. Here we're using the internal RC oscillator of the ATtiny13 as the clock, which is not very accurate. To obtain a stable timing signal we make use of the bit-clock of the serial signal from the PC. The first character received from the PC is analysed and the result is used to generate the bit-clock for the UART.

Apart from the routines for the UART and the A/D converter, there is also a bit of software that implements an auto-ranging function. If required, the software can automatically switch the reference voltage for individual channels between the built-in 1.1 V and the 5 V supply voltage. Because the 5 V supply is a lot less stable than the 1.1 V reference voltage, it is possible to turn off this feature.

In use

Because the circuit uses a microcontroller and RS232 signals, it is fairly straightforward to control. When it is connected to a serial port you can use a terminal emulation program such as Hyperterm (Windows) or Minicom (Linux). The serial port settings are: 1200 baud, no parity, 8 data bits and 1 stop bit. Pressing 'enter' will display the initial menu. From the menu you can adjust several settings. Choosing 'run' will make the measured samples of the three channels scroll down the display. These can be looked at straight away, or they can be stored in a file by the terminal program, so that they can be analysed at a later date, using Excel for example.

On the other hand...


An 'instrument' with so few components also has some disadvantages. The inputs, for example, are not galvanically isolated from the serial port. Keep this in mind when you take measurements from devices connected to the same PC or even the same mains ring.

The circuit is also fairly easily affected by the voltage levels on the serial port. If the voltage on the DTR line drops below 6 V, or the RxD line doesn't accept a signal of only 5 V you'll find that the circuit won't function reliably. The source code may be freely downloaded from the

About the author

Jeroen Domburg is a student at the Saxion Technical University in Enschede, the Netherlands. Jeroen is an enthusiastic hobbyist, with interests in microcontrollers, electronics and computers.

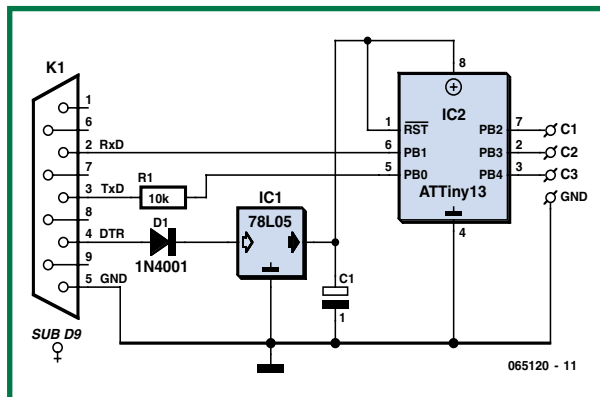In this column he displays his personal handiwork, modifications and other interesting circuits, which do not necessarily have to be useful. In most cases they are not likely to win a beauty contest and safety is generally taken with a grain of salt. But that doesn't concern the author at all. As long as the circuit does what it was intended for then all is well. You have been warned!



websites of the author [1] or *Elektor Electronics* [2]. You are therefore free to modify the software if you wish to change or add some extra functions.

(065120)


Web links:

- [1] <http://sprite.student.utwente.nl/~jeroen/projects/serad>
- [2] www.elektor.com




And this is the end result.

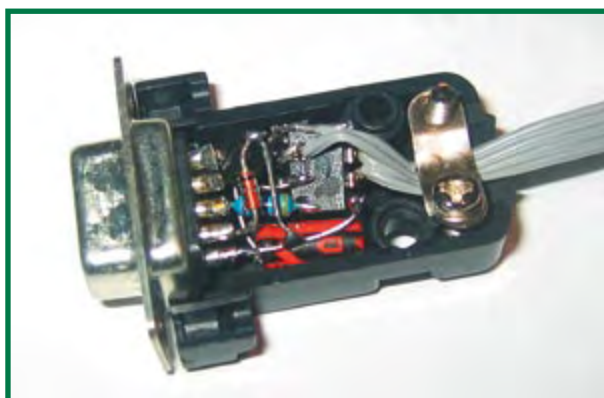Nobody would guess that this contains a three-channel voltmeter.



It's a perfect fit.

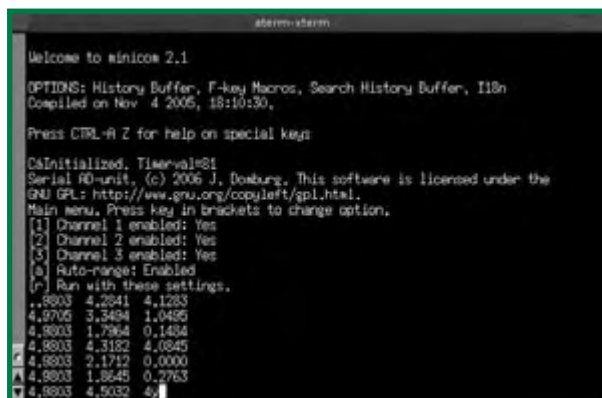This way we don't need to buy a special enclosure either.



And this is what the computer display looks like. The three columns can also be logged, for analysis at a later date.


A Wire with Total Recall

Exploring the properties of 'memory wire'

Burkhard Kainka

Memory metal is often thought of as 'a solution looking for a problem'. It's an intriguing material; warming it makes it return to its original shape. The application described here is academic in that it doesn't provide a solution to any great problem but instead produces a novel visual effect.

This design should provide some relief for those of you who are irritated by the sight of continually blinking LEDs. This circuit grabs attention by swaying an LED gently back and forth like a tree bending in the wind. The movement could have easily been produced by a servo or electric motor but memory wire has the advantage of moving silently. This type of wire is also known as Nitinol, indicating that it is an alloy of nickel and titanium. The wire can be deformed into any shape which is retained until heat is applied then it returns to its original shape. The original shape is 'programmed' into the wire by heating it to a much higher temperature. A bent wire returns to its original straight shape or a straight wire returns to its original pattern. This looks particularly bizarre if the original shape is something like a paper clip; straighten it out then apply a little heat and watch it fold back up into a paper clip!

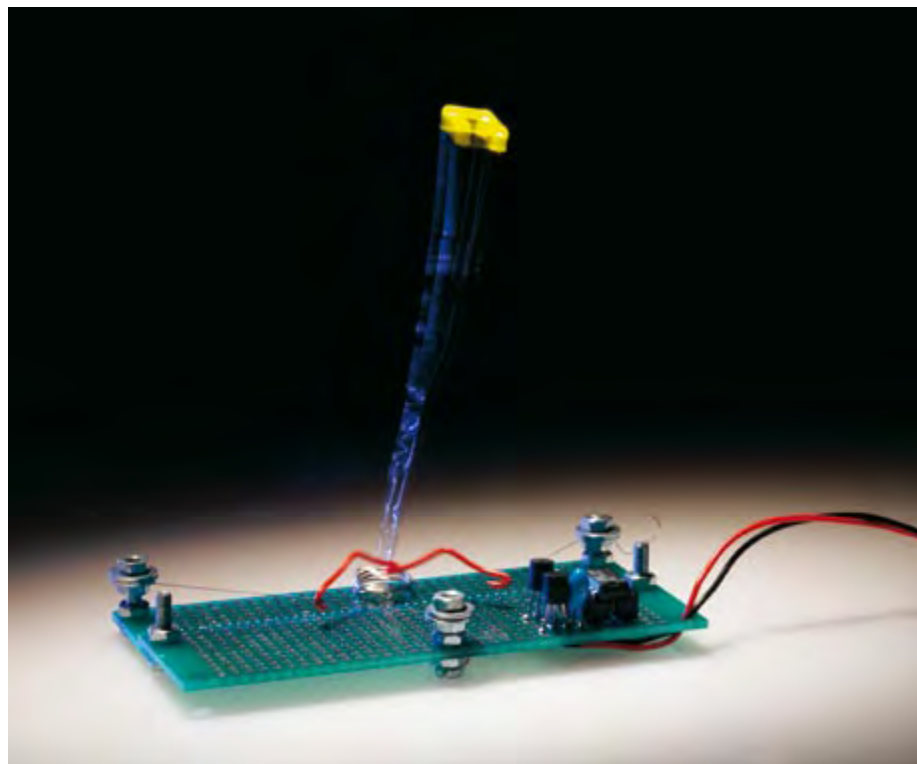

Memory wire can also be used to provide mechanical propulsion; in this setup the wire is fixed between two points and then deformed by tensioning the wire. When heat is applied it shrinks back to its original length producing a pulling force between the two points. The wire is available in different diameters and from a number of suppliers [2] [3] [4].

The Mechanics

This design repeatedly swings the LED along a trapezoidal shaped path. The motive force is provided by a 15 cm length of 0.15 mm diameter memory wire. It is necessary to put the wire under sufficient tension so that when heat is applied it shrinks by 4 to 5 % back to its original length. Heating is achieved by passing a current of around 300 mA through the wire.

The wire is fixed at either end and in the middle forming an angle of 90

degrees. The shortening and lengthening of these small lengths of wire is barely perceptible so the movement is magnified by the mechanical leverage produced in the LED fixture (see **Figure 1**). Two lengths of insulated wire with hooked ends provide tension to the memory wire from a 1 cm diameter spring made up of four turns of 0.5 mm copper wire mounted on the circuit board. A small steel spring could be substituted to provide the tension.

Each time current passes through one section of the memory wire it contracts and pulls the hook which makes the LED sway. A 10 cm long lever produces around 1 to 2 cm of movement in the LED which can be further increased by lengthening the lever. The complete mechanical structure and electronics are contained on the prototyping board. **Figure 2** is a side view of the assembly and shows the memory wire particularly well.

Figure 1.

The memory wire is clamped at three points and tensioned from a spring via two hooked wires. The LED is fitted to the top of the spring.

Electronic control

The memory wire used in this application is called Flex-150 [2]; it has a resistance of 50 ohms/m and can carry a maximum of 400 mA. Each 7.5 cm length of wire has a resistance of almost 4 Ohm and should be used with a voltage supply of less than 1.6 V. A single 1.5 V battery or 1.2 V rechargeable battery can be used for test purposes. A microcontroller is used to switch current through the wires so that the LED repeatedly moves along a two-axis path defined by values stored in the software (Figure 3).

The switching waveforms have a relatively small 'on to off' ratio so it is possible to switch current through the memory wire directly from the 4 to 6 V supply (four NiMH cells would be a suitable power source). The BC337 transistors can handle up to 1 A and the PWM switching waveforms are arranged so that there is never more than one transistor conducting at any one time. The program causes the LED to sway between four positions.

Source code for the Tiny11 program can be downloaded free of charge from the *Elektor Electronics* website [5]. You can also access additional memory wire information along with some suggestions for further experimentation.

(060144)

Web links

- [1] www.stiquito.com
- [2] www.mikromodellbau.de
- [3] www.robotstore.com
- [4] www.memory-metalle.de
- [5] www.elektor.com (month of publication)

Figure 3.

Current through the wires is switched by a microcontroller, this ensures consistent, repeatable LED movement.


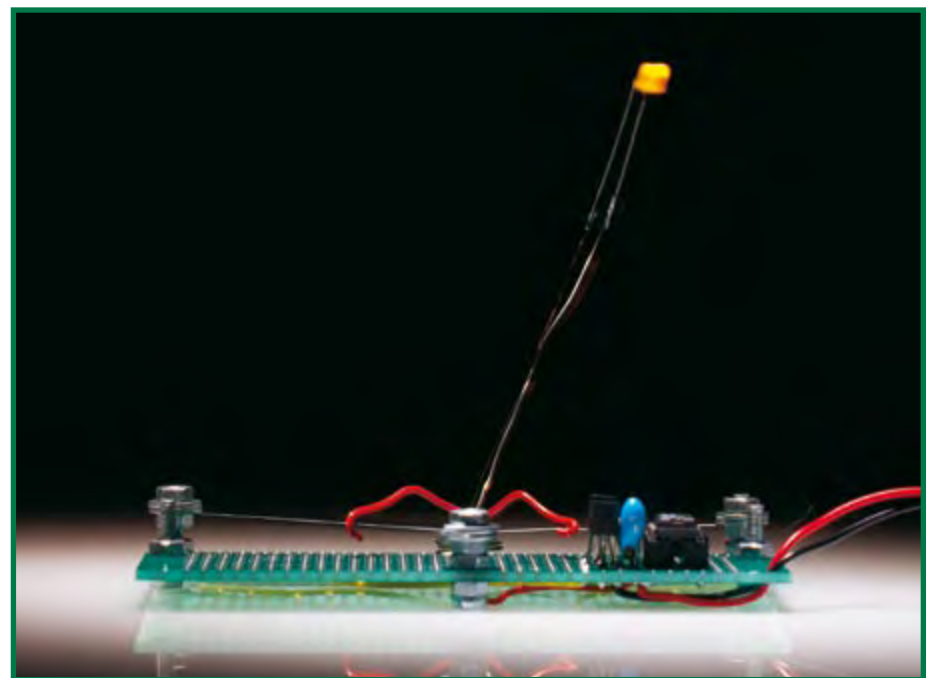
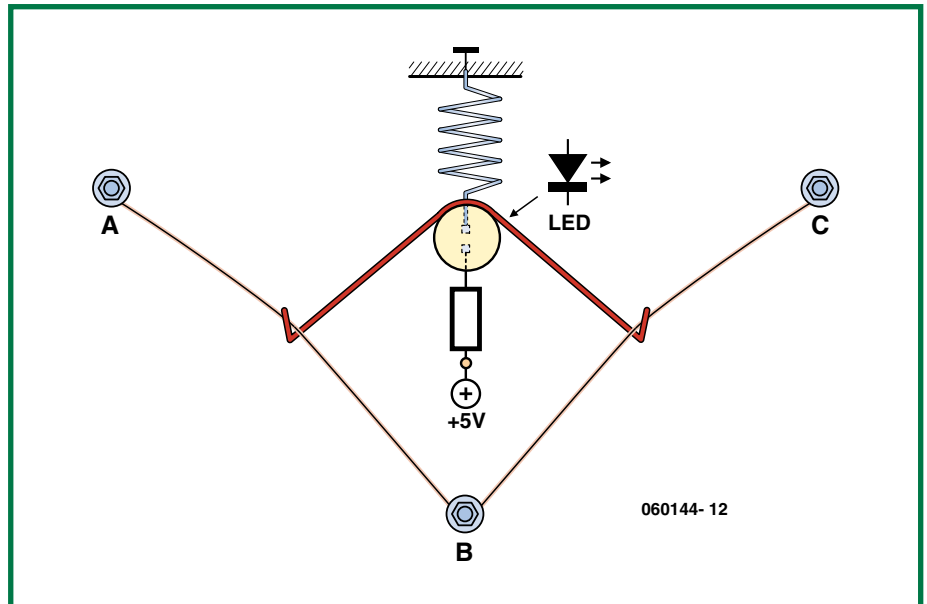


Figure 2. A side view of the assembly shows the memory wire fixing. Current through the memory wire causes it to pull the LED in that direction.

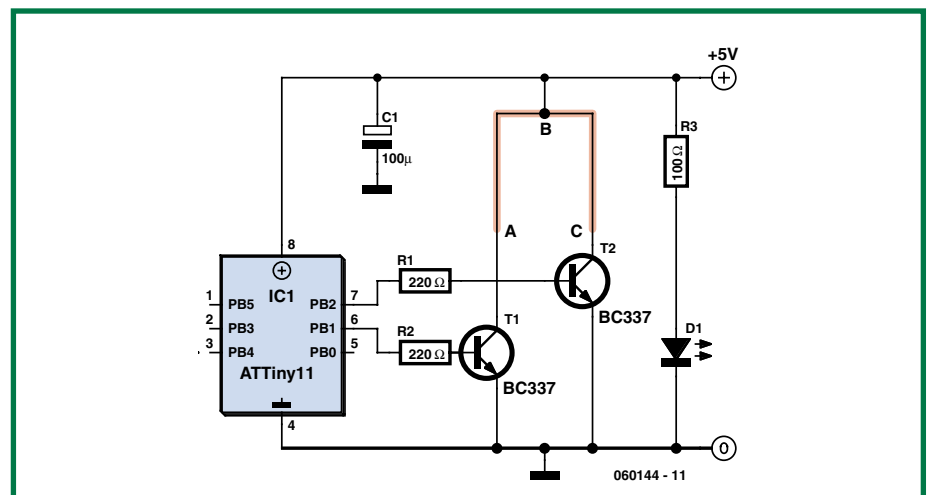

Smaller is not Always Better

Faultfinding on inaccessible IC connections


Karel Walraven

Most of our readers will appreciate that miniaturisation has brought many benefits. It is certainly the case that those small, modern mobile phones look better and are more practical than those old-fashioned bricks you had to lug around (see Retronics elsewhere in this issue). At least as long as they work. Should something go wrong, it seems hopeless to repair it, but it isn't impossible. We'll look into this in more detail here.

Have you ever wondered why it is that when you're looking for a place on a map, you often find it nearer the edge? That is because the edge of a map takes up a much larger area than you would expect. For example, say you have a map of 1 by 1 m. Half the area of this map is taken up by a square in the middle with dimensions of 70 by 70 cm, and the other half is taken up by a strip along the edge, which is just 15 cm wide. It doesn't seem much, a strip of just 15 cm, but in practice you find yourself staring at those wretched 15 centimetres for half the time...

In a similar way, the introduction of 'pin-less' components

has had a big impact on miniaturisation. The space taken up by the pins along the edge is just wasted space really. It would be much better if we could mount the ICs right next to each other, with all connections made on the underside. The so-called 'Square Packs' have therefore proved to be very popular (see main photo). The area gained becomes relatively bigger as the chips get smaller. This is because the connecting pins are of a fixed size, so smaller chips have a relatively larger area

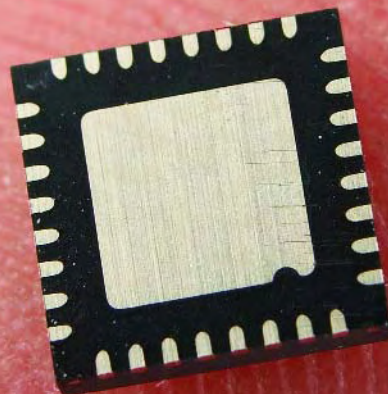



taken up by the pins compared to larger chips. The difference in area can be as much as a factor of two. Just like our example with the map, a lot of area is 'lost' by the use of connecting pins along the edge.

One of the main rules in faultfinding is that you should always take measurements at the pins of components. After all, you can never be certain that there is a perfect connection between the pin and the PCB track. With square packs it is no longer possible to physically access these connections, so we have to find some other way. However, all is not lost when you're unsure of one of these connections. Although you can't directly access this connection, you can use a handy trick to test the connection with a multimeter (1). This technique also comes in very handy for those of you who solder SMDs, for example, with our SMD Oven from the January 2006 issue. When the circuit works straight away there is nothing to worry about, otherwise there is a possibility that there is a bad connection between one of the pads underneath a square pack (or another difficult to reach IC) and the IC itself. Even boards manufactured on an industrial scale have a certain percentage of failures, and with some patience and a bit of luck it is possible to repair these PCBs.

Most multimeters have a setting that measures diode properties. In this setting the forward voltage drop of the diode is measured when a small test current (usually about 1 mA) is passed through it. That's exactly what we're looking for. First, check that your multimeter comes equipped with this setting (Figure 1). Then try it out with a normal silicon diode and then a Schottky diode. These should give readings of about 0.65 and 0.35 V respectively.

And now for the big trick: how can we use the diode-test setting of a multimeter to check the connection of a pin that is inaccessible? Fortunately, virtually every pin on an IC has protection diodes built in (there are a few exceptions, such as oscillator circuits and open-collector outputs). Usually, there is a reverse-biased diode between the pin and ground, and another between the pin and the positive supply (Figure 2). We therefore connect the **positive** probe of the multimeter to the ground of the circuit and connect the **negative** probe to the track going to the pin. When there is a good connection between the track and the chip we get a measurement of the internal protection diode and the meter usually gives a reading of about 0.6 to 0.7 V. On the other hand, if there is an open circuit the meter won't give a reading. It is fairly obvious that when the fault is in the ground connection to the IC, all measurements to the pins will show a faulty connection.

Unfortunately, the readings don't always give a clear-cut result. This is because the track doesn't only go to the suspect pin, but also to other components, and these extra connections will often influence the measurement. You should therefore refer to the circuit diagram and estimate how much of an effect these connections have (Figure 3). If there is a high-impedance resistor or FET then they can be ignored. Should the track go to another pin on an IC then it is impossible to know from which pin you're measuring the protection diode. In such cases you're left with just one option: you have to (temporarily) cut the track.

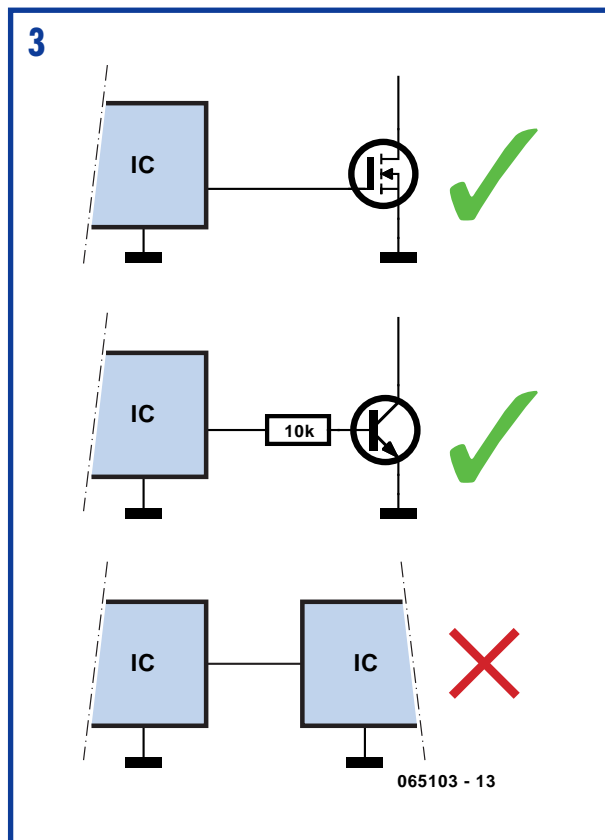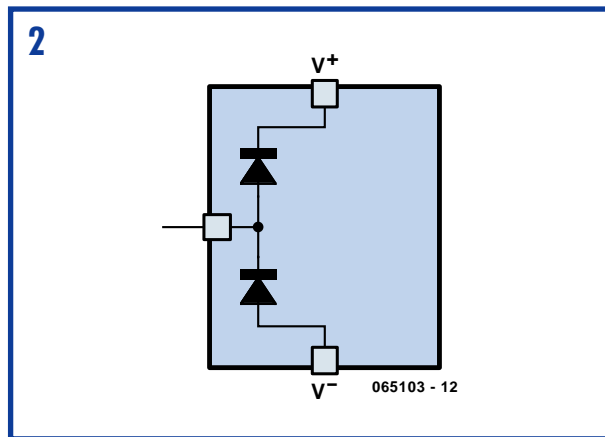


(065103-1)

FIRE YOUR IMAGINATION



The Vinculum family of USB Host Controller not only handles the USB Host interface and data transfer functions, but owing to the inbuilt processor core and embedded Flash memory, Vinculum encapsulates the USB device classes as well. When interfacing to mass storage devices such as USB Flash drive, digital camera, or PDA, Vinculum also transparently handles the FAT File structure communicating via UART, SPI or parallel FIFO interfaces via a simple to implement command set. Vinculum provides a new cost effective solution for providing USB Host capability into products that previously did not have the hardware resources available.

CONNECTS

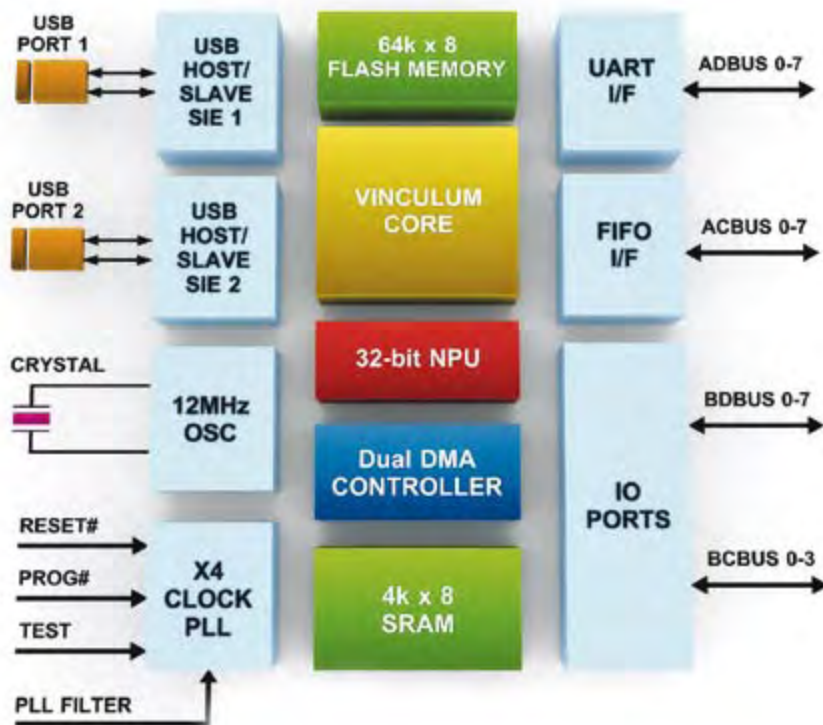

WITH



Vinculum Evaluation Modules & Application Areas



The **VNDIP1** module is an MCU to USB Host Controller development module for the VNC1L device and is ideal for rapid prototyping and development of VNC1L designs.

- Jumper selectable UART, SPI or FIFO MCU Interfaces
- USB "A" type socket to interface with USB peripherals
- 2nd USB Interface available via module pins if required
- Single 5V supply input
- Auxiliary 3.3V/200mA power output to power external logic
- Traffic Indicator LEDs



VDRIVE1 is possibly the easiest solution for adding a USB Flash Drive interface to existing products. Only four signal lines plus 5V/GND are required to be connected.

- One USB "A" socket to connect to USB Flash Drive
- Link Selectable UART or SPI interface
- Only 4 signals to connect excluding PWR/GND
- Single 5V supply required
- Easy to implement command set



VMUSIC1 is a product that not only lets you add USB Flash Drive interfacing to your product but allows you to play back MP3 and other popular digital music formats direct from a USB Flash Drive.

- One USB "A" socket to connect to USB Flash Drive
- Stereo 3.5mm headphone jack socket and audio line-out connector for audio playback.
- Link Selectable UART or SPI interface
- Only 4 signals to connect excluding PWR/GND
- Single 5V supply required
- Easy to implement command set

VINCULUM · IMAGINE WHAT YOU COULD DESIGN WITH IT...

SSB receiver for 20 and 80 m (1987)

Jan Buiting, PE1CSI

Elsewhere in this issue you'll find an article describing a short-wave receiver (150 kHz - 30 MHz) with contemporary components like a DDS synthesizer, an ARM microcontroller and an LCD. Valuable as they are and adding considerably to ease of use, the micro and the LCD are really just peripherals around the real thing: the receiver proper, i.e., the RF and AF circuitry. Out of curiosity I delved into the Elektor relics cabinet and pulled out an almost intact example of the 20/80 m SSB receiver we published in the November 1987 issue. About 20 years ago (time flies!) no eye catching 'design highlights' or 'quick specs' boxes were included in technical articles, which look grim and dry by today's standards, but are really a wonder of technical comprehensiveness. The style of the article text is 'techie' throughout. I recall writing it, the way it was done in 1987, and a success it was.

For the RF enthusiasts and old hands among you, a *quick spec* of the 1987 design would read like this: single-conversion USB/LSB receiver with 9-MHz IF; single free-running DG-MOSFET VCO; DG-MOSFET input stages with soft bandpass and IF notches, manual 20/80 m antenna switching; DG-MOSFET mixers; AGC acting on IF amp, 2.2-kHz audio.

There were not too many design quirks in this receiver. The single (!) varicap-controlled VCO has a frequency range of 5.0-5.5 MHz. Mixing is additive for the 80-m band ($3.5+5.5 = 9$ MHz) and subtractive for the 20-m band ($14-5 = 9$ MHz). Three parallel-connected 27-MHz quartz crystals operating at their funda-

mental frequency (9 MHz) form the IF filter with a bandwidth of about 2 kHz.

The design has no fewer than five dual-gate MOSFETs from the BF98x series, which were extremely popular at the time, approaching – to a considerable extent – the response and behaviour of valves. However the devices were also notorious for the ongoing confusion about their pinning. Depending on the manufacturer and sometimes even the production batch, the drain and source pins on these devices were identified in different ways (studs, longer/shorter pin, etc.). To help constructors of the receiver (and prevent lengthy technical discussions over the telephone), the DG-MOSFET circuit symbol and all three pinout variants of the BF981/982 were clearly printed in the circuit diagram.

I realise the 1987 receiver has

just two amateur radio bands as opposed to 'general coverage' for this month's DDS/ARM version but then the 20-m and 80-m bands are by far the most popular hotspots in the short-wave spectrum and SSB is the default mode for voice communications, local (80 m) and DX (20 m). Also, a block diagram and concluding piece of text in the 1987 article explain how the receiver can be used as the tuneable IF section of a 0-30 MHz communication receiver. Food for thought for advanced constructors of RF gear.

Having fitting two knobs that were missing from the front panel of the 1987 receiver I gave it a quick 'electrical' inspection — everything was still in place as assembled 20 years ago by Jan Barendrecht our RF expert. The receiver came alive when connected to a 20-m/80-m com-


bined dipole I had access to at my local radio club. The results were not bad, but not convincing either, particularly when compared to a vintage Yaesu FRG-7 I had also brought along. The first, glaring, shortcoming is the lack of a frequency readout — you really have no idea where you are on the band when turning that multiturn tuning control. Not admitting defeat, on 20 m I simply pitched reception of a mid-strength Balkanish SSB station against the FRG-7. The frequency stability, BFO and AGC of the Elektor receiver were beyond reproach but the receiver as a whole was let down quite badly by none other than its audio section, more specifically, the loudspeaker fitted in the case! A world of difference when I connected headphones, and even better results when I bypassed the

flaky LM386, tapping the audio signal at the wiper of the volume pot and feeding it to a dedicated headphone amplifier.

Although the receiver has poor prestige filtering, the BF982 MOSFETs go a long way in preventing intermodulation and other effects owing to RF overloading. None the less it will require an antenna tuner / attenuator when the bands open up due to propagation. Also, the 2.2-kHz bandwidth afforded by the 27 MHz xtals appears to be too wide nowadays and the IF filter slopes are not accurately defined. But then, the price tag compared to an FRG-7... in 1987, of course!

(065089-1)

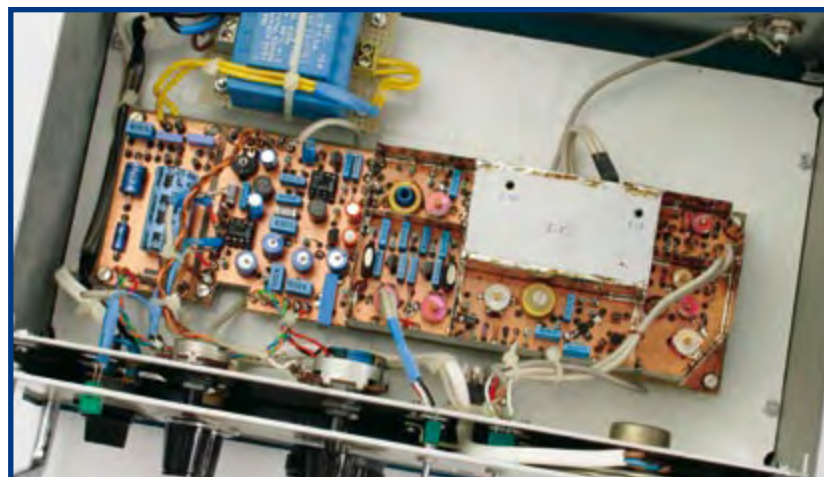A scanned copy of the 1987 article is available free of charge from our website. Go to [MAGAZINE](#) → December 2006.



Hexadoku

Puzzle with an electronic touch

Time flies when you're having fun but also when... solving an Elektor Hexadoku! Here's the last puzzle for this year 2006 — we hope you or your family members enjoy solving it.

If it's your first attempt, don't give up — persist and win a super prize!

The instructions for this puzzle are straightforward. In the diagram composed of 16 x 16 boxes, enter numbers such that **all** hexadecimal numbers 0 through F (that's 0-9 and A-F) occur once only in each row, once in each column and in each of the 4x4 boxes (marked by the thicker black lines). A number of clues are given in the puzzle and these

determine the start situation. All correct entries received for each month's puzzle go into a draw for a main prize and three lesser prizes. All you need to do is send us the numbers in the grey boxes.

The puzzle is also available as a free download from our website (Magazine → 2006 → December).

2	3	4		1			0	C	A	8		D		5	
		B		C	3			7			4			8	1
	5	6	9	F				0	D	E		B	3		
8					4			5			B	E		7	2
					5		4	6		A	7	9	8		E
		5	8			2		9		F	3		4	D	
3	A		0		F	B			1		8		6		7
6		9	D		A			2		C					1
E	7		1		9	C		3		0	A		2	F	8
9		A	F	0				4		5	C			B	6
		3	4		6			1					D		C
			B	2					8	D		1	A	9	5
B			3	4	C	1			5		F				
	E		C		2					9	0				4
4	0			B		F	E		C		2	8		3	9
		F	5								D		1	C	

Participate!

Please send your solution (the numbers in the grey boxes) by email, fax or post to:

Elektor Electronics Hexadoku
Regus Brentford
1000 Great West Road
Brentford TW8 9HH
United Kingdom.
Fax (+44)(0)208 2614447
Email:
editor@elektor-electronics.co.uk
Subject: hexadoku 12-2006.

The closing date is **1 January 2006.**

The competition is not open to employees of Segment b.v., its business partners and/or associated publishing houses.

Prize winners

The solution of the October 2006 Hexadoku is: **754C1.**

The **E-blocks Starter Kit Professional** goes to:
 Tomas Bakke
 (Horte, Norway).

An **Elektor SHOP voucher worth £35.00** goes to:

- L. Bailey (Wheatley);
- Andrew Larkin (Wivenhoe);
- Jim Orchard (Chelmsford).

Congratulations everybody!

Solve Hexadoku and win!

Correct solutions received enter a prize draw for an **E-blocks**

Starter Kit Professional worth **£248.55**



and three **Elektor Electronics SHOP Vouchers** worth £35.00 each.

We believe these prizes should encourage all our readers to participate!

ELEKTOR SHOWCASE

To book your showcase space contact Huson International Media

Tel. 0044 (0) 1932 564999 Fax 0044 (0) 1932 564998

ATC SEMITEC LTD

www.atcsemitec.co.uk

Thermal and current-sensitive components for temperature control and circuit protection;

- NTC Thermistors
- Current Diodes
- Thermostats
- Re-settable Fuses
- Thermal Fuses
- Temperature Sensors

Call today for free samples and pricing

Tel: 0870 901 0777 Fax: 0870 901 0888

AVIT RESEARCH

www.avitresearch.co.uk

USB has never been so simple...

with our USB to Microcontroller Interface cable. Appears just like a serial port to both PC and Microcontroller, for really easy USB connection to your projects, or replacement of existing RS232 interfaces.



See our webpage for more details. Only £29.99 inc vat.

BAEC

<http://baec.tripod.com>

"The British Amateur Electronics Club Archive Website. Archiving extracts from 140+ Newsletters from 1966-2002. Currently have interesting and useful selected articles from 12 Newsletters. Also a section about built electronics projects with schematics and photos. Plus useful info., downloads and links. NO ADVERTS!"



BETA LAYOUT

www.pcb-pool.com

Beta layout Ltd Award-winning site in both English and German offers prototype

PCBs at a fraction of the cost of the usual manufacturer's prices.



COMPULOGIC LTD

www.compulogic.co.uk

Internet Remote Control Starter Kit £139.99

Create a simple web based remote control interface for many applications

- Miniature Web Server Module
- Analogue/Digital Module
- PSU
- Manuals, software, example HTML code



CONFORD ELECTRONICS

<http://www.confordelec.co.uk>

Lightweight portable battery/mains audio units offering the highest technical performance.

Microphone, Phantom Power and Headphone Amplifiers. Balanced/unbalanced signal lines with extensive RFI protection.

DANBURY ELECTRONICS

<http://www.DanburyElectronics.co.uk>

Transformer manufacturers since 1983. Visit our new site! Also link directly to Mike Holme's Valve/-Tube DIY amplifier site, featuring our standard Audio Transformers (Mains, Output, Chokes, PP, SE, etc).

EASYSYNC

<http://www.easysync.co.uk>

EasySync Ltd sells a wide range of single and multi-port USB to RS232/RS422 and RS485 converters at competitive prices.



ELNEC

www.elnec.com

- device programmer manufacturer
- selling through contracted distributors all over the world
- universal and dedicated device programmers
- excellent support and after sale support
- free SW updates
- reliable HW
- once a months new SW release
- three years warranty for most programmers



FIRST TECHNOLOGY TRANSFER LTD.

<http://www.ftt.co.uk/PICProTrng.html>

Microchip Professional C and Assembly Programming Courses.

The future is embedded.

Microchip Consultant / Training Partner developed courses:

- Distance learning / instructor led
- Assembly / C-Programming of PIC16, PIC18, PIC24, dsPIC microcontrollers
- Foundation / Intermediate



FUTURE TECHNOLOGY DEVICES

<http://www.ftdichip.com>

FTDI designs and sells USB-UART and USB-FIFO interface i.c.'s.

Complete with PC drivers, these devices simplify the task of designing or upgrading peripherals to USB



FUTURLEC

<http://www.futurlec.com>

Save up to 60% on

- Electronic Components
 - Microcontrollers, PIC, Atmel
 - Development Boards, Programmers
- Huge range of products available on-line for immediate delivery, at very competitive prices.



HEROS TECHNOLOGY LTD

www.herostechnology.co.uk

Introducing Modular Concept for microcontrollers.

Suitable for Developers, Pre-production, Educational and Hobby applications.

- WinPIC2006 USB full speed programmer.
- CPU microcontroller modules.
- Peripheral modules for all microcontrollers.



JLB ELECTRONICS

www.jlbelectronics.com


Suppliers of electrical / electronic parts and consumables. Including:

- Cable ties / bases
- Tools / hardware
- Bootlace ferrules
- Connectors
- Solvent sprays & cleaners
- PVC Tape
- Heat Sink compound

KMK TECHNOLOGIES Ltd.

<http://www.kmk.com.hk>

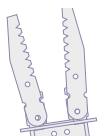Low Cost DIY Robotic Kits and Computer Controller Boards.



products and services directory

LONDON ELECTRONICS COLLEGE

<http://www.lec.org.uk>

Vocational training and education for national qualifications in Electronics Engineering and Information Technology (BTEC First National, Higher National NVQs, GCSEs and Advanced Qualifications). Also Technical Management and Languages.

MODular ELECTRONics

www.modetron.com

- Plug and Program
- FREE application s/w
- Hobbyist ease-of-use
- Professional finish with enclosure and LEXAN faceplate
- We will design and brand your custom application
- Growing range of PSU's, i/o modules, displays and microcontrollers



MQP ELECTRONICS

<http://www.mqpelectronics.co.uk>

Leaders in Device Programming Solutions.

- Online shop
- Low Cost Adapters for all Programmers
- Single Site and Gang Programmers
- Support for virtually any Programmable Device



NEW WAVE CONCEPTS

www.new-wave-concepts.com

Software for Hobbyists:

- Livewire - circuit simulation software, only £34.99
- PCB Wizard - PCB design software, only £34.99
- Circuit Wizard - circuit, PCB and breadboard design software, only £59.99



Available from all Maplin Electronics stores and www.maplin.co.uk

PCB WORLD

<http://www.pcbworld.org.uk>

World-class site: Your magazine project or prototype PCB from the artwork of your choice for less. Call Lee on 07946 846159 for details. Prompt service.

ROBOT ELECTRONICS

<http://www.robot-electronics.co.uk>

Advanced Sensors and Electronics for Robotics

- Ultrasonic Range Finders
- Compass modules
- Infra-Red Thermal sensors
- Motor Controllers
- Vision Systems
- Wireless Telemetry Links
- Embedded Controllers



SOURCEBOOST TECHNOLOGIES

<http://www.sourceboost.com>

Next generation C compiler and development products at highly affordable prices:

- C, C++, and Basic compilers for PIC12, PIC16, PIC18
- Modern IDE, with PIC simulator, source level debugger and virtual devices.
- RTOS for PICmicro.
- PIC based controller and Development boards.
- Download and try for Free from <http://www.sourceboost.com>



SYTRONIC TECHNOLOGY LTD

www.m2mtelemetry.com

Supplier of wireless modules and accessories for remote monitoring M2M applications.

- GSM/GPRS TCP/IP modules
 - Embedded GSM/GPRS modem
 - Development Kits
 - GPS modules
 - GSM/GPS antennas
 - Adapter cables
- Online ordering facilities.
Tel: 01728 685802



SHOWCASE YOUR COMPANY HERE

Elektor Electronics has a feature to help customers promote their business, Showcase - a permanent feature of the magazine where you will be able to showcase your products and services.

- For just £220 + VAT (£20 per issue for eleven issues) Elektor will publish your company name, website address and a 30-word description

- For £330 + VAT for the year (£30 per issue for eleven issues) we will publish the above plus run a 3cm deep full colour image - e.g. a product shot, a screen shot from your site, a company logo - your choice

Places are limited and spaces will go on a strictly first come, first served basis. So please fax back your order today!

I wish to promote my company, please book my space:

- Text insertion only for £220 + VAT
- Text and photo for £330 + VAT

NAME:.....ORGANISATION:.....

JOB TITLE:.....

ADDRESS:.....

.....TEL:.....

PLEASE COMPLETE COUPON BELOW AND FAX BACK TO 00-44-(0)1932 564998

COMPANY NAME.....

WEB ADDRESS.....

30-WORD DESCRIPTION.....

.....

.....

.....

.....

.....

USB INSTRUMENTS

<http://www.usb-instruments.com>

USB Instruments specialises in PC based instrumentation products and software such as Oscilloscopes, Data

Loggers, Logic Analysers which interface to your PC via USB.



VIRTINS TECHNOLOGY

www.virtins.com

PC and Pocket PC based virtual instrument for electronics enthusiasts, students, professionals and scientists, including sound card real time oscilloscope, spectrum analyzer, and signal generator. Free to download and try.





Quasar Electronics Limited
 PO Box 6935, Bishops Stortford
 CM23 4WP, United Kingdom
 Tel: 0870 246 1826
 Fax: 0870 460 1045
 E-mail: sales@quasarelectronics.com
 Web: www.QuasarElectronics.com

All prices INCLUDE 17.5% VAT.
 Postage & Packing Options (Up to 2Kg gross weight): UK Standard 3-7 Day Delivery - £3.95; UK Mainland Next Day Delivery - £8.95; Europe (EU) - £6.95; Rest of World - £9.95 (up to 0.5Kg).
 Order online for reduced price UK Postage!
 Payment: We accept all major credit/debit cards. Make cheques/PO's payable to Quasar Electronics.
 Call now for our FREE CATALOGUE with details of over 300 kits, projects, modules and publications. Discounts for bulk quantities.



08717 Credit Card Sales 177 168



**Ho! Ho! Ho! Christmas 2006 is on it's way
 BUT DON'T PANIC!!**

We have some fantastic gift ideas for young (and old) enquiring minds



Electronic Project Labs

An electronics course in a box! All assume no previous knowledge and require NO solder. See website for full details



30 in ONE - £15.95
 Order Code EPL030KT



130 in ONE - £37.95
 Order Code EPL130KT



300 in ONE - £59.95
 Order Code EPL300KT



500 in ONE - £149.95
 Order Code EPL500KT



Robot Sensor - £19.95
 Order Code EPLR20KT



Digital Recording Laboratory - £29.95
 Order Code EPLDRKT

Solderless Electronic Project Kits



AM-FM Radio Kit - £6.95
 Order Code ERKAFKT



Short Wave Kit - £6.95
 Order Code ERKSWKT



Crystal Radio Kit - £6.95
 Order Code ERKCKT



Electronic Bell - £8.95
 Order Code EAKEBKT



Electronic Motor - £8.95
 Order Code EAKEMKT



Generator - £8.95
 Order Code EAKEGKT



Room Alarm - £4.95
 Order Code EAKRAKT



Hand Held Metal Detector - £9.95
 Order Code ELMDX7KT



Metal Detector - £9.95
 Order Code ELMDDKT

Mechanical Motorised Wooden Kits

Future engineers can learn about the operation of transmissions steered through gears or pulleys. Easy to build, no glue or soldering required.



Automech - £12.95
 Order Code C21-605KT



Coptermech - £12.95
 Order Code C21-604KT



Trainmech - £12.95
 Order Code C21-606KT



Robomech - £12.95
 Order Code C21-603KT



Stegomech - £12.95
 Order Code C21-602KT



Tyrannomech - £12.95
 Order Code C21-601KT

Festive Electronic Project Kits



Musical LED Jingle Bells - £17.95
 Order Code 1176KT



Flashing LED Christmas Tree - £6.95
 Order Code 4080KT

See our website for even more great gift ideas!



www.QuasarElectronics.com

Secure Online Ordering Facilities • Full Product Listing, Descriptions & Photos • Kit Documentation & Software Downloads

Order now using the Order Form in the Readers Services section in this issue.

CD-ROM BESTSELLERS

USB TOOLBOX

This CD-ROM contains technical data about the USB interface. It also includes a large collection of data sheets for specific USB components from a wide range of manufacturers. There are two ways to incorporate a USB interface in a microcontroller circuit: add a USB controller to an existing circuit, or use a microcontroller with an integrated USB interface. Included on this CD-ROM are USB Basic Facts, several useful design tools for hardware and software, and all Elektor Electronics articles on the subject of USB. **£18.95 (US\$ 34.95)**



1

Home Automation


This CD-ROM provides an overview of what manufacturers offer today in the field of Home Networking, both wired and wireless. The CD-ROM contains specifications, standards and protocols of commercially available bus and network systems. For developers, there are datasheets of specific components and various items with application data. End-users and hobbyists will find ready-made applications that can be used immediately. **£12.95 (US\$ 22.90)**



2

ECD Edition 3

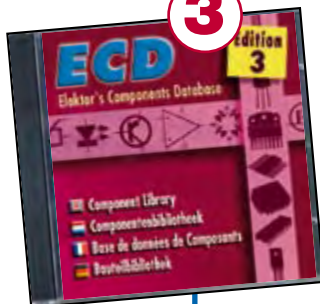Elektor's Components Database gives you easy access to design data for over 5,000 ICs, more than 35,000 transistors, FETs, thyristors and triacs, just under 25,000 diodes and 1,800 optocouplers. All databank applications are fully interactive, allowing the user to add, edit and complete component data. **£14.95 (US\$ 26.50)**




3

More information on www.elektor.com

Microcontroller Basics

Microcontrollers have become an indispensable part of modern electronics. They make things possible that vastly exceed what could be done previously. Innumerable applications show that almost nothing is impossible. There's thus every reason to learn more about them. This book offers more than just a basic introduction. It clearly explains the technology using various microcontroller circuits and programs written in several different programming languages. In the course of the book, the reader gradually develops increased competence in converting his or her ideas into microcontroller circuitry.

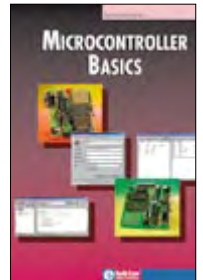

ISBN 0-905705-67-X
230 Pages
£18.70 (US\$ 33.70)

Visual Basic for Electronics Engineering Applications

This book is targeted towards those people that want to control existing or home made hardware from their computer. After familiarizing yourself with Visual Basic, its development environment and the toolset it offers are discussed in detail. Each topic is accompanied by clear, ready to run code, and where necessary, schematics are provided that will get your projects up to speed in no time.



ISBN 0-905705-68-8
476 Pages
£27.50 (US\$ 51.50)

BESTSELLING BOOKS

Top-5

- 1 **Visual Basic for Electronics Engineering Applications**
ISBN 0-905705-68-8 **£27.50 (US\$ 51.50)**
- 2 **Microcontroller Basics**
ISBN 0-905705-67-X **£18.70 (US\$ 33.70)**
- 3 **PC-Interfaces under Windows**
ISBN 0-905705-65-3 **£25.95 (US\$ 52.00)**
- 4 **Modern High-end Valve Amplifiers**
ISBN 0-905705-63-7 **£25.95 (US\$ 52.00)**
- 5 **308 Circuits**
ISBN 0-905705-66-1 **£18.20 (US\$ 37.00)**

More information on www.elektor.com

Order now using the Order Form in
the Readers Services section in this issue.

USB-stick with ARM and RS232

(November 2006)

Assembled and tested board

060006-91
£ 79.90 / \$ 149.95



GameBoy ElectroCardioGraph

(October 2006)

PCB, ready built and tested

050280-91
£ 55.20 / \$ 103.95



PIC In-Circuit Debugger/Programmer

(October 2006)

Kit of parts including PCB,
programmed controller and
all components.

050348-71
£ 34.50 / \$ 64.95



RC Servo Tester / Exerciser

(July/August 2006)

Kit of parts including
PCB, programmed
controller and all
components.

040259-71
£ 22.70 / \$ 42.85



MORE READY-BUILT PROJECTS

	£	\$
ClariTy 300-W Class-T Amplifier		
030217-91 Amplifier board with SMDs pre-fitted; cores for L1 & L2	34.50	55.70
Electrosmog Tester		
050008-91 PCB, ready built and tested	50.00	94.25
050008-71 Matching enclosure	10.25	19.30
Flash Microcontroller Starter Kit		
010208-91 Ready-assembled PCB incl. software, cable, adapter & related articles	69.00	112.50
Gameboy Digital Sampling Oscilloscope (GBDSO)		
990082-91 Ready-assembled board, incl. the PC software and related articles	103.00	183.00
LPC210x ARMeE Development System		
040444-91 Processor board, ready-made and tested	25.50	48.05
Micro Webserver with MSC1210 Board		
030060-91 Microprocessor Board, ready-assembled	75.90	142.95
044026-91 Network Extension Board, ready-assembled	44.50	83.95
044026-92 Combined package (030060-91 & 044026-91 & related articles)	117.50	220.95

ECG using a Sound Card

040479-1 PCB	5.20	9.75
040479-81 CD-ROM, all project software	5.20	9.75

NO. 358 SEPTEMBER 2006

Elektor RFID Reader		
060132-91 PCB, ready assembled & tested, with USB cable	41.50	77.95
030451-72 Standard back-lit LC display	7.25	13.65
060132-71 Matching enclosure	8.90	16.85
060132-81 CD-ROM, all project software	5.20	9.75

Experimental RFID Reader

060221-11 Disk, all project software	5.20	9.75
060221-41 ATmega16, programmed	8.90	16.85

DiSEqC Monitor

040398-11 Disk, PIC source & hex code	5.20	9.75
040398-41 PIC16F628A-20/P, programmed	5.50	10.35

USB/DMX512 Converter

060012-11 Disk, all project software	5.20	9.75
060012-41 PIC16C745, programmed	6.90	12.95

NO. 356/357 JULY/AUGUST 2006

RC Servo Tester/Exerciser		
040172-11 Disk, project software	5.20	9.75
040172-41 PIC16F84(A), programmed	10.30	19.40
040172-71 Kit, incl. PCB, controller, all parts	22.70	42.85

LED Thermometer

030190-11 Disk, project software	5.20	9.75
030190-41 PIC16F873-20/SP, programmed	16.50	31.00

Toothbrush Timer

050146-11 Disk, project software	5.20	9.75
050146-41 AT90S2313-10PC, programmed	6.90	12.95

Easy Home Control

050233-11 Disk, project software	5.20	9.75
050233-41 PIC16F84, programmed	10.30	19.40

Universal LCD Module

050259-11 Disk, project software	5.20	9.75
050259-41 AT90S2313, programmed	6.90	12.95

NO. 361 DECEMBER 2006

Shortwave Capture		
030417-1 PCB, bare (receiver board)	www.thepcbshop.com	
030417-2 PCB, bare (control & display boards)	www.thepcbshop.com	
030417-41 AT90S8515-8PC, programmed	11.40	21.45

NO. 360 NOVEMBER 2006

USB Stick with ARM and RS232		
060006-1 PCB, bare	11.00	20.75
060006-41 AT91SAM7S64, programmed	27.60	51.95
060006-91 assembled & tested board	79.90	149.95
060006-81 CD-ROM, all project software	5.20	9.75

NO. 359 OCTOBER 2006

PIC In-Circuit Debugger/Programmer		
050348-1 PCB	5.20	9.75
050348-41 PIC16F877, programmed	17.90	33.75
050348-71 Kit, incl. PCB, controller, all parts	34.50	64.95

GBECG – Gameboy ElectroCardioGraph

050280-91 PCB, ready built and tested	55.20	103.95
---------------------------------------	-------	--------

Due to practical constraints, final illustrations and specifications may differ from published designs. Prices subject to change. See www.elektor.com for up to date information.

Elektor RFID-reader

(September 2006)

Ready-built and tested PCB with USB port for connection to the PC. Including USB cable; not including display and enclosure.

- Read and write 13.56 MHz RFID cards
- MIFARE and ISO 14443-A compatible
- Programmable

060132-91

£ 41.50 / \$ 77.95

LC-display

030451-72

£ 7.25 / \$ 13.65

Matching enclosure

060132-71

£ 8.90 / \$ 16.85

CD-ROM (all project software)

060132-81

£ 5.20 / \$ 9.75



Elektor Electronics (Publishing)
Regus Brentford
1000 Great West Road
Brentford TW8 9HH
United Kingdom
Tel.: +44 (0) 208 261 4509
Fax: +44 (0) 208 261 4447
Email: sales@elektor.com

Kits & Modules

GameBoy Programmable Logic Controller

(July/August 2006)

GBPLC Module

Ready-assembled and tested GBPLC Module and Programming Interface

050190-91

£ 84.95 / \$ 159.95



GBPLC I²C I/O Box

Ready assembled and tested board

060098-91

£ 84.95 / \$ 159.95



Combined package

GBPLC Module and I/O Extension

£ 149.80 / \$ 279.00

**PRICE
SLASHED!**

1-Wire Thermometer with LCD

060090-11	Disk, project software	5.20	9.75
060090-41	PIC16F84A-04CP, programmed	10.30	19.40

GBPLC - Gameboy PLC

050190-1+2	PCBs, bare, GBPLC Module & Programming Interface	11.70	22.00
050190-51	Programmed PAL, EEPROM and Flash IC	11.00	20.75
050190-91	Ready-built and tested GBPLC Module and Programming Interface	84.95	159.95

GBPLC - I²C I/O Box

060098-1	PCB, bare	17.90	33.75
060098-91	Ready-built and tested board	84.95	159.95

Binary Clock

020390-11	disk, project software	5.20	9.75
020390-41	PIC6C54-04/P, programmed	8.05	15.10

NO. 355 JUNE 2006

FM Stereo Test Transmitter

050268-1	PCB	11.70	22.00
----------	-----	-------	-------

Network Cable Analyser

050302-1	PCB	8.20	15.55
050302-11	Disk, PIC source code	5.20	9.75
050302-41	PIC16F874-20/P	16.90	31.85

NO. 354 MAY 2006

Onboard OBD-2 Analyser

050176-72	Kit of parts, incl. 050176-1, 050176-2, 050176-42, all components, excl. LCD and Case	24.80	46.70
050176-73	LCD, 4x20 characters with backlight	28.80	54.50
050176-74	Case, Bopla Unimas 160 with Perspex cover and mounting plate	15.80	29.90
050176-42	ATmega16, programmed	10.30	19.45
050092-71	OBD-2 Analyser: Kit of parts without cable	52.50	96.95
050092-72	OBD-2 Analyser: DB9 to OBD adapter cable	27.55	51.95

Mini ATmega Board

050176-1	PCB, includes adapter PCB 050176-2	8.95	16.85
----------	------------------------------------	------	-------

NO. 353 APRIL 2006

Simple rechargeable A Cell Analyser

050394-1	PCB, bare	4.80	9.04
050394-11	Disk, PC Software	5.18	9.75

Universal SPI Box

050198-41	AT89C2051-24PC, Programmed	7.25	13.65
-----------	----------------------------	------	-------

NO. 352 MARCH 2006

Application Board for R8C/13

050179-92	Ready-assembled board	48.27	90.94
050179-1	PCB	13.77	25.94
030451-72	LCD with backlight	7.25	13.65
030451-73	Poly-LED display	25.50	48.05

FPGA-Prototyping board

050370-91	Ready assembled board		
	For subscribers	181.80	333.50
	For non-subscribers	216.30	398.50

Telephone Eavesdropper

030379-1	PCB	9.05	17.05
----------	-----	------	-------

Versatile FPGA Module

040477-91	Ready assembled plug-on module		
	For subscribers	181.80	333.50
	For non-subscribers	216.30	398.50

NO. 351 FEBRUARY 2006

Brushless Motor Controller

050157-41	ST7MC1, programmed	3.80	7.15
-----------	--------------------	------	------

A 16-bit Tom Thumb

050179-91	R8C Starter Kit	8.30	15.60
050179-C5	Set of 5 pcs. R8C13 microcontroller only	20.70	39.00

NO. 350 JANUARY 2006

95-watt Laptop PSU Adaptor

050029-1	PCB	4.80	9.05
----------	-----	------	------

Automatic Attic Window Controller

050139-11	Disk, PIC source & hex code	5.20	9.75
050139-41	PIC16F84A-20/P, programmed	13.10	24.65

Products for older projects (if available) may be found on our website www.elektor.com

home construction = fun and added value



Free CD-ROM from Microchip/Labcenter/Elektor

In the January 2007 issue we launch **EXPLORER-16**, a 16-bit PIC microcontroller project brought to you jointly by Microchip, Labcenter and *Elektor Electronics* magazine. The project is based on a number of hardware and software components, exclusively gathered for *Elektor* readers. The first instalment of the series covers the installation and practical use of two Microchip software contributions to the free CD-ROM: the MPLAB development suite for PIC micros and — buckle up — the C30 Compiler! Space allowing we will also introduce you to the workings of Proteus VSM, Labcenter's software that's so powerful it can simulate the interaction between a microcontroller and any analogue or digital hardware connected to it!

Overclocking CPUs and Micros

For as long as we can remember, CPUs in PCs have been subjected to overclocking experiments, sometimes with catastrophic results. Whenever a new CPU appears on the market, it does not take speed tweakers long to make things run faster. What's rarely seen however is information on overclocking of laptop PCs. In our January issue we venture to cover the subject in some detail with a Centrino-based laptop as the guinea pig.

Also...

Multi-purpose Milling Machine; LED Rotating Text Display; Berlin Clock Remake; Texas Instruments Clock Generator; FPGA Course (8); Hexadoku.

Nixie Clock in Sputnik Design

Entirely fitting a January issue we have several articles on clocks and clocking systems. One of the pinnacles, we're sure, is our Sputnik Clock which uses nixie tubes for the time readout. The clock is designed to look like a miniature version of the first man-made satellite to make it into an orbit around the earth.



RESERVE YOUR COPY NOW!

UK mainland subscribers will receive the magazine between 18 and 20 December 2006.

The January 2007 issue goes on sale on Thursday 21 December 2006 (UK distribution only).

Article titles and magazine contents subject to change, please check www.elektor.com.

NEWSAGENTS ORDER FORM

SHOP SAVE / HOME DELIVERY

Please save / deliver one copy of *Elektor Electronics* magazine for me each month

Name:

Address:

Post code:

Telephone:

Date:

Signature:



Please cut out or photocopy this form, complete details and hand to your newsagent. *Elektor Electronics* is published on the third Thursday of each month, except in July.

www.elektor.com www.elektor.com www.elektor.com www.elektor.com www.elektor.com

Elektor Electronics on the web

All magazine articles back to volume 2000 are available online in pdf format. The article summary and parts list (if applicable) can be instantly viewed to help you positively identify an article. Article related items are also shown, including software downloads, circuit boards, programmed ICs and corrections and updates if applicable. Complete magazine issues may also be downloaded.

In the *Elektor Electronics* Shop you'll find all other products sold by the publishers, like CD-ROMs, kits and books. A powerful search function allows you to search for items and references across the entire website.

Also on the *Elektor Electronics* website:

- Electronics news and *Elektor* announcements
- Readers Forum
- PCB, software and e-magazine downloads
- Surveys and polls
- FAQ, Author Guidelines and Contact



ORDERING INSTRUCTIONS, P&P CHARGES

Except in the USA and Canada, all orders, except for subscriptions (for which see below), must be sent BY POST or FAX to our Brentford address using the Order Form overleaf. On-line ordering: <http://www.elektor-electronics.co.uk>

Readers in the USA and Canada may (but are not obliged to) send orders, except for subscriptions (for which see below), to the USA address given on the order form. Please apply to Old Colony Sound for applicable P&P charges. Please allow 4-6 weeks for delivery.

Orders placed on our Brentford office must include P&P charges (Priority or Standard) as follows:

UK: £4.00 Europe: £5.00 (Standard) or £7.00 (Priority) Outside Europe: £8.00 (Standard) or £12.00 (Priority)

HOW TO PAY

All orders must be accompanied by the full payment, including postage and packing charges as stated above or advised by Customer Services staff.

Bank transfer into account no. 40209520 held by Elektor Electronics (Publishing) / Segment b.v. with ABN-AMRO Bank, London. IBAN: GB35 ABNA 4050 3040 2095 20. BIC: ABNAGB2L. Currency: sterling (UKP). Please ensure your full name and address gets communicated to us.

Cheque sent by post, made payable to Elektor Electronics (Publishing) / Segment b.v.. We can only accept sterling cheques and bank drafts from UK-resident customers or subscribers. We regret that no cheques can be accepted from customers or subscribers in any other country.

Giro transfer into account no. 34-152-3801, held by Elektor Electronics (Publishing) / Segment b.v. Please do not send giro transfer/deposit forms directly to us, but instead use the National Giro postage paid envelope and send it to your National Giro Centre.

Credit card VISA, Access, MasterCard, JCBCard and Switch cards can be processed by mail, email, web, fax and telephone. Online ordering through our website is SSL-protected for your security.

COMPONENTS

Components for projects appearing in Elektor Electronics are usually available from certain advertisers in this magazine. If difficulties in the supply of components are envisaged, a source will normally be advised in the article. Note, however, that the source(s) given is (are) not exclusive.

TERMS OF BUSINESS

Delivery Although every effort will be made to dispatch your order within 2-3 weeks from receipt of your instructions, we can not guarantee this time scale for all orders. **Returns** Faulty goods or goods sent in error may be returned for replacement or refund, but not before obtaining our consent. All goods returned should be packed securely in a padded bag or box, enclosing a covering letter stating the dispatch note number. If the goods are returned because of a mistake on our part, we will refund the return postage. **Damaged goods** Claims for damaged goods must be received at our Brentford office within 10-days (UK); 14-days (Europe) or 21-days (all other countries). **Cancelled orders** All cancelled orders will be subject to a 10% handling charge with a minimum charge of £5.00. **Patents** Patent protection may exist in respect of circuits, devices, components, and so on, described in our books and magazines. Elektor Electronics (Publishing) does not accept responsibility or liability for failing to identify such patent or other protection. **Copyright** All drawings, photographs, articles, printed circuit boards, programmed integrated circuits, diskettes and software carriers published in our books and magazines (other than in third-party advertisements) are copyright and may not be reproduced or transmitted in any form or by any means, including photocopying and recording, in whole or in part, without the prior permission of Elektor Electronics (Publishing) in writing. Such written permission must also be obtained before any part of these publications is stored in a retrieval system of any nature. Notwithstanding the above, printed-circuit boards may be produced for private and personal use without prior permission. **Limitation of liability** Elektor Electronics (Publishing) shall not be liable in contract, tort, or otherwise, for any loss or damage suffered by the purchaser whatsoever or howsoever arising out of, or in connexion with, the supply of goods or services by Elektor Electronics (Publishing) other than to supply goods as described or, at the option of Elektor Electronics (Publishing), to refund the purchaser any money paid in respect of the goods.

Law Any question relating to the supply of goods and services by Elektor Electronics (Publishing) shall be determined in all respects by the laws of England.

January 2006

SUBSCRIPTION RATES FOR ANNUAL SUBSCRIPTION

	Standard	Plus
United Kingdom	£41.90	£48.80
Surface Mail		
Rest of the World	£54.50	£61.40
USA & Canada	US\$ 95.50	US\$106.50
Airmail		
Rest of the World	£68.90	£75.80
USA & Canada	US\$120.00	US\$131.00

HOW TO PAY

Bank transfer into account no. 40209520 held by Elektor Electronics (Publishing) / Segment b.v. with ABN-AMRO Bank, London. IBAN: GB35 ABNA 4050 3040 2095 20. BIC: ABNAGB2L. Currency: sterling (UKP). Please ensure your full name and address gets communicated to us.

Cheque sent by post, made payable to Elektor Electronics (Publishing) / Segment b.v.. We can only accept sterling cheques and bank drafts from UK-resident customers or subscribers. We regret that no cheques can be accepted from customers or subscribers in any other country.

Giro transfer into account no. 34-152-3801, held by Elektor Electronics (Publishing) / Segment b.v. Please do not send giro transfer/deposit forms directly to us, but instead use the National Giro postage paid envelope and send it to your National Giro Centre.

Credit card VISA, Access, MasterCard, JCBCard and Switch cards can be processed by mail, email, web, fax and telephone. Online ordering through our website is SSL-protected for your security.

SUBSCRIPTION CONDITIONS

The standard subscription order period is twelve months. If a permanent change of address during the subscription period means that copies have to be despatched by a more expensive service, no extra charge will be made. Conversely, no refund will be made, nor expiry date extended, if a change of address allows the use of a cheaper service.

Student applications, which qualify for a 20% (twenty per cent) reduction in current rates, must be supported by evidence of studentship signed by the head of the college, school or university faculty. A standard Student Subscription costs £33.50, a Student Subscription-Plus costs £40.40 (UK only).

Please note that new subscriptions take about four weeks from receipt of order to become effective.

Cancelled subscriptions will be subject to a charge of 25% (twenty-five per cent) of the full subscription price or £7.50, whichever is the higher, plus the cost of any issues already dispatched. Subscriptions cannot be cancelled after they have run for six months or more.

January 2006

New

CD-ROM USB TOOLBOX

This CD-ROM contains all the essential information a designer needs to start working with the USB interface. It includes a large collection of data sheets for specific USB components from a wide range of manufacturers.

There are two ways to incorporate a USB interface in a microcontroller circuit. You can add a USB controller to an existing circuit, or use a microcontroller with an integrated USB interface. Both options are available on this CD-ROM.

USB Toolbox provides information on all ICs suitable for different applications. A sub-division has been made in controllers, hubs, microcontrollers and others. What is perhaps more interesting for many designers however, is the extremely extensive software collection which contains drivers, tools and components for Windows, Delphi and various microcontroller families. Of course, none of the Elektor Electronics articles on the subject of USB are missing on this CD-ROM

ISBN 90-5381-212-1
£ 18.95 / US\$ 34.95

*Embedded
USB Know How*



Order now using the Order Form in the Readers Services section in this issue.

Elektor Electronics (Publishing)
Regus Brentford
1000 Great West Road
Brentford TW8 9HH
United Kingdom
Tel. +44 208 261 4509

See also www.elektor.com

INDEX OF ADVERTISERS

ATC Semitec Ltd, Showcase	www.atcsemitec.co.uk	102	London Electronics College, Showcase	www.lec.org.uk	103
Avit Research, Showcase	www.avitresearch.co.uk	102	MQP Electronics, Showcase	www.mqpelectronics.co.uk	103
BAEC, Showcase	http://baec.tripod.com	102	New Wave Concepts, Showcase	www.new-wave-concepts.com	103
Beijing Draco	www.ezpcb.com	37	Newbury Electronics	www.newburelectronics.co.uk	22
Beta Layout, Showcase	www.pcb-pool.com	7, 102	Number One Systems	www.numberone.com	69
Bitscope Designs	www.bitscope.com	3	Nurve Networks	www.xgamestation.com	22
ByVac	www.byvac.co.uk	69	PCB World, Showcase	www.pcbworld.org.uk	103
Compulogic, Showcase	www.compulogic.co.uk	102	Pico	www.picotech.com	7
Conford Electronics, Showcase	www.confordelec.co.uk	102	Quasar Electronics	www.quasarelectronics.com	104
Cricklewood	www.cctvcentre.co.uk	69	Redline	www.redlineplc.com	78
Danbury, Showcase	www.DanburyElectronics.co.uk	102	Robot Electronics, Showcase	www.robot-electronics.co.uk	103
Easysync, Showcase	www.easysync.co.uk	102	Scantool	www.ElmScan5.com/elektor	6
Eltec, Showcase	www.eltec.com	102	Showcase		102, 103
Eptsoft	www.eptsoft.com	78	SourceBoost Technologies, Showcase	www.sourceboost.com	103
Eurocircuits	www.eurocircuits.com	6	Sytronic Technology Ltd, Showcase	www.m2mtelemetry.com	103
First Technology Transfer Ltd, Showcase	www.ftt.co.uk	102	Ultraleds, Showcase	www.ultraleds.co.uk	103
Future Technology Devices, Showcase	www.ftdichip.com	98, 99, 102	USB Instruments, Showcase	www.usb-instruments.com	103
Futurlec, Showcase	www.futurlec.com	102	Velleman	www.velleman.eu	i-TRIXX backcover
Heros Technology, Showcase	www.herostechnology.co.uk	102	Virtins Technology, Showcase	www.virtins.com	103
Intronix Test Instruments	www.pcTestInstruments.com	41			
Jaycar Electronics	www.jaycarelectronics.co.uk	2			
JB Systems, Showcase	www.modetron.com	103			
JLB Electronics, Showcase	www.jlbelectronics.com	102			
KMK Technologies Ltd, Showcase	www.kmk.com.hk	102			
Labcenter	www.labcenter.co.uk	112			
Lichfield Electronics	www.lichfieldelectronics.co.uk	37			

**Advertising space for the issue of 22 January 2007
may be reserved not later than 22 December 2006**

with Huson International Media – Cambridge House – Gogmore Lane –
Chertsey, Surrey KT16 9AP – England – Telephone 01932 564 999 –
Fax 01932 564998 – e-mail: gerryb@husonmedia.com to whom all
correspondence, copy instructions and artwork should be addressed.

PROTEUS

ELECTRONIC DESIGN

FROM CONCEPT

TO COMPLETION

SCHEMATIC CAPTURE PROSPICE EMBEDDED SIMULATION PCB DESIGN

ISIS SCHEMATIC CAPTURE

A powerful capture package tailored for today's engineer and designed to allow rapid entry of complex schematics for simulation and PCB Layout.

PROSPICE MIXED MODE SIMULATOR

A customised implementation of the industry standard Berkeley SPICE 3F5 engine with extensive optimisations and enhancements for true mixed mode simulation and circuit animation.

VSM VIRTUAL SYSTEM MODELLING

The world's first and best schematic based microcontroller co-simulation software. Proteus VSM allows you to simulate the interaction between software running on a microcontroller and any analog or digital electronics connected to it. This streamlines the project lifecycle and obviates the need for expensive hardware analysis tools.

ARES PCB DESIGN

A modern and professional layout package which seamlessly integrates with the ISIS capture software. Features such as autoplacement and autorouting, interactive DRC and an intuitive interface all serve to maximise productivity and reduce time to market.

LABCENTER ELECTRONICS LTD.

A technology pioneer in the EDA industry since 1988.
Technical support direct from the program authors.
Flexible packages and pricing tailored to customer requirements.

CONTACT US NOW

to discuss requirements or
request a **FREE** evaluation copy.

Tel: 01756 753440

Fax: 01756 752857

Email: info@labcenter.co.uk

labcenter  www.labcenter.co.uk
Electronics

Labcenter Electronics Ltd., 53-55 Main Street, Grassington,
North Yorks, BD23 5AA. Registered in England 4692454