 


**SENSORS
THE WORKS**

+ The 5532 OpAmp Amplifier - part 2

elektor

www.elektor.com



+ Sensorless Motor Speed Measurement



+ Designing & Making Basic Antennas

+ Wireless Instrumentation Network

+ Real Time Gas Measurements

+ Portable Oxygen Meter

+ Camera Interval Timer

  

US \$ 7.95 - Canada \$ 7.95



Make GREAT STUFF!




TAB Books are Wired for Fun



Electricity Experiments You Can Do At Home
by Stan Gibilisco

ISBN: 978-0-07-162164-9

 


30 Arduino Projects for the Evil Genius
by Simon Monk

ISBN: 978-0-07-174133-0



Making Things Move: DIY Mechanisms for Inventors, Hobbyists, and Artists
by Dustyn Roberts

ISBN: 978-0-07-174167-5

 

Designing Audio Power Amplifiers
by Bob Cordell

ISBN: 978-0-07-164024-4



How to Diagnose & Fix Anything Electronic
by Michael Geier

ISBN: 978-0-07-174423-2



Programming and Customizing the Multicore Propeller Microcontroller: The Official Guide
by Parallax Inc.

ISBN: 978-0-07-166450-9




Programming the Propeller with Spin: A Beginner's Guide to Parallel Processing
by Harprit Sandhu

ISBN: 978-0-07-171666-6



Programming & Customizing the PICAXE Microcontroller
by David Lincoln

ISBN: 978-0-07-174554-3

 


Electronic Circuits for the Evil Genius, Second Edition
by Dave Cutcher

ISBN: 978-0-07-174412-6




Teardowns: Learn How Electronics Work by Taking them Apart
by Bryan Bergeron

 Foreword by Forrest M. Mims III
ISBN: 978-0-07-171334-4



PICAXE Microcontroller Projects for the Evil Genius
by Ron Hackett

ISBN: 978-0-07-170326-0

 

tinyAVR Microcontroller Projects for the Evil Genius
by Dhananjay Gadre and Nehul Malhotra

ISBN: 978-0-07-174454-6

Special discount for Elektor readers!

Visit www.mhprofessional.com and use promo code ELEK1110.

Learn more.  Do more.

SAVE YOUR POWER WITH

mikroC, mikroBASIC and mikroPASCAL PRO for dsPIC30/33 and PIC24 COMPILERS SUPPORTED

POWERED BY PIC24F16KA102 WITH XLP TECHNOLOGY

WIRELESS SUPPORTED

Touch Sense ON BOARD

PIC24/
dsPIC33

USB 2.0

IN-CIRCUIT
PROGRAMMER

mikroICD
IN-CIRCUIT
DEBUGGER

TOUCH
SENSITIVE



Easy24-33 v6

The **Easy24-33 v6** development system supports 14-, 18-, 20- and 28-pin PIC24 and dsPIC33 devices from Microchip. It comes with a PIC24F16KA102 (PIC24 16-bit Microcontroller featuring nanoWatt XLP™ for eXtreme Low Power consumption) designed for power constrained and battery powered applications. The system features a USB 2.0 programmer with mikroICD and many peripheral modules, such as Touch Sense, Serial RAM, EEPROM, etc, suitable for developing low power, sensor and wireless devices.

CHECK OUT our accessory boards compatible with Easy24-33 v6!



THE EASIEST WAY TO CREATE YOUR OWN LOW POWER DEVICES

MikroElektronika
DEVELOPMENT TOOLS | COMPILERS | BOOKS

...making it simple

GET IT NOW
www.mikroe.com



Privileged

When it comes to (high end) audio, Elektor has standards and a reputation to maintain. Many of our amplifier designs have reached 'legendary' status and apparently are still built. In recent years, audio as a subject has suffered under the weight of microcontroller projects, and we promise to make amends.

Unusually, our current audio amplifier project (of which the first installment appeared last month), is not a pure in-house design but originally developed by Douglas Self, a widely respected author of articles and books on the design of audio amplifiers. However in good Elektor fashion the 5532 OpAmp design was tweaked and optimized. Ton Giesberts here at Elektor Labs was asked to supervise the post engineering phase of the project. And what do you think happens if let two ambitious audio designers work together on a project? They will not take each other's word for any decibel when approaching the noise floor of the AP analyzer! Questions, comments, criticisms and amendments got sent back and forth over the past few months. Eventually this led to a design that's improved and polished in some areas; 'the best of two minds', so to speak, right up to the board design and the publication proper. The resulting project is a rather unusual power amplifier with an output stage that consists of cheap, paralleled opamps — lots of them! If you are interested, do not hesitate to build your own OpAmp. In terms of parts cost, it won't break the bank, apart from the power supply of course which is traditionally the biggest cost factor. Let us know what you think of it! My colleague Harry Baggen was the first to be able to listen to the OpAmp within the peace of his own home and he was pleasantly surprised by the performance of all those little opamps. It sure is a privilege to be an Elektor editor — with the soldering irons still smoking you can listen to the latest audio creations straight away.

Jan Buiting, Editor

- 6 Colophon**
Who's who at Elektor magazine.
- 8 News & New Products**
A monthly roundup of all the latest in electronics land.
- 14 Introducing mbed**
Our NXP/mbed Contest launch.
- 16 What's That in the Air?**
Here we tackle the theory and methods of real-time oxygen and hydrocarbon compound measurements.
- 20 MicroFuel Cell Measures Oxygen Concentration**
A must read and must have not just for divers and cave explorers.
- 24 The 5532 OpAmp (2)**
Besides construction and test results, the closing instalment also covers bridged operation and modification for 4 ohms.
- 32 Sensorless Motor Speed Measurement**
A technology is described that enables the speed of an electric motor to be measured by means of an ammeter circuit.
- 36 Wireless Instrumentation Network**
Add Maxstream and Xbee modules, stir in some Arduino and you have a measurement network with no wires.
- 41 Portable Energy**
Alternative energy sources for your cell phone, iPod and other gizmos normally operating from rechargeable batteries.
- 43 JTAG Live Buzz (E-Labs Inside)**
JTAG is increasingly used for boundary scan methods, calling for new IC architectures.
- 44 USB port from a 9-pin sub-D connector (E-Labs Inside)**
FTDI have again come up with the goods!

  

CONTENTS

Volume 2
November 2010
no. 23



20 MicroFuel Cell Measures Oxygen Concentration

We have previously described carbon dioxide sensors based on chemical and optical principles in Elektor, and an oxygen sensor complements these designs nicely. The meter described here is based around an Elektor Minimod18 micro-controller board featuring an ATmega328 microcontroller and a two-line backlit LCD panel.



24 The 5532 OpAmp (2)

This month we get real by building the 5532 OpAmp project and putting it through its paces. The test results are pleasing if not impressive and definitely put the design in the high-end audio class. Bridging and 4 ohm conversion are also described.



36 Wireless Instrumentation Network

In this project, the node consists of an Arduino nodule with an XBee shield module. The gateway also consists of these two modules, plus an EtherShield module for communication with the Internet. The resulting measurement data can be retrieved from the Pachube website.



70 Camera Interval Timer

The camera shutter operating system described here enables you to take photos at a predefined interval, or to trigger two cameras together for stereoscopic shots. This way you can take a series of photos every 30 minutes of a flower as it opens, a baby bird hatching, etc. so as to include them in a video. The system was originally designed for a Canon EOS camera, but it can readily be adapted for other cameras that are able to be remote controlled.

46 Rapid Prototyping (E-Labs Inside)

The AutoFab product from Muvium presents a new approach to circuit prototyping.

48 Image Processing Made Easy

Bluff your way into motion detection with a webcam.

54 Designing and Making Basic Antennas

It's surprisingly easy to make monopoles, dipoles and directional antennas for the 2.4 GHz ISM band.

60 Talk Show (ATM18 series)

VRBot, SpeakJet and ATM18 are the main ingredients of an experimental voice synthesizer with a giant 1-pixel indicator thrown in for fun.

66 Unilab Duo

Here we show how the Unilab bench PSU gets converted into a twin supply together with the September 2010 V/I readout.

69 Design Tips

From Microphone to Line Input

70 Camera Interval Timer

A fully programmable timer & multishot controller for photo cameras like the Canon EOS.

74 Gerard's Columns

Simulation.

75 Hexadoku

Our monthly puzzle with an electronics touch.

76 Retronics: Chauvin-Arnoux MF7 Precision Astatic Wattmeter

Regular feature on electronics 'odd & ancient'. Series Editor: Jan Buiting

84 Coming Attractions

Next month in Elektor magazine.

Elektor International Media provides a multimedia and interactive platform for everyone interested in electronics. From professionals passionate about their work to enthusiasts with professional ambitions. From beginner to diehard, from student to lecturer. Information, education, inspiration and entertainment. Analog and digital; practical and theoretical; software and hardware.



**ANALOG • DIGITAL
MICROCONTROLLERS & EMBEDDED
AUDIO • TEST & MEASUREMENT**

No. 22, NOVEMBER 2010

ISSN 1947-3753

Elektor aims at inspiring people to master electronics at any personal level by presenting construction projects and spotting developments in electronics and information technology.

Elektor (ISSN 1947-3753) is published monthly (except for one issue in July/August) at \$39.95 per year, Canada add \$11.00 per year; by Elektor International Media LLC, 4 Park Street, Vernon, CT 06066, USA. Phone: 860-875-2199, Fax: 860-871-0411. www.elektor.com

Elektor is also published in French, Spanish, German and Dutch. Together with franchised editions the magazine is on circulation in more than 50 countries.

International Editor:
Wisse Hettinga (w.hettinga@elektor.com)
Editor: Jan Buiting (editor@elektor.com)

International editorial staff: Harry Baggen, Thijs Beckers, Eduardo Corral, Ernst Krempelsauer, Jens Nickel, Clemens Valens

Design staff: Christian Vossen (Head), Ton Giesberts, Luc Lemmens, Jan Visser

Graphic design / DTP: Giel Dols, Mart Schroijen

Publisher: Hugo Van haecke
(h.vanhaecke@elektor.com)

Marketing: Carlo van Nistelrooy

Customer Services: sales@elektor.com

Subscriptions:
Elektor US, 4 Park Street, Vernon, CT 06066, USA.
Phone: 860-875-2199, Fax: 860-871-0411
Internet: www.elektor.com
E-mail: subscriptionsus@elektor.com

Elektor Personal Organizer 2011

NEW!

➔ Contents refill available separately

The Elektor Personal Organizer 2011 makes planning your appointments a real pleasure, and you always have ready access to have handy information that everyone who works with electronics needs to know.



elektor

The Organizer 2011 at a glance:

- 2011 calendar (two pages per week)
- Appointments calendar (with corner perforations) in six languages
- 60 pages of technical information on electronics
- Seven sections, separated by tab sheets
- Alphabetic address and telephone book
- Handy monthly planner
- Lined pages for your notes
- Five credit-card pockets and a pocket for business cards
- Push-button closure
- Six-ring binder mechanism
- Luxurious grey imitation-leather binding
- Free pen and SMD Tool (with complete package only)

Contents refill 2011

If you purchased the Elektor Organizer last year, the content refill for 2011 can be ordered separately for \$23.90.

ISBN 978-90-5381-259-4 • \$40.20

Contains 60 pages
of technical information
on Electronics!

Further information and ordering at
www.elektor.com/organizer

Head Office:

Elektor International Media b.v.
PO Box 11 NL-6114-ZG Susteren The Netherlands
Telephone: (+31) 46 4389444. Fax: (+31) 46 4370161

US Advertising:

Strategic Media Marketing, Peter Wostrel,
1187 Washington St., Gloucester MA 01930 USA.
Phone: 978-281-7708, Fax: 978-281-7706
E-mail: peter@smmarketing.us
Advertising rates and terms available on request.

Copyright Notice

The circuits described in this magazine are for domestic use only. All drawings, photographs, printed circuit board layouts, programmed integrated circuits, disks, CD-ROMs, DVDs, software carriers and article texts published in our books and magazines (other than third-party advertisements) are copyright Elektor International Media b.v. and may not be reproduced or transmitted in any form or by any means, including photocopying, scanning or recording, in whole or in part without prior written permission from the Publisher. Such written permission must also be obtained before any part of this publication is stored in a retrieval system of any nature. Patent protection may exist in respect of circuits, devices, components etc. described in this magazine. The Publisher does

not accept responsibility for failing to identify such patent(s) or other protection. The submission of designs or articles implies permission to the Publisher to alter the text and design, and to use the contents in other Elektor International Media publications and activities. The Publisher cannot guarantee to return any material submitted.


Disclaimer

Prices and descriptions of publication-related items subject to change. Errors and omissions excluded.

© Elektor International Media b.v. 2010 Printed in the USA

Xbee SIP adapter

Parallax's new XBee SIP Adapter (#32402; \$24.99) is a fully-assembled, small-footprint solution for interfacing the most commonly-used XBee module features with your 3.3 V or 5 V microcontrollers. With many XBee adapters on the market, Parallax gave this design very careful consideration to the specification to customize the product for educational and hobby uses. The 2 x 5 dual SIP header makes a sturdy connection to your breadboard or through-hole board, and brings the basic connections to your prototyping area without taking up a lot of space. The more advanced XBee features are still accessible, through additional headers on the module.

 

Features:


- Onboard 3.3 V regulator
- 5 V to 3.3 V logic translator buffers common I/O pins
- Six status indicator LEDs for Power, Tx, Rx, RSSI, Associate and mode (Sleep/ON)
- Small footprint dual SIP header provides support and allows easy interfacing to DOUT (TX), DIN (RX), RTS, 5 V supply and ground
- 5-pin female header connections provides interfacing to other XBee pins such as sleep, reset and associate
- A row of 10 plated through-holes with 0.1" spacing allows the option of soldering jumper wires or a header (not included) for access to the remaining XBee pins in advanced applications
- An additional plated through-hole gives access to 3.3 V output for ADC reference (VREF) when required
- Adapter board is pre-assembled — no soldering required for using most common XBee features
- Compatible with all Parallax microcontrollers, including the 5 V BASIC Stamp modules and 3.3 V Propeller P8X32A

www.parallax.com
(100639-1)

Handheld spectrum analyzer with frequency coverage up to 43 GHz

Anritsu Company introduces the MS272xC Spectrum Master series that provides the broadest frequency range ever available in a handheld spectrum analyzer. Providing frequency coverage up to 43 GHz in an instrument that weighs less than 8 lbs., the MS272xC series is also designed with an assortment of applications to test the RF physical layer, making it easier than ever for field technicians, monitoring agencies and engineers to monitor over-the-air signals, locate interferers, and detect hidden transmitters. Five models, with high-end frequency coverage of 9 GHz, 13 GHz, 20 GHz, 32 GHz and 43 GHz, respectively, are available in the new family.

The MS272xC Spectrum Master is a vastly superior product compared to existing handheld and benchtop spectrum analyzers. It eliminates the need to carry heavy benchtop spectrum analyzers into the field to measure signals above 20 GHz, such as those used in microwave backhaul applications. To further lighten the load, the MS272xC Spectrum Master is integrated with a spectrum analyzer, and can be ordered with a channel scanner and inter-

 

ference analyzer to conduct all common field measurements, eliminating the need for multiple instruments. A number of 3G/4G options can be easily incorporated into the handheld spectrum analyzers to measure LTE, HSPA+, W-CDMA, CDMA/EV-DO, GSM/EDGE, TD-SCDMA/HSDPA, and WiMAX signals.

Users can monitor and measure the spectrum quickly, as the MS2726C Spectrum Master has a fast sweep time of 27 seconds for a 43 GHz span with a 30 kHz RBW. Accuracy is not sacrificed for speed, however, as the MS2726C delivers excellent phase noise of -100 dBc/Hz at 10 kHz offset at 1 GHz and

dynamic range of 104 dB. Designed with a broadband preamplifier, the handheld spectrum analyzers have high sensitivity of -160 dBm at 1 GHz and -147 dBm at 40 GHz to detect small signals. An intuitive menu-driven screen makes it easy to conduct all measurements.


An analysis package and Anritsu's Master Software Tools provide users with the capability to conduct detailed evaluation of measurement data. Interference sources can be easily identified using built-in reporting tools, mapping, folder spectrograms, and 3D Spectrograms. These tools eliminate the need for more expensive, larger, heavier benchtop instruments, as well as third-party spectrum monitoring software. The MS272xC series utilizes the field-proven Spectrum Master design. A rugged housing can withstand the day-to-day operations associated with field use and its light weight makes it easy to carry the MS272xC analyzer up towers. It has a field-replaceable long-life battery and wide operating temperature of -10 to $+55$ degrees celcius. A large daylight viewable display makes it easy for users to see results in any environment. Display modes include a red night vision mode a black and white mode as well as two full color modes.

www.anritsu.com
(100639-VI)

6 GHz RMS power detector with digital output

Linear Technology introduces the LTC5587, an industry first 40 dB dynamic range 6 GHz RMS detector integrated with a high sampling rate 12-bit serial A/D converter. The digital output RMS RF detector provides ± 1 dB measurement accuracy of high crest-factor signals, independent of the modulation used. The detector is capable of operating over a wide frequency range from 10 MHz to 6 GHz. The integrated 12-bit ADC captures and digitizes the detector measurement at a rate of up to 500 ksamples/second and delivers the data via a bit stream over a serial SPI port. The RF detector operates with single-ended input and requires no external balun transformer. Its small 3mm x 3mm DFN package provides a highly compact solution.

 The LTC5587's ± 1 dB accuracy over a 40 dB



dynamic range and over the full temperature range from -40°C to 85°C offers best-in-class performance. Combined with a 12-bit A/D converter, the device provides 0.014 dB per bit measurement resolution. Its low power consumption is ideal for applications in cellular basestations, picocells, and femtocells supporting all standards including LTE, W-CDMA, TD-SCDMA, CDMA/2k, GSM/EDGE and WiMAX. Other applications include MIMO radios, repeaters, point-to-point microwave links, military radios with complex modulation, remote power measurements, and portable test and measurement instruments. The detector is particularly useful in FPGA-based systems where no A/D converters are available.

The LTC5587 is powered from a single 3.3 V supply. During sampling mode, its total operating current is 3 mA, consuming only 10 mW of power. Its consumption is further reduced by one-half when the ADC is idled, making the LTC5587 suitable for battery powered or portable remote RF measurement systems. The device also has shut-down capability, drawing less than $10\ \mu\text{A}$ supply current when disabled. The LTC5587 is offered in a small 3mm x 3mm 12-pin DFN package, providing a compact solution footprint. The LTC5587 is available from stock.

www.linear.com/5587

World's first ultra-thin waterproof piezoelectric speaker

Featuring a thickness of only 0.9 mm, Murata has launched the world's first ultra-thin waterproof piezoelectric speaker. Based on Murata's proprietary piezoelectric technology, the speaker is waterproof to IPX5/IPX7. The speaker measures 19.5 by 14.1 by 0.9 mm; its rectangular shape reduces dead-space from designs while its ultra-thin

dimensions contribute to greater freedom in equipment design.

Of the 50 new Japanese mobile phone models announced for 2010, almost one in four will be waterproof mobile phones, one of numerous indicators of a growing trend towards the waterproofing of mobile equipment. Given there are so many different areas that require waterproofing, there were many technical challenges and cost issues to overcome when developing the waterproof speaker. Conventional methods of waterproofing dynamic speakers used waterproof sheets which covered the output sound holes, reducing sound quality. Murata's approach incorporates a rubber film into the speaker itself, leaving the output sound holes open. The width of the


metal frame housing the speaker has been increased to improve the seal between the metal frame and the chassis, preventing water penetration.

The new waterproof speaker has been designated part number VSLBG1914E1400-



\$51^{For 3} PCBs

 FREE Layout Software!
FREE Schematic Software!



- 01 DOWNLOAD our free CAD software
- 02 DESIGN your two or four layer PC board
- 03 SEND us your design with just a click
- 04 RECEIVE top quality boards in just days

expresspcb.com

To. Its average sound pressure level (SPL) is 92.0 ± 3.0 dB (1500 Hz/2000 Hz/2500 Hz/3000 Hz average) with a resonant frequency of $1400 \text{ Hz} \pm 20\%$. Since no magnets are used, there is no possibility of malfunctions caused by iron sand, or electromagnetic effects on magnetic sensors.

www.murata.eu
(100639-IX)

Copy protection and license-management security over a single-contact interface



Maxim Integrated Products introduces the DS28E10, a challenge-and-response secure authentication IC that includes user-programmable nonvolatile (NV) memory. Authentication is implemented with the industry-proven FIPS 180-3 secure hash algorithm (SHA-1) combined with commands that operate on a programmable private secret and random challenge from a host controller. The device provides flexibility to implement private secret sizes from 64 bits to 288 bits; the host challenge size is 96 bits. These large secret and challenge sizes make algorithmic brute-force attacks to discover the private secret mathematically impractical. Because die-level probe methods are the more likely method of security attack, the DS28E10 implements proprietary circuits and methods to protect sensitive data from being captured. This authentication solution is well suited for a broad range of cost-sensitive consumer, medical, and industrial products. The DS28E10 provides 28 bytes of user-programmable OTP-EEPROM portioned with programmable protection modes. This memory can be used to store end-product


information such as calibration constants, manufacturing data, and feature settings. Additionally, a unique, unalterable, factory-programmed, 64-bit serial number (ROM ID) is included and can be used as an input parameter for authentication security functions and/or as a unique identifier for the end product.

Communication with the DS28E10 is implemented using Maxim's 1-Wire interface. The single-contact I/O interface enables the part to be easily added to a design from a spare microcontroller or FPGA port pin. The DS28E10 operates from 2.8 V to 3.6 V and is fully specified over the -40 degrees Celsius to +85 degrees Celsius extended temperature range. It is available in small, 3-pin SOT23 and 6-pin TSOC packages. An evaluation kit (DS28E10EVKIT+) is also available to assist with end application development and to program device memory.

www.maxim-ic.com/DS28E10
(100639-XIII)

3D LED cube comes in colors

 
The 3D LED Cube kit from Images Scientific Instruments (also available pre-assembled) features 64 monochromatic LEDs arranged in a 4 x 4 x 4 matrix. It is available in a choice



Multicore processor targets top-end media applications

The MIPS32® 1074K™ Coherent Processing System (CPS) is the latest coherent multiprocessor IP product from MIPS Technologies. It sets a new standard of performance within MIPS' portfolio of licensable processor core IP, delivering over 15,000 CoreMark and up to 12,000 DMIPS in 40-nm technology at 1.5 GHz. The 1074K CPS is available as fully synthesizable multicore IP that can deliver high performance using commercially available, non-custom standard cells and memories. According to MIPS, the 1074K CPS enables easy implementation of very high performance multicore systems with maximum configuration flexibility for specific features and facilitates design migration across foundries, process nodes and geometries.

The 1074K CPS is based on a combination of two high-performance technologies: coherent multiprocessing and the superscalar, out-of-order (OoO) MIPS32 74K® processor core as the base CPU. The 74K core has a multi-issue, 15-stage OoO architecture and is already in production by numerous customers for use in digital televisions, set-top boxes and a variety of home networking applications, as well as Internet-connected digital home products. To further optimize the core for this growing trend, MIPS Technologies recently enhanced the 74K core to deliver as much as 30% more performance in JavaScript and Web applications. With the 74K core at its heart, the 1074K CPS is conceived as a high-performance platform for today's SoC designs, with headroom for tomorrow's designs as well.

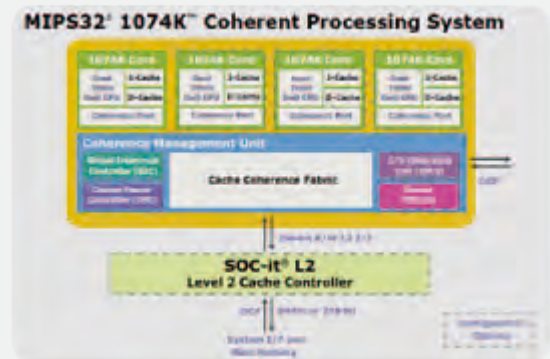

www.mips.com/products/cores/32-64-bit-cores/mips32-1074k/
(100711-III)

of four LED colors: red, green, blue and yellow.

The LEDs in the cube matrix create animated patterns that blink, morph, and change. Four buttons on the bottom of the 3D LED Cube allow the user to select the operating mode and scroll through the available 3D animation options.

The 3D LED Cube powers up in demo mode, which automatically cycles through all 29 pre-programmed 3D animation sequences. The play time in demo mode is 6 minutes and 30 seconds for all 29 sequences, after which the pattern repeats.

The 3D LED Cube measures 97 × 97 × 107 mm (3.8 × 3.8 × 4.2 in) and comes with an AC adapter. The pre-assembled version is supplied with a transparent plastic enclosure.

www.imagesco.com/led/cube.html
(100711-I)

New sensor enables wireless cardiac monitoring

In future, a miniature passive sensor implanted in a patient's heart could be used to transmit on-demand cardiac pressure readings to the attending physician. Increased pressure in the left chamber of the heart may be an indication of cardiac insufficiency or heart failure. The traditional method for measuring this pressure is cardiac angiography, in which the investigating



physician punctures an artery in the groin, inserts a catheter, and injects a contrast medium to visualize the catheter's path to the heart, where it can be used to monitor cardiac activity. The patient must remain prone in bed for the duration of this process, and the pressure in the heart chamber can only be measured during this period. Longer-term measurements under vari-

ous stress conditions would be considerably more useful, and now an innovative pressure sensor system developed by the Fraunhofer Institute for Microelectronic Circuits and Systems IMS in Duisburg (Germany) promises to make this possible. It provides up to 200 readings per second, compared to a heart rate of 3 to 4 times per second under extreme stress in an average fit adult, allowing even the smallest malfunction of the heart to be detected.

The rod-shaped sensor, measuring 2 × 10 mm, is attached to the wall of the heart with the aid of a catheter and remains in place after the catheter is withdrawn. If necessary, it can provide pressure data over a period of several months, although it transmits only on demand. Like a passive RFID transponder, the sensor only operates when the associated reader supplies it with energy by inductive coupling. The sensor does not need any form of battery. A power level of 90 µW is sufficient to take a pressure reading and transmit the data over a distance of up to 40 cm. As the sensor and its integrated antenna can only be positioned longitudinally in the heart, it must be read laterally alongside the patient's rib cage. The system operates in the 10 MHz band to minimize signal attenuation by bone, body tissues and liquids. The sensor is encapsulated in a biocompatible polymer shell that is transparent to radio waves.

www.fraunhofer.de/en/
(100711-II)

PlayStation servo motor controllers feature integrated voltage regulation

The PS-SMC-06 family of PlayStation servo motor controllers from Images Scientific Instruments Inc. enable manual control of six hobby-type servo motors (Hitec or Futaba). The servomotors are controlled by two joysticks on the controller module.

The X and Y axes of each joystick control a single servomotor, which enables the operation of four servomotors in total. The other two servomotors (numbers 5 and 6) can be controlled with the right joystick by pressing the left shoulder button at the same time. The servomotor speed is proportional to the tilt of the joystick.

Vinculum VNC2 SPEED. FLEXIBILITY. PERFORMANCE.

A programmable system-on-chip
USB 2.0 Host / Slave controller


- Dual channel USB 2.0 interface, handles all USB host and data transfer functions in single IC.
- On-chip 16-bit Harvard architecture MCU core with 256 Kbyte Flash and 16kbyte RAM.
- External UART, FIFO, SPI Slave, SPI Master, GPIO and PWM interfaces.
- Vinculum-II software development tools available for user application development.
- Multiple package size options including VNC1L backwards compatible package option.
- Targeted for range of USB applications, from portable media devices and cell phones to industrial and automotive applications.

Vinculum-II evaluation modules

- V2DIP1/2 - Miniature VNC2 Development Module with Single or Dual USB Connectors
- V2-EVAL - Complete Evaluation & Development Kit for VNC2
- VNC2 Debug Module

VISIT US AT
ELECTRONICA 2010


Hall A5, Stand 351

 

USB MADE EASY

www.ftdichip.com



 


A rumble function is activated when the servomotor reaches the end of its rotation in either direction (clockwise or anti-clockwise).

The new IPS line of servo motor controllers with integrated voltage regulation allows a variety of inexpensive power supplies to be used to operate both the controller board and the servomotors. They can be powered from a wide variety of existing power sources, including transformers, batteries, AC adapters, or anything that can supply power in the range of 6 to 30 V AC or DC. The IPS module regulates the source power to operate the servomotors efficiently. Power is input via an on-board 2.5-mm power socket. A separate 2.5-mm power plug is included for connecting the user's power source.

www.imagesco.com/servo/pssmc.html
(100711-IV)

CMOS image sensor operates over extended temperature range

Image sensors used for electronic parking assistance in cars or quality control in production systems must be able to withstand the prevailing temperature range in these environments, which can be relatively severe. To meet this demand, researchers at the Fraunhofer Institute for Microelectronic Circuits and Systems IMS in Duisburg (Ger-

 

many) have developed a CMOS image sensor for an industrial customer which can operate over a temperature range of -40 to +115 °C, unlike conventional CCD image sensors, which are often limited to an upper operating temperature of around 60 °C.

For the new sensor, the researchers developed a pixel structure with extremely low dark current. This makes it possible to capture high-quality images even at extremely high temperatures. The dark current doubles with each 8-degree rise in temperature, causing increased image noise and reducing the dynamic range of the imagery, as well as ghosting or fuzziness that degrades image quality.

Another special feature of the sensor is its

image area of 25 × 25 mm, which allows it to be connected directly to an electronic image intensifier for applications with weak illumination or image capture in the infrared or UV range. The sensor has a resolution of 256 × 256 pixels and a dynamic range of 90 dB for enhanced contrast and high detail in both dark and bright areas and provides excellent tonal rendering. Its high illumination efficiency allows the image sensor to perform well even under weak light conditions, which makes it suitable for use in night vision equipment.

www.fraunhofer.de/en/
(100711-V)

Demodulator cores for FPGAs provide advanced multichannel capability


RF Engines Limited (RFEL) has extended its expertise in digital RF channelizers to include the next processing stage of the communication system pipeline: demodulator cores. According to RFEL CEO John Summers, there is a growing demand, particularly in the surveillance market, for the ability to monitor large numbers of channels simultaneously. In response, RFEL is extending its capability in high speed channelizers for FPGAs to create a new generation of demodulator cores that efficiently complement its channelizers.

RFEL customers who are already using RFEL's multi-channel channelizer solutions have commissioned RFEL to design demodulator cores that will facilitate the simultaneous monitoring of a large number of modulated channels. Example applications include targeting over 50 channels with the limited resources of a

single Xilinx Virtex-II FPGA or handling more than 120 channels in a Virtex 6 device. The building blocks include many typical demodulation functions, such as symbol timing recovery, fine frequency/phase estimation and correction, and SNR estimation. RFEL engineers are now combining these functions to support multiple demodulation schemes simultaneously and provide parallel soft-symbol data stream outputs.

RFEL plans to release several demodulator functions as stand-alone IP that its customers can use in their own designs in the same way as RFEL has offered extensive libraries of functionality to the DSP market over the last 10 years. RFEL claim that their compact demodulator and channelizer solutions cost less than competitive products, take up a fraction of the rack space of current products on the market, and use less power. The new range of demodulator cores will be available for licensing in the fourth quarter of 2010.

www.rfel.com/ (100711-VI)

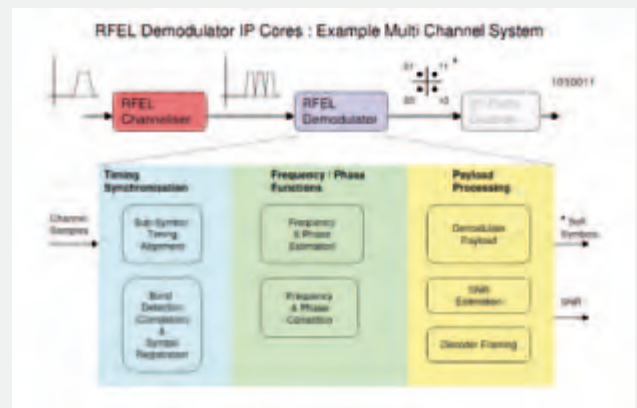

PAiA

Back-to-school discounts
on basic kits at paia.com

Electronic Kits for Enthusiasts

BUILD YOUR OWN!

PAiA 9700s
Modular Synthesizer



FatMan
Analog MIDI Synth



Theremax
The Ultimate Theremin



Check out these
and other exciting
D.I.Y. projects!


PAiA

paia.com

Music/Tutorials/Kits
Guitar Effects
Tube Electronics
Studio Gear

Item #975 \$99.95


Save 10%
with coupon code
ELEKTOR3PI4

 

3pi Robot

**A High-Performance,
Ready-to-Program
Robot for Beginners
through Experts**

 All peripherals are connected to an ATmega328P micro-controller running at 20 MHz, with free C-programming tools, libraries, and support for the Arduino environment.



- Buzzer and LEDs
- Two metal gearmotors
- Five reflectance sensors
- High-traction silicone tires
- 8x2 character LCD and 3 pushbuttons
- Speeds exceeding 3 ft/sec using innovative constant-voltage motor supply

Find out more at www.pololu.com/3pi

Pololu
Robotics & Electronics

Introducing mbed

Ready to start prototyping the mbed way? Here you learn how mbed's co-creator Simon Ford took the design from concept to creation! The mbed microcontroller and tools now make rapid prototyping a cinch.



By Simon Ford (UK)

When Circuit Cellar and Elektor approached me about running a "design challenge" around mbed, I saw an opportunity to do something special. Bringing together the mbed platform we've been developing and a gaggle of innovative engineers should be a recipe for some great results! We're setting out to help make the microcontroller world a better place by laying down a very specific, yet wide-ranging, challenge: What technology can you help unlock for your fellow innovators?

I grew up on magazines like Circuit Cellar and Elektor, and many of my early experiments were inspired by the projects people had sent in. A few years on, I wrote a couple of articles about projects I had designed, and got them published too. My hope was that the articles would serve to inspire my comrades in the same way. I was still at school at the time, so getting paid to do my hobby was a huge novelty. Interestingly, it is a novelty I have managed to keep going at ARM, and one that I plan to continue! The point: progress is all about standing on the shoulders of giants, but sometimes I wonder if the embedded world missed that memo.

I started mbed as a skunk works project with Chris, a friend from work. We were both volunteering, trying to help people with microcontroller projects, and it was really painful. You can only make so many excuses for the tools, processes, and general fiddliness until you have to step back and ask, "Why does it have to be so hard?" That led to many evenings of research and experiments to understand how we could help people get stuff done. Fast forward a few years and it has become an official ARM project and we've grown an excellent team that is making the idea a reality. But what makes me really proud is the great community springing up around it; everyone has been incredibly supportive of each other, and it is a nice reminder that engineers are fundamentally enthusiastic, inventive, selfless, and helpful.

If you haven't already seen what we are up to, take a look at <http://mbed.org>. The mbed Microcontroller is the hardware component,

taking a top-end ARM microcontroller and packaging it in a 0.1" pitch form factor with built-in USB programmer. The mbed Compiler aims to simplify tools too, making them accessible online just like webmail, so it "just works." And the developer website we're building is helping to provide the support, the resources, and the tools to allow you to share your developments, programs, libraries, and write-ups to help others get the next job done faster. This is where the challenge really kicks in.

We're looking for you to collectively enable as much technology as possible: get components talking, create a killer library, build an innovative reference design, or invent some form of interesting product prototype. This basically means anything that can be shared on <http://mbed.org> and reused by the next person to inspire and build their prototypes even faster. In reality, this is less of a competition against other developers (although that is very much encouraged!) than it is a challenge against the stranglehold of complexity and obscurity that hangs around microcontroller technology.

I'll be at Elektor Live! in Eindhoven, The Netherlands, on November 20, 2010. So, if you are around, please track me down and say hello. It would be great to hear your plans, problems, and progress first hand.

The most successful projects are ones where you scratch your own itch. Our itch was a full-on allergic reaction to all the barriers to prototyping with microcontrollers. We've tried to get things moving, and I hope you'll take up the challenge to join us. So, get yourself an mbed, get involved in the design challenge, and get building the foundations for enabling the products of the future. Help us set embedded technology free!

(100617)

Simon Ford, co-creator of mbed, is a lifelong electronics and computer engineer. He works at ARM, and before starting mbed was technical lead for the ARMv7/NEON architecture now found in most new smartphones.

To enter the NXP mbed Design Challenge 2010, go to: www.circuitcellar.com/nxpmbeddesignchallenge/

NXP
mbed
DESIGN
CHALLENGE



Start prototyping the
mbed way!



Redefine the way people build prototypes! NXP and ARM/mbed are challenging you to use the mbed NXP LPC1768 prototyping board and mbed online "Cloud" compiler to develop an innovative hardware- or software-based application. Succeed, and you could walk away with part of a prize pool worth \$10,000!

**Deadline for entries is
February 28, 2011**

Register for the challenge at
www.circuitcellar.com/nxpmbeddesignchallenge

NXP mbed Design Challenge empowered by:





What's That in the Air?

By Rolf Blijleven (The Netherlands)

Detection and analysis of gasses is a requirement for numerous branches of industry and science, from petrochemical to medical instrumentation. In this article we discuss the theory and methods of real-time gas measurements of two important groups: oxygen and hydrocarbon compounds.

All real-time gas analyzers measure partial pressure. The reading you take from a barometer is actually nothing more than the weight of the molecules in the air around us. Dry air consists of 78.02% nitrogen (N_2), 20.94% oxygen (O_2), 0.04% carbon-dioxide (CO_2) and a small amount of noble gasses and water vapor. All together, these gasses at sea level add up to a pressure of 760 mm Hg = 101.3 kPa = 1.01 bar. At higher altitudes the density of the air is less and the pressure reduces. When the weather is nice the total pressure increases — that's the high-pressure region that the weatherman always talks about. Unless there is a severe frost, the air is usually not dry, but has a certain humidity, which is usually expressed as a Relative Humidity (RH) in percent.

Principles of gas measurements

Before the gas can be measured, steps have to be taken to prevent water vapor from being included. In addition, you don't want the gas in the analyzer to be stationary: you are usually interested in changes of the gas concentrations. That is why gas analyzers nearly always take samples using a sample-pump, which draws the gas through the analyzer. Furthermore, an analyzer needs to be calibrated and you are usually also interested in the flow rate through the analyzer, so that you can calculate the *concentration* of the measured gas. **Figure 1** shows the diagram of a typical gas analyzer. At the far right is the sample-pump, which draws the gas through the analyzer. A pressure sensor is connected with a T-coupling in front of the analyzer. This measures the barometric pressure when the sample-pump is off. You need to know this so that you can calculate the partial pressure. When the sample-pump is on, the sensor gives an indication of the flow rate through the analyzer(s).

Moisture problem?

Before the gas enters the analyzer, it passes through a sample tube. These things come in different variations. Sometimes it is a column of anhydrous (containing no water) calcium sulphate, which absorbs

all water vapor. In other cases it is a cooling chamber, which ensures that the water vapor condenses and which can then be drained as liquid water. A third, very common method uses Nafion, a derivative of Teflon, which has a very high permeability to water. Make this into a tube and the tube will then ensure that the concentrations of water molecules on the inside and outside are nearly identical.

An analyzer is usually calibrated in two places: zero and range, that is, at the zero point and at the upper limit of the measuring range. This requires two bottles of calibration gas, the gas concentrations of which are accurately known. First one and then the other calibration gas is sent through the analyzer. The gas that comes from the bottle has an RH = 0%. At the end of the sample tube this dry gas is humidified to the RH in the room: ambient, in jargon. After the calibration, the sampling is switched to the measuring input. When you measure air from the room, the RH does not change, ambient remains ambient. When you measure gas with a higher RH, such as exhaled gas, then at the end of the sample tube that gas has dried out and again has the same RH as the ambient. The analyzer therefore always 'sees' a gas with the same humidity, so this uncertainty is now eliminated from the measurement!

In some cases it is sufficient to have only one calibration gas. When calibrating oxygen, we can assume that the ambient air contains 20.94% O_2 . This number is virtually constant across the entire world, thanks to the production of oxygen by tropical forests and oceans. However, this is certainly not true for CO_2 . After a day in a meeting room with all the windows closed the amount of CO_2 can easily increase to one percent.

Sufficiently fast and sensitive?

Gas analyzers are usually not fast, a speed of response measured in minutes is not at all unusual. For some applications — such as the three-gas measurement for the annual car certification — this is not a problem. In other cases, a response time shorter than 150 milliseconds is a necessity, monitoring anaesthetics is an example. While

Real-time gas measurements with special sensors


it is possible to design analyzers with improved response time this is sometimes still not sufficient. The solution is software, the operating principle is outlined in **Figure 2**. With a step-change of input signal, the response time is generally accepted as being the time (t_1) required for the output to reach 90% of the full swing. But you can also just sample the beginning of the output signal as soon as it starts to increase and based on the rate of change in that region estimate what the final value will be. Response times in the order of 90 ms are possible. Pure guesswork? It is not that bad: the result of this 'guess' can be verified during the calibration. The disadvantage of this method is that the equipment usually has to be calibrated before each measurement.

As most readers will know already, the sensitivity of gas analyzers is usually expressed as parts per million, ppm. One litre of water (1 kg) polluted with 1 milligram of lead has a lead concentration of 1 ppm.


With this basic knowledge let's take a look at a few types of practical gas analyzers.

Oxygen

Electrochemical gas sensors have been around since the 1950s. The operating principle is illustrated in **Figure 3**. The gas is pumped through the top of the cell past a membrane and diffuses through it into an electrolyte. The membrane is hydrophobic, literally 'scared of water', and ensures that the electrolyte does not leak out. At the bottom of the electrolyte is an anode made from lead (Pb) or cadmium (Cd) which oxidizes. This releases electrons, which travel to the cathode via an external circuit, where they are consumed by the oxygen molecules. The chemical reactions are as follows. With an acidic electrolyte:

 

and with an alkaline electrolyte:

 

The total reaction in both cases is: $2\text{Pb} + \text{O}_2 \rightarrow 2\text{PbO}_2$. The oxidizing reaction consumes the anode material, so this type of cell will not last forever. If the sensor is continually exposed to high oxygen concentrations then its life expectancy will be shortened.

There is a lot of choice in oxygen cells. The life expectancy of most cells is around one and a half to two years, but, for example, the KS-50 from the Japanese JS Yuasa [1] has an extremely long life expectancy of 10 years at 21% O_2 and 20°C. The response time is quite slow at 60 s, response times of 6 to 10 s are more usual [2]. Teledyne calls its A-1, for industrial applications, with less than 4 s, ultra fast [3], but for medical application Teledyne can also supply the UFO-130-2 (**Figure 4**), which at 130 ms is another 30 (!) times faster. A measuring range of 0 to 100% O_2 is typical, but a smaller range, from 0 to 30% is also common.

 


Figure 1. Functional diagram of gas detection.

 


Figure 2. By measuring the shape of the slope at the start of the rise time the response time can be improved.

 


Figure 3. Functional schematic of an electrochemical oxygen cell.



Figure 4. The UFO-130-2 oxygen sensor from Teledyne has a very short response time of 130 ms (photo: Teledyne).

 


Figure 5. A CO₂ molecule.

 


Figure 6. The principle of infrared gas detection (see text).

Hydrocarbons and family: non-dispersed infrared

Gas molecules consist of atoms. Figure 5 shows a carbon-dioxide atom (CO₂), but such a picture also applies to carbon-monoxide (CO), nitrogen-dioxide (NO₂), nitrogen-monoxide (NO), ozone (O₃), methane (CH₄), sulphur-dioxide (SO₂), etc. The bond between atoms has one or more resonant frequencies which are a characteristic of a particular molecule and so for the gas of interest. Infrared (IR) is a generic term for radiation with a wavelength of 0.75 μm near the visible red light up to about 1000 μm for far infrared (FIR). Heat radiation or thermal IR has a wavelength of about 3 tot 15 μm.

When a gas is radiated with infra red energy in that spectrum, then gas molecules will absorb energy at their characteristic resonant frequencies. At the other end of the gas we detect the remaining IR-energy. From the frequencies that are no longer present, follows which gas has been detected.

The generation of radiation with a frequency range of 3 tot 15 μm is possible using bundled infrared light which passes through a prism, so that the radiation is dispersed into a range of wavelengths. This is called dispersed infrared, but is not very common in practice. Non-dispersed infrared (NDIR) is by far the most common method of IR-detection, the principle of which is illustrated in Figure 6.

At the far left is the IR source. This can be a simple IR-LED, an incandescent lamp that gives off a little heat, or a special IR-source [4]. This light passes through the gas in the sample cell, at the other end of which is the detector. Filter B, usually made from coloured glass, forms a band-pass filter, the center frequency if which is equal to that of the gas to be detected. This filter can also be placed in front of the IR source, in the position of filter A.

The gas sample normally also contains other gasses which also absorb a small amount of IR, but we do not want to detect those. The absorption spectra of CO and CO₂ are right next to each other (Figure 7). Say we want to measure CO, but the gas sample also contains CO₂ and the combination of detector and band-pass filter is not selective enough. A solution is to place a block of 100% CO₂ after the IR source, in the position of filter A. This acts as a steep band-stop filter: all IR energy that the CO₂ can absorb is completely absorbed before the radiation enters the sample cell; how much CO₂ that contains is now no longer relevant. In this way the detector contains a signal related only to CO.

All gas analyzers have unavoidable problems with fluctuation of the zero point (zero drift). In addition, the signal from the gas is buried deep in noise — not unexpected if you want to measure 0.3% gas. The most popular solution for this is shown in Figure 8. The chopper is a rotating disk with a hole in it. An IR beam passes through this hole onto the concave mirror on the left, and in turn through the sample-cell followed by the reference cell. By subtracting one signal from the other it is possible to automatically compensate for zero drift and eliminate the noise. Furthermore, the IR radiation takes a longer path, which results in greater absorption and improves the signal.

Because of all the mechanical parts such an analyzer is quite size-able, count on a box of about 20x10x10 cm. Thanks to mathemati-

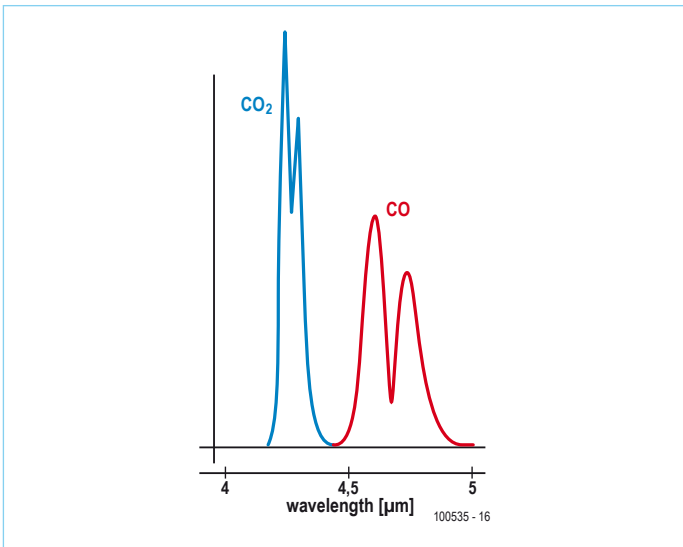


Figure 7. The absorption spectra of CO and CO₂ are right next to each other.

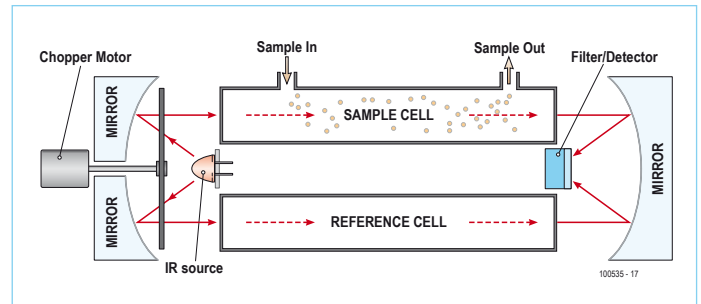


Figure 8. Infrared analyzer with chopper motor, reference cell and concave mirrors (source: [8])



Figure 9. The ZG-02 IR-module from ZyAura (photo: ZyAura)

 


Figure 10. This detector from Shinyei uses IR light for the detection of dust particles and pollen.



Figure 11. The SensorChip-CO₂ is a MEMS chip for measuring CO₂ (photo: ICX Technologies).

cal noise reduction and fast Fourier analysis (FFT, Fast Fourier Transform) the chopper and reference cell can be omitted. Miniature versions of the design of **Figure 5** are now possible, such as the ZG-01 and ZG02 IR modules from ZyAura [7] (**Figure 9**), which we used in our CO₂ monitor in the May 2010 edition of *Elektor*. The Japanese Shinyei uses the principle of IR detection in integrated detectors for dust particles and pollen [5], fully integrated with sample-pump and measuring cell on a board measuring about 6 by 5 cm (see **Figure 10**).

And those are not the only ones. ICx Technologies came in 2006 with the SensorChip-CO₂ (**Figure 11**), an integrated MEMS chip (Micro Electro-Mechanical System). This sensor measures 0.45 cm square, has a response time of less than one second, uses only 70 mW and detects CO₂ from 0 to 100% with a resolution of better than ±50 ppm [6].

Detection of gasses is a subject on its own with many specializations. In this article we showed a few of the common techniques. As a matter of course this also involves a lot of pneumatics and mechanics. We hope you have enjoyed this overview crossing the borders off the purely electronics domain.

(100535-1)

Sources and Internet links

1. www.gs-yuasa.com/gyid/us/products/ke_series/index.html
2. www.aii1.com/Rep_O2_sensors.htm
3. www.teledyne-ai.com/industrialsensors.asp
4. <http://photonics.icxt.com/index.php?page=pulsir>
5. www.shinyei.co.jp/STC/optical/dust_e.html
6. <http://photonics.icxt.com/uploads/files/Datasheets/SensorChipCO2-ds.pdf>
7. www.zyaura.com/products/ZG%20module.asp
8. [www.intlsensor.com/pdf/infrared.pdf](http://intlsensor.com/pdf/infrared.pdf)
9. <http://intlsensor.com/pdf/electrochemical.pdf>

Micro Fuel Cell Measures Oxygen Concentration

By Helge Weber (Germany)



Oxygen makes up about 21 % of the air in the atmosphere.

Normally we take this for granted but for some, oxygen concentration can be a matter of life and death. For a diver it is essential to know the oxygen concentration in the breathing gas in his cylinder, and a cave explorer needs to know the oxygen level in the ambient air he is breathing. This article describes an oxygen concentration sensor and how to process its output.

We have previously described carbon dioxide sensors based on chemical [1] and optical [2] principles in *Elektron*, and an oxygen sensor complements these designs nicely. The meter described here is based around a Minimod18 microcontroller board [3] featuring an ATmega328 microcontroller and a two-line backlit LCD panel.

Background

Hypoxia (inadequate oxygen supply to the body) can lead to life-threatening situations, in particular for divers and cavers. Symptoms range from a general reduction of awareness through uncontrolled movements to complete loss of consciousness. In such cases medical treatment involves providing emergency respiration, ideally with 100 % oxygen.

Oxygen concentration meters are useful in recreational diving. On many dives these days a breathing gas is used with a higher

concentration of oxygen than that found in atmospheric air. These 'nitrox' [4] mixtures usually have an oxygen level of between 22 % and 40 %. A further application is in so-called 'rebreathers' used by divers.

It is vital for divers to know the concentration of oxygen in the gas they are to breathe. If the concentration is more than 1 % away from the correct value the gas should not be used: the discrepancy must be checked and the dive planned afresh.

The oxygen meter described here will give a sufficiently accurate indication of the oxygen concentration of the gas in scuba breathing equipment.

A second use for the oxygen concentration meter is in caving, for example to monitor the oxygen concentration in the air in a cave. European standard EN50104 for 'Electrical apparatus for the detection and measurement of oxygen' applies in this case. Oxygen meters used for professional pur-

poses must behave according to the specifications in this standard and be tested against it. Hazards when caving include dangerously high levels of gases such as CO, CO₂, CH₄ and H₂S as well as reduced levels of oxygen. The oxygen meter can thus be a useful addition to gas detector tubes and other monitoring devices.

Principle of operation

Oxygen can be detected relatively straightforwardly using an electrochemical sensor [5][6], also known as a micro fuel cell. The method was first used (and patented) in 1964 for medical applications by the American company Teledyne Analytical Instruments as a sensor in artificial respiration systems.

The internals of the sensor (**Figure 1**) are based around a Teflon membrane with a gold cathode and a lead anode. Oxygen gas molecules diffuse through the Teflon membrane and are electrochemically reduced

Portable oxygen meter using the Minimod18

at the gold cathode. The electrons for this reduction are provided by oxidation of the lead cathode, resulting in a flow of anions and cations between the electrodes. This ion flow corresponds to a current which will increase in magnitude as more oxygen molecules diffuse. The current flow is turned into a voltage using a resistor, and the output of the sensor is in the region of a few millivolts. The transfer characteristics of the sensor change with age (**Figure 2**).

In normal atmospheric air the output voltage of the sensor lies somewhere between 7 mV and 13 mV, rising linearly with increased oxygen concentration. The lifetime of a micro fuel cell sensor of this type varies from manufacturer to manufacturer and depending on the environment in which it is used, and is typically two or three years.

The meter circuit

The first task is to convert the output of the sensor into a level suitable for input to the A/D converter in the microcontroller. Alternatively, if the sensor is to be used without the microcontroller circuit, the output of the front-end can be connected directly to a millivoltmeter capable of displaying voltages from 0 mV to 199.9 mV. The conversion is done using an operational amplifier

connected in a non-inverting configuration. **Figure 3** shows the complete circuit of the front-end stage built around an OP90 [7], with the output taken to the A/D converter input of the microcontroller or to the millivoltmeter as appropriate.

The gain A of the amplifier is set by feedback resistors $R1$ and $R2$ and is given by the formula $A=1+(R2/R1)$. The values given in the circuit diagram result in a gain of 16. Offset compensation of the opamp in **Figure 3** is done by $R3$ and $R4$. If the output of the opamp is being used to drive a millivoltmeter for display purposes it is worth connecting a trimmer to pins 1 and 5 and adjusting it to cancel the offset voltage of the opamp. Furthermore, a second trimmer potentiometer can be added in series with resistor $R2$, to allow the output voltage to be set to exactly 20.9 mV in atmospheric air so that the concentration can be read directly from the meter's display.

Construction

The Minimod18 is at the heart of the meter unit. The module includes everything needed for rapid and trouble-free system



Figure 1. Sensor with adapter for connecting to a diver's breathing kit.

construction and integration. The oxygen sensor itself is built into the enclosure (see **Figure 5**).

The front-end circuit of **Figure 4** can be assembled on a piece of prototyping board. All the required connections are to K1 on the Minimod18 board:

pin 1	AREF	reference voltage connection
pin 2	+5 V	power supply
pin 3	ADC6	sensor signal
pin 9	GND	power supply

 


Figure 2. Typical characteristic curve of an oxygen sensor.

 


Figure 3. Front-end amplifier circuit to interface the oxygen sensor to an A/D converter.

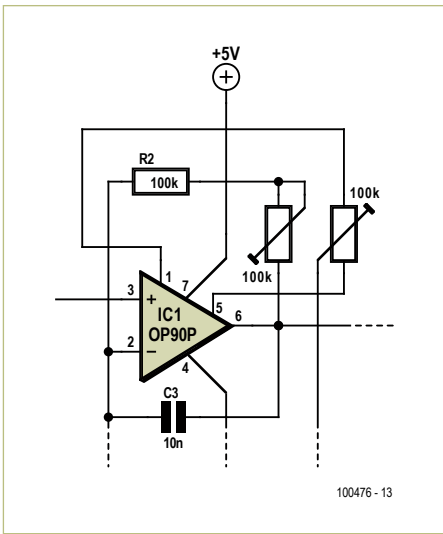


Figure 4. If a millivoltmeter is to be used as a display readout, two calibration potentiometers should be added to the amplifier circuit.

A suitable voltage reference is the LM336-2.5V from National Semiconductor [8]. The amplified sensor signal must of course be calibrated against the reference voltage. The other pins can be used for further expansion. For example, pin 4 (ADC7) could be used to connect another sensor; other inputs could be used to add buttons and so on.

Software

Software for the Minimod18 can easily be written using, for example, BASCOM AVR or CodeVisionAVR. In this case, the author developed software for the prototype

using BASCOM. Figure 6 gives an overview of the program as a flowchart; source and hex files for the project are available for download from the *Elektor* web pages for this article [9]. Two versions of the code are available: the first is intended for use as a breathing gas (nitrox) analyzer; the second is designed for monitoring ambient oxygen levels in air.

The unit can be calibrated using either a one-point method or a two-point method. In the one-point method we assume that the sensor plus front-end circuit have a linear characteristic that passes through the



Figure 5. View of the prototype.

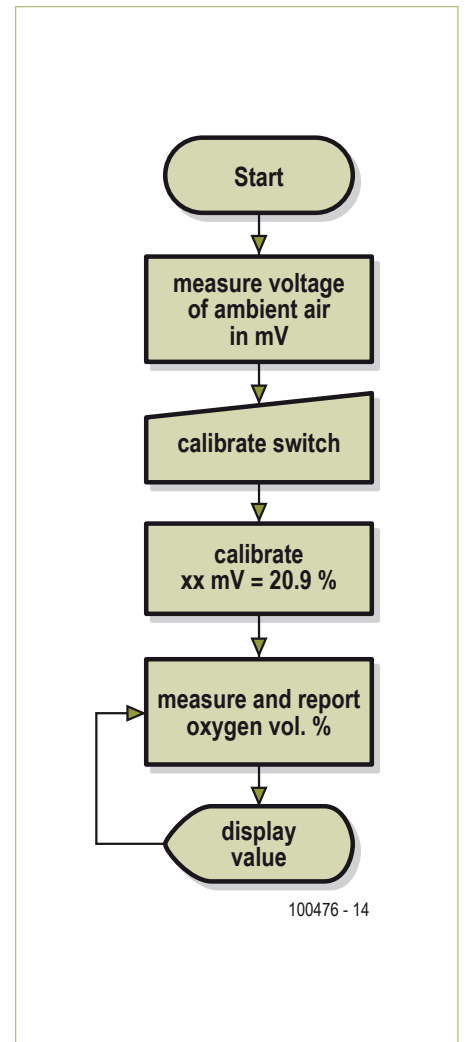


Figure 6. The flowchart illustrates the simple structure of the program.

origin, and so we only need to calibrate the meter to one other point, for example the 20.9 % concentration of oxygen in ordinary atmospheric air.

However, the circuit might exhibit an overall offset, with the straight-line transfer function not passing exactly through the origin. In such cases a two-point calibration gives better accuracy. A reference gas sample, ideally pure oxygen, is needed. The first calibration point is the reading in atmospheric air (concentration 20.9 %, as stated above), and the second point is the reading in the reference gas, with known oxygen concentration. It should be noted that even this process is not perfectly accurate, as the oxygen concentration in atmospheric air is not exactly 20.9 % since the partial pressure of oxygen varies with barometric pressure, humidity and temperature. Inaccuracy due to these effects can however be neglected in the two applications we are considering here.

The unit in practice

A suitable gas sampling device is needed to use the unit to measure the oxygen content of breathing gases. One option is the 'Quick Ox' [10].

When using the unit to monitor ambient air it is a good idea to add warning indicators using LEDs and a buzzer. The author fitted three LEDs to his prototype. A green LED lights when the ambient oxygen concentra-

About the author

Helge Weber is a power electronics engineer and works as a site manager specialising in metallurgy. In his free time he is a rescue diver and diving teacher with the German Life Saving Association.

tion is close to the normal level of 20.9 %. If the concentration falls below 19 % a red LED lights, and if the concentration further falls to below 17 % the buzzer also sounds. A blue LED lights to indicate a concentration of above 22 %, which is useful when checking for leaks when refilling or mixing with oxygen.

The source code can be freely modified to implement further functions. As we have

seen, the hardware required to make an oxygen meter is minimal: just the sensor, an opamp and either a millivoltmeter, or for more sophisticated applications, the Mini-mod18 and a voltage reference.

(100476)

References and links

- [1] Elektor January 2008: <http://www.elektor.com/070802>
- [2] Elektor May 2010: <http://www.elektor.com/100020>
- [3] Elektor January 2010: <http://www.elektor.com/090773>
- [4] <http://en.wikipedia.org/wiki/Nitrox>
- [5] www.teledyne-ai.com/oem/diving.asp (Teledyne oxygen sensors)
- [6] www.aii1.com/Rep_O2_sensors.htm (Analytic Industries oxygen sensors)
- [7] www.analog.com/static/imported-files/data_sheets/OP90.pdf (opamp datasheet)
- [8] www.national.com/ds/LM/LM136-2.5.pdf (voltage reference datasheet)
- [9] www.elektor.com/100476 (pages for this article, including downloads)
- [10] www.vandagraph.co.uk/?page=catagory&cat=294&subcat=296 (Quick Ox gas sampling adaptor)

Advertisement



Take out a free subscription to E-weekly now!

Do you want to stay up to date with electronics and computer technology? Always looking for useful hints, tips and interesting offers? Subscribe now to E-weekly, the free Elektor Newsletter.

- Your benefits:**
- The latest news on electronics in your own mailbox each Friday
 - Free access to the News Archive on the Elektor website
 - You're authorized to post replies and new topics in our forum



Register today on
www.elektor.com/newsletter

The 5532 OpAmplifier (2)

Part 2: construction, bridged operation and test results

By Douglas Self (UK) and Ton Giesberts (Elektor Labs)

In this second and closing installment we get real with two times 32 NE5532 opamps paralleled to form a high-end audio power amplifier with eminent specifications in terms of distortion and general sonic performance. There are also challenges for you: bridged operation for higher output power, and modifying the amplifier for 4-ohm operation.

If you thought that paralleling a few dozen NE5532 opamps is a curious way of designing a high-end audio amplifier and typical of Elektor's off-the-beaten track approach to electronics you are probably right. Last month's design considerations did not fail to trigger responses from you, our readership, in particular from all and sundry aspiring or even claiming to be a high-end audio designer. This month we get real by building the 5532 OpAmplifier project and putting it through its paces.

Construction — amp board

The amplifier proper is built on a double-sided through plated circuit board of which the component overlay is shown in **Figure 1**. Two of these boards are required for a stereo amplifier. Boards supplied by Elektor come with through plating, a solder mask and holes predrilled. As such they are the best guarantee for success in replicating the project. While on the subject of quality, you are looking at an expensive, high-end amplifier. If you use mishmash components and *ditto* assembly methods and tools, you'll get mishmash results. More on selecting the best NE5532 brand to use in the **inset**.

Construction on the 205 × 84 mm board should not present problems as only standard through-hole parts are used. A properly functioning amp can be expected if you work with care and precision, like Ton Giesberts of Elektor Audio Labs who designed, built and tested all the boards pictured. Some notes and *caveats* deserve mentioning, however.

Most resistors are mounted vertically. Use a uniform method of bending the long terminal twice to obtain right angles. Semicircles indicate where the resistors sit on the board. Where rectangles are printed, the resistor is mounted flat on the board.

Although it's possible to solder all opamps directly on the board, you do so at a risk (see part 1), hence the prototype was built using turned-pin 8-way DIL sockets for all opamps. It is essential to use premium quality sockets here — don't be tempted to use cheap ones with dodgy spring contacts; it is false economy.

The tallest components on the board are capacitors C2, coil L1, relay RE1 and the screw terminal blocks for the loudspeaker and supply connections. The coil consists of 10 turns of 1 mm diameter (AWG18) enamelled copper wire (ECW) with an internal diameter of 20 mm. The coil windings should be spread evenly to obtain an overall length to suit the footprint on the board. Fit the coil first, then R106 at a height of 5-10 mm above the board surface and not touching L1 anywhere.

Although printed on the silk screen PCB overlay, **capacitors C24, C25, C26 and C27 are not fitted**. Instead, a single 1,000 µF, 63 V electrolytic capacitor is used, its terminals being inserted directly into terminal blocks K16/K17 (observe the polarity and provide the leads with sleeving for insulation). This should be a high quality electrolytic capacitor with low ESR. The modification proved necessary to get rid of unex-

pected distortion levels occurring at about 20 kHz in the initial design and was found to totally cure the problem. The amplifier specifications printed last month apply to the capacitor-modified version only.

The four corners of the amplifier board have holes for PCB standoffs — we used 10 mm tall ones.

The finished amplifier board should be given a thorough visual inspection before taking into use. Did you get all the polarized components' orientations right? Are all solder joints beyond reproach? It often helps to have a friend look at the board. **Figure 1** once again shows the amp board for your reference. See how close you can get to this level of sophistication in building high-end audio circuitry.

Construction — PSU board

This is also a classic board with nothing but standard components, hence should be easy to assemble and get working. It's just the heatsinking of the voltage regulators that requires some mechanical work.

The two bridge rectifiers B1 and B2 should be fitted with 2 mm thick 70 × 35 mm aluminium plates bolted directly to the flat sides. The two voltage regulators IC1 and IC2 are secured to a single black, finned, extruded aluminium heatsink of which the mounting outline is shown on the component overlay. The heatsink is secured to the board with three M4 screws or bolts, for which holes need to be drilled and tapped in the underside. Venting holes are provided in the PCB area under the heatsink

 


Figure 1. Perfect sound from perfect construction. Can you match it? Please note that capacitor positions C24–C27 must remain empty.

 


Figure 2. The power supply board is conventional as far as construction and assembly is concerned, but do make sure you get the mounting of the heatsink and the voltage regulators right. An ABS suitcase as shown here is not recommended as a permanent housing for the amplifier.

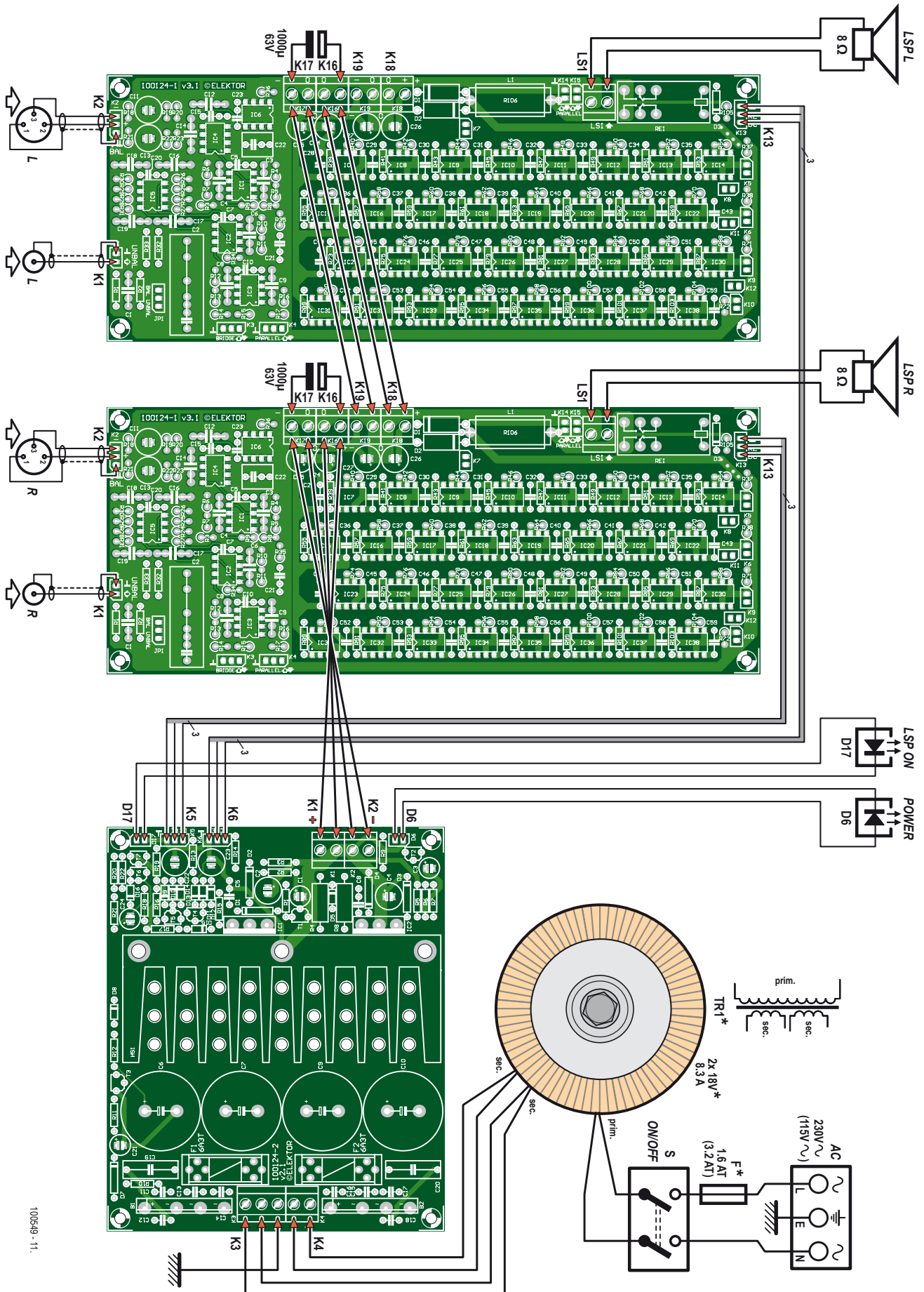


Figure 3. OpAmp wiring diagram. Note that this is for the 2 x 15 watts, 8-ohm version. The electrical ratings of the toroidal transformer and the fuse should match your local AC line voltage. High amps and loudspeaker connections are shown in slightly thicker lines.

Masterclass #1: Extension of design for 4 ohm speakers

It is an inherent property of the 5532 power amplifier that its output current is limited by the internal overload protection of the opamps used. This means that if more current is needed in the load, you need to put more opamps in parallel. The basic design is intended to drive 8 Ohm loudspeakers with a reasonable safety margin, but as it stands it is definitely not recommended for 4 ohm operation.

To extend the 5532 amplifier for 4 ohm operation, it is necessary to double the number of 5532 sections driving the output. This is easier than it might sound because facilities are provided for adding one or more power amplifier PCBs in parallel. The connector K4 (see circuit schematic published last month) is used as an output from the main power amplifier PCB; it comes from the ‘zero-impedance’ stage IC3A, so the output is at a very low impedance (I measured 0.24 ohms at 1 kHz) but is immune to HF instability caused by cable capacitance. Any desired length of cable can be used. The output from K4 drives an identical power amplifier PCB that has the all the output opamps in place, but the redundant input amplifier circuitry

omitted. The equivalent connector K4 on this PCB is used as an input, and drives the output opamps in exactly the same way as on the main power amplifier PCB.

The connectors K14, K15 are used to connect together the outputs of the two amplifier PCBs. Note that this connection is made upstream of the output muting relay RE1, to preserve full protection for the loudspeaker in case of a DC fault.

While this conversion for 4 ohm operation is relatively straightforward, it is essential to remember that the power supply requirements are doubled along with the current output. You will need to consider a larger power transformer, more capable rectifiers, larger reservoir capacitors, and increased supply regulator capacity. In view of these various requirements, this 4 ohm version is mentioned here more as an option for the experimenter rather than a fully cut-and-dried design.

 


Figure 4. The OpAmplifier was duly ‘grilled’ on our AP System 2 analyzer.
Graph (a): THD & noise vs. output power. Graph (b): distortion vs. output power (1 kHz, BW = 22 KHz).
Graph (c): FFT graph for 1 kHz, 1 watt, 8 ohms.

to assist cooling. The LT1083CP devices are secured to the heatsink with a heat conducting washer inserted. Two holes have to be drilled for the M3 bolts and nuts that hold the regulators firmly on the heatsink. First, determine the location of the holes for the regulators; then secure the heatsink to the board. The regulator terminals should be ‘kinked outward’ slightly for thermal relief. The two LT1083 regulators should be mounted, secured and soldered last.

Figure 2 shows the PSU board in a “travel & demo” version of the amplifier. PCB stand-

offs are used as with the amplifier board. The PSU can be tested (carefully) by temporarily connecting the secondaries of the toroidal transformer to the AC input terminals and checking for the correct output voltage of $18.0\text{ VDC} \pm 0.7\text{ V}$ on each rail.

The complete amplifier

The OpAmplifier should be built into in a metal case observing all relevant precautions in respect of electrical safety, specifically with respect to earthing and the use of wiring carrying the AC grid voltage (230 V or 115 V). The size and shape of the

case will depend on the number of amplifier boards used, as well as the associated power supply, see the **insets on bridged operation and 4-ohm conversion**. Allow for quite some heat developing in the amplifier case, from the heatsink as well as from the NE5532s. All those milliwatts add up!


Everything ahead of the bridge rectifier AC terminals should be built, secured and wired with the high currents and voltages always in mind. If possible, do not extend the transformer wires. The amplifier wiring diagram for the 8 ohm 2 x 15 watts

Masterclass #2: Extension of design for bridged operation

Two power amplifiers are bridged when they are driven with anti-phase signals and the load connected between their outputs; the load is not connected to ground in any way. This method of working doubles the signal voltage across the load, which in theory at least quadruples the output power. It is a convenient and inexpensive way to turn a stereo amplifier into a more powerful mono amplifier. Most conventional power amplifiers do not give anything close to power quadrupling- in reality the increase in available power will be considerably less, due to the power supply sagging and extra voltage losses in the two output stages, which are effectively in series. In most cases you will get something like three times the power rather than four times, and it may be less. I have come across many power amplifiers where the bridged mode only gave twice the output power, and it has to be said that in many cases the bridged mode looks like something of an afterthought.

The 5532 power amplifier will give better results than that for two reasons — firstly the power supply rails are regulated, and will not droop significantly under heavy loading. Secondly, the parallel structure minimises voltage losses; for example, all the 1 ohm output combining resistors are in parallel and their effective resistance is therefore very small.

 Bridged mode is so called because if you draw the four output transistors of a conventional amplifier with the load connected between them, as in **Figure A**, it looks something like the four arms of a Wheatstone bridge.



In the drawing, the 8 ohm load has been divided into two 4 ohm halves, to emphasize that the voltage at their center is zero, and so

as far as current output is concerned, both amplifiers are effectively driving 4 Ohms loads to ground. The current capability required is therefore doubled, with all that that implies for increased losses in the output stages. A unity-gain inverting stage is shown generating the anti-phase signal; there are other ways to do it but this is the most straightforward and it simply adds one more 5532 section to a design that already contains quite a few of them. The simple shunt-feedback unity-gain stage shown does the job very nicely, and the 5532 power amplifier incorporates a version of this circuit. The resistors in the inverting stage need to be kept as low in value as possible to reduce their Johnson noise contribution, but not of course made so low that the opamp distortion is increased by driving them. The capacitor C1 across the feedback resistor R2 assures HF stability — with the circuit values shown it gives a roll-off that is -3 dB at 5 MHz, so it does not in any way imbalance the audio frequency response of the two amplifiers.

You sometimes see the glib statement that bridging always reduces the distortion seen across the load because the push-pull action causes cancellation of the distortion products. It is not true. Push-pull systems can cancel even-order distortion products; odd-order harmonics will not be cancelled.

The 5532 power amplifier has facilities for bridging built in. The last stage in the input amplifier is the inverting stage around IC3A, which is needed to get the phase between amplifier input and output correct. If we take the signal off from before this stage, then it is inverted with respect to the amplifier output and can so be used to drive another power amplifier board in anti-phase; this PCB can be built with the input amplifier circuitry omitted, as for the 4 ohm conversion described above. This inverted signal is available at connector K3. The loudspeaker is connected between the two output terminals on the amplifier PCBs and the output ground terminals are not used. As explained above, driving an 8 ohm load with two bridged power amplifiers means that each amplifier is effectively driving a 4 ohm load to ground, so to take full advantage of the bridging capability requires the output stages to be doubled up, so that there are two power amplifier PCBs in parallel driving in-phase, and two power amplifier PCBs in parallel driving in anti-phase. This is of course quite a serious undertaking, as the number of output opamps has been doubled for bridging, and then doubled again to give adequate output current capability. The power supply capability will also need to be suitably increased.


stereo version of the amplifier is shown in **Figure 3**. The rating of the AC power fuse should match the line voltage in your area (115 V/60 Hz or 230 V/50 Hz). Whichever, an approved IEC style appliance socket with integral fuseholder and double-pole rocker switch **must be used**.

We should emphasise that the 8.3-amp toroidal transformer indicated in the

drawing is advised for the 2 x 15 watt, 8-ohm version of the OpAmplifier. A much beefier transformer is required if you decide to build a 4-ohm or bridged version of the amplifier. As with nearly all audio power amplifiers, it's essential to have a good deal of spare capacity in the 'amps department' so do not skimp on the transformer.

The test results

 The basic concept behind the 5532 power amplifier is to create an amplifier which has the very low distortion of the 5532 opamp. Preserving this performance when large currents are flowing to and fro on a circuit board is something of a challenge and requires very careful attention to grounding topology, supply-rail routing, and



COMPONENT LIST

Amplifier board (one channel)

Resistors

5%, 0.25W, Farnell/Multicomp MCF series, unless otherwise indicated.

R1, R14, R17 = 47 Ω
 R2 = 220k Ω
 R3 = 47k Ω
 R4, R6 = 910 Ω 1% 0.25W, Multicomp type MF25 910R
 R5, R7, R10, R11, R15, R16 = 2.2k Ω
 R8, R9, R32, R33 = 10 Ω
 R12 = 1k Ω
 R13 = 2.00k Ω 1% 0.25W, Multicomp type MF25 2K
 R18, R21 = 150k Ω
 R19, R22 = 100 Ω
 R20, R23 = 68k Ω
 R24-R31 = 820 Ω
 R34, R35 = 10M Ω
 R36 = 100k Ω
 R37, R38, R71, R72 = 22k Ω

R39-R70, R73-R104 = 1 Ω
 R105 = 10k Ω
 R106 = 10 Ω 5% 3W, Tyco Electronics type ROX35J10R

Capacitors

C1, C12, C14, C16-C19 = 100pF, 2.5%, 160V, polystyrene, axial (LCR Components)
 C2 = 2.2 μ F 5% 250V, polypropylene, Evox Rifa type PHE426HF7220JR06L2
 C3, C4, C6, C8, C9 = 33pF \pm 1pF 160V, axial, polystyrene (LCR Components)
 C5, C7, C10, C15, C20, C23, C28-C59 = 100nF 10% 100V, lead pitch 7.5mm, Epcos type B32560J1104K
 C11, C13 = 47 μ F 20% 35V non polarised, Multicomp type NP35V476M8X11.5 (Farnell # 1236671)
 C21 = 22nF 10%, 400V, lead pitch 7.5mm, Epcos type B32560J6223K (Farnell # 9752366)
 C22 = 1 μ F, 10%, 10V, lead pitch 7.5mm, Epcos type B32560J1105K (Farnell # 9752382)
 C24-C27 = not fitted, see text

Inductors

L1 = 1.7 μ H; 10 turns 1 mm (18AWG) ECW,

diameter 20mm, effective length 20mm

Semiconductors

D1, D2 = 1N5402
 D3 = 1N4148
 IC1-IC5, IC7-IC38 = NE5532 (see text for notes on device selection)
 IC6 = OP177 (Analog Devices)

Miscellaneous

K1, K5-K12, K14, K15 = 2-pin SIL pinheader, lead pitch 0.1 inch
 K2, K3, K4, K13 = 3-pin SIL pinheader, lead pitch 0.1 inch
 K16-K19, LS1 = 2-way PCB terminal block, lead pitch 5mm
 JP1 = 3-pin SIL pinheader and jumper, lead pitch 0.1 inch
 RE1 = PCB mount relay, PCB, DPCO, 24VDC/1100 Ω /5A, Omron type G2R-2 24DC Phono socket, chassis mount, black, Neutrik type NYS367-0
 XLR socket, chassis mount, 3-way, Pro Signal type PSG01588
 PCB # 100124-1, Elektor Shop, see www.elektor.com/100549

decoupling arrangements. For this reason it is strongly recommended that you use the Elektor PCB design — better still, ready-made boards supplied by Elektor.

The completed prototype was measured using Elektor Labs' **Audio Precision System Two Cascade Plus 2722 Dual Domain** test-set, and **Figures 4a, 4b and 4c** show

the pleasing and impressive results. **Figure 4a** shows the harmonic distortion and noise as a function of signal frequency. Measurements carried out at 1 watt (red) and 8 watts (blue) of output power within 80 kHz bandwidth. The graph in **Figure 4b** shows distortion as a function of output power at 1 kHz and a bandwidth of 22 kHz. From about 3 watts the amplifier actu-

ally gets close to the lower measurement threshold and noise floor of our analyser! At 15 watts (roughly) the amplifier veers off into clipping. The curve in **Figure 4c**, finally, is an FFT plot for 1 kHz, 1 watt into 8 ohms. The fundamental frequency is suppressed. The second harmonic is way down at -121 dB and the third harmonic slightly higher at -115 dB. At a bandwidth

COMPONENT LIST

Power supply board

Resistors

5%, 0.25W, Farnell/Multicomp MCF series, unless otherwise indicated.


- R1, R5 = 100Ω
- R2, R6 = 1.30kΩ 1% 0.25W, Multicomp MF25 1K3
- R3, R7 = 39Ω
- R4, R8 = 1.5kΩ 5% 1W, Multicomp MCF 1W 1K5
- R9, R11, R16, R20-R22 = 2.2kΩ
- R10, R12-R15, R19 = 47kΩ
- R17 = 150kΩ
- R18 = 470kΩ

Capacitors

- C1, C3, C24 = 47μF 20% 25V, lead pitch 2.5mm, Rubycon type 25ZLG47M6.3X7
- C2, C4 = 100μF 20% 25V, lead pitch 2.5mm, 1.43A AC, Nichicon type UPM1E101MED
- C5, C8 = 100nF 10% 100V, lead pitch 7.5mm, Epcos type B32560J1104K
- C6, C7, C9, C10 = 4700μF 20% 35V, lead pitch 10mm, snap in, Panasonic type ECOS1VP-472BA (25mm max. diameter)
- C11-C18 = 47nF 10% 50V ceramic, lead pitch 5mm
- C19, C20 = 47nF 20%, 630VDC X2, lead pitch 15mm, Vishay BCcomponents BFC233620473
- C21 = 4.7μF 20% 63V, lead pitch 2.5mm
- C22, C23 = 22μF 20% 35V, non polarised, lead pitch 2.5mm, Multicomp NP35V226M6.3X11

Semiconductors

 - D1-D4, D7 = 1N4002
- D5, D8-D16 = 1N4148
- D6, D17 = LED, green, 3mm



- T1, T3, T4, T6 = BC337
- T2, T5, T7 = BC327
- IC1, IC2 = LT1083 (Linear Technology)
- B1, B2 = GSIB1520 (15A/200V bridge rectifier) (Vishay General Semiconductor)

Miscellaneous

- K1, K2, K4 = 2-way PCB terminal block, lead pitch 5mm
- K3 = 3-way PCB terminal block, lead pitch 5mm
- D6, D17, S1 = 2-pin SIL pinheader, lead pitch 0.1 inch
- K5, K6 = 3-pin SIL pinheader, lead pitch 0.1 inch

- F1, F2 = fuse, 6.3A antisurge (time lag), with 20x5mm PCB mount fuseholder and cover
- Heatsink, Fischer Elektronik type SK92/75SA 1.6 K/W, size: 100x40mm, Farnell # 4621578, Reichelt # V7331G

Miscellaneous, mechanical

- M3 screws, nuts and washers for mounting IC1 and IC2 to heatsink (see text)
- TO-3P thermal pad, (Bergquist type K6-104)
- M4x10 screws for mounting heatsink to PCB PCB # 100124-2, Elektør Shop, see www.elektor.com/100549

of 22 kHz, the total level of noise and harmonics is about 0.0005%. If the distortion is measured for the two strongest harmonics only, it is at a level of 0.0002%.

Conclusion

To the non-initiated, the OpAmplifier with its case closed may be just another high-end audio amplifier albeit with quite impressive specs relative to the investment. To the discerning electronic engineer, it's a delightful and off-the-beaten path approach to getting high-quality audio watts from a dead common component like the NE5532 you

normally associate with nano-ampères and microvolts electronics-wise, and pennies in the financial department!

The proof of the pudding is in the eating. That's why a demo version of the OpAmplifier was cased up in a rugged suitcase for easy transporting, packaging and demoing. At the time of writing, it's about to leave Elektor House on a journey along several audiophiles and audio communities around the world for listening tests. Their feedback is awaited eagerly.

(100549)

Spoil for choice — which 5532?

It is an unsettling fact that not all 5532 opamps are created equal. The design is made by a number of manufacturers, and there are definite performance differences. While the noise characteristics appear to show little variation in my experience, the distortion performance does appear to vary significantly from one manufacturer to another. Although, to the best of my knowledge, all versions of the 5532 have the same internal circuitry, they are not necessarily made from the same masks, and even if they were, there would inevitably be process variations between manufacturers.



Since the distortion performance of the amplifier is unusually, and possibly uniquely, dependent on only one type of semiconductor, it makes sense to use the best parts you can get. In the course of the development of this project 5532s from several sources were tested. I took as wide a range of samples as I could, ranging from brand-new devices to parts over twenty years old, and it was reassuring to find that without exception, every part tested gave the good linearity we expect from a 5532. The information here will be of use not only in the 5532 power amplifier project, but should prove very valuable for anyone using 5532s in high-quality applications.

The main sources at present are Texas Instruments, Fairchild Semiconductor, ON Semiconductor, (was Motorola) NJR, (New Japan Radio) and JRC (Japan Radio Company). TI, ON Semi and Fairchild samples were compared in the Elektor labs by Ton Giesberts. The author for his part did THD tests on six samples from Fairchild, JRC, and Texas, plus one old Signetics 5532 for historical interest. The Elektor lab tests were carried out on an actual and very crucial section of the OpAmp design: the driver section! See **Figure A** for the circuit and **Figure B** for the AP2 plots.

As it turned out, the Texas 5532s (green line) proved to be distinctly inferior, both in the Elektor Labs and in the author's tests. We have to admit this surprised us, as we have always thought that the Texas part was one of the best available, but the measurements say otherwise. Distortion at 20 kHz ranges from 0.001% to 0.002%, showing more variation than Fairchild and ON Semi as well as being higher in general level. The low-frequency section of the plot, below 10 kHz, is approaching the measurement floor, as for all the other devices, and distortion is only just visible in the noise.

Compared with other maker's parts, the THD above 20 kHz is much higher—and at least 3 times greater at 30 kHz. Fortunately this should have no effect unless you have very high levels of ultrasonic signals that could cause intermodulation. If you have, then you have bigger problems on your hands than picking the best opamp manufacturer...

The graphs show beyond doubt that the Fairchild 5532s (blue line) are top of the bill and true audio purists should select these devices even if they come at a slightly higher price as well as being awkward in terms of type code print on the device. Check with your supplier, it should be worth your while. There is effectively no distortion visible above the noise floor up to about 12 kHz, and distortion at 20 kHz is less than 0.0005%.

  

Sensorless Motor Speed Measurement

A new method based on current monitoring

By Ernesto Vázquez Sánchez and Jaime Gómez Gil (Spain)

A characteristic property of DC motors is that they can also act as generators, due to the complementary nature of Faraday’s and Lenz’s laws of magnetic induction. Thanks to this relationship, it is possible to devise a technique that measures the speed of a DC motor by monitoring the current drawn by the motor. In this article we describe a method of this sort, which can be used in a wide variety of applications.

 


Figure 1. Supply current waveform of a DC motor.

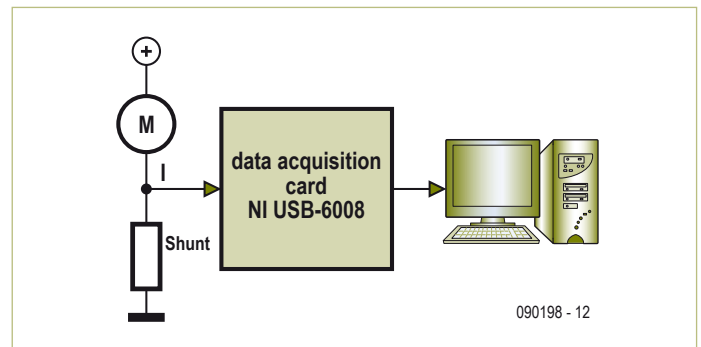


Figure 2. Wiring diagram of the various components.

Technological progress and the automation of all sorts of tasks that were formerly performed manually has led to a dramatic increase in the use of motors in various applications. For example, the simple task of manually opening or closing a car window, formerly performed manually with a crank mechanism, is now performed by pressing a button, which causes a motor to raise or lower the window. DC motors of this sort (and their relatives, such as stepper motors, servo motors and brushless DC motors) are primarily used in situations where positioning speed and positioning accuracy are the main considerations, rather than efficiency or power consumption. Their popularity is partly due to the fact that it is easy to drive a DC motor.

Table 1. DC motor specifications.	
Parameter	EMG30
Rated voltage	12 V
No-load current	530 mA
Rated speed	3000 rpm
Resistance (R_a)	1.8 Ω
Back EMF constant (c)	0.0178 V/rpm

In many applications of DC motors, the motor speed (rpm) must be controlled by a closed-loop system, which means that it is necessary to measure how fast the motor is turning. Transducers and sensors such as tachometers, encoders and Hall-effect devices are commonly used for this purpose. They are fitted on or near the motor shaft, preferably close to the load. These components increase the risk of malfunctions, as well as the overall cost of the system.

As an alternative to sensors and transducers of this sort, here we describe a method for measuring the motor speed that operates solely on the basis of the current drawn by the DC motor. This method is based on the electromotive force (EMF) generated in the motor windings. As you know, the EMF



Figure 3. The system hardware.

induced in a coil rotating in the magnetic field of a motor has a sinusoidal waveform. This signal is rectified by the commutator on the rotor. After it is rectified, a small ripple voltage remains.

The amplitude of this ripple voltage is proportional to the number of windings in the motor. This ripple voltage is an AC voltage whose frequency is directly proportional to the speed of the DC motor as indicated by equation (1), where f is the frequency of the AC voltage (this is called the ripple frequency), p is the number of pole pairs in the DC motor, k_d is the number of commutator segments on the rotor, n is the speed of the motor in rpm, and η is the greatest common denominator of $2p$ and k .

$$f = \frac{2pk_d n}{60\eta} \quad [1]$$

Figure 1 shows an example of the current measured at the terminals of a DC motor. Here you can see that the current consists of a DC component with a value of approximately 0.3 A and an AC component with a peak-to-peak amplitude of 0.1 A.

System hardware

Figure 2 shows the schematic diagram of our system hardware. It includes a DC motor, in this case a type EMG30, whose specifications are listed in Table 1. The current is sensed by a 20 mΩ sense resistor. The voltage across this resistor is measured by an inexpensive data acquisition card (NI USB-6008), which has a maximum sampling rate of 10 kHz. This card has four differential analog inputs, which can be configured to have a measuring range from ±1 V to ±20 V. One of these inputs is used here to sample the motor current by means of the sense resistor.

The data acquisition card is connected to a PC, which processes the sampled signal and determines the speed of the DC motor. The PC is a laptop model with an Intel T8300 CPU, 3 GB of RAM and a 320-GB hard disk. The operating system is Windows Vista, and the development environment is LabVIEW 8.5. Figure 3 shows a photo of the hardware used in the system.

Measurement algorithm

Now let's look at the algorithm we used to determine the motor speed. Figure 4 depicts the method in block diagram form. It consists of three blocks: a ripple detector, a frequency meter, and a con-

 


Figure 4. Block diagram of the motor speed detection method.

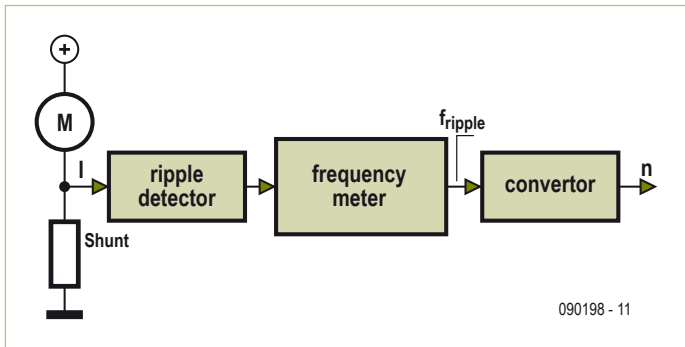


Figure 5. Block diagram of the ripple detector.

verter. The ripple detector ensures that all variations in the motor current waveform are detected. The frequency meter calculates the period of each waveform cycle, thereby determining the frequency of the AC component. Finally, the converter translates this frequency into the speed of the motor.

Ripple detector

This function of this block is to detect the starting point of every waveform cycle of the AC component of the motor current. **Figure 5** shows the block diagram of the ripple detector. The signal from the sense resistor is fed to a maximum peak detector and a minimum peak detector, which determine the minimum and maximum signal levels. The threshold level of the peak detectors is successively reduced at regular intervals. As a result, the detector circuit can

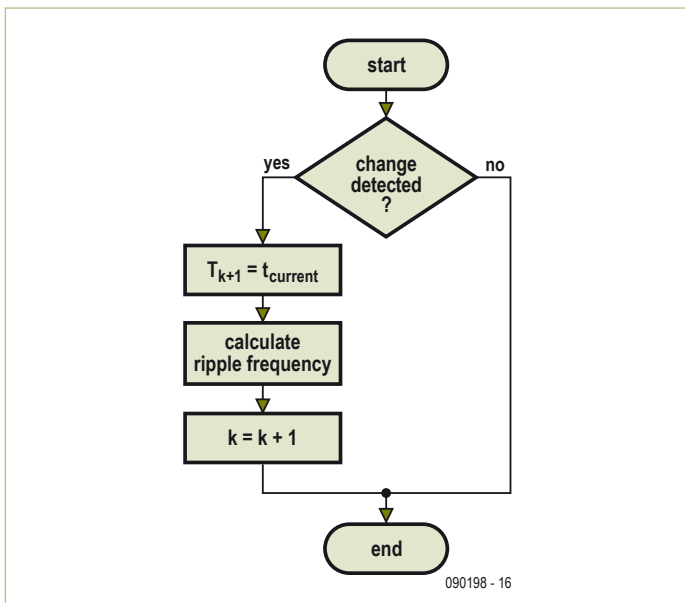


Figure 6. Flow chart of the frequency meter.

adapt quickly and dynamically to the actual minimum and maximum signal levels.

After detection, the average value of the minimum and maximum values (I_{avg}) is calculated. This value is then compared to the total current by a comparator, which operates with hysteresis to suppress the effects of small noise signals. The square-wave output signal from the comparator is fed to an edge detector. The logical output of the edge detector is ‘True’ if the sampled signal is high and the previously sampled signal was low.

Here we should also mention that the system processes each sample in turn and the processing takes place in real time. This means that when the output of the edge detector is ‘True’, the crossover point of the signal has already occurred at the time when the signal was sampled.

Frequency meter

This block calculates the motor speed based on the signal crossover times. The flow chart is shown in **Figure 6**. First it checks whether a level change has occurred. If nothing has changed, no action is taken. Otherwise, when a level change has occurred, the time when the change occurred is added to the list of crossover points T_{k+1} , where k is the number of detected crossover times.

After this, the ripple frequency is calculated using an approximation formula (2), where N is the number of crossover points for which the average value must be calculated as indicated in equation (3), f_k is the ripple frequency determined for the most recently detected crossover, f_{k+1} is the ripple frequency currently being calculated, and T_p is the length of time over which the average value is calculated. The operation $[\cdot]$ determines the integer value. This method yields a noise-free motor speed measurement, and it tracks changes in the motor speed well if the value of T_p is chosen properly. Finally, the number of detected crossover points k is incremented by 1.

$$f_{k+1} = \frac{N}{\sum_{i=0}^{N-1} T_{k+1-i} - T_{k-i}} \quad [2]$$

$$N = [T_p f_k] \quad [3]$$

Converter

This block is responsible for deriving the DC motor speed in rpm from the ripple frequency determined by the previous block. Equation (1) is used for this purpose.

Testing and results

To see whether the described method for the determining the motor speed works properly, we performed a variety of tests. First we determined the mean error and the deviation of the error with the motor running at a constant speed. Next we measured the error and the lag with the motor speed changing linearly (constant acceleration). Finally, we made step changes in the motor speed

 


Figure 7. Linear speed change with an EMG30 motor.

 


Figure 8. Step change in motor speed with an EMG30 motor.

and measured how long it took for the new speed to be indicated. The results at various speeds are summarized in **Table 2**. **Figure 7** shows the performance with linearly changing motor speed. The mean error in tracking the motor speed was 17.39 rpm in this situation, with a deviation of 8.90 rpm. The time lag for tracking the motor speed was 0.2 s, which is negligible for many applications. The error that occurred with a step change in the motor speed can be seen in **Figure 8**. The time required for the indicated speed to reach the actual speed was 0.4 s.

Conclusions

In this article, we have described a method for determining the speed (rpm) of DC motors by observing only the motor current. Although the method described here is based on a system incorporating a computer, this does not mean that it cannot be implemented in other ways. The ripple detector could also be constructed using opamps, and the other two blocks could be implemented with an inexpensive microcontroller, or with the microcontroller used to control the motor. Various tests were performed after the system was put together. The measured performance of the system is good enough for use in a large number of applications. This method has several advantages: it is not necessary to fit any objects on the motor shaft, the risk of malfunctions is lower, and the cost of the total system is lower. We can therefore conclude that this method forms a good alternative for measuring the speed of a DC motor under normal conditions. Multiplexing techniques could also be used with this method

to measure the speeds of several motors, which is not possible with conventional methods.

(090198-I)

Table 2. Measurement errors in the measured speed of the EMG30 motor.

Actual speed (rpm)	Mean error (rpm)	Deviation (rpm)
500	676.18	157.82
721	117.60	73.47
1023	1.86	7.91
1242	0.74	3.74
1516	0.23	5.08
2015	0.19	4.86
2514	0.30	5.75
3021	1.28	5.97
3502	1.96	7.15
4037	0.06	4.36
4492	0.50	7.31
5000	0.51	9.69
5518	1.27	11.94

About the authors


Jaime Gómez-Gil was born in 1971 in Aguilar de Bureba, Spain. He studied at the University of Valladolid, where he received a degree in telecommunication engineering in 2000 and was subsequently awarded a PhD degree in 2005. He has been employed there since 2001 as a lecturer in signal and communication theory and telecommunication engineering. His research areas are communication, GPS applications for agricultural use, sensorless technology for motors, artificial vision and augmented reality.

Ernesto Vázquez-Sánchez was born in 1985 in Plasencia, Spain. He studied at the University of Valladolid, where he received a degree in telecommunication engineering in 2008 and a degree in electrical engineering in 2010. He is currently working on his doctoral thesis. He has been employed in the Department of Signal and Communication Theory of the University of Valladolid since 2009, with a study contract as a recently graduated staff researcher. His interests and research encompass communication and sensorless technology for motors

Wireless Instrumentation Network Measuring with Arduino and XBee

By Johan van den Brande (Belgium) (johan@vandenbrande.com)

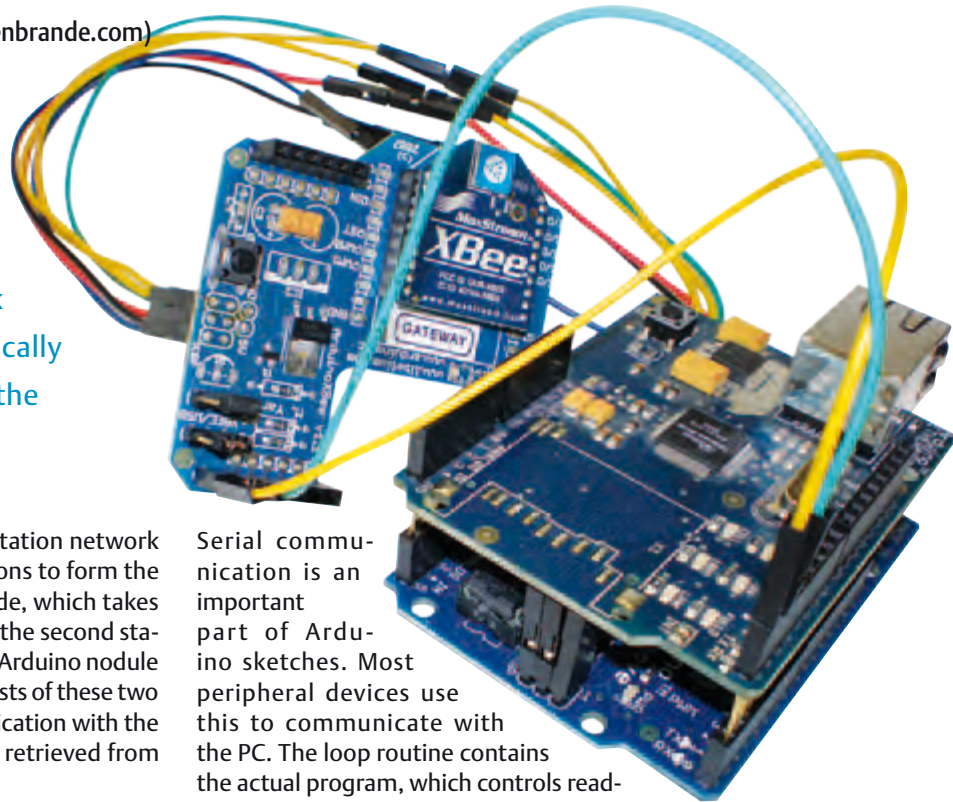In this article we describe how to put together a wireless instrumentation network with the Arduino platform and MaxStream XBee modules. The network uses an EtherShield module to automatically make measurement data accessible via the Internet.



It's not difficult to construct a wireless instrumentation network with the Arduino platform. Here we use two stations to form the network (see **Figure 1**). The first station is the node, which takes readings from the sensors and sends the results to the second station, which is the gateway. The node consists of an Arduino module with an XBee shield module. The gateway also consists of these two modules, plus an EtherShield module for communication with the Internet. The resulting measurement data can be retrieved from the Pachube website [1].

Arduino

Arduino is an open-source microcontroller platform with a user-friendly development environment, based on an 8-bit Atmel AVR microcontroller. It is used primarily by hobbyists and artists to create interactive projects. The Arduino platform has a low entry threshold. You don't need to know how to program in assembly language or write your own boot loader. The programming language you use is a lot like C, but all of the difficult tasks such as initialising the microcontroller and communication with a PC are already taken care of. The Arduino development environment is based on a program called Processing, which is used by graphic artists to create visual masterpieces. It includes a handy library with lots of routines to help you achieve useful results quickly.

The Arduino module has several digital ports and analogue inputs. The analogue inputs utilise the A/D converter of the AVR microcontroller. Some of the outputs can be driven in pulse width modulation (PWM) mode. If you add a small RC filter, the result is a nice analogue signal. The basic functionality can be extended with modules called shields, which can be plugged onto headers on the Arduino module. Shields are available for all sorts of applications, such as video and audio, joysticks, MP3 and so on.

A program for the Arduino module is called a sketch, and it includes a setup routine and a loop routine. In the setup routine, the ports are defined as inputs or outputs and the serial port is initialised.

Serial communication is an important part of Arduino sketches. Most peripheral devices use this to communicate with the PC. The loop routine contains the actual program, which controls reading data or a signal from individual inputs, responding to the input signals, and driving the outputs.

XBee

XBee modules are a convenient way to add wireless communication to a design. The modules from MaxStream are an implementation of the ZigBee technology developed by the ZigBee Alliance, a nonprofit consortium of chip makers, technology providers, OEMs and end users. ZigBee technology is intended to facilitate the creation of inexpensive, low-power wireless sensor networks. The modules transmit data at rates up to 250 kbps over a range of 30 to 100 m, depending on the version (1 mW or 10 mW) and the ambient conditions.

The modules can be used to replace a serial communication cable, but they can also be controlled through the Application Programming Interface (API) mode to form a more complex wireless network. The modules are configured using AT commands. For serial line emulation, it is important that both modules are configured with the same network ID and the same channel (CH). By default, the MY parameter (the 16-bit module address), the DL parameter and the DH parameter are set to '0'. This means that both modules can identify each other. The DL and DH parameters specify the destination address (DL = lower 16 bits, DH = upper 16 bits). They determine the reception options. These parameters may be configured in various ways. If DH is '0' and DL is less than '0xFFFF', every module whose MY parameter matches the value of DL receives data from the trans-

Readers Circuits contain contributions from Elektor readers for experimental purposes and further development by others. The circuit(s) presented on these pages have not been tested for reproducibility or actual use in the Elektor Lab.

mitting module. If DH is '0' and DL is '0xFFFF', every module receives the data transmitted by this module. If DH is not '0' and DL is greater than '0xFFFF', data is received only by modules whose serial number matches the destination address of the transmitting module (SH of the receiving module = DH of the transmitting module and SL of the receiving module = DL of the transmitting module).

Extension shields

In this project we use a ready-made shield called EtherShield, which provides Internet access capability for the Arduino module. It has an RJ45 connector and can be linked to a router or a switch by a UTP cable. A separate software library is available for the EtherShield module. It's usually possible to stack several Arduino shields on top of each other, as long as there aren't any conflicts between the inputs and outputs that are used. Although a standard XBee shield is available for the Arduino module, it poses a problem here because it cannot be stacked with the EtherShield module. For this reason, we developed a shield that can accept an XBee module and can also be plugged on top of the EtherShield module.

The design of our shield module is reasonably straightforward (see **Figure 2**). We included the voltage regulator because the Pro version of the XBee module can draw up to 100 mA, which is too much for the integrated regulator of the Arduino module. The XBee module also requires a 3.3-V supply voltage.

The XBee module communicates with the Arduino module via pins 1 (RX) and 2 (TX). The Arduino module also uses these pins for serial communication with the PC. As we want to be able to program the Arduino module with the XBee shield fitted, we inserted a pair of switches in the communication path. The Arduino module normally communicates with TTL-level signals on pins 1 and 2, so a voltage divider reduces the level of the input signal on the XBee RX pin to 3 V. Level adjustment is not necessary in the other direction, since the Arduino sees 3.3 V as a high level.

The PCB layout has been kept simple, and all of the components (except the pushbutton) are leaded types. The Eagle and PDF files of the PCB layout are included in the download file for this article [2].

Sensor options

We use the analogue inputs of the Arduino module in this project, which means we can use simple sensors, such as an LDR to measure light intensity. Another interesting application is measuring relative humidity. You can make a simple sensor for this by embedding two nails about half a centimetre apart in plaster of Paris inside a length of plastic pipe. Connect one of the nails to +5 V and the other to an analogue input pin and to ground via a 10-kΩ resistor (see **Figure 3**).

A lot of other quantities can be measured using the digital inputs. The number of ports can be expanded with an I²C bus device, such as the Texas Instruments PCA9535.

All together now

As already mentioned, our system consists of two stations: the node formed by the Arduino and XBee shield modules (**Figure 4**) and the gateway formed by the Arduino, XBee shield and Ether-

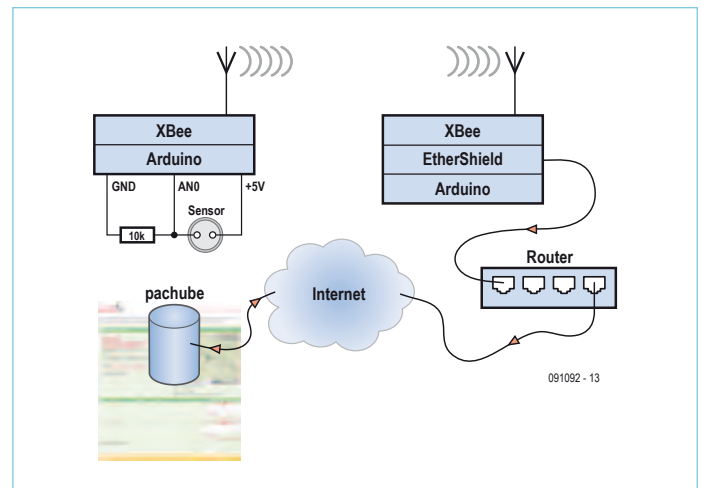


Figure 1. The instrumentation network consists of a node, a gateway and a data platform at www.pachube.com.

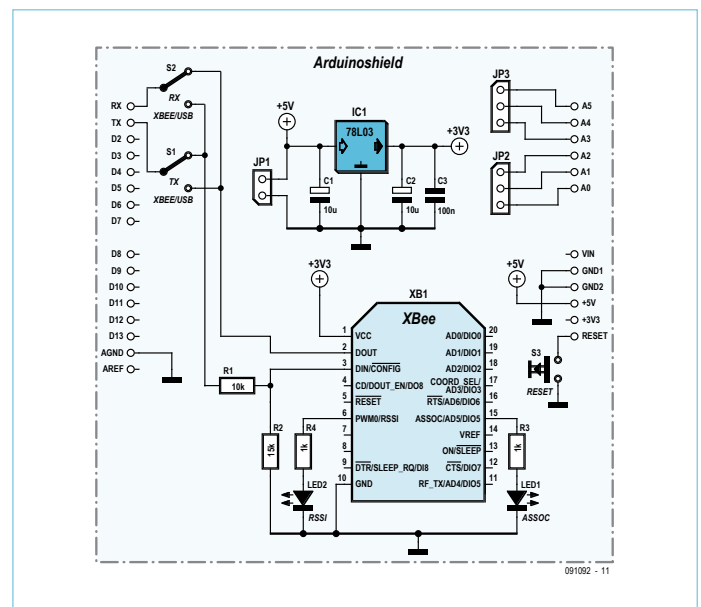


Figure 2. The schematic diagram of our Arduino shield is reasonably straightforward.

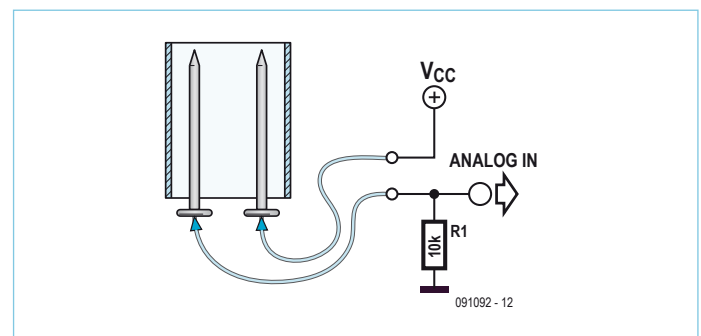


Figure 3. A simple humidity sensor can be made by embedding two nails in plaster of Paris inside a length of plastic pipe.

The Internet of Things

In the last while there's been a lot of activity related to the 'Internet of Things', which means connecting everyday objects to the Internet. Sensor data platforms such as the Pachube website are a good example of this. On this site you can store and retrieve sensor data for purposes such as displaying a chart or maintaining a log. Another potential application is monitoring sensor values and performing a suitable action if they exceed a defined level, such as sending an e-mail or text message. Pachube is a publicly accessible site with a simple protocol for sending data to the site. You can assign geographic coordinates to your sensors, which are then shown on a map of the world. The data can be viewed in the form of charts, and you can also grant other people access to your data. Instead of sending data directly to other parties, you can publish it once on the Pachube site, where other parties can subscribe to receive your data stream.

After registering on the Pachube site, you have to create a feed. You should click 'Manual update' when you configure your feed, since this allows the microcontroller to determine when to publish new data. With the other option, 'Automatic', the Pachube site actively sends Web request commands to fetch the data. To make this possible, you would have to embed a web server in the microcontroller and configure your network to allow access to the microcontroller from the Internet. After you create your feed, you are assigned an API key.

The microcontroller uses the HTTP protocol for manual updating. This is a very simple text-based protocol that supports the usual task of retrieving data (GET command), as well as sending data (PUT command), modifying data (POST command), and deleting data (DELETE command).

An HTTP request consists of a header and a body, separated by a blank line. The first header line contains the protocol version, the command

type (GET, POST, PUT or DELETE) and the resource, which is where the command is supposed to do its work. It may be followed by other header lines that supply various parameters to the web server, such as the type of content your client is able to process. A header line consists of a name and value. For the application described in this article, the API key belonging to the feed is placed in a header line.

The header is followed by the data. The following is an example of a PUT request to the Pachube website:

```
PUT /v2/feeds/ENTER_FEED_ID_HERE.csv HTTP/1.1
Host: api.pachube.com
X-PachubeApiKey: ENTER_YOUR_PACHUBE_API_KEY_HERE
Content-Length: 10
Connection: close

0,100
1,244
```

The HTTP protocol is easy to implement in a sketch (an HTTP-based protocol of this sort is called a REST API). It is even possible to test the adaptation of the feed from the console, for example with the *curl* command:

```
curl --request PUT --header "X-PachubeApiKey: YOUR_API_KEY" --data "0,100" "http://www.pachube.com/api/feeds/YOUR_FEED_ID.csv"
```

The *curl* function is available in the standard OS X installation and can easily be installed under Linux. Windows users can download it from <http://curl.haxx.se/download.html>.

Shield modules (**Figure 5**). Plug the EtherShield module onto the Arduino gateway module first, and then plug the XBee shield module on top so its pins and switches are readily accessible. Set both switches in the USB position when you want to program the Arduino module, and set them to the XBee position when you want to transmit or receive data with the XBee module. If you only want to receive data from the XBee module, set the RX switch to the XBee position and the TX switch to the USB position. This allows you to display IDE debug information on the serial port console of the Arduino module. It may be convenient to fit the board with headers with jumpers instead of switches so you can open the TX signal path between the Arduino and XBee modules, which is handy for debugging.

XBee modules must be properly configured in order to communicate with each other. They are supplied with a factory default configuration for operation in serial line emulation mode. You can configure them by using the terminal emulator utility in a Windows, Minicom or Linux environment to send them Hayes AT commands, or by using the X-CTU software supplied by MaxStream [3]. This does not require any special hardware. Set both switches to the USB position and unplug the AVR microcontroller from the Arduino module. Now you can use the USB link to communicate with the XBee module via the PC.

Firmware

This brings us to the firmware, or as it is called, the sketches. The sketch that runs in the node (see the program code in the download package [2]) is the simplest. Briefly, it waits for a certain time, takes a snapshot of the analogue inputs, and sends it via a serial link to the XBee module. The following description is based on the program listing with line numbers provided in a separate document.

The time interval for reading and forwarding the measurement data is specified in line 10. Here it is set to 5 seconds, which is the shortest allowable interval for sending data to Pachube with a non-professional account. Line 11 assigns a unique name to the node. This name is not used at present, but you could use it in the gateway to distinguish between different nodes. In the *setup* routine, the transmission rate is set to 9600 baud in line 42 (the standard value for the XBee modules). Furthermore, serial communication is configured to 8 bits, no parity and 1 stop bit without any additional parameters. The *loop* routine is fairly simple. It calls the *intervalPassed* routine, which determines whether the configured interval (5 seconds) has expired. If it has, the *measure* routine is called. First we send the name of the node to the XBee module (lines 29 and 30), followed by a colon (:). The *for* loop in lines 32–35 polls all of the analogue ports and sends their values to the XBee module (line 32). Line 34

Embedded WiFi

“ Making Your Devices Smart & Simple! ”

inserts a comma after each analogue value (except the last one) to separate the values. Line 37 finishes off with a new line.

The sketch for the gateway is more complex because it also looks after the Internet link to the Pachube website (see inset ‘The Internet of Things’). The gateway waits until a full line has been received from the serial link and then sends the name of the measurement method and the sensor values to the Pachube site.

Before using this sketch, you must edit it to have the right parameter values for your Pachube account and network. In line 13, enter the ID of the feed you have created, and in line 14, enter your API key (from My Profile > Settings at [1]). Connect the gateway to a router or switch so it can access the


 


Figure 4. The node for reading the sensors consists of an Arduino module and an Xbee shield.

Internet directly. Configure the network parameters in lines 16 to 18 by putting the MAC of the EtherShield module in line 16 and its IP address in line 17. A MAC address identifies a specific device in an Ethernet network. You can use nearly any value you want for the MAC as long as it does not cause a conflict with other devices connected to the router or switch. Choose an unused IP address in the address space of your local area network and enter it in line 17. Here you must replace the dots in the IP address with commas, since the code in lines 16–18 defines a set of arrays. The IP address of the Pachube site is specified in line 18. In more elaborate software you could use the Domain Name Service (DNS), which translates domain names into IP addresses, but the approach used here is adequate for our purposes.

 Line 20 allows you to set a debug flag that activates the `_LOG` macro in line 23. This macro first reserves 256 bytes on the stack



WiFi implement with RS232/MII interface

Serial to WiFi / Ethernet to WiFi

Fast booting

Support AP mode, Station mode and Gateway mode

Easy Configuration - Web, Wizard software, Serial Command

Support WIZ-VSP (Virture Serial COM Port)

WEB 64/128, WPA/WPA2, PSK/AES/TKIP

Support for CE, FCC KCC Certification

WIZnet
Innovative Embedded Network

Get more information at www.wiznettechnology.com
3003 North First Street, San Jose, CA 408-232-5415 / Sales@wiznettechnology.com

 


Figure 5. The gateway, with an adapter board that allows the XBee shield to be used together with an EtherShield module.

as a C string in the *m* variable. This is followed by a formatted print command (*snprintf*) for this string. Like the *printf* (and *snprintf*) function, this macro can receive a variable number of parameters. This is indicated to the compiler by the ellipsis (...) in the macro definition. The construction `##_VA_ARGS__` expands this variable number of parameters in code that calls *snprintf*. If you disable the debug function by commenting out line 20, the `_LOG` macro is expanded to nothing (line 25).

Lines 27 and 28 link in the *Ethernet* library. This library is necessary for using the EtherShield module. The *string* library (line 29) is necessary for *snprintf* and *strncat*, among other things.

Line 30 specifies that six sensors will be read, and lines 31–34 define the *sensor* structure. The data received from the remote sensor is transformed to this structure. Line 35 creates an EtherShield client object: the TCP client, which establishes a connection to *server* on port 80 at the Pachube IP address.

The core of the sketch is the *loop* function in lines 103–112, which runs reiteratively. Lines 105 and 106 define a character buffer (*buf*) for the data read from the remote node. The data is read in by calling the function *readRemoteSensors* (line 109). After a full line has been received, it is analysed in line 110. The *parse* function converts the data to the *sensor* structure. The *pachubePost* function in line 111 sends the converted data to the Pachube site.

The *readRemoteSensor* function defined in lines 85–97 reads data from the serial port and places it in the buffer (*buf*) until the ‘new line’ character `\n` is received or the buffer is full (*while* loop at line 90). Line 91 checks for new data on the serial input. If new data is present, it is read in line 92 and placed in the buffer, and the buffer pointer *i* is shifted one position to the right. When all the data for the buffer has been read, the routine sets the current buffer location to ‘0’ and exits.

The *parse* function in lines 67–84 uses the *strtok* function to analyse the data in the *buf* variable. It split the string each time it encounters any of the characters defined in the *sep* (separator) variable, which in this case are the colon (`:`) and comma (`,`) characters. The *strtok*

function returns the next token or character each time it is called. As a result, when the *for* loop in lines 78–82 has completed execution, the full line has been analysed and the corresponding sensor values are located in the *sensor* structure. The *atoi* function converts an ASCII number to an integer value.

The connection to the Pachube site is established by the *pachubePost* function (line 36). It receives the sensor structure as an input parameter. The name is not used, but you could use it to select a different feed. Lines 42–46 convert the sensor values into comma-separated values. The format consists of the sequential number of the sensor and the value, separated by a comma. Each sensor is on a separate line.

Lines 49–61 handle the actual data transfer between the gateway and the Pachube site. Line 49 establishes a connection to the Pachube site at the TCP level. Once this connection is available, the *print* and *println* functions can send data to the Pachube site. Line 52 outputs a PUT command to Pachube, along with the feed name (*FEED_ID*). The data is sent as a CSV file, which is why the key has the `.csv` extension. The HTTP 1.1 protocol is used for this. Several header lines are sent as well. Line 53 sends the *host* header line, which indicates that the data is intended for the pachube.com host. This construction allows more than one domain to be hosted from a single IP address. Line 54 sends the API key. Pachube uses this unique key instead of a user name and password. Line 59 terminates the header with a blank line, after which the sensor data is sent by line 60. The data length must be the same as the value stated in the *Content-Length* header. After this operation, the feed has been supplied with new data and the current values and history can be retrieved from the Pachube website.

Final remarks

It’s easy to put together a wireless instrumentation network with MaxStream XBee modules linked to Arduino modules. Serial line emulation allows data to be sent and received relatively easily. An EtherShield module handles the connection to the Internet. Although it is possible to use more than one sensor node, you have to watch out for interference when two nodes send data at the same time. It’s therefore better to switch to API operation and configure a mesh network or star network. This requires considerably more complex software, although the hardware remains the same.

(091092-1)

Internet links

- [1] www.pachube.com
- [2] www.elektor.com/091092
- [3] www.digi.com/support/kbase/kbaseresultdetl.jsp?kb=125
- [4] www.arduino.cc/en/Main/ArduinoXbeeShield
- [5] www.ladyada.net/make/xbee/arduino.html
- [6] www.faludi.com/projects/common-xbee-mistakes
- [7] www.adafruit.com/index.php?main_page=product_info&cPath=29&products_id=126

Portable Energy


For cell phone, iPod and co.

Harry Baggen (Elektor Netherlands Editorial)

These days we all carry a whole array of portable devices along with us. Very handy, but those mobile phones and MP3 players have to be recharged frequently and a convenient power point is unfortunately not always at hand. Fortunately there are a multitude of alternative energy sources available, or so manufacturers have us believe...

Tug-of-war

The Universal Mobile-device Charger made by Yogen uses hand power to generate electrical energy. The idea is ancient: You pull a rope to get something else to rotate, in this case a kind of miniature flywheel. Add some electronics to regulate the voltage and a handy power cord with different adaptor plugs, and your universal hand-powered charger is complete. It does, however, not mention anywhere how long you have to

 

can power the radio using either the handle, a built-in solar panel, three batteries or an AC power adaptor. To store energy, the radio has a built-in NiMH battery. The digital AM/FM tuner has a display with RDS and the device can also operate as a torch. The built-in battery can also be used to charge your mobile phone or other portable equipment. Price is about \$80.

www.shopetoncorp.com/detail/ETO+NFR600B+BLK



If there is no wind then you can charge the battery from a wall socket using the supplied adaptor. Available in three colours, the unit is priced at around \$50. All sorts of mounting hardware is available separately.

www.hymini.com/html/HYmini.html#detail_1

Mini-hydrogen power station

The Hydrogen Power Station made by Horizon Fuel Cell Technologies is the first affordable mini-hydrogen power station for use at home. The hydrogen, which is generated using solar energy, is stored in small tanks, so-called Hydrosticks, which



pull the cord before your phone is charged up. Available in black and transparent plastic — expect to pay around \$50.

www.yogenstore.com/index.html

Gust of wind

With the HYmini wind generator you can generate energy while cycling or jogging. Mount the device on your upper arm, or on the handlebar of your bicycle or scooter. Depending on the force of the wind, the built-in Li-ion battery, rated at 1200 mAh, is charged slower or faster. Afterwards this energy can then be used to charge your mobile phone or iPod.



have dimensions similar to a battery. A full Hydrostick can be plugged into a small power generator which goes by the name of MiniPAK and can generate about 2.5 watts. The amount of hydrogen in the Hydrostick is sufficient to completely recharge a depleted mobile phone battery several times. The only thing standing in the way of purchasing this handy device

PORTABLE ENERGY



is probably the price, which is around the \$750 mark.

www.horizonfuelcell.com/electronics.htm

Sturdy dyno-torch

Who does not remember them from the past? This type of torch, which required repeated squeezing to get some light, is available these days in modern, high-efficiency versions. The Shark Diving Torch is a waterproof torch fitted with a generator which produces energy when cranking the handle. This energy is stored in the built-in battery and can be used to power the built-in LEDs or charge your mobile phone. The torch is fitted with several standard LEDs plus a powerful 1-watt LED, so that a considerable amount of light is available. The manufacturer claims that after one minute of cranking the handle, the battery will have sufficient energy to power the 1-watt LED for 20 minutes, a respectable time! Expect to pay about \$50.

http://shop.ecogadgets.com/index.php?cat=Eco_Torches_Lanterns&ActionID=df7232c6bab7b44952aef49dca635420

http://shop.ecogadgets.com/index.php?cat=Eco_Torches_Lanterns&ActionID=df7232c6bab7b44952aef49dca635420



Walking is healthy!

Using the nPower PEG you can charge practically any mobile phone, MP3 player or any other hand-held device while you walk. The device is in the shape of a pipe with a bulge in the middle. Put it in your backpack or attach it to your belt. As a result of the repetitive motion of your body the nPower PEG produces sufficient electricity to quickly charge your mobile phone — says the manufacturer Tremont Electric. A normal phone battery can supposedly be charged to 80% of its nominal capacity in only one hour. The device is able to deliver no less than 4 watts.



You can register your interest at the manufacturer's website, but the exact date it becomes available is not known. The price is around the \$150 mark.

www.greenpower.com

Pumping for a full battery

The companies Gotwind and Orange present an alternative method to charge the battery of your mobile phone or iPod, the Power Pump. This is a small wind generator where you generate the wind yourself using a foot pump. Handy while going camping, and thanks to its small dimensions it is unlikely not to fit in your backpack somewhere! Orange presented this device last




year at the Glastonbury Festival, where visitors could try it for themselves. As far as we know the device is not yet available for sale.

www.gotwind.org/orange_power_pump.htm


Batteries on water

For a number of years already the Japanese manufacturer APS (Aqua Power System) has been offering AA and AAA batteries which work using water, juice, coffee or other liquids. When you want to use a battery you fill it with a few drops of liquid and it is immediately ready for use. You can re-fill the battery about 10 times, according to the manufacturer. The second generation of the so-called NoPoPo-batteries is now in production and D-size cells will be available soon as well. Not really energy saving, but nevertheless very alternative. Perhaps they will also be available in US and European shops in the near future.


www.aps-j.jp/english/index.html

 

JTAG Live Buzz

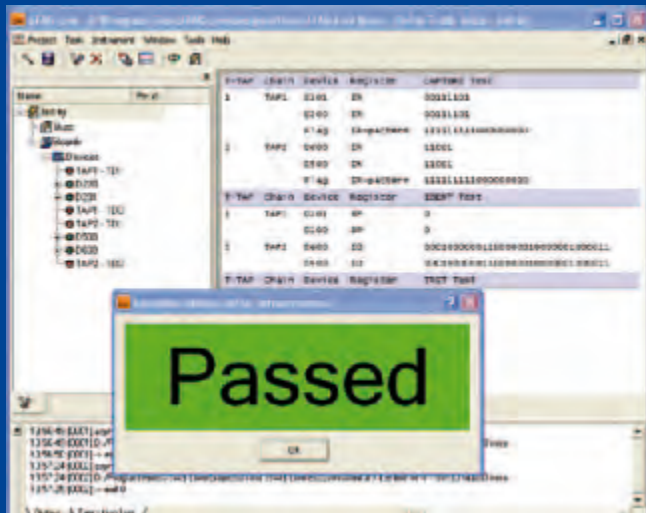

1

 

2

By Luc Lemmens (Elektor Labs)

For most of us, the term 'JTAG' primarily means an interface for in-system programming. Few people realise that it also refers to a test method called 'boundary scan', and even then they probably couldn't say exactly what this means. As early as the 1980s it became clear that traditional measurement methods using instruments such as multimeters and oscilloscopes would eventually become unfeasible due to the ongoing miniaturization of electronic devices. Multilayer PCBs went mainstream, with the result that many interconnects were inaccessible, and with modern components (such as BGA packages) it is often impossible to put a probe on device contacts. To deal with this problem, JTAG developed the boundary scan method. Of course, in-system programming is also important, and it can be done using the same JTAG interface.

Boundary scan requires adaptation of the IC architecture. A boundary scan cell is added, containing a multiplexer and a latch for each pin of the device. This cell can read data from each pin or read logic levels from signals originating from the core of the device, and it can place data on the pins of the IC. The data that is read is output serially from the IC and compared with the expected result.

In practice, the boundary scan cells of several ICs are connected in series to form a scan path or scan chain. The first IC in the chain receives JTAG data directly from the interface connector on its TDI (Data In) pin, while its TDO (Data Out) pin is connected to the TDI pin of the next IC in the chain. Finally, the TDO pin of the last device in the chain is connected back to the



JTAG interface connector.

In theory, with this arrangement a complete connectivity test of the components on the PCB can be carried out, based on the netlist of the complete circuit and the Boundary Scan Description Language (BSDL) files of the components. In practice, there are limitations because some components do not have boundary scan capability – for example, passive components and buffers. Nevertheless, the majority of the PCB can be tested for open connections and shorts with this method.


To familiarize (potential) users with boundary scan technology, JTAG Technology [1] offers the free program JTAG Live Buzz. The functionality of this program can also be enhanced with the Clip and Script modules, which require payment.

To work with JTAG Live, you also need a JTAG pod and a PCB with a boundary scan chain, as well as the schematic diagram and the BSDL files of the components on the board. For our hands-on evaluation of JTAG Live Buzz, we were provided with two scan chains and a USB boundary scan controller with two JTAG taps.

The first thing JTAG Live needs to know is the configuration of the scan chains, for

which you need to know which type of JTAG controller you have and which ICs are in the chains (and in which sequence). The ICs are characterized by their BSDL files. Once all this data is complete, the real work can begin.

 After everything is connected, the first thing you have to do is to select 'Test Infrastructure', which causes JTAG Live to



check whether the scan chain is correct and works properly. Beside configuration errors, there may be a bad connection or a short in the chain, which will prevent the boundary scan from working. If everything is OK the message shown in **Figure 1** is displayed, and you can continue with the functional testing of the rest of the hardware.

The actual measurement process starts with 'Open Buzz'. The inputs and outputs of the ICs in the scan chain are listed in the column on the left in **Figure 2**. You can drag them one by one to the measurement panels in the window.

The 'Watch' panel lets you observe the state of an IC input. In the example shown here, this is an input of a CPLD (pin 17 of D500), which is driven by a switch on the demo board. The 'Value' field shows the current logic state of the selected input in real time. This allow you to check whether the connection between the switch and the IC is OK.

The 'Buzz' panel lets you check a connection between two pins of ICs in the scan chain, which is comparable to conventional continuity testing with a multimeter.

The 'Measure' panel offers tests similar to the 'Buzz' panel, but with the added feature that you can directly set the state of an output to 0, 1 or HiZ in the 'Value (Drive)' column. In this example, a 74138 (decoder/demultiplexer) is located between

the outputs of D5000 (left column) and the inputs in the right column, and it is not included in the scan chain. This function allows the operation of this IC to be checked, despite this fact. The 'Constraints' panel allows you to cause specific control signals on the PCB (such as Chip Select or Output Enable) to assume defined states for the tests in the 'Measure' panel. Although all of this may not sound especially spectacular, you should bear in mind that here we are performing tests with a PC that would be difficult or impossible with a multimeter or oscilloscope, for the simple reason that the connections on the PCB are not physically accessible to a probe. The boundary scan method allows the hardware to be tested (for the most part) despite this difficulty.

The Buzz program is solely intended to demonstrate the power and simplicity of boundary scan technology. With complex hardware, it would be far too cumbersome to enter and check each connection by hand, which is why you would need the resources of the more powerful JTAG Live modules Clip and Script.

(100590-1)

Internet Links

[1] www.jtag.com

USB port from a 9-pin Sub-D connector




By Ernst Krempelsauer (Elektor Germany Editorial)

The company FDTI specialise in products providing interconnection solutions. At first glance their latest offerings look like standard 9-way sub-D RS232 PCB mount connectors and indeed fit the hole-spacing for such a connector on a PCB. A closer look reveals a mini-B USB socket where the RS232 cable should plug in! For sure there must be a lot more in the plastic housing than just 9 bent wires. These novel converter/connectors allow a USB port to be easily added to any PCB fitted with an RS232 connector. No layout, circuit or firmware changes are necessary. The unit on test here is the male sub-D version; a female version is also available.

Elektor readers familiar with the USB to RS232 cable from FTDI will probably be thinking that the engineers have fitted the same circuit into the RS232 connector housing. The block diagram in **Figure 1** confirms this, two ICs are shown: an FT232R converts between USB 2.0 and serial TTL data and a voltage level shifter interfaces TTL and RS232 levels.

 With the first sample sitting on the work bench we looked for a suitable PCB to adapt. The Elektor Internet Radio project (April 2008) looked like a good candidate; among its connectors is an RS232 de-bug port using a sub-D PCB mounted 9-way connector, perfect! We set to work de-soldering the sub-D







and then mounted the FTDI USB sub-D male module (it fits!). Next we plugged a USB cable into the socket (needs a bit of coaxing to get it all the way home), switched on and connected to a PC. The FTDI driver practically installs itself; you only need enter a virtual COM port number and select a baud rate.

The FTDI data sheet gives more details of this procedure and the function of the device. It behaves in exactly the same way as if the USB/RS232 converter cable from FTDI had been plugged in to the original 9-way RS232 port on the board. A disadvantage of fitting the DB9-USB-RS232 module is that if you ever need to communicate with the board via an RS232 port it would be necessary to swap the connector back again. The advantage however is that the equipment now has a new lease of life and can connect to any modern PC using a standard USB cable.

Speed is another advantage, the virtual COM port driver software can be configured to operate at up to 921,600 Baud. Ensure that the board can make use of the higher data rate by changing the port configuration or modifying the firmware as necessary.

    Natural curiosity prompted us to pop the cover of the housing and check out the internals



of this device. The complete PCB now lifts out for closer inspection. The manufacturing process is not quite as trivial as we might have expected; the nine pins of the sub-D module are soldered from one side of the board only (the component side). The pins do not extend through the PCB but instead are fitted into blind holes ('buried via') which extend approximately 0.5 mm into the PCB. Our Lab manager Antoine Authier removed one pin with a soldering iron and has sketched the approximate dimensions.

The more-complex manufacturing process is reflected in the price of the unit which works out a little bit more expensive than the cheapest USB/RS232 converter cable from FTDI. I can't imagine a quicker or more simple method (excluding the use of an USB/RS232 cable) of providing an older piece of kit with an up-to-date comms port. It can of course be used in new designs also and like all good ideas it makes me wonder why nobody thought of it before.

(100104)

Internet Link

www.ftdichip.com/Products/Modules.htm



Rapid Prototyping

By Jens Nickel (Elektor Germany Editorial)

After you've drafted the schematic, there comes a step in the design process that many electronics enthusiasts and professionals don't enjoy at all: putting together the bill of materials and the time-consuming process of ordering the components. This despite the fact that the day-to-day work of designers frequently involves the same mundane tasks, such as providing a regulated supply voltage, equipping a microcontroller board with a USB interface, or integrating a display.

The aim of the AutoFAB system from the Dutch tool foundry Muvium is to solve this problem by adding another level of abstraction [1]. The system is based on small PCB modules called FlexTiles, which provide commonly used circuit functions. For example, there is a Flex-Tile module with a dual 5-V power supply, a module with two potentiometers, a module with an LCD, a module with an FT232, and many more. Intelligence is provided by FlexTiles fitted with a PIC microcontroller, and an Arduino-compatible module is also available.

Unlike similar modular systems, all modules in this system have the same width and are fitted with pins facing downward. This allows the FlexTiles to be plugged into a special breadboard called the Flex Router board, similar to a perforated prototyping board.

When a FlexTile module is plugged in, each of its contact pins is connected to a row of solder pads on the Flex Router board. The system also has a board of the same size with tracks perpendicular to the rows on the Flex Router board, which is secured to the latter board at the end of the process. The clever part of this scheme consists of small contact pins fitted between these two boards, which allow the contact rows for the module pins to be connected to the tracks on the rear board. For example, if the module pin is the output of a 5-V voltage regulator, a 5-V supply voltage will be available over the length of the connected track. Using additional contact pins, other modules can be connected to this track to supply them with power.

Based on our experience with an evaluation system, the hardware (which is being regularly extended with additional modules) is well made, although working with the small metal pins is somewhat fiddly. Nevertheless, the result after the two boards are screwed together is a prototype that is very robust and compact, since it lacks the interconnect wiring of a conventional breadboard.

There's even more to the story. The latest version of the free Virtual Breadboard (VBB) software — a simulator program from the same supplier, which has been available for some time already — also supports virtual design with the AutoFAB boards. For this purpose, virtual FlexTiles are selected from a list and plugged into a simulated Flex Router board on the computer. At the press of button, the software imports the components into the simulator. As usual with programs of this sort, you use the mouse to connect the component in this view, after which the resulting circuit can be simulated. An especially unusual feature here is that you can program the microcontroller in Java, which is converted into executable hex code by a special compiler [2]. Of course, it takes a certain amount of time to master the simulator's learning curve.

If you are interested in this concept, we recommend attending a workshop to be held during the Elektor Live! event in Eindhoven, The Netherlands on November 20, 2010 [3]. During the workshop, Muvium CEO and principal engineer James Caska will demonstrate how quickly prototypes can be developed using AutoFAB and the Virtual Breadboard system.

A brand-new development here is a stripped-down version of the virtual breadboard concept, which runs in any browser environment (Java required) and is specifically tailored to the AutoFAB system [4]. After you have placed the FlexTiles on the virtual Flex Router board, you use the mouse to interconnect the pins in a sort of schematic view. However, this version lacks the simulation function. Once the connections have been made, both programs allow you to view the rear of the Flex Router board to see where the metal pins must be fitted. All you need to do now is to copy this on the real hardware. This means that putting together a prototype still requires some manual effort, which may disappoint users with poor eyesight or clumsy fingers. The ideal solution (for lazy users) would be a small software configurable component that inserts the pins for you, so you can enjoy a cup of coffee while it interconnects the rows and columns.

(100413-1)

[1] www.virtualbreadboard.com

[2] www.muvium.com

[3] www.elektorlive.nl

[4] www.virtualbreadboard.com/diky/diky.html

DISTANCE LEARNING COURSE

Programming Embedded PIC Microcontrollers

→ using Assembly, C and Flowcode

Limited Time Offer:
\$70 DISCOUNT
Benefit now!

In this course you will learn how to program an embedded microcontroller. We will start with the absolute basics and we will go into a lot of detail. You cannot learn about software without understanding the hardware so we will also take a close look at the components and schematics. At the end of the course you will be able to design your own embedded applications and write the appropriate software for it.

Contents:

- Background
- Digital Ports
- Serial Communication (RS232)
- Analog Signals
- Pulse Width Modulation
- Timers/Counters/Interrupts
- Memory
- LCD Display
- I²C Communication
- SPI Communication
- USB Communication
- Configuration (Fuses)
- Answers to the assignments
- Appendix



Your course package:

- Courseware Ring Binder (747 pages)
- CD-ROM including software and example files
- Application Board
- Support at Elektor Forum
- Elektor Certificate

Price: ~~\$645.00~~ \$575.00

Please note: to be able to follow this course, E-blocks hardware is required which you may already have (in part). All relevant products are available individually but also as a set at a discounted price. Please check www.elektor.com/distancelearning for further information.



Further information and ordering at
www.elektor.com/distancelearning

Image Processing Made Easy

Motion detection with a webcam

By Jens Nickel (Elektor Germany Editorial)

An Elektor issue with a focus on sensors is hardly complete without an article on image processing. However, this highly interesting field is widely regarded as enormously complex. This is by no means true, as we demonstrate here with a simple example. A webcam and a few basic algorithms are all you need to get started.

As already clearly demonstrated by the article 'Vision System for Small Micro-controllers' [1], you don't need expensive hardware to implement a simple presence detection system or similar application. Our objective here is to show that the software also does not need to be overly complex. A small experimental program demonstrates a basic approach to implementing a simple motion detection system. All it takes to show that everything works is a PC, a webcam and a free software development environment, such as Visual Studio Express.

From the idea ...

It all started on a Friday afternoon when the author was reading through a book on computer vision in search of inspiration for this topic. In addition to the theory, this book discusses the practical aspects of image processing in detail, including motion detection and object recognition. Suitable algorithms are presented in pseudocode, which makes it easy to implement them in the programming language of your choice. The author thought it would be a good idea to try this in Visual Basic, which is especially familiar to many readers. While reading the first practical example for motion detection (for purposes such as detecting an unauthorized visitor), the author — an enthusiastic programmer — could hardly wait to get his hands on a keyboard. He already had the Basic-language version of Visual Studio Express (available free of charge) installed on the computer, so it took only two or three hours to program the necessary algorithms for motion detection and a simple user interface. To quickly check everything out, he used the editorial department's digi-



Figure 1. Two original images to be compared



Figure 2. Grayscale versions of the original images.

tal camera to snap a couple of pictures, with a chair shifted by a small distance in the second photo. And lo and behold, it worked: the approximate size and location of the moved object could be detected by image comparison.

... to the software

Here's how it works. First the program has to get its hands on the colour data of the

individual pixels. In modern versions of Visual Basic (2008 and 2010) supported by the .NET framework, this is fairly easy. After an image file (in *.bmp* or *.jpg* format) has been loaded as a bitmap image with the name *pic*, the colour data of an individual pixel can be accessed with the following commands:

```
intR = pic.GetPixel(intX, intY).R
```




Figure 3. The difference image produced by pixelwise greyscale value subtraction and discarding negative values.

```
intG = pic.GetPixel(intX, intY).G
intB = pic.GetPixel(intX, intY).B
```

Here *intX* and *intY* are the pixel coordinates, and the variables *intR*, *intG* and *intB* are assigned the values of the color bytes for red, green and blue (value range 0–255). For motion detection we can restrict ourselves to the grayscale value of each pixel, which can be obtained in a straightforward manner from the color data:

```
intGrey = (intR + intG + intB) / 3
```

Pixel by pixel comparison of the grayscale values suffices for a simple image comparison. This is done by synchronously iterating over all pixels. To avoid potential problems, both images should have the same size (*intX* range: 0 to *intXmax* – 1, *intY* range: 0 to *intYmax* – 1).

The pixels can be compared by a simple subtraction operation. The results for all of the pixel coordinates can then be displayed again as an image, as long as we take care to avoid including any results with negative values. In our example, we simply sweep these values under the carpet (more about his later on):

```
intDiff = intGrey1 - intGrey2
if intDiff < 0 then intDiff = 0
```

Figure 3 shows the result of applying this processing to the pair of images shown in **Figure 1** and the grayscale representations shown in **Figure 2**.

Due to ever-present image noise, small changes in overall image brightness and the like, it is unfortunately not possible to distinguish moving objects especially well with this representation, since even the smallest change in the pixel grayscale values is displayed.



Figure 4. The result of the next step: the pixels in this image are white where the grayscale difference is greater than a defined threshold.

We can obtain better results by discarding small changes in grayscale values before generating the output image. For this purpose, we define a threshold *intLimit* (with a reasonable range of 1 to 100). If the difference *intDiff* is larger than *intLimit*, the change in intensity (grayscale level) should be regarded as valid and displayed as a white pixel in the output image. If the change is less than the threshold level or there is no change at all, the pixel remains black.

A new bitmap image can be constructed from the resulting pixels fairly easily in VB.NET by setting the red, green and blue values to 255 where a white pixel should appear in the image:

```
pic.SetPixel(intX, intY, _
Color.FromArgb(intResult, _
intResult, intResult))
```

for all *intX* = 0..*intXmax*-1 and *intY* = 0..*intYmax*-1, with *intResult* being either 255 or 0.

The result of this is shown in **Figure 4**, where the part of the image that has moved can be clearly recognized. However, it may be difficult to associate the result with an object in the original image (not all objects are as easy to identify from their outlines as the author's colleague ;-)). For this reason, we need to combine the data from the original image with the detected pixels to form a new image. The following commands are executed for each pixel. If the pixel is a detected pixel, we set the pixel to medium green, but if no motion has been detected for the pixel, it retains the color it had in the original image:



Figure 5. Here the detected pixels have been melded with the original image. The red spot marks the centre of mass of the detected motion.

```
If intResult = 255 Then
pic.SetPixel(intX, intY, _
Color.FromArgb(0, 150, 0))
Else
pic.SetPixel(intX, intY, _
Color.FromArgb(intR, intG, intB))
End If
```

The result is shown in **Figure 5**. This sort of image could be fed to a head-up display or something similar to create a form of augmented reality (a live video image enhanced with supplementary data).

Motion detection

The results so far are very nice to look at, but we still need to extract machine-readable values if we want to use them to send a signal to an alarm system or the like. For example, we need to have an indication of whether the detected motion is actually 'critical'. It would also be useful to detect the center of the moving object. Among other things, this would allow us to aim a second camera at the object in order to record a detailed image.


Both of these tasks are relatively easy to implement. A simple estimate of the relevance of the motion can be obtained by just counting the pixels for which *intResult* is 255. If we also sum the *intX* and *intY* coordinates of the detected pixels and then divide the sums by the number of detected pixels, we obtain the center of mass of the object represented by these coordinates, as shown in **Figure 4**.

In the example program available for download from the Elektor website [2], a separate procedure has been implemented for each of the algorithms mentioned above. This makes the program a good basis for developing your own applications or just playing with the code (source code file: *PicProce-*

Installing Visual Studio Express


If you do not already have the Visual Studio Express 2010 development environment (for Visual Basic 2010) installed on your computer, you first need to download it [3].

 Click the download file to start the installation program, which downloads additional files (Internet connection required). After completion of the installation process, you should find *Microsoft Visual Studio 2010 Express* in the *All Programs* list, with the Basic-language version of the development environment under the main entry.



As usual, the example software for this article can be downloaded free of charge from the Elektor website [3]. You should copy the contents of the Zip file to the folder provided by VS 2010 for project files, which is usually `C:\... \User_name \My Documents \Visual Studio 2010 \Projects`.

 After launching the development environment, click *Project* in the *File* menu and then select the *Pics* project. All files belonging to the project are shown in the *Solution Explorer* window at the top right (projects are called 'solutions' in Visual Studio jargon).



Double-click *Form.vb* to open the main form of the example software in the design view (see **Figure 7**). Here you can edit the controls, such as buttons and text boxes. If you wish to add new controls, select *View >> Other Windows >> Toolbox* to open the toolbox.

Right-click *Form.vb* in the *Solution Explorer* window to display the corresponding code, which defines how the form responds to events such as button clicks. The actual image processing procedures are contained in a separate code module named *PicProcedures.vb*.

Unfortunately, there is not enough room here to describe how to perform tasks such as placing new buttons on the form and linking them to corresponding code, but a free online tutorial on Visual Studio and Visual Basic .NET is available from Microsoft. If you want to work more extensively with this very powerful and entirely free PC development environment, it would certainly be worthwhile to buy a book on Visual Basic 2010. Several books are available at prices ranging from 30 to 50 pounds/euros. Before purchasing one of these books, you should check whether the learning curve demanded by the book matches your existing knowledge; the levels of the various books differ considerably.

Before you try out the software by clicking the green arrow (*Debugging*), you should also ensure that *WIAAut.dll* is installed correctly. After opening the *Pics* project in the *Solution Explorer* window, you will see a *References* folder. Click the '+' sign next to the folder icon to see a list of the software libraries used by the program. You should see *WIA* in this list. If the *WIA* icon is marked with an X, Visual Studio cannot access the *WIAAut.dll* file.

dures.vb).

Add a webcam ...

All of this is somewhat pointless without a source of live imagery. Fortunately, the .NET framework facilitates access to all sorts of hardware, including webcams. For this purpose the framework comes with a collection of classes that encapsulate hardware accesses via the corresponding Windows library (.dll) files. If you want to use the classes (i.e. the corresponding commands, status variables and so on) in your own software, you only need to give Visual Studio a suitable reference. Unfortunately, many of these classes are not especially well documented. In the course of a long Saturday afternoon, the author finally discovered which .dll file is the most suitable for this purpose (*WIAAut.dll*) and how to get a webcam to take snapshots under VB.NET so they can be used in user-developed software. A major advantage of this approach is that it does not require any manufacturer-specific drivers. Once the webcam has been recognized as a USB device, it's all systems go.

After a bit of fiddling around, the author persuaded his Logitech QuickCam S5500 to start producing a continuous stream of snapshots that could be used for live image processing. However, we have to live with a couple of limitations here. Everything is very (very!) slow, probably because the images are stored in webcam memory. Furthermore, this memory eventually becomes full. To clear the memory, you have to click the webcam camera icon under 'My Computer' (in Windows XP) and then click 'Delete pictures on camera' to clear the stored images (see **Figure 6**). After the memory was cleared, the author's webcam achieved a dizzying speed of one frame per second, which would certainly leave something to be desired for security-critical applications. However, all we were interested in at this point was trying a few things out.

... and go live

If we compare each webcam image with its previous image, it's possible to detect motion 'continuously'. However, even with the low resolution of the webcam snapshots it would take far too much time to first cal-

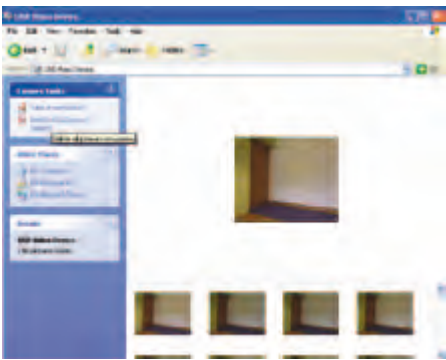


Figure 6. The image memory of the webcam should be cleared from time to time.



Figure 7. The development environment for Visual Basic 2010 can be downloaded free of charge. Even beginners can quickly achieve useful results.

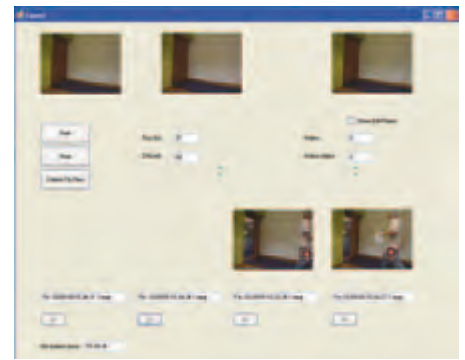


Figure 8. The demo software forms a good basis for DIY projects.

culate the grayscale values of both images and then compare them pixel by pixel, analyze the differential image again, and so on. A significant increase in speed can be achieved by storing the grayscale representation of each image in a sort of buffer, so that it is available for comparison with the

next image. As we do not display the actual grayscale images, we can also omit the division by 3 and simply sum the red, green and blue components.

The *MotionPicture* function in the example software contains all the code for motion

detection. It outputs a bitmap image showing a combination of the original image and the supplementary motion data melded with the image. This function expects the following inputs: the original image *picNew*, the parameter *intLimit*, and the Boolean variable *boolDrawDiffPoints*, which specifies

Advertisement

Open-Source Hardware Designs from Parallax

Parallax has long supported and encouraged open-source development. All of our code for the Propeller, and all third-party code hosted on the Propeller Object Exchange (<http://obex.parallax.com>), is distributed under the MIT license. To bring the same free, open licensing to our hardware, we are releasing many of our design files under the Creative Commons Attribution Only license. You can now incorporate our product designs directly into your projects, free of charge.

Visit www.parallax.com/go/opensource for details.



PARALLAX

www.parallax.com

"ParallaxInc" on Twitter, Facebook, and YouTube



See **Open-Source hardware designs** at www.parallax.com/go/opensource. Order online or call our Sales toll-free: 888-512-1024 (M-F, 7am-5pm, PDT).


Friendly microcontrollers, legendary resources.™

Parallax and the Parallax logo are trademarks of Parallax Inc.

Installing WIAut.dll

WIAut.dll is not included in all Windows installations. If the *WIAut.dll* file is missing in the C:\WINDOWS\system32 folder, it must be downloaded from the Web [4]. After extracting the .dll file from the downloaded Zip file (*WIAut.sdk*), drag it to the above-mentioned folder (which also holds the other .dll files).

 Next you must register the new library with the operating system. To do this, open the small Windows command line window by clicking *Run...* in the *Start* menu (with Windows XP). Enter the command `regsvr32 wiaaut.dll` in the window and click *OK*.



After this you must re-configure the corresponding reference in Visual Studio. You can view all the references in the *Solution Explorer* window after you open the *Pics* project (see the 'Installing Visual Studio' inset). If *WIA* is marked with an X, you must first delete the reference (by right-clicking *WIA*) and then create a new reference. To do this, right-click *References* and click *Add Reference* in the pop-up menu. In the window that this opens up, select the *COM* tab and then select *Microsoft Windows Image Acquisition Library v2.0* in the long list. A valid reference should then appear in the *Solution Explorer* window.

After this you must re-configure the corresponding reference in Visual Studio. You can view all the references in the *Solution Explorer* window after you open the *Pics* project (see the 'Installing Visual Studio' inset). If *WIA* is marked with an X, you must first delete the reference (by right-clicking *WIA*) and then create a new reference. To do this, right-click *References* and click *Add Reference* in the pop-up menu. In the

whether the detected pixels are to be colored green. The 'relevance' of the motion is returned to the calling routine in the *intMotion* parameter. The value of this parameter corresponds to the square root of the number of detected pixels. *MotionPicture* also loads the image into a greyscale buffer for the subsequent image comparison. This buffer is empty when the function is first called, so it must be initialized with the data of the first image before the first image comparison (this is handled by the subroutine *InitGreyBuffer*).

Demo program

The author has written a small sample program to demonstrate everything described in this article. Although the user interface isn't likely to win any design prizes, it is fully adequate for initial experiments. This software is solely intended to form a starting point for developing your own applications. Users can also change the values of constants in the source code (see the code for this). For this reason, the author has not generated an .exe file; the software must always be run inside the development environment. The installation process for Visual Basic Studio 2010 is described in an inset, while linking in the webcam library is described in another inset.

After you open the example project in Visual Studio (see **Figure 7**), click the green arrow on the toolbar to run the program. The main form (**Figure 8**) appears after you select the webcam. After you click *Start*, the webcam starts taking snapshots. The current and previous images are shown at the top left, and the result of the motion detection process is shown at the top right. The left slider adjusts the value of *intLimit*, while the right slider sets the value of *intMotion*, which is the threshold level for triggering an alarm (see above). When this happens, the corresponding image is shown below the slider and saved as a file. The 'X' buttons are provided to delete the displayed 'false alarm' images.

False alarms occur regularly when the automatic brightness control of the webcam causes the entire image to become brighter or darker. To partially filter out this effect, the *MotionPicture* function includes an algorithm that detects global intensity changes. In addition, you should always avoid allowing too much daylight to enter the room under observation, since outdoor lighting conditions are almost always constantly changing.

If you play with this program for a while,

you will quickly discover a significant shortcoming of the motion detection scheme described here: it only works with dark objects moving in front of a light background, and furthermore, in case of objects with different colors the system primary detects the motion of their dark-colored portions (see **Figure 3**). This is a consequence of the fact that we discard negative changes in the grayscale values, as previously mentioned. If you wish, you can try using the magnitude of the grayscale difference instead of the signed value. With the latter approach, both bright and dark objects will be detected. However, if the moving object is already visible in the first image, it will appear twice in the output image: once in its original location, and again in its new location. This is because the grayscale values of the pixels change at both locations.

The described experimental scheme is reasonably well suited to checking for the presence of an object, or for similar non-critical monitoring tasks. If you wish to use this motion detection scheme in a security context, increasing the frame rate is essential. It should be at least 5 frames per second (10 would be better) for use in practical situations, so that fast motions can also be detected reliably. Unfortunately, due to lack of time the author was not able to try out other image sources, such as a TV card or the like. We would certainly appreciate reader feedback in this regard.

(100539-1)

Internet Links

- [1] www.elektor.com/090334
- [2] www.elektor.com/100539
- [3] www.microsoft.com/express/Downloads/
- [4] www.microsoft.com/downloads/details.aspx?familyid=a332a77a-01b8-4de6-91c2-b7ea32537e29&displaylang=en

USB Add USB to your next project.
It's easier than you might think!

DLP-USB1232H: USB 2.0 UART/FIFO

HIGH-SPEED
480Mb/s



Only \$28.95!

- Multipurpose: 7 interfaces
- Royalty-free, robust USB drivers
- No in-depth knowledge of USB required
- Standard 18-pin DIP interface; 0.6x1.26-inch footprint

DLP-IO8-G

8-Channel Data Acquisition



Only \$29.95!

- 8 I/Os: Digital I/O
- Analog In
- Temperature
- USB Port Powered
- Single-Byte Commands

DLP-IOR4

4-Channel Relay Cable

DLP-TH1b

Temp/Humidity Cable

DLP-RFID1

HF RFID Reader/Writer

DLP-FPGA

USB-to-Xilinx FPGA Module



www.dlpdesign.com



AP CIRCUITS

PCB Fabrication Since 1984

As low as...

\$9.95

each!

Two Boards
Two Layers
Two Masks
One Legend

Unmasked boards ship next day!

www.apcircuits.com



Saelig

UNIQUE PRODUCTS + FREE SUPPORT!

www.saelig.com 1-888-7-SAELIG info@saelig.com

We have the testgear you need!

Call us for technical advice!

<p>60 - 300MHz DSOs</p> <p>SALE!</p> <p>60/100/200/300MHz 2 ch, 2GS/s DSO 2000 wfm/s refresh rate. High quality, ultra Compact Design with small footprint. Totally new price.</p> <p>DS1052E \$399</p> <p>•• thru ••</p> <p>DS1302CA \$1995</p> <p>Free Case!</p>	<p>Thumb-sized USB Tools</p> <p>Tiny sophisticated PC-based tools for any toolkit. 10MHz Scope, 50MHz Counter, 12MHz Waveform Generator, 100MHz Pulse Generator. USB isol.</p>	<p>Mixed -Signal PC Oscilloscopes</p> <p>100 MHz Scope and Logic Analyzer lets you do complex triggering to find hard-to-get-at glitches, spikes, etc. Huge 4 or 8 MS buffer for deep data drilling and zooming. Optional built-in swept signal generator. 2 Analog channels x 10, 12, 14 bit with more than 60 dB dynamic range. 8 digital inputs for mixed signal display/trigger.</p> <p>CS328A-4 (4MS Buffer) \$1259</p> <p>CS328A-8 (8MS Buffer) \$1474</p> <p>CS700A (signal generator) \$299</p>	<p>LCD Scopes</p> <p>BEST SELLER</p> <p>Owon - 25 or 60MHz color LCD 2-ch bench scope OR 20MHz handheld scope/meter. USB interface for printouts. Includes scope probes! Battery versions available.</p> <p>PDS5022S / 6062T \$287 / \$419</p> <p>HDS1022MN / 2062MN \$589 / \$699</p>	
<p>USB Bus Analyzers</p> <p>Packet-Master™ - best value USB1.1/2.0 USB analyzers and generators. Identify USB problems fast, fine-tune performance, easily view Host commands, emulate host/device sequences, etc.</p> <p>USB12 (USB1.1) \$699</p> <p>USB480+ (USB1.1/2.0) \$1199</p> <p>USB500AG (USB1.1/2.0/Gen) \$1399</p>	<p>7 in 1 USB Scope</p> <p>NEW!</p> <p>2-ch 10-bit 2MHz scope/spectrum-analyzer, 3MHz 8-bit wfm gen; 16 x I/O; Network Analyzer; Noise Generator; PWM. Windows/Linux/Mac compatible! USB-powered, great for toolbox, education, etc. CGR-101™ \$199</p>	<p>EMC Spectrum Analyzers</p> <p>EMC RF & EMF Spectrum - Analyzer 1Hz to 7GHz for measuring transmissions from radar, radio/tv towers, WLAN, WiFi, WiMAX, Bluetooth, microwave ovens, etc.</p> <p>from \$835 / \$1395</p>	<p>microCAM</p> <p>Compact compressed-serial output camera module for any host system. JPEG OmniVision™ CMOS VGA color camera for embedded imaging.</p> <p>uCAM TTL or 232 \$58</p>	<p>Sound Module</p> <p>14-pin Tiny Audio-Sound Module plays back pre-stored audio files (voice and music) from micro-SD card - ideal for embedded audio output.</p> <p>SOMO-14D \$25</p>
<p>USB to I2C</p> <p>Devasys - Provides a simple "drop-in" solution for connecting I2C/SMBUS to 1Mbps; 32 I/O. Free software. Use multiple boards for more I2C/I/O.</p> <p>USB I2C/I/O \$89</p>	<p>XP Emb Touchpanels</p> <p>Touch-input 10.2/15" Atom/Geode processor backlit TFT color LCDs USB 2.0 + Ethernet 12V-powered complete Windows PC.</p> <p>CUPC-P80/P100 from \$849</p>	<p>Custom Meters</p> <p>Customizable high contrast, 2.4" TFT color LCD, built-in touch screen, dual analog inputs, alarm outputs and SPI and I2C bus creating a wide range of meters.</p> <p>SGD 24-M Panel Pilot \$90</p>	<p>RF Testing/EMI Tents</p> <p>Economical, portable RF test enclosures, for initial compliance testing.</p> <p>Shielding Tents with external frame, instant up/down for emissions-free room.</p> <p>from \$1295</p> <p>from \$2000</p>	<p>I started Saelig as an engineer - for engineers - for engineers! Saelig is an olde English word means 'happy, prosperous, blessed'</p> <p>Check our website for lots of neat stuff!</p> <p>Alan Lowne • Saelig CEO</p> <p>Saelig <small>COMMERCIAL ELECTRONICS</small></p>

Designing and Making Basic Antennas

based on dipoles and monopoles



By Jean Marie Floc'h (France)

The antennas presented in this article were designed for a frequency of 2.45 GHz. This frequency is within the 2.4 GHz ISM band (Industrial, Scientific, and Medical) that can be used without a licence in many countries in the world.

Some simple rules explained below make it easy to design antennas for other frequencies. The prototypes were made from (adhe-

sive) copper laminate to make them easier to adjust to the correct frequencies (using a craft knife). But we recommend you to make the final versions of these anten-

 
 
nas on double-sided PCB laminate, so they will stand up to the weather better. Unless otherwise stated all antennas have a base impedance of 50 ohms.



Simple dipole

The dipole is one of the simplest antenna you can make. The simple dipole comes in the form of a $\lambda/2$ -long metal conductor divided in two. It is fed from the centre. The currents in the two elements must be in opposite phase, so that the current is maximum at the centre of the dipole. Feeding a dipole requires the use of a balun (for **balanced-unbalanced**) device to produce currents in antiphase and in order to present it with the correct impedance.

  
The impedance across the terminals has a value close to 73Ω , and it radiates omnidirectionally, except in line with the elements, where the radiation is zero. The theoretical gain of the dipole is 2.15 dBi. The term dBi denotes decibels with respect to an isotropic antenna radiating uniformly in all directions and which has absolute unity gain.




Coaxial dipole

One trick for avoiding the balun and the impedance transformer is to feed the dipole directly via a coaxial feeder. In practice, the physical length of the dipole is slightly shorter (a few percent) than the electrical length.


One of the elements is soldered directly to the center core of the coax, the other to the ground. The length here is set at 56 mm (two 27 mm elements with a 2 mm gap) so as to obtain a resonant frequency close to 2.45 GHz. At this frequency, the half-wave length is 60 mm. It's best to start with elements that are a little bit longer (making sure that both elements stay the same length), so as to be able to then adjust them to get the resonant frequency required. Bandwidth is around 400 MHz, i.e. 16% of the band's center frequency. A maximum gain of the order of 2 dBi has been measured. The red curve shows the radiation pattern in line with the dipole (referred to as the E plane, note the humps); the radiation in the plane at 90°, referred to as the H plane, (green curve) is virtually omnidirectional.

 

 

Dual dipole with ground plane

You can try to reduce the backwards radiation from the coaxial dipole by placing a metal ground plane approximately $\lambda/4$ away. To be effective, the diameter of this ground plane must be at least 0.75λ . To keep the radiation pattern symmetrical, it's best to use a disc. Watch out, a slight shift in the resonant frequency is often noticed, so it's necessary to re-trim the lengths of the dipoles. If you want a cross-polarized (H/V) antenna, you can use two coaxial dipoles together.

 


Bandwidth is around 450 MHz (18%). The dual resonance is due to the effect of mutual coupling between the two dipoles. It's best to terminate the unused feed with a 50Ω resistor to avoid spurious effects.

Measurements on the antenna reveal the hole in the radiation in line with the dipole (green curve) and the reduction in backwards radiation (around -15 dB). You can also see greater directivity in both planes, due to the presence of the second dipole in the plane perpendicular to the first one. This results in a significant gain value of 6 dBi. The same results are noted for the other feed point.




Monopole

 If you want to reduce antenna size, one simple way is to make use of the electrical images generated by a ground plane. In this way, you obtain a monopole whose size is $\lambda/4$, i.e. half the size. The ground plane also reduces the backwards radiation.




The monopole shown here is fed via a micro stripline (1.5 mm wide) produced on FR-4 PCB laminate. The monopole's 30 mm long element is soldered directly to the line. This is a very simple technique for producing antennas directly on PCBs. You get a bandwidth of around 450 MHz (18%).

 A hole is seen in the radiation on the axis of the monopole, and omnidirectional radiation in the perpendicular plane. A slight reduction in the rear radiation due to the presence of the ground plane can be seen. The gain is of the order of 1 dBi.




091095 - 14

 

Broadband monopole

If you want to achieve greater bandwidths, you need to adapt the shape of the monopole. Thus you can use an ellipse (see photo). The dimensions of this ellipse — made from 0.3 mm thick copper sheet — are 45 mm high by 30 mm wide. The height of the ellipse corresponds to the antenna resonance center frequency (here, 1.86 GHz) and is around $\lambda/4$.

 The bandwidth is 550 MHz (30%), twice that of dipoles and simple monopoles. The radiation pattern looks the same as that of the simple monopole and the gain too has a value of the same order.





Printed dipole

The two elements of the dipole are now printed each on one side of the substrate. They are fed via a 2-wire feeder, to which an SMA connector is soldered (the center pin to one element and bulkhead to ground). The antenna proper was made from copper foil, so as to make it easier to adjust the dimensions. But once you've got the dimensions right, we recommend you to make the antennas on double-sided copper-clad board, to improve performance (particularly gain) and get an antenna that will last.

The length of the dipole elements and the distance between the elements and ground is $\lambda/4$. The board used is 0.8 mm thick and has low permittivity (2.2), resulting in slightly higher gain (of the order of 2.4 dBi) and improved bandwidth (of the order of 470 MHz, i.e. 19%).

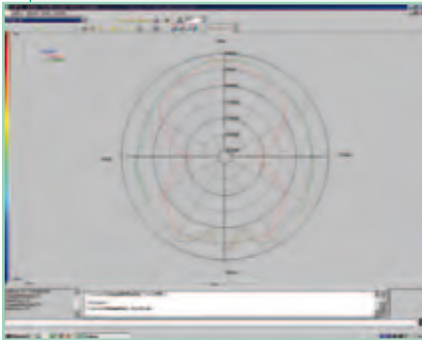 The disruption in the radiation pattern beneath the dipole is due to the measuring system and the presence of the feeder and connector.





Printed dipole with reflector

If you want to radiate in a half-space and limit backwards radiation, one widely-used technique is to place a reflector soldered to the ground side of the feeder line. The size will be chosen to be slightly larger than the two elements of the dipole. For good matching, the dimensions change slightly compared to the simple dipole. This antenna has a bandwidth of 350 MHz (14%), i.e. narrower than the simple printed dipole.

With this antenna, you can look forward to a reduction in backwards radiation of over 10 dB. The maximum gain is 5 dBi. Also note the radiation 'hole' in line with the dipole elements.

  If you want to increase the antenna's gain, simply place a director in front of the dipole elements, at a distance of around $\lambda/4$. This director is markedly shorter than the two dipole elements. In this way, the gain increases by 1.5 dBi. There is a reduction in rear radiation and an increase in directivity (narrower forward angle in the E and H planes).




Electromagnetically-coupled printed dipole

In this type of configuration, the dipole is positioned above a micro stripline by the use of a substrate. In this way, you get a dual-layer structure with a feed layer and a radiating layer with the dipole. The energy is coupled to the dipole by proximity or by a capacitive effect. Two configurations are possible:


- **Longitudinal coupling:** the substrate used is FR-4 PCB laminate, 0.8 mm thick for the feeder line and 1.6 mm for the dipole. The dipole measures 9×30 mm (a half wavelength). The feeder line is 1.5 mm wide, in order to obtain a characteristic impedance of 50Ω .

 The position of the dipole is adjusted by hand to obtain good coupling and hence good matching of the antenna. To avoid air bubbles and



for better reproducibility, it's advisable to put some Vaseline® between the two substrates.

 The bandwidth of 55 MHz (2%) is narrower than for a simple dipole. The measured gain is around 1 dBi. This low value is explained by the use of FR-4 laminate, which exhibits significant losses.



● **Transverse coupling:** this time, the dipole is positioned laterally with respect to the feeder line. The dimensions of the dipole and the characteristics of the substrates are identical with the previous antenna. The dipole position is adjusted in the same way to obtain good coupling between the line and the dipole. The bandwidth is of the order of 40 MHz (1.5%), i.e. slightly narrower than the longitudinally-coupled antenna. The measured gain is around 1.5 dBi.

Patch fed by a micro stripline

Numerous possible patch structures exist for producing antennas. Here, we're going to confine ourselves to just the following two types:

● **Fed by micro stripline** the patch is a 30 mm × 30 mm square on standard FR-4 PCB (thickness 1.6 mm, permittivity $\epsilon_r \approx 4.3$ @ 2.45 GHz, $\lambda \approx c/(f\sqrt{\epsilon_r})$). The patch feeder is a 1.5 mm wide micro stripline, with a characteristic impedance of 50 Ω. Matching to the patch is achieved using a 9 mm long stub (short section of micro stripline connected at one end only, thus presenting a purely reactive impedance), positioned 20 mm from the patch. This matching can also be achieved using a quarter-wave transformer. Bandwidth is around 55 MHz, i.e. a little over 2%. The measured gain is of the order of 0.5 dBi.

Publicité

N e w n e s P r e s s


Education Never Ends. Everything you need to know to get started.




By: Michael Parker
ISBN: 9781856179218
\$54.95



 By: Gina Smith
ISBN: 9781856177061
\$44.95



 By: William Kafig
ISBN: 9781856177047
\$44.95



By: Lou Frenzel
ISBN: 9781856177009
\$44.95





Visit newnespress.com today and sign up for our Newnes Online Membership.

Receive our best discounts · Hear about books before they publish
Access to free sample chapters, video tutorials and more!

www.newnespress.com


**Find these books and more at newnespress.com
or your favorite online retailer!**

Order today!

  

● **Coax fed:** the dimensions of the patch are also 30×30 mm. Coax feed is achieved using an SMA connector soldered to the ground plane on the other side of the board, with the center core to the patch. Feeding in this way makes it possible to reduce the losses in the substrate. Experience shows that the patch should be fed at a point centred $1/3$ of the way in from the edge of the patch (10 mm in our case). The measured gain is of the order of 4 dBi.

 If you want circular polarization, you need to make a notch of about 10% (here 3 mm) at 45° in the two opposite corners of the patch. Depending on the position of the slots with respect to the feed point, you will get either right- or left-hand (RH/LH) polarization.



Achieving matching using the Smith chart


In order to achieve matching, you first measure the impedance of the patch at resonance using a network analyzer (on the edge of the patch). The impedance for the prototype was 125Ω , purely real at the resonant frequency. You then use a Smith chart to carry out the matching:

- the patch's impedance normalized to 50Ω is $125/50 = 2.5$, i.e. a normalized admittance of $y = 1/2.5 = 0.4$. The constant-reflection coefficient circle (with the point $r = 1$ as its center) intersects the circle $r = 1$ at $1 + 0.95j$ and $1 - 0.95j$. You accept the solution $1 \pm 0.95j$.

- When the antenna is matched, you are at the center of the chart at point 1. Hence the stub needs to contribute an imaginary component of $0.95j$ in order to compensate for the patch's admittance, i.e. $(1 - 0.95j) + 0.95j = 1$

- to get from $y = 0.4$ to $1 \pm 0.95j$, you need to move 0.34λ round the perimeter of the Smith chart in the direction of the generator, which means that the stub will need to be positioned $0.34 \times 60 \text{ mm} = 20.4 \text{ mm}$ from the patch. In the prototype, the stub was positioned at around 20 mm.

 - Still on the perimeter of the Smith chart, going from y_{co} (open-circuit admittance) to a value of $0.95j$, you find 0.12λ as the stub length, i.e. $0.12 \times 60 \text{ mm} = 7.2 \text{ mm}$. In order to be able to cut it down to adjust, you'll make it slightly longer. The stub on the prototype was 9 mm long.



Near-field measurement setup

Radiation diagrams illustrating the antennas covered in this article were obtained using a Satimo Stargate 32 near-field measurement setup. This makes it possible to perform measurements between 400 MHz and 6 GHz. The system consists of an arch fitted with detectors that measure in real time a cross-section of the radiation pattern of the antenna under test. The antenna is then rotated in order to obtain a 3D diagram. The measurements made below the antenna need to be interpreted with care, as there are no detectors under the antenna and these values are extrapolated.





Things of the past



Elektor is now & tomorrow

Secure a head start in electronics
with a **subscription!**

Advantages to subscribers



11 Issues
including the
summer double
issue for just
\$39.95*

- Cheaper than 11 issues from the newsstand:
Save 57% off the cover price of \$92.45
- With every issue subscribers get up to **40% discount**
on selected Elektor products
- No lines, travelling, parking fees or 'sold out';
Elektor is mailed to you every month
- Always up to date – read your copy before
everyone else


* Offer available in US and Canada only. Canada add \$11 per year.

www.elektor.com/usa • Phone 860-875-2199

Or use the subscription order form near the end of the magazine.



elektor

 

Talk Show

Display what you say

By Grégory Ester (France)

Would you like to equip your project with voice recognition, a voice synthesizer, or maybe a giant RGB pixel? Well, here we're offering you some building-blocks you can put together to suit yourself

Since April 2008, to the delight of many of our readers, the pages of this magazine have been liberally sprinkled with a multitude of applications based on use of the ATM18 AVR board. On the Elektor forum, under the topic heading "Elektor ATM18 // overview of installments published [1] you'll find convenient links to all installments in the Elektor / CC2 ATM18 series.

In this article, it's not our aim to enter into the details of a complex implementation of the now world famous ATM18. No! Quite the reverse. For once, let's leave aside the structural and mathematical aspects, and spend a little time looking at how to use 'prefabricated' modules.

These days, the manufacturers' constant efforts to offer us ready-to-use modules mean we can forget the hardware in order to concentrate a bit more on putting these building-blocks together and programming them. It's now easy to create, put together, take apart, and combine functions to produce your latest 'toy'.

Of course, we shouldn't ever lose sight of the fact that electronics leaves no room for chance, and our keyword must be rigorousness. After all, there's no reason why you can't have fun and learn at the same time, is there?

For this particular construction game, I wanted to use voice recognition as well as the reproduction of sound effects and words. To make it a bit more fun, I've added a driver for an RGB module... so "Look, no hands!" Here are the building-blocks (easy to find [3])

we're going to be using:

- **VRbot:** voice recognition module.
- **Speakjet:** a board that can generate voice messages and complex sounds.
- **BlinkM MaxM:** module with three RGB high-brightness 10 mm LEDs designed to be driven via an I²C bus.

The whole project is based on solid foundations: Elektor ATM18, the 2-wire LCD display, and all the software developments that have already appeared and can be downloaded for free (BASCOM-AVR or AVR-GCC) and which can be used as a starting-point to modify or expand as necessary.


What would you say to a third hand?

What do you think of the ability to react to voice commands to replace pressing a button while your two poor little hands are busy holding test probes for precision measurements?

The VRbot voice recognition module can make this dream come true. The recognition is virtually Speaker Dependent (SD), i.e. the timbre of the voice is taken into account in the voice recognition. Say "Open Sesame!" and VRbot will respond to you, and only you! By default, VRbot also offers 25 pre-recorded words in a Speaker Independent (SI) mode.

Table 1. The VRbot vocabulary, divided into seven groups.

Group	Number of words	words
SD1	11	Red, Green, Blue, Mood light, Seasons, Thunderstorm, S.O.S., Black, Hue cycle, Virtual candle, White flash
SD2	6	Left, Right, Up, Down, Forward, Back
SD3	8	Action, Move, Turn, Run, Look, Attack, Stop, Hello
SD4	4	Elektor, VRbot, CC2, Adelek
SI1	8	Action, Move, Turn, Run, Look, Attack, Stop, Hello
SI2	6	Left, Right, Up, Down, Forward, Backward
SI3	11	Zero, One, Two, Three, Four, Five, Six, Seven, Eight, Nine, Ten

 

The user stores a collection of words in groups. At start-up, pressing button S1 on the ATM18 board (connected to PB0) allows you to navigate through a menu to choose one of seven groups: SD1 to SD4 (SPEAKJET_VRBOT_TEST_SD.bas) and SI1 to SI3 (SPEAKJET_VRBOT_TEST_SI.bas). The program loops through the selected test to let you test all the words in the group and, where applicable, see the action produced.

You have a few seconds in which to speak. If VRbot understands what you say, it displays the word spoken on the 2-wire LCD display. If it hears noise or if the word is poorly-pronounced or isn't in the memory, it will display "What?!?" If you take too long speaking when you are supposed to, it will display "Too late". VRbot originally does not speak French, so the author decided to teach it a few words of his native language (SD2 and SD3 in Table 1, English equivalents are shown). In group SD4, it's also taught four new words: Elektor, VRbot, CC2, Adelek. The first group (SD1) contains the names of the mood lights you need to say to drive the RGB module.

Let's take a moment to see how to teach VRbot one of the words in group SD1. To do this, we're going to use the famous USB/5 V TTL serial umbilical cord [4] that will allow us to connect the module to the PC on which you will already have installed VRbot GUI (V1.1.5) [5]. Connect the module to the USB/TTL cable, following the colours as shown in Figure 1, to end up with a cross-wired serial link. Plug the other end into a vacant USB port on your PC. Start the VRbot GUI software and select the language you want to use to speak the words in the SI group. Select the appropriate COM port and establish the link ('connect'); the software automatically imports words already recorded. A progress bar indicates how the import process is progressing. It's worth noting here that by default, VRbot is configured to operate at 9600 baud.

Now click on the group you want to add words to. Select 'add command' and give it a name, like WHITE_FLASH (for example) for index 10 in group 1 (SD1). Figure 2 shows that the command has been created, but not yet recorded ('Trained: 0'). This is not the moment to be struck dumb with excitement, you're going to

have to speak: soprano or tenor, it doesn't matter! You just need to repeat the same word twice with the same intonation at about 40 cm from the mic so that the command can then be recognized

 


Figure 1. VRbot and the USB link. Don't forget to connect up a microphone.

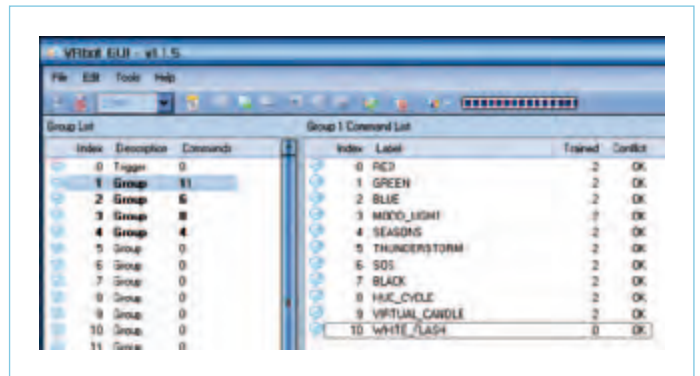


Figure 2. Eleven mood lights. The last one has not been taught ('Trained = 0').

 


Figure 3. How to connect VRbot to the ATM18 board. Connect the ATM18 board's S1 push-button to PBO.

 


Figure 4. Connecting up the 2-wire LCD display, as described in [2].

 


Figure 5. Speakjet and the USB link. This is a one-way connection: this talkative module is too snobby to talk to the computer!

by the system ('train command'). Once the groups have been created, you can have fun testing them ('tool', then 'test group'); if the word is recognized, it is highlighted in flashing green.

At this stage, the VRbot module is ready to be built in to the system. Figure 3 shows the pin-out to follow for connecting to the ATM18 board, Figure 4 shows the same thing for the 2-wire LCD display.

Speakjet...

...uses a 'phoneme'-based voice synthesis technique, just as humans do. Phonemes are the building-blocks that allow us to construct words. An allophone is a possible sound variant of a phoneme. Combined end-to-end, the phonemes form words or phrases. There are 72 sound components available, and using them we're going to be able to form the word 'Elektor'. It's also possible to adjust a multitude of parameters to add tone of voice, a slangy pronunciation, or a question at the end of a sentence, for example. So you need to think of it in terms of the sounds that come out of our mouths, while also allowing for the fact that sounds will be pronounced differently according to their position in the word and the influence of the surrounding vowels. For example, the B in book will not be pronounced the same way as the B in baby.

There are numerous nuances, but the device's technical documentation is very comprehensive and you'll find it essential reading. You'll be able to learn all about the use of diphthongs, silences, stressed and unstressed intonations, and so on.

A bit more fun is the possibility of producing 43 sound effects (alarm, biological noises, etc.) and 12 DTMF frequencies.

So we're going to implement the board based around the Speakjet IC. The Phrase-A-Lator [6] software lets you communicate directly with the module so you can test the words in the built-in dictionary or ones you've made up yourself, along with the sounds. It's also possible to control events according to the state of certain inputs, and to store words in EEPROM memory so that you can then very easily call them up using just a few lines of code. A small area with solder pads will let you very quickly solder an adjacent row of six male pins, which will let you program the board directly, once again using the USB/5 V TTL serial cable. To do this, you need to solder three wires as shown in Figure 5: TxD of the USB/TTL serial cable (pin 4, orange) to the 'pin 2' on the Speakjet board that's next to the 'TX'

Table 2. Here's how a few other words can be formed.

And	\SLOW \AY \SLOW \NE \OD
ATM18	\EYIY \IY \TU \IY \IY \EH \EH \MM \NTF#2 \EYIY \P4 \TT \IY \NE
Present	\PO \FAST \RR \EY \SE \EH \NE \TT
Speakjet	\SE \PE \SLOW \IY \EK \JH \EH \TT
VRbot	\SLOW \VV \SLOW \IY \P6 \P6 \AWRR \P6 \P6 \BO \OH \TT

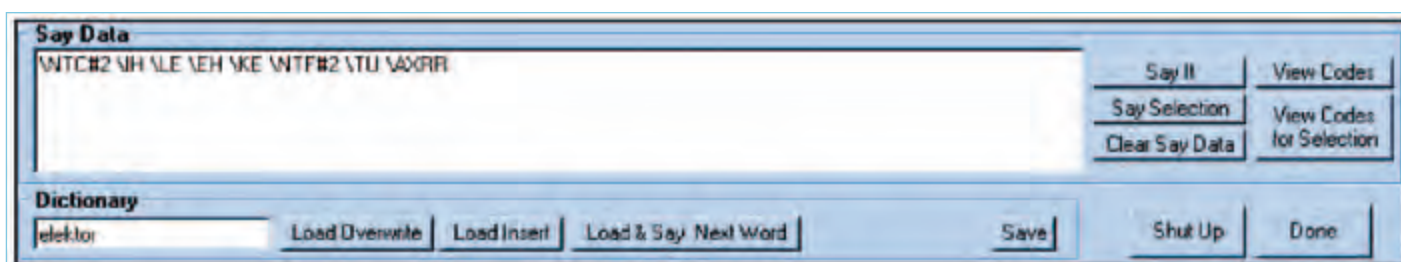


Figure 6. Make it say what you want it to.

pin; the +5 V rail (pin 3, red) and ground (pin 1, black) for powering the board will be derived from the USB port via the same connector. After installing the Phrase-A-Lator software, connect the whole thing to a vacant USB port on your PC. You should then hear a robotic voice say “ready”, telling you that everything is in order. Run the software, select the COM port and click ‘Test serial connection’; you should hear another “ready” to indicate the link is working. Now click on Phrase-A-Lator and compose the word ‘Elektor’, with the help of Figure 6. Click on the ‘say it?’ button, and hey presto! it’s said it.

Table 2 shows how to construct the other words of the welcome message “Elektor and ATM18 present Speakjet and VRbot” which will be heard when the Talk Show is powered up.

You’ll need to save the words into EEPROM memory so you’ll be able to call them later on using a few lines written in BASCOM-AVR. The procedure is simple. Run the Phrase-A-Lator software, then select ‘EEPROM editor’. When editing the last word (in this case, ‘Elektor’), refer to Figure 7 for the four steps to follow for saving all the words to the EEPROM. You’ll need to take care to store all the terms in the correct places in the EEPROM memory.

Clicking on ‘view codes’ will let you generate part of the code

needed to complete the program in BASCOM-AVR (Figure 8). Click the ‘save’ button to save your composition into the dictionary. Lastly, Figure 9 shows how to connect the Speakjet module to the ATM18 board. Make sure you use the right ‘pin 2’ — it’s the one next to the ‘TX’ pin.

Mega 1-pixel display

The last building-block we’re going to be using (Figure 10) includes three 10 mm high-brightness RGB LEDs. Figure 11 shows how to connect this “mega” pixel to the ATM18 board.

The whole thing is designed to be driven via an I²C bus. Additive synthesis is used, and 3×8 bits allow the colour mix to be controlled very precisely. And that’s not all — there are lots of options for configuring this giant pixel, like the generation of various display sequences in stand-alone mode, the choice of transition speed, random illumination, etc.

At start-up, by way of a test, the color displayed will be Elektor red (217 / 0 / 0 in decimal). Our ‘smart pixel’ will follow pre-defined scripts. Say one of the eleven mood lights in group SD1 in order to see it appear on the RGB LEDs: ‘storm’, ‘virtual candle’, ‘seasons’, etc. — whatever you feel like.

Summary of Talk Show operation


At start-up, you’ll hear ‘ready’, so Speakjet is ready to speak. The I²C address of the RGB module is detected automatically. The welcome screen comes up and Speakjet speaks the text at the same time. Next it displays the number of words in VRbot’s first four SD groups (Table 1).

Pressing S1, accompanied by a pretty tinkling sound, will let you browse a menu where you can select the group to be tested. By default, group SD1 or SI1 is active (depending on the program loaded).

Speak when you are prompted to. If you take too long, you’ll get the reply “Too late”; if you pronounce the word badly or there is background noise, the reply is “What !?!” If the word spoken is recognized (“Fine!!!”), it is displayed and, where applicable, the event is triggered. As it stands, the mood lights (SD1) are activated and emitted by BlinkM MaxM or the word “Elektor” is spoken (SD4).

Pressing S1 will take you back to the main menu, otherwise the test will loop indefinitely through the selected group.

Note that if a problem arises while the VRbot module is being detected, a superb alarm generated by Speakjet is set off and the message “YOU MUST RESET!!!” is displayed. In this event, press button S4 (RST) on your ATM18 board (μ C reset) or wait ten seconds for the program to re-boot of its own accord.

 

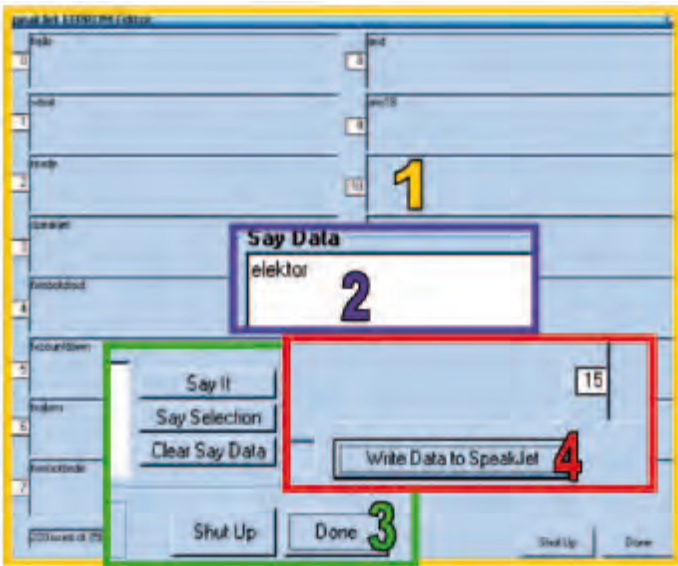


Figure 7. End with “Elektor” so you can then finally save the words in the EEPROM memory (step 4). And have you tried number seven (fxrobotbede)? Does it remind you of anything?

 


Figure 8. The code generated for the word “Elektor”. The values mean that the volume (20) is set to 96, speed (21) to 114, pitch (22) to 88, bend (23) to 5, then 22 and 65 (sets the frequency to C#2), 129 (\IH), 145 (\LE), 131 (\EH), 194 (\KE), 22 and 87 (sets the frequency to F#2), 192 (\TU), and to end 151 (\AXRR).

P.S. The author used the ATM18-DIP version (090896) as published in the 2010 Summer edition instead of the ATM18 controller board (# 071035-91)

(100360)



Figure 9. Connecting up the Speakjet. Note that the pin referred to as ‘2’ is the one next to the ‘TX’ pin.



Figure 10. The mega-pixel BlinkM MaxM display is amazingly powerful, it generates a light source 1000 times brighter than a standard high-brightness LED! So it’s vital never to look directly at the light source, at risk of serious eye damage.

Internet Links

- [1] www.elektor.com/forum/elektor-forums/recent-main-projects-and-articles/elektor-atm18.1149868.lynkx
- [2] www.elektor.com/071035
- [3] Modules: www.lextronic.fr
- [4] USB / TTL serial cable: www.elektor.com/usb-ttl
- [5] VRbot: www.tigal.com/1770
- [6] Speakjet: <http://www.magnevation.com> (Download page)
- [7] BlinkM MaxM: www.sparkfun.com/commerce/product_info.php?products_id=9000
- [8] Project software: www.elektor.com/100360

 


Figure 11. Connecting up the giant pixel.

Subscribe to Circuit Cellar now!

This magazine has a topic that keeps me busy on making prototype projects, advances in electronic design ideas, & always wondering what would be the next. For me, being informed in my field of expertise, it really adds confidence in my career.

R. Arcilla,
Celestica Philippines, Inc.

Circuit Cellar Magazine

- Influencing the design and production of embedded hardware and software systems by providing in-depth articles & highly technical content since 1988.

- Enabling readers to make intelligent assessments and decisions in real-world project development scenarios when informed decisions are required.

- Delivering thousands of samples to engineers through global sampling and contest programs.



Sign up today and
save up to 66% off the
cover price!
Digital 2.0 for
just \$38

CC 2.0: Enhanced Subscription Services Give You More!

- Quickly link to code and project files
- Search the CC Library by author, title or topic
- Receive exclusive specials and "deals" from preferred vendors
- Access Circuit Cellar's contest archives for inspiration and abstracts from recent design contests

Visit www.CC-Access.com today to sign up for your preferred delivery method: Print, Digital or Combo 2.0! Every option provides exclusive entry to CC-Access and the incredible subscriber benefits listed above.

Take out your 2.0 subscription now: www.CC-Access.com

Phone 860.875.2199

CIRCUIT CELLAR
CC-ACCESS

SUBSCRIBERS RESERVED AREA

www.circuitcellar.com

**CIRCUIT
CELLAR®**

UniLab Duo

2 x 0–30 V 3 A bench PSU

The UniLab bench supply we published in the April 2010 issue of *Elektor* has proved very popular. Here we show how to extend the project into a twin-output supply taking full advantage of the dual voltage/current display published in the September 2010 issue, including wiring plan and front panel design.

UniLab is a bench power supply based on a switching regulator. Technical details and a circuit description can be found on the *Elektor* website [1]; and you can purchase the printed circuit board (order code 090786-1) from the Elektor Shop, as well as a kit of parts (090786-71) which includes the printed circuit board along with all components apart from the mains transformer. For the twin-output version of the supply we need two populated boards plus the dual voltage/current display circuit. The four-line by twenty-character display shows the two



output voltages and output currents as well as the temperature inside the unit's enclosure. Again, the display circuit is available as a complete kit of parts from the *Elektor* shop (order code 100166-71), including printed circuit board.


Optionally you can add the soft-start circuit from our 1997 Summer Circuits issue ('Mains on delay circuit'), included in the wiring plan in **Figure 1**, which limits the input current on the mains side to avoid those embarrassing moments when you

switch the power supply on and trip the circuit breaker in your consumer unit, plunging the house into darkness. The printed circuit board can be obtained via the project web page [3].

Transformer and enclosure

For the prototype shown here we used a toroidal transformer with two 25 V secondaries rated at 3.2 A. The two 8 V windings for powering the voltage/current display were manually added to the transformer, as described in the original article in Septem-

  

 

ber 2010. It is of course also possible to use a separate 3.3 VA transformer with two 8 V windings to power the display, assuming it will fit in the enclosure.

The two-part metal enclosure we used is the Telet LC1050, which has been used in *Elektor* projects in the past. Sadly Telet has since disappeared from the market. The case measures 22 cm wide by 25 cm deep by 12 cm high (8.7 x 10 x 4.7 inch). A front panel was designed for use with the enclosure (**Figure 2**), and the layout is available as a freely downloadable PDF file on the project web page [4]. Various methods for making the front panel overlay were described in an *Elektor* article in November 1997 (article available, see [5]).

It is of course possible to use a different model of enclosure as long as it is large enough to hold all the boards and transformer (or transformers). The dimensions of the front panel will need to be adjusted accordingly.

Construction

The first step is to equip the enclosure with an extra baseplate made from 2 mm (0.08 in.) aluminium sheet, designed to fit the enclosure's side mounting rails. This 'mezzanine floor' simplifies mounting the various parts and avoids modifying the enclosure's bottom panel. Everything apart from the voltage/current display, the current-limit LEDs, the output sockets and the mains inlet is fixed to this plate.


 


Figure 1. Overall wiring diagram for the twin-output bench supply.

To economise on space the two UniLab boards are mounted vertically. The required mounting brackets can be made from 1.5 mm (0.06 in.) sheet aluminium: mark the fold line and bend the sheet in a vice with the help of a short wooden batten. The dimensions of the brackets are available as

a downloadable PDF along with the front panel drawings [4].

 The mounting positions of the two UniLab boards are determined by the position of the holes for the potentiometer spindles in the front panel. In our prototype the potentiometers were bolted to the mounting



100529 - FRONT

Figure 2. The front panel design can be downloaded free from the *Elektor* website and printed out onto a suitable film.

brackets behind the front panel rather than to the panel itself, but at the same height as the holes in the panel. The bracket and the UniLab boards were then fixed to the baseplate using M3 screws. Take care to ensure that there is enough space for the display board and the three output sockets between the two UniLab boards. If necessary, fit pieces of insulating material to prevent short circuits.

The toroidal transformer is mounted on the baseplate behind the UniLab boards using the M6 screw and nut supplied with it. On the right next to the transformer there is enough space on the rear panel of the enclosure to fit a mains inlet module, incorporating a mains switch and fuseholder. The optional soft-start circuit board can be mounted to the left of the transformer. The display requires a rectangular cut-out in the aluminium front panel measuring 76 mm by 25 mm (3 x 2 in.). This can be made using a fine-toothed fretsaw, neatening up the results with a warding file. To mount the voltage/current display we fixed M3 bolts to the inside of the front

panel using a two-component adhesive. It is important to key and degrease the relevant areas of the panel before applying the glue.

Wiring

The complete wiring plan is shown in Figure 1. It is important to observe the gauges of the various wires involved: the connections to the output sockets should be made using 2.5 mm² (approx. 13 AWG) wire, while ordinary 0.75 mm² (approx. 18 AWG) insulated stranded hook-up wire can be used for all the other connections.

Exposed metal on all wires carrying mains voltages should be carefully insulated at the AC power inlet module using heatshrink tubing, and of course you must ensure that the chassis is securely connected to AC power-line Earth.

The voltage/current display is simply connected using six-way flat cables and headers.

(100529)

Internet Links

- [1] www.elektor.com/090786 (UniLab bench supply)
- [2] www.elektor.com/100166 (dual voltage/current display)
- [3] 'Mains On Delay Circuit', *Elektor Electronics* July & August 1997 (article on Elektor 1990-1999 DVD)
- [4] www.elektor.com/100529 (front panel artwork)
- [5] 'Make your own Front Panels', *Elektor Electronics* November 1997 (article on Elektor 1990-1999 DVD)

From Microphone to Line Input

By A.J. Ribbink (The Netherlands)




The requirements a microphone preamplifier is expected to meet are very different from those formulated for a line amplifier. For the first, a large gain and a low noise contribution are very important, while a line amplifier has to be able to handle a much larger signal without generating distortion. A microphone input has a sensitivity of a few millivolts; a line input must be able to cope with several volts.

In most cases a different type of circuit is used for each of these different types of input. With the circuit described here it is however possible to meet both requirements at the same time. Using only a single potentiometer, both the gain and the volume can be adjusted.

A dead common (audio) amplifier is shown in **Figure 1**. In this circuit the amplification (gain) A is determined by the ratio of the feedback resistor R to R_1 as follows:

$$A = (R+R_1) / R_1.$$

   Volume control R_p is really nothing more than a voltage divider comprising R_3 and R_2 , where $R_2 + R_3 = R_p$. Drawing it in a different way



results in the schematic of **Figure 2**. The operation of the voltage divider can be expressed as:

$$D = R_2 / (R_2 + R_3).$$

Gain factor A and division ratio D together determine the amplification of the overall circuit as in

$$U_{out} = A \times D \times U_{in}.$$

The output voltage is therefore adjustable by changing R_1 and/or R_2 .

Because of the opposite actions of R_1 and R_2 — a larger value of R_1 results in a smaller output voltage, while a larger value of R_2 increases the output voltage — these two resistors can be combined as illustrated in **Figure 3**. In this way, using only a single potentiometer,

both gain and volume can be controlled.

R_1 is still present in **Figure 3**, where its function is to limit the maximum gain. The additional resistor R_4 has two purposes: it prevents a potential (and undesired) short circuit of the amplifier output and forms the voltage divider for the volume control, together with the R_3 part of the potentiometer.

The circuit can be used with ICs as well as amplifiers built from discrete components. The value of R_4 can be changed to the desired output impedance and the volume control curve. If control all the way down to zero volts at U_{out} is not required, then U_{out} can also be taken directly from the output of the amplifier circuit.

A bad contact in the wiper of the potentiometer will not result in too much of a cracking noise, because $R_1 + R_p + R_4$ are connected in parallel with feedback resistor R . The gain is reduced in the event of poor wiper contact, which means that cracking noise remains limited. In most circuits R_1 has a much smaller value than R_2 . For a smooth control, R_1 should therefore change value much slower than R_2 . A (reverse) logarithmic potentiometer is therefore recommended. With a normal logarithmic potentiometer the volume will reduce

when the potentiometer is turned clockwise! A reverse-log potentiometer or a logarithmic slide potentiometer mounted 'upside down' gives a normal, familiar control.

Suitable resistance values are, for example, 50 k Ω for R_p , 22 k Ω for R , 56 Ω for R_1 and 220 Ω for R_4 . Using these values the maximum and minimum amplification are about 360 and 1.5, respectively.

At the lowest operating frequency the capacitors need to have a (much) smaller impedance than R_1 and R_4 . The input impedance of the circuit is mostly determined by resistor R_{in} and can be adjusted to suit whatever signal sources are likely to be connected. Noise suppression filters and/or frequency dependent networks can be connected in front of this. Frequency dependent feedback is not recommended for this circuit, because the the RC filter characteristic will change when the gain and volume are adjusted.

(090182-1)

Camera Interval Timer

With infrared remote control



By Jean-Pierre Gauthier (France)

As a passionate orchid-grower, I wanted to photograph these beautiful flowers as they opened, so as to understand and admire their blossoming. I first tried to do it using my camera's remote control, but that wasn't very practical. Taking a closer look at my camera's instructions, I noticed that the shutter and focus commands were accessible via a jack socket. That was just what I needed...

Technical characteristics

- PIC16F886 microcontroller
- Compatible with Sony SIRC remote controls
- Number of photos programmable between 1 and 100
- Interval programmable between 1 and 3,599 s
- Automatic standby
- Optimized for Canon EOS camera, but can be used for any other purpose

The camera shutter operating system described here makes it possible to take photos at a predefined interval, or to trigger two cameras together for stereoscopic shots. This device makes it possible, for example, to take a series of photos every 30 minutes of a flower as it opens, a baby bird hatching, etc. so as to include them in a video. The system was originally designed

for a Canon EOS camera, but it can readily be adapted for other cameras that are able to be remote controlled.

The timer is capable of taking from 1 to 100 photos at intervals from 1 second to 59 minutes, 59 seconds, with or without pre-focusing. The parameters are stored in EEPROM. An alphanumeric LCD uses four lines of 20 characters to show the number of shots taken and display menus to help you configure the device. The backlight is controlled by the microcontroller.

If necessary, you can adjust the focus and shot at any time between shots by using a remote control compatible with Sony's SIRC protocol [3]. Once all the photos have been taken, the timer goes into stand-by mode to save power.

A simple circuit

Thanks to the use of a microcontroller, the circuit itself (Figure 1) has been kept simple: four push-buttons, a liquid crystal display, and a few additional components are all it

 


Figure 2. Here's how to wire up the control plug for the Canon camera.

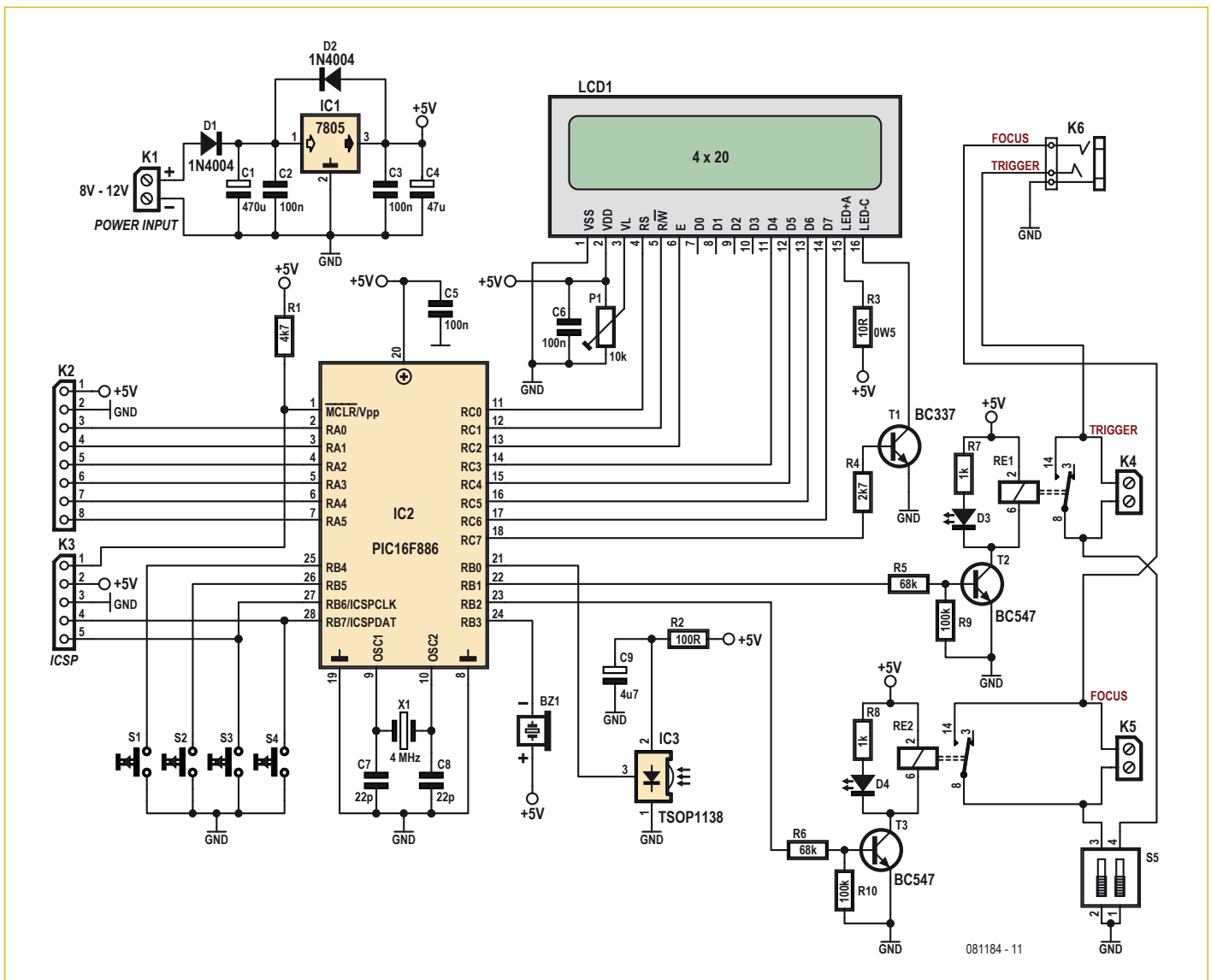


Figure 1. The timer is a basic microcontroller project.

 


Figure 3. Setting key 1 of the remote.

 


Figure 4. Setting key 2 of the remote.



Figure 5. Setting the number of photos to be taken.

 


Figure 6. The first menu in 'Normal' mode.

 


Figure 7. Setting the interval between two shots.

 


Figure 8. The screen during shooting.

takes to control the camera. The shutter and focus commands are produced using two relays RE1 and RE2, driven by transistors T2 and T3. The two relays connect the contacts of the jack socket K6 to ground via the switches in S5. **Figure 2** shows how to wire the jack so as to be compatible with a Canon camera.

Provision has been made for two additional terminal blocks (K4 and K5) in case the project is going to be used to drive something other than a Canon camera. In this case, the positions of the S5 switches depend on the application.

Each output has an LED to let you see at a distance if one of the relays is on or not. The buzzer BZ1 offers the possibility of producing an audible signal, for those instances where you might not be able to see the LEDs.

The remote control signal is picked up by IR detector IC3.

Transistor T1 is used to enable the backlight only when it is needed – a handy function that all too often still gets overlooked.

Thanks to regulator IC1, the circuit can be powered from any voltage between 8 and 12 Vdc.

Software

As for every microcontroller circuit, the software is what makes all the functions possible. Here, the software (available free from [1]) has been written in C and compiled using the free 'lite' version of the Hi-Tech C for PIC10/12/16 compiler (version 9.70) [2]. Interaction with the software is achieved via a series of menus, around which we navigate with the help of the four push-buttons S1–S4. Their function depends on the menu selected and is displayed on the LCD using little 'icons'.

If S1 is pressed while power is applied to the circuit, the software goes first into configuration mode before going into normal mode. A series of menus appear that let you configure the remote-control keys (**Figures 3 and 4**) that will be recognized by the timer (see **Table 1**, don't use the same code twice!) and the number of photos to be taken (**Figure 5**). In these menus, pressing S2 decreases the value displayed, while pressing S3 increases it. S1 lets you store the value in the EEPROM and go on

to the next menu. S4 is only used in the third menu, where it offers the possibility of enabling the backlight.

In normal mode, a menu is displayed (**Figure 6**) that shows the status of the buzzer (S3) and pre-focus (S2). Pressing S4 brings up a new menu where S2 and S3 are used to set the time delay between shots from 0 to 3,599 seconds (i.e. 1 hour less 1 second, **Figure 7**). For user convenience, if you keep one of these two switches pressed, the value increases or decreases automatically. This function works in the other menus too.

Table 1:

The codes for some of the keys on an SIRC remote control, as seen by the timer. It only accepts codes between 128 and 137, i.e. the '0' to '9' keys.

HEX	decimal	key
0x80	128	1
0x81	129	2
0x82	130	3
0x83	131	4
0x84	132	5
0x85	133	6
0x86	134	7
0x87	135	8
0x88	136	9
0x89	137	0
0x8C	140	1-
0x8D	141	2-
0x90	144	Program+
0x91	145	Program-
0x92	146	Volume+
0x93	147	Volume-
0x94	148	Mute
0x95	149	Standby
0x96	150	Normal
0xA5	165	TV/Video
0xB4	180	+
0xB5	181	-
0xB6	182	Sleep
0xBA	186	Display
0xBC	188	Select

COMPONENT LIST

Resistors

(5%, 0.25 W unless otherwise indicated)

R1 = 4.7k Ω
 R2 = 100 Ω
 R3 = 10 Ω , 0.5 W
 R4 = 2.7 k Ω
 R5,R6 = 68k Ω
 R7,R8 = 1k Ω
 R9,R10 = 100k Ω
 P1 = 10k Ω trimpot, horizontal

Capacitors

C1 = 470 μ F 25V radial
 C2,C3,C5,C6 = 100nF ceramic
 C4 = 47 μ F 16V radial
 C7,C8 = 22pF ceramic NPO
 C9 = 4.7 μ F 16V radial

Semiconductors

D1,D2 = 1N4004
 D3,D4 = LED, red, low current, 3mm
 IC1 = 7805, TO-220 case
 IC2 = PIC16F886-I/SP, SPDIP28
 IC3 = TSOP1138, 38 kHz IR receiver (e.g. Farnell # 4913036)

T1 = BC337

T2,T3 = BC547

Miscellaneous

BZ1 = piezo buzzer, lead pitch 7.62mm (e.g. Farnell # 1502726)
 RE1,RE2 = relay, miniature SPST-NO, 5 VDC (e.g. Farnell # 9561757)
 K1,K4,K5 = PCB terminal block, lead pitch 5mm
 K2 = 8-pin pinheader, lead pitch 0.1 inch
 K3 = 5-pin pinheader, lead pitch 0.1 inch
 K6 = 2.5mm 3-way jack socket (e.g. Farnell # 1308867)
 LCD1 = LCD, 4x20 (e.g. Elektor # 050176-73)
 S1-S4 = SPNO pushbutton (e.g. Farnell # 1555982)
 S5 = 2-element DIP switch
 X1 = 4MHz quartz crystal
 SPDIP28 socket for IC2
 PCB, Elektor # 081184-1 [1]



If your version of the timer works first time, it's thanks to Daniel in the Elektor lab. If it doesn't work, then it's entirely your own fault.


Pressing S4 starts shooting. The Focus output is active for 400 ms ten seconds before each shot is taken (if pre-focusing has been enabled, of course). Depending on how the buzzer is configured, this event may be accompanied by an audible signal. Firing the Trigger output, also for 400 ms, also activates the buzzer (if enabled). The elapsed time is displayed briefly, and pressing S3 lets you mute the buzzer.

The number of photos taken is updated then displayed on the LCD after each shot (Figure 8). Pressing S4 for at least 2 s allows you to stop the count at any time and go back to the start menu.

If the timer finishes its program without being interrupted, it plays a little tune and then goes into stand-by. You then have to reboot it, or 'wake it up' using the remote control, followed by a long (at least 2 s) press on S4 to start a new series of photos.

Remote control

 As indicated above, the timer can be controlled by a Sony remote control or any other remote capable of 'speaking' SIRC [3] — for example, a 'universal' remote. The remote lets you activate the Trigger or Focus outputs manually at any moment (except in stand-by) without affecting the



program currently running. It also lets you 'wake up' the circuit, in association with S4. This is possible through the use of an external interrupt, provided by IC3.


Table 1 shows the correspondence between the remote control key number (as seen by the timer) and its function as envisaged by Sony.

(081184)

Internet Links

- [1] www.elektor.com/081184
- [2] www.htsoft.com/downloads/
- [3] picprojects.org.uk/projects/sirc/

Simulation

 

By Gerard Fonte (USA)

There have been countless simulators around for a very long time. Some, like aircraft simulators, cost millions of dollars. Some, like Ltspice are free (www.linear.com). Simulators are powerful tools that provide insight into how your circuit operates. However, it is important to remember that simulators are tools and they cannot guarantee that your circuit (or aircraft) will operate as indicated.

Smoke and Mirrors

A good simulation mirrors how a device will operate under certain conditions. The operative phrase is “certain conditions”. Quite simply, if the conditions that are assumed to be in place are not in place, all bets are off. For example, your simulator may predict perfect operation. Yet, your breadboard circuit with a very expensive IC, blissfully and immediately starts smoking as soon as you apply power. It cannot be overstated that a simulation is not real. It is only an estimate of what is possible.

Try this experiment with your analog simulator. Select an audio amplifier design that directly drives a speaker (preferably one that works off a single supply). Place the speaker in series with the input power and ground the speaker output. In reality, there will be reasonable audio coming out of the speaker because the current into the amplifier will vary with the amplitude of the input signal. However, if you measure the simulated voltage across the speaker, most likely there will be no audio signal. This is because most simulators assume that the power supply pin is a fixed voltage. This peculiar hook-up is not something that is considered.

Model Behavior

Digital simulators are easier to design than analog ones. The reason is pretty obvious. Digital signals are much simpler and easier to define. Timing relationships are easy to calculate. Even the effects of heat and voltage variation create predictable effects. In general, digital simulations are much more accurate than analog ones.

Analog simulators require many more factors to process. As such, they are more complicated. In theory, any analog circuit can be defined by its resistance, capacitance and inductance. Of course, it's very difficult to build an amplifier with just resistors, capacitors and coils. You need transistors and other semiconductors. The problem here is that semiconductors exhibit non-linear performance characteristics. That is, their operation changes according to changes in voltage, current, frequency, loading and a lot of other variables. This is why things get very complicated very fast for analog simulators.

The solution is to build models of how a particular device operates. Obviously it is not practical for an individual to fabricate a model of a manufacturer's IC. In order to do so requires intimate knowledge of the actual internal circuit as well as the wafer processing techniques. So the user is required to blindly accept the model that the manufacturer provides. Some manufacturers go to great lengths to provide very accurate models so that typical SPICE simulations are as good as possible. Some manufacturers provide models that are

not as accurate. The only way to know if the model is good or bad is to test it. This takes time and effort that few people are willing to expend. The result is that all manufacturer's models are generally assumed to be perfectly accurate, even though nothing is perfect.

Outside Influence

The other weak point about simulators is that they assume an ideal world. Clearly, the real world is not ideal. If you breadboard a circuit using a typical prototyping-board, (white board with the rows of holes) you probably didn't simulate the 3 pF capacitance that exists between adjacent rows of holes. Then there is the noise of the power supply you are using. And the internal resistance of the batteries. And the unintended ground-loop in the PCB layout. And on and on. It is critical to realize that the physical design of the circuit can be, and often is, the defining factor in its performance.

At the start, I mentioned that a good simulation resulted in a spectacular failure. Now it's easy to see how this happened. The high-speed current-amplifier PCB layout was bad and the amplifier oscillated. This resulted in the amplifier drawing excessive current which overheated the part and caused it to fail (not uncommon for oscillating current-amplifiers).

There are lots of outside factors that cannot be simulated or even anticipated. Oftentimes these factors are only identified in the prototyping or debugging process. They may not come from the simulated circuit at all. For example, there may be excessive heat from some different circuit. An opening relay may cause a voltage spike. Again, there are an indeterminate number of outside factors that can affect your circuit. It is simply impossible to simulate this.

Great Expectations

A simulation should be considered as the best possible theoretical performance of a circuit. A good simulation is a starting point for your design. It should have an excess performance margin for the loss you will experience when going to a physical construction. A good simulation is really a confidence check on your design concept. It gives you an idea of what to expect.

Now, if your simulation doesn't work, you can be nearly certain that a real circuit won't work either. One very strong advantage of simulations is that they can quickly rule out non-functioning designs. Additionally, it is often easier to determine why your circuit fails with a simulation than with a real prototype. This is because of all the virtual tools that are available. You can monitor a dozen voltage points easily and have the equivalent of a six channel oscilloscope. Having a test-bench with all the possible instruments you could want is very nice. In this situation, simulation is a very powerful learning tool. Understanding why things don't work can provide considerable insight into why things do work.

But it must always be remembered that simulation is just a tool. It's important to know how to get the most out of any tool you use. Every tool has its limits. Any tool can be mis-applied. And, while you can't drop this tool on your toe, abusing simulations can affect your mental health.

(100692)

Hexadoku

Puzzle with an electronics touch

It's gratifying to see the monthly response to Hexadoku measured in terms of correct solutions received from readers all over the globe. Thank you all for making this a success and do you reckon you can solve the one below? Enter the right numbers in the puzzle, send the ones in the gray boxes to us and you automatically enter the prize draw for four Elektor Shop vouchers. Have fun!

The instructions for this puzzle are straightforward. Fully geared to electronics fans and programmers, the Hexadoku puzzle employs the hexadecimal range 0 through F. In the diagram composed of 16 × 16 boxes, enter numbers such that **all** hexadecimal numbers 0 through F (that's 0-9 and A-F) occur once only in each row, once

in each column and in each of the 4×4 boxes (marked by the thicker black lines). A number of clues are given in the puzzle and these determine the start situation. Correct entries received enter a draw for a main prize and three lesser prizes. All you need to do is send us the numbers in the gray boxes.

Solve Hexadoku and win!

Correct solutions received from the entire Elektor readership automatically enter a prize draw for one Elektor Shop voucher worth \$140.00* and three Elektor Shop Vouchers worth \$70.00* each, which should encourage all Elektor readers to participate.

* subject to exchange rate.

Participate!

Before December 1, 2010, send your solution (the numbers in the gray boxes) by email, fax or post to

Elektor Hexadoku – 4 Park Street – Vernon CT 06066
USA.

Fax 860 8751-0411

Email: hexadoku@elektor.com

Prize winners

The solution of the September 2010 Hexadoku is: 3AE58.

The £80.00 voucher has been awarded to: Udo Altmann (Germany).

The £40.00 vouchers have been awarded to: Stefanie Kalkbrenner (Germany),

Suzanne Pecado (France) and W.J. Vis (the Netherlands).

Congratulations everyone!

F				1		2	D			A			0	C
6				9	7	5	1			3	A	F	2	E
D		A	2	E		0			8	9	B	5	6	
4				A			6			C		D	3	
		B	E			3	0	C		D		6	5	
0	D					1	4	E		2	8		A	9
		2		5		9		3		7	F	B	0	E
9	3	8		C	6	A				B	5		7	
5			D	F	8	2								
		1							F	6	0		4	
C	7		8	4		6				3				A
	F	6	A	1	3		7			4		2		B
	C				5					2				
	B			8		D	C	0						5
	5	F			2		6	A		1			C	
	A	7			4	F			9			3	8	B

(c) PZZL.com

F	8	3	4	C	2	B	7	1	0	D	5	6	9	E	A
A	0	5	6	D	4	F	9	C	E	7	3	B	8	2	1
E	D	C	1	8	0	5	A	2	6	B	9	F	7	3	4
2	9	B	7	E	6	1	3	F	4	A	8	C	D	0	5
D	3	A	E	5	8	6	0	B	7	4	F	9	1	C	2
9	1	0	C	4	F	7	B	E	D	6	2	3	5	A	8
5	7	6	8	1	9	2	D	0	C	3	A	E	4	F	B
4	B	2	F	3	A	E	C	5	8	9	1	7	0	6	D
1	6	4	D	9	B	8	E	3	2	5	0	A	F	7	C
3	E	8	B	A	C	4	2	D	1	F	7	5	6	9	0
0	C	9	5	F	7	3	1	6	A	8	B	D	2	4	E
7	A	F	2	0	5	D	6	4	9	C	E	8	B	1	3
6	4	7	9	2	D	A	5	8	3	1	C	0	E	B	F
B	F	1	A	6	E	C	4	9	5	0	D	2	3	8	7
8	2	D	0	7	3	9	F	A	B	E	4	1	C	5	6
C	5	E	3	B	1	0	8	7	F	2	6	4	A	D	9

The competition is not open to employees of Elektor International Media, its business partners and/or associated publishing houses.


Chauvin-Arnoux MD7



By Jean-Marc Dubrunfaut (France)

Since the famous compass that Ampère christened a 'galvanometer', two successive types of voltmeter have held sway. The first of these combined the idea of having the conductor wire make several turns around the needle with Ampère's astatic system (the idea of using two mechanically-coupled magnetic needles with opposing poles, with only one of the needles subject to the influence of the electrical current, in order to get round the problem of the Earth's magnetic field). The second was the moving-coil voltmeter, where it is no longer a magnet that moves within a coil, but a coil that moves within a magnet.

 If we combine these two principles by placing one moving coil within another coil, the deviation obtained depends on the product



The switch wiring.

of the two currents: we have created an analog multiplier. The stationary coil consists of a small number of turns of large-diameter wire and is connected in series with the device under test (DUT). The moving coil has a large number of turns of fine wire and is connected, via a series resistor, in parallel with the DUT. The first is called a 'current winding', the second a 'voltage winding'. This very special voltmeter is the heart of the commonest analog wattmeters: electrodynamic wattmeters.

Unlike the ferromagnetic voltmeter, the magneto-electric voltmeter can only operate on direct current, since the sense of the deviation depends

on the direction of the current. But in the case of a wattmeter, the fact that the polarities to both stationary and moving windings are inverted together means that it works just as well on AC as DC, and without the user even needing to change ranges! Better still, the value obtained in AC is inherently the active power. The deviation is linked to the product of the instantaneous values of voltage and current. This product is smoothed by the inertia of the moving element and by the air damper, hence we obtain the mean value of the instantaneous power, which is what is measured by the supply authority's meter, i.e. $U \times I \times \cos(\phi)$ in the case of a pure sinewave.

And we don't need to do anything further to obtain a value that integrates both AC and DC components, as this is what happens by default. However, one real limitation compared to digital wattmeters is that the frequency of the current to be measured must remain within narrow limits. If it's too low, the mechanical smoothing would be insufficient; if it's too high, the measurement will be distorted by the self-inductance of the coils. The usable operating frequency range of this type of device never exceeds a few hundred hertz (the dial of the MD7 indicates 50 Hz, but our experiments show that it manages ten times that). So this bandwidth excludes high-frequency signals if they are too distorted, because of their harmonics. But at low frequencies, and in particular at 50 Hz, the measurement is accurate for signals of any shape (including squarewaves and clipped sinewaves).

The separate I and U circuits (they are even electrically isolated) offer several advantages. Firstly, they allow a choice between upstream and downstream measurement, which is useful, given the Z_{in} of 5 k Ω . Then, when making measurements on a transformer, there's nothing to stop you measuring the current in the primary and the voltage on the secondary, or vice-versa (not forgetting to take the transformer ratio into account), with the object of making the best use of the input ranges of the device depending on the values to be measured. Lastly, the four terminals makes it possible to significantly extend the range of measurements possible. In this way, it can be adapted to very high currents by using a measuring

Precision Astatic Wattmeter


transformer (the principle of the current clamp), measure just the reactive power, etc.

Astaticism requires the moving element to be doubled up: two moving coils fitted head-to-tail react in an opposing fashion when they are subjected to the same magnetic field. So that they move when under the influence of the current to be measured, each is placed within a dedicated stationary coil, both of which are also wired head-to-tail. So for the system to be astatic, i.e. very little influenced by the Earth's magnetic field or pollutants like motors, dynamos, or high-current conductors, we need four coils. So why this costly astaticism when just some good magnetic shielding would have sufficed? Probably because the manufacturer knows, because of their long experience, that such an instrument can lose a great deal of its accuracy because of Foucault currents. In the presence of a massive metallic element, and even more so if it is enclosed in a metal case, a device generating a variable magnetic field will induce Foucault currents into the conductive mass, which will create a magnetic field in opposition to the field that induced them, whence a measurement that is disrupted in a not very predictable manner. "All wood and Bakelite" is not only an aesthetic choice: minimizing the amount of metal as much as possible is also the best technical option, even though that may not be intuitively obvious.

What's more, the designers have taken advantage of this doubling-up of the windings and offered the possibility of wiring the stationary windings in parallel or series, in order to have two current ranges available: 5 A and 10 A. But the selector switch offers a mysterious third position 'CC' to that is not described in the instructions and with no maximum current value.

In fact, in the 'CC' position the current measurement inputs are simply bypassed. So 'CC' doesn't stand for 'DC' (French CC: courant continu), but rather, 'short circuit'! The astatic operation means that the MD7 works as a real synchronous demodulator, i.e. even when placed in a noisy electromagnetic environment, it only extracts that which is at the exact frequency of the current passing through the DUT. It does not react to either static fields or those at different frequencies. But if the DUT itself radiates, the MD7 will include this unwanted field into its measurement. In this event, the 'CC' position makes it possible to measure the spurious field alone. A simple subtraction and the measured value becomes accurate again!

But there's a price to be paid for the accuracy of this fine device. It would be out of the question to subject such a delicate mechanism to any kind of shock. Or to use it without first using a spirit-level to check it is level. What's more, it's obvious that compensating for spurious fields using the famous 'CC' position is only valid if one is careful not to move the instrument at all between the two measurements, nor to change its orientation. And the most important thing of all: be wary of 'invisible' range overloads. You can merrily burn out your collector's piece while the needle is innocently showing very modest values. Not only can the current exceed the set range if the voltage is very low (and vice-versa), but, since what we see is the product of three value (the third being

 

The stationary windings are offset to reduce mutual coupling.

the phase angle $\cos(\phi)$), we can unwittingly burn out both U and I circuits at the same time when the phase angle gets close to 90° . And with a 'single-/3-phase' selector switch connected directly to the voltages being measured, we're a long way from IEC1010 measuring instruments!

(100381)



The range resistors are wound flat so as to have negligible self-inductance and hence an extended frequency response, and are trimmed to the nearest ohm. There are 14 of them (for six ranges), which makes it possible to reduce the power dissipated in each of them (never more than 1.5 watts) and hence the thermal drift — all the more so, since they are particularly well ventilated: accuracy, accuracy, accuracy!

Retronics is a monthly column covering vintage electronics including legendary Elektor designs. Contributions, suggestions and requests are welcomed; please send an email to editor@elektor.com

ELEKTOR SHOWCASE

To book your showcase space contact Strategic Media Marketing Inc.

Tel. 1-978-281-7708

Fax 1-978-281-7706

Email ElektorUSA@smmarketing.us

HAMEG® Instruments

A Rohde & Schwarz Company

- ☑ Oscilloscopes
- ☑ Power Supplies
- ☑ Spectrum Analyzers
- ☑ RF Instruments
- ☑ Programmable Measuring Instruments

HAPRO Electronics

Tel: +1-516-794-4080
sales@haproelectronics.com
www.haproelectronics.com

7 in 1 Scope !



CircuitGear CGR-101™ is a unique new, low-cost PC-based instrument which provides the features of seven devices in one USB-powered compact box: 2-ch 10-bit 20MS/sec 2MHz oscilloscope, 2-ch spectrum-analyzer, 3MHz 8-bit arbitrary-waveform/standard-function generator with 8 digital I/O lines. It also functions as a Network Analyzer, a Noise Generator and a PWM Output source. What's more – its open-source software runs with Windows, Linux and Mac OS's!

Only \$199



1-888-7SAELIG
info@saelig.com
www.saelig.com



- Best products, low cost, no frills
- USB powered, 4 relays + 4 DIO channels
 - Will switch 120/240VAC @ 10amps
 - Screw terminal access
 - LV, CVI, VB-C, C#, JV
 - Free shipping
 - From \$57*



Design & supply of
 USB, Wireless, LAN,
 Serial & Internet DAQ,
 Relay/DIO card products www.easydaq.biz
 & custom design work info@easydaq.biz

Build Your Own:

THEREMIN

Theremax
The Ultimate Theremin

PAIA paia.com Music/Tutorials/Kits
 Analog Synthesizers
 Guitar Effects
 Tube Electronics
 Studio Gear
 Makers since 1959

SCIENCE, ROBOTICS & ELECTRONICS

IMAGES Scientific Instruments Inc.

Microcontrollers
 Servo Motor Controllers
 Artificial Vision
 Speech Recognition
 Flex Sensors

www.imagesco.com
 Tele: (718) 966-3694 Fax: (718) 966-3695

MaxSonar

Ultrasonic Ranging is EZ

www.maxbotix.com

Pololu Robotics & Electronics

Robot chassis, wheels, casters, motors & servos

RP5 chassis \$49.95

Jrk USB motor controller with feedback \$49.95

Controllers, sensors, cables, batteries & more!

Plastic SMT stencils & custom laser cutting

Save 10% on motor controllers with coupon code **ELEKTORMC94**

www.pololu.com

bob-4

basic overlay board for NTSC & PAL

NEW REDUCED PRICING

Automatic text scroll & crawl · TTL-232 & SPI control ports
 Any size for custom fonts · Vector & bitmap graphics

DECADE ENGINEERING
www.decadenet.com

AP CIRCUITS

PCB Fabrication Since 1984

As low as... **\$9.95** each!

Two Boards
 Two Layers
 Two Masks
 One Legend

Unmasked boards ship next day!

www.apcircuits.com

VISA MasterCard Discovernet IPC MEMBER

www.elektor.com

Microcontroller modules
 Communications modules
 Support modules
 Accessories
 Kits available.

With BASIC On Board — development tools and compilers are no longer necessary.

Prototypes quickly and easily

Learn programming

Explore microcontrollers

Experiment

BASIC ON BOARD !

ATRIA Technologies Inc
www.AtriaTechnologies.com

TO BOOK YOUR SHOWCASE SPACE CONTACT STRATEGIC MEDIA MARKETING INC.

Tel. 1-978-281-7708
 Fax 1-978-281-7706
 Email ElektorUSA@smmarketing.us

products and services directory

SHOWCASE YOUR COMPANY HERE

Elektor provides you with more ways to promote your business with our Showcase section -- a permanent feature of the magazine where you will be able to further highlight your products and services.

- For just \$715 (\$65,00 per issue for eleven issues), Elektor will publish your company name, website address and a 30-word description.
- For \$1100 (\$100,00 per issue for eleven issues), we will publish the above plus run a 2-inch square, full-color image

– i.e., product shot, screen shot from your website, company logo, catalog cover – or whatever you choose to showcase.

Places are limited and spaces will go on a strictly first come, first served basis. So please fax back your order today!

I wish to promote my company, please book my space:

- Text insertion only for \$715
- Text and photo for \$1,100

NAME: ORGANISATION:

JOB TITLE:

ADDRESS:

..... TEL:

PLEASE COMPLETE COUPON BELOW AND FAX BACK TO 1-978-281-7706

COMPANY NAME

WEB ADDRESS

30-WORD DESCRIPTION

WIRELESS MADE SIMPLE®

QUICKLY AND COST-EFFECTIVELY MAKE YOUR PRODUCT WIRELESS

RF MODULES
LOW COST • LONG RANGE

TRANSMITTERS • RECEIVERS • TRANSCEIVERS

INTEGRATED CIRCUITS
ENCODERS • DECODERS • TRANSCIVERS

COMMAND • CONTROL • KEYLESS ENTRY

OEM PRODUCTS
EASILY CUSTOMIZED

ANTENNAS
FROM WHIPS TO CHIPS

Featured Products:

LT Series Transceiver

- 315 MHz
- 410 MHz
- 433 MHz

- Data Rates to 10K bps
- Direct Serial Interface
- Low Power Consumption
- Low Cost
- Long Range
- Ultra Compact

Ideal for the bi-directional wireless transfer of serial data, control, or command information in the favorable 250-470MHz band. Its advanced synthesized architecture delivers outstanding stability and frequency accuracy.

Function Relay Module

Provides four latched or momentary relay outputs that are capable of switching external AC or DC powered loads of up to 5 amps.

- 315 MHz
- 415 MHz
- 433 MHz
- Dual Power Inputs
- 256 Unique Addresses
- Wide Operational Voltage
- FCC and Industry Canada Pre-Tested

linx technologies 800-736-6677
159 Ort Lane
Merlin, OR 97532
linxtechnologies.com

V-M

v-module

Big power in a small package

VMA2016 (7.2cc(11u))

Vcc : 10V-24V
Pomax : 10W x 2(8Ω)
THD+N : 0.07%(5W)
SNR : >90dB
Size : 25x15x3.8mm

Compact size No heat sink Minimum external parts

Other Audio Amplifier Modules
VMP2012 2.7V-5.5V 3W x 2 Audio Amplifier
VMP2013 6W Mono Audio Amplifier
VMP2015 15W Mono Audio Amplifier
VMP2014 5W x 2 Stereo Audio Amplifier
VMP2016 10W x 2 Stereo Audio Amplifier

URL : <http://www.v-module.com>
Email : sales@v-module.com

Going Strong

A world of electronics from a single shop!



Books

Visual Studio

C# 2010 Programming and PC interfacing

This book is aimed at anyone who wants to learn about C# programming and interfacing to a PC. It covers programming concepts from the basics to object oriented programming, displaying graphs, threading and databases. The book is complete with many full program examples, self assessment exercises and links to supporting videos. All code examples used are available –free of charge– from the www.elektor.com support website; you can easily create your own results to demonstrate the concepts explained and reinforce your learning in the process. Professional quality software tools are downloadable –also free of charge– from Microsoft. The Microsoft Visual Studio 2010 environment is extensively covered with user controls and their properties, methods and events. Detailed guidance is provided for those wishing to control hardware from a PC with PC interfacing chapters which explain the legacy serial and parallel ports, analogue interfacing using the sound card and use of Microsoft DirectX drivers. Interfacing to the ubiquitous USB port is explained in-depth with a detailed hardware and software design for a USB connected PIC-based hardware target included.

306 pages • ISBN 978-0-905705-95-8 • \$47.60




Use only free or open source software!

ARM Microcontroller Interfacing

Learn to interface and program hardware devices in a wide range of useful applications, using ARM7 microcontrollers and the C programming language. Examples covered in full detail include a simple LED to a multi-megabyte SD card running the FAT file system. Interface to LEDs, transistors, optocouplers, relays, solenoids, switches, keypads, LCD displays, seven segment displays, DC motors, stepper motors, external analogue signals using the ADC, RS-232, RS-485, TWI, USB, SPI and SD memory cards.

 250 pages • ISBN 978-0-905705-91-0 • \$47.60



Get started quickly and proceed rapidly

Python Programming and GUIs

This book is aimed at people who want to interface PCs with hardware projects using graphic user interfaces. The programming language used is Python, an object-oriented scripting language. The book guides you through starting with Linux by way of a free downloadable, live bootable distribution that can be ported around different computers without requiring hard drive installation.

224 pages • ISBN 978-0-905705-87-3 • \$47.60

Going Strong

A world of electronics from a single shop!



Books

Visual Studio

C# 2010 Programming and PC interfacing

This book is aimed at anyone who wants to learn about C# programming and interfacing to a PC. It covers programming concepts from the basics to object oriented programming, displaying graphs, threading and databases. The book is complete with many full program examples, self assessment exercises and links to supporting videos. All code examples used are available –free of charge– from the www.elektor.com support website; you can easily create your own results to demonstrate the concepts explained and reinforce your learning in the process. Professional quality software tools are downloadable –also free of charge– from Microsoft. The Microsoft Visual Studio 2010 environment is extensively covered with user controls and their properties, methods and events. Detailed guidance is provided for those wishing to control hardware from a PC with PC interfacing chapters which explain the legacy serial and parallel ports, analogue interfacing using the sound card and use of Microsoft DirectX drivers. Interfacing to the ubiquitous USB port is explained in-depth with a detailed hardware and software design for a USB connected PIC-based hardware target included.

306 pages • ISBN 978-0-905705-95-8 • \$47.60




Bestseller!

Use only free or open source software!

ARM Microcontroller Interfacing

Learn to interface and program hardware devices in a wide range of useful applications, using ARM7 microcontrollers and the C programming language. Examples covered in full detail include a simple LED to a multi-megabyte SD card running the FAT file system. Interface to LEDs, transistors, optocouplers, relays, solenoids, switches, keypads, LCD displays, seven segment displays, DC motors, stepper motors, external analogue signals using the ADC, RS-232, RS-485, TWI, USB, SPI and SD memory cards.

 250 pages • ISBN 978-0-905705-91-0 • \$47.60



Get started quickly and proceed rapidly

Python Programming and GUIs

This book is aimed at people who want to interface PCs with hardware projects using graphic user interfaces. The programming language used is Python, an object-oriented scripting language. The book guides you through starting with Linux by way of a free downloadable, live bootable distribution that can be ported around different computers without requiring hard drive installation.

224 pages • ISBN 978-0-905705-87-3 • \$47.60



See the light on Solid State Lighting
DVD LED Toolbox

This DVD-ROM contains carefully-sorted comprehensive technical documentation about and around LEDs. For standard models, and for a selection of LED modules, this Toolbox gathers together data sheets from all the manufacturers, application notes, design guides, white papers and so on. It offers several hundred drivers for powering and controlling LEDs in different configurations, along with ready-to-use modules (power supply units, DMX controllers, dimmers, etc.). In addition to optical systems, light detectors, hardware, etc., this DVD also addresses the main shortcoming of power LEDs: heating. This DVD contains more than 100 Elektor articles on the subject of LEDs.

ISBN 978-90-5381-245-7 • \$46.00



110 issues, more than 2,100 articles
**DVD Elektor
1990 through 1999**

This DVD-ROM contains the full range of 1990-1999 volumes (all 110 issues) of Elektor Electronics magazine (PDF). The more than 2,100 separate articles have been classified chronologically by their dates of publication (month/year), but are also listed alphabetically by topic. A comprehensive index enables you to search the entire DVD.

ISBN 978-0-905705-76-7 • \$100.00



Bestseller!

The Elektor DSP radio

(July/August 2010)

Many radio amateurs in practice use two receivers, one portable and the other a fixed receiver with a PC control facility. The Elektor DSP radio can operate in either capacity, with a USB interface giving the option of PC control. An additional feature of the USB interface is that it can be used as the source of power for the receiver, the audio output being connected to the PC's powered speakers. To allow portable 6V battery operation the circuit also provides for an audio amplifier with one or two loudspeakers.

PCB, assembled and tested

Art.# 100126-91 • \$240.40



InterSceptre

(June 2010)

In our March issue, we introduced Sceptre, a fast prototyping system fitted with a 32-bit microcontroller. Even on its own, this board will let you produce some great results, but if we add an extension board to make it easier to access all its peripherals, the Sceptre platform becomes downright powerful. What's more, if you fit this extension board into a suitable case, you'll be able right from the start to develop a prototype that you can use 'properly' in a installation, with no trailing wires or bits of sticky tape holding everything together. Now that's what you call fast, convenient prototyping!

Kit of parts, contains PCB and components

Art.# 100174-71 • \$187.10




dsPIC Control Board

(May 2010)

This control board has been designed for incorporation into typical industrial electronics applications like controlling motors or adjustment of static up- or down-converters. The objectives were to obtain a board with a large number of pulswidth modulation (PWM) generators, which enables us to control several motors and static converters at the same time. The cost of the control board needed to be as low as possible too. In addition, it must be possible to construct the board using a soldering iron, without requiring use of a reflow oven.

PCB, populated and tested

Art.# 090073-91 • \$225.90

 

Reign with the Sceptre

(March 2010)

This open-source & open-hardware project aims to be more than just a little board with a big microcontroller and a few useful peripherals — it seeks to be a fast prototyping system. To justify this title, in addition to a very useful little board, we also need user-friendly development tools and libraries that allow fast implementation of the board's peripherals. Ambitious? Maybe, but nothing should deter you from becoming Master of Embedded Systems Universe with the help of the Elektor Sceptre.

PCB, populated and tested, test software loaded

Art.# 090559-91 • \$143.60

November 2010 (No. 23)

+ + + Product Shortlist November: See www.elektor.com + + +

October 2010 (No. 22)

CL-3 Digital Rotary Combination Lock

100026-41 Atmel ATTINY2313-20PU, programmed 12.90

Wheelie GT

100479-71 Kit of parts upgrade kit controller board +
2x Hall sensor board 169.40

September 2010 (No. 21)

Elektor Project Case

100500-71 Predrilled Lexan sheets with standoffs 24.10

Digital Multi-Effects Unit

090835-31 EEPROM 24LC32 6.50

090835-41 ATmega8-16PU 13.40

090835-42 ATtiny2313-20PU 13.40

090835-71 Kit of parts including PCBs, programmed controllers
and EEPROM 266.20

Dual Voltage/Current Display

100166-71 Kit of parts incl. PCB, item -41, LCD 100.00

Vision System for Small Microcontrollers

090334-1 PCB 32.10

090334-41 PIC16F690-I/P, programmed 12.90

July/August 2010 (No. 19/20)

The Elektor DSP radio

100126-41 ATmega168 PU 20.20

100126-91 PCB, assembled and tested 240.40

Daggerboard Position Detector

080307-41 PIC16F628A-DIL-18, programmed 12.90

PIC RJ-45 Cable Tester

090643-41 PIC16F72, programmed 12.90

3D LED Pyramid

090940-41 ATtiny2313-20SU, programmed 12.90

Digital Thumbwheel Switch

090538-41 ATtiny2313 dip20, programmed 12.90

Whistler: Electronic Trainer/Coach

100203-41 PIC16F88 DIP18, programmed 12.90

Solar Cell Battery Charger/Monitor

090544-41 PIC16F877A, programmed 26.70

Universal Timer with Zero Standby Current

090534-41 ATtiny2313, programmed 12.90

Tiny Timer

091044-41 ATtiny2313, programmed 12.90

Universal PWM Driver

090856-41 PIC16F628-1/P, programmed 12.90

Binary Clock

090187-41 PIC165F877-20/P DIP40, programmed 29.90

USB Tilt Sensor

070829-41 ATmega8-16AU (TQFP), programmed 12.90

090645-91 MMA7620 breakout board 13.80

Bench PSU for PC

090863-41 PIC16F616-I/P, programmed 12.90

Sailor's Battery Meter

090117-41 PIC16F690 DIP, programmed 12.90

Tiny Pulsar

090444-41 ATTINY13-20P4, programmed 12.90

MicroMinimal Thermometer

090634-41 ATTINY13(A)dip8, programmed 12.90

Waterproof Bathroom Switch

090537-41 ATtiny13A, programmed 12.90

Lights Control for Model Cars

090834-41 Programmed controller ATtiny45 DIP-8 12.90

Modeller's Clock

090023-41 PIC18LF1320 I/P DIL18, programmed 12.90

Bestsellers

Books

- 1 → **ARM Microcontroller Interfacing**
ISBN 978-0-905705-91-0 \$47.60
- 2 ↗ **High-End Valve Amplifiers 2**
ISBN 978-0-905705-90-3 \$59.70
- 3 ↘ **Power Electronics in Motor Drives**
ISBN 978-0-905705-89-7 \$47.60
- 4 ↑ **Elektor Personal Organizer 2011**
ISBN 978-90-5381-259-4 \$40.20
- 5 ↙ **50 PIC Microcontroller projects**
ISBN 978-0-905705-88-0 \$58.10

CD/DVD-ROMs

- 1 → **DVD The Audio Collection 3**
ISBN 978-90-5381-263-1 \$28.90
- 2 → Masterclass
DVD High-End Valve Amplifiers
ISBN 978-0-905705-86-6 \$40.20
- 3 ↗ **DVD Elektor 1990 through 1999**
ISBN 978-0-905705-76-7 \$100.00
- 4 ↘ **DVD LED Toolbox**
ISBN 978-90-5381-245-7 \$46.00
- 5 → **DVD Elektor 2009**
ISBN 978-90-5381-251-8 \$28.30


Kits & Modules

- 1 → **Elektor DSP radio**
Art. # 100126-91 \$240.40
- 2 → **Reign with the Sceptre**
Art. # 090559-91 \$143.60
- 3 ↗ **OBD2 Mini Simulator**
Art. # 080804-71 \$135.50
- 4 ↘ **InterSceptre**
Art. # 100174-71 \$187.10
- 5 ↑ **Wheelie GT**
Art. # 100479-71 \$169.40

Order quickly and securely through
www.elektor.com/shop
or use the Order Form near the end
of the magazine!




 Elektor US
PO Box 180
Vernon, CT 06066
USA
Phone: 860-875-2199
Fax: 860-871-0411
E-mail: sales@elektor.com



Stroboscopic PC Fan

Many PC users constantly attempt to adorn their computers with visual gadgets whose main purpose is to draw attention. PC cases with a transparent side panel in particular offer super opportunities for special effects. Our circuit based on an ATtiny25 micro controls an LED in such a way as to make the PC ventilator fan blades appear to stand still, turn slowly in either direction, or turn at intervals. A fascinating effect!

 

Ethernet Module

Adding an Ethernet connection to your circuit allows you to easily capture data from sensors, actuators and other devices, through the Internet. Unfortunately, many electronics enthusiasts find it hard to master or at least get to grips with the relevant hardware and software. Now, a handy solution is found in a small module comprising a PIC micro with an on-chip Ethernet transceiver, an isolating transformer and a network connector. The project is completed with a free software library and lots of examples to get you going.



Elektor Embedded Special

In the December 2010 edition you can look forward to finding a special insert totally dedicated to embedded projects. Space allowing we'll be covering: an infrared thermometer, a USB-to-RS485 converter with galvanic isolation, an intelligent modular LED display, a breadboard interface for an XPort module, a carrier board for the Arduino Nano, several projects for our own MiniMod18 and lots more!

Article titles and magazine contents subject to change; please check the Magazine tab on www.elektor.com

Elektor UK/European edition: on sale November 18, 2010. Elektor USA edition: published November 11, 2010.

www.elektor.com www.elektor.com www.elektor.com www.elektor.com www.elektor.com www.elektor.com

Elektor on the web

All magazine articles back to volume 2000 are available online in pdf format. The article summary and parts list (if applicable) can be instantly viewed to help you positively identify an article. Article related items are also shown, including software downloads, circuit boards, programmed ICs and corrections and updates if applicable. Complete magazine issues may also be downloaded.

In the Elektor Shop you'll find all other products sold by the publishers, like CD-ROMs, DVDs, kits, modules, equipment, tools and books. A powerful search function allows you to search for items and references across the entire website.

Also on the Elektor website:

- Electronics news and Elektor announcements
- Readers Forum
- PCB, software and e-magazine downloads
- Time limited offers
- FAQ, Author Guidelines and Contact



ORDERING INFORMATION

To order contact customer service:

Phone: 860-875-2199
Fax: 860-871-0411
Mail: Elektor US
PO Box 180
Vernon, CT 06066
USA
E-mail: sales@elektor.com
On-line at www.elektor.com

Customer service hours: 8:00 AM–4:30 PM Monday–Thursday. Voice mail available at other times.
When leaving a message please be sure to leave a daytime telephone number where we can return your call.

PLEASE NOTE: While we strive to provide the best possible information in this issue, pricing and availability are subject to change without notice. To find out about current pricing and stock, please call or email customer service.

COMPONENTS

Components for projects appearing in Elektor are usually available from certain advertisers in the magazine. If difficulties in obtaining components are suspected, a source will normally be identified in the article. Please note, however, that the source(s) given is (are) not exclusive.

PAYMENT

Orders must be prepaid. We accept checks or money orders (in US \$ drawn on a US bank only), VISA, Mastercard, Discover, and American Express credit cards. We do not accept C.O.D. orders.
We also accept wire transfers. Add \$20 to cover fees charged for these transfers.

TERMS OF BUSINESS

Shipping Note: All orders will be shipped from Europe. Please allow 3–4 weeks for delivery. Shipping and handling via airmail: US \$20.00 per order. **Returns** Damaged or miss-shipped goods may be returned for replacement or refund. All returns must have an RA #. Call or email customer service to receive an RA# before returning the merchandise and be sure to put the RA# on the outside of the package. Please save shipping materials for possible carrier inspection. Requests for RA# must be received 30 days from invoice. **Patents** Patent protection may exist with respect to circuits, devices, components, and items described in our books and magazines. Elektor accepts no responsibility or liability for failing to identify such patent or other protection. **Copyright** All drawing, photographs, articles, printed circuit boards, programmed integrated circuits, diskettes, and software carriers published in our books and magazines (other than in third-party advertisements) are copyrighted and may not be reproduced (or stored in any sort of retrieval system) without written permission from Elektor. Notwithstanding, printed circuit boards may be produced for private and personal use without prior permission. **Limitation of liability** Elektor shall not be liable in contract, tort, or otherwise, for any loss or damage suffered by the purchaser whatsoever or howsoever arising out of, or in connection with, the supply of goods or services by Elektor other than to supply goods as described or, at the option of Elektor, to refund the purchaser any money paid with respect to the goods.

SUBSCRIPTIONS (US & CANADA ONLY)

Subscription rates (1 Yr.)

Standard Subscription: \$39.95
Plus Subscription: \$54.95

Canada add \$11 per year for postage

All subscriptions begin with the current issue. Expect 3–4 weeks for receipt of the first issue. Subscriptions, renewals, and change of address should be sent to:

Elektor US
PO Box 180
Vernon, CT 06066
USA

E-mail: sales@elektor.com

Order subscriptions on-line at www.elektor.com/subs

Subscriptions may be paid for by check or money order (in US \$ drawn on a US bank only). We accept Mastercard, VISA, Discover and American Express credit cards.

For gift subscriptions, please include gift recipient's name and address as well as your own, with remittance. A gift card will be sent on request.
Subscriptions may be cancelled at any time for a refund of all unmailed issues.

Does your subscription expire soon?

Renew it online at www.elektor.com/renew

LEDs 1

Elektor Special Project

This special edition offers not only theoretical information but also shows how and where LEDs are applied nowadays. Additionally, this edition contains some tested electronic circuits for DIY.

Theory and applications:

- Control electronics and heat management for LED lighting
- LED projector technology
- Voltage converter with constant-current output for Power LEDs
- LED power and control unit on a single chip

DIY projects:

- Ambilight with Bluetooth
- Budget LED dimmer
- Computerised LED Christmas light
- Programmable LED lamp

And much more!



NEW

100 pages • \$16.00

Elektor US
PO Box 180
Vernon, CT 06066
USA
Phone: 860-875-2199
Fax: 860-871-0411
E-mail: sales@elektor.com

Further information and ordering at www.elektor.com/shop

INDEX OF ADVERTISERS

AP Circuits, Showcase www.apcircuits.com	53, 78	Maxbotix, Showcase www.maxbotix.com	78
Atria Technologies, Showcase www.AtriaTechnologies.com	78	McGraw-Hill. www.mhprofessional.com	2
Circuit Cellar www.circuitcellar.com	65	MikroElektronika. www.mikroe.com	3
Decade Engineering, Showcase www.decadenet.com	78	NXP Contest. www.circuitcellar.com/nxpmbeddesignchallenge	15
DLP Design www.dlpdesign.com	53	Paia Electronics, Showcase www.paia.com	13, 78
EasyDAQ, Showcase www.easydaq.biz	78	Parallax www.parallax.com	51
Elsevier www.newnespress.com	57	Pololu Corporation, Showcase www.pololu.com/3pi	13, 78
ExpressPCB www.expresspcb.com	9	Saelig, Showcase. www.saelig.com	53, 78
EzPCB/V-Module www.v-module.com	79	Showcase	78, 79
Future Technology Devices. www.ftdichip.com	11	WIZnet. www.wiznettechnology.com	39
Hameg Instruments, Showcase www.haproelectronics.com	78		
Images Scientific, Showcase www.imagesco.com	78		
Jameco www.jameco.com	88		
Linx Technologies. www.linxtechnologies.com	79		

Advertising space for the issue of 16 December 2010
may be reserved not later than 23 November 2010
with Strategic Media Marketing, Inc. - 2 Main Street -
Gloucester, MA 01930 - USA - Telephone 1.978.281.7708 -
Fax 1.978.281.7706 - e-mail: ElektorUSA@smmarketing.us to whom all
correspondence, copy instructions and artwork should be addressed.

Can You Solve This Puzzle?



What is the missing component?



A Physics professor planned to illustrate a lecture with demonstrations of how light can be intercepted by certain phosphors or various optoelectronic sensors and transformed into entirely new light. He wanted an ultra-simple demonstration of how an LED would glow when biased by a forward current provided by a suitable sensor. He rummaged through his optoelectronic drawer and found two silicon solar cells, several cadmium sulfide photo resistors, a couple of AlGaAs red LEDs, some silicon phototransistors and half a dozen silicon photodiodes. In his parts cabinet he found some transistors, miniature chokes and assorted resistors and capacitors. How did he combine the smallest number of components to do what the phosphor card did? Go to www.jameco.com/solve8 to see if you are correct.

Sign up for our e-newsletter
and get a bonus puzzle.
www.Jameco.com/enevs

JAMECO[®]
ELECTRONICS

1-800-831-4242 | www.Jameco.com